

Suggested Bread Board Wiring Layout

Set the Power supply to
 $\pm 10V$, 50mA current limit

Only comparator circuit is shown.
Adjust the wiring for other
configurations

