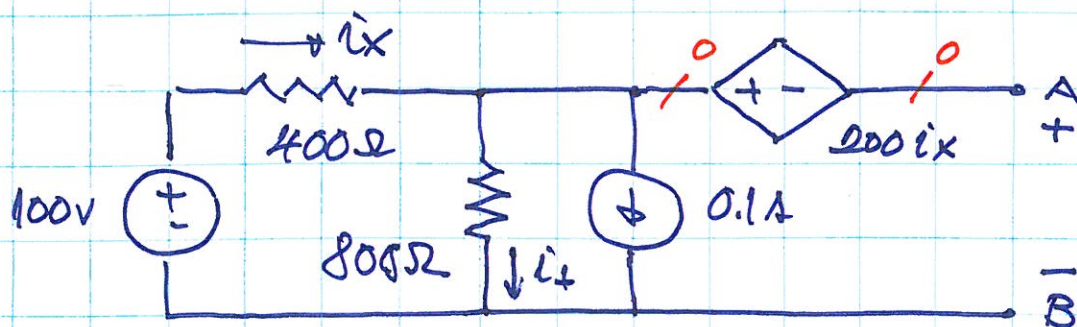


(a) Thévenin equivalent:

V_{th} : Terminals A-B : open



KCL: $i_x = i_1 + 0.1$ $V_{th} = V_{AB}$

KVL:

$$100 - 400 \cdot i_x - 800 \cdot i_1 = 0$$

$$V_{AB} + 200 \cdot i_x - 800 \cdot i_1 = 0$$

or:

$$400 \cdot i_x + 800 \cdot (i_x - 0.1) = 100 \quad /: 100$$

$$4i_x + 8i_x - 0.8 = 1 \quad ; \quad 12i_x = 1.8$$

$$i_x = \frac{18}{120} \quad ; \quad i_1 = \frac{3}{20}$$

Then: $V_{AB} = -200 \cdot i_x + 800 \cdot i_1$

$$V_{AB} = -200 \cdot i_x + 800(i_x - 0.1)$$

$$V_{AB} = 600 \cdot i_x - 80$$


$$V_{AB} = 600 \cdot \frac{3}{20} - 80$$

$$V_{AB} = 90 - 80 ; V_{AB} = 10V$$

$$\underline{V_{Th} = 10V}$$

(b)

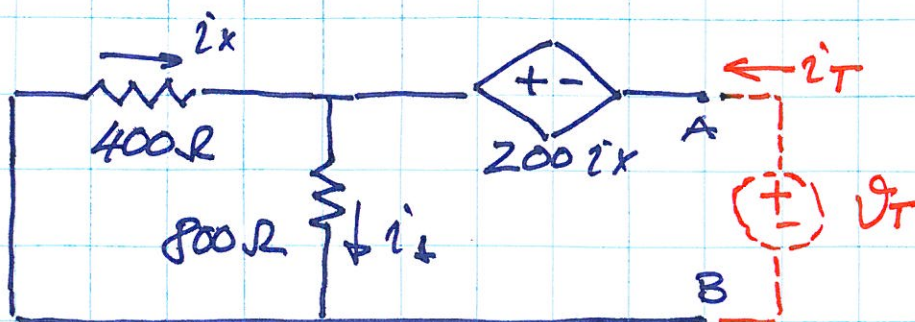R_{Th} : Disconnect the independent sources:



$$KVL: 400 \cdot i_x + 800 \cdot i_1 = 0 \rightarrow i_x + 2i_1 = 0$$

$$i_1 = -\frac{1}{2} i_x$$

$$KCL: i_x + i_T = i_1 ; i_x = i_1 - i_T$$

or

$$i_x = -\frac{1}{2} i_x - i_T$$


$$\frac{3}{2} i_x = -i_T ; i_x = -\frac{2}{3} \cdot i_T$$

$$KVL: V_T + 200 \cdot i_x + 400 \cdot i_x = 0$$

$$V_T = -600 \cdot i_x ; V_T = -600 \times \left(-\frac{2}{3} i_T\right)$$

$$\frac{V_T}{i_T} = 400 ; R_{Th} = 400 \Omega$$

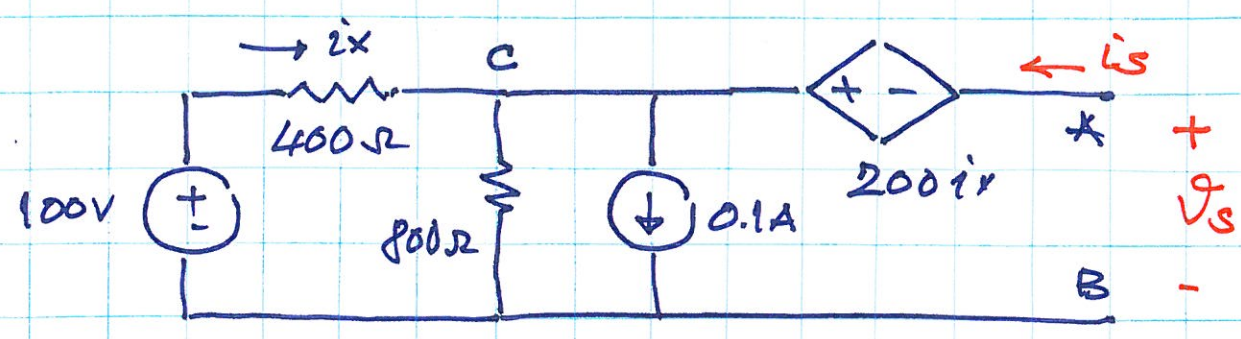* One may find V_{th} and R_{th} in one step:



Node equation:

$$\frac{V_c - 100}{400} + \frac{V_c}{800} + 0.1 - i_s = 0 \quad / \times 800$$

$$2(V_c - 100) + V_c + 80 - 800 i_s = 0$$

$$3V_c - 800 i_s = 120$$

$$V_c = 40 + \frac{800}{3} \cdot i_s \quad (1)$$

KVL:

$$V_s + 200 \cdot i_x - V_c = 0$$

$$V_s = V_c - 200 \cdot i_x$$

Since


$$i_x = \frac{100 - V_c}{400}$$

$$V_s = V_c - 200 \cdot \frac{100 - V_c}{400} \quad ; \quad V_s = \frac{3}{2} V_c - 50 \quad (2)$$

using (1):

$$V_s = \frac{3}{2} \cdot \left(40 + \frac{800}{3} \cdot i_s \right) - 50$$

$$V_s = 10 + 400 \cdot i_s$$

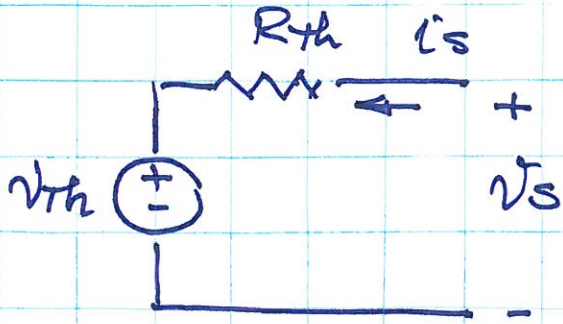

$$v_s - R_{th} \cdot i_s - v_{th} = 0$$

$$v_s = v_{th} + R_{th} \cdot i_s$$


$$v_s = 10 + 400 \cdot i_s$$

then:

$$v_{th} = 10 \text{ V}$$

$$R_{th} = 400 \Omega$$


2

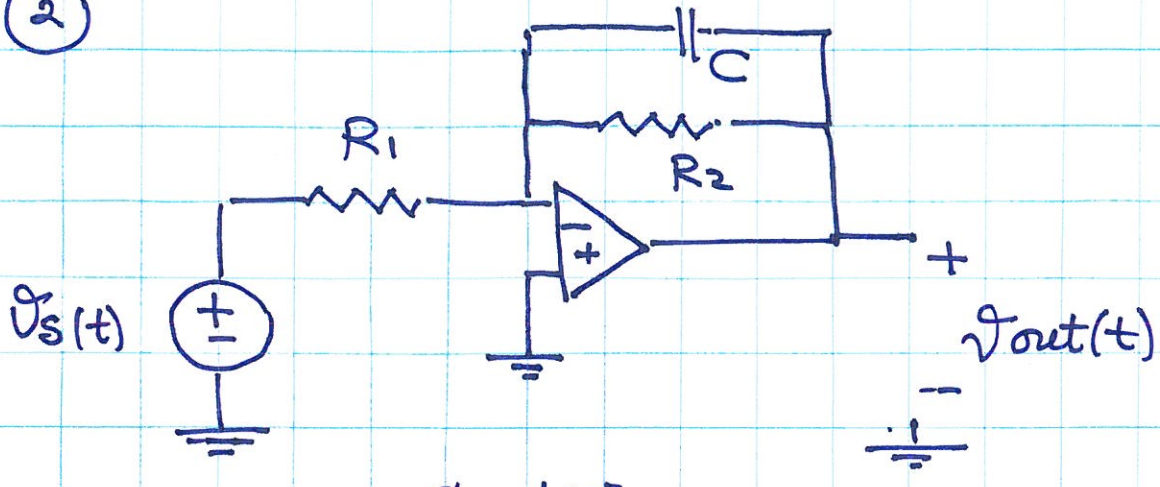

$C = 1 \mu F$
 $R_2 = 10 M\Omega$
 $V_s(t) = -5u(t)$

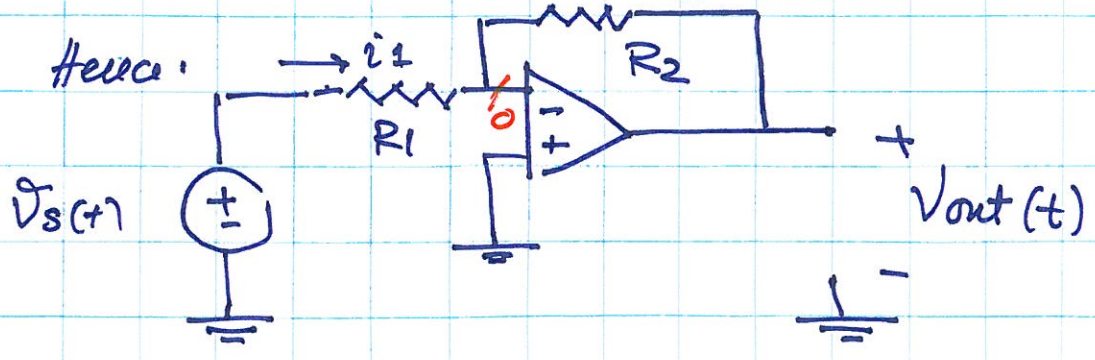(a) gain = ?

At $t \rightarrow \infty$, C behaves as an open circuit



$V_- = V_+ \text{ (ideal op-amp)}$
 $V_- = 0$

$V_s - R_1 \cdot i_1 = 0 ; i_1 = \frac{V_s}{R_1} ; V_+ = i_2 \text{ (KCL)}$

$V_{out} + R_2 \cdot i_2 = 0 ; V_{out} = -R_2 \cdot i_2$

gain = $-\frac{R_2}{R_1}$

$V_{out} = -R_2 \cdot i_1 ;$
 $V_{out} = -R_2 \cdot \frac{V_s}{R_1}$

(6)

For gain to be equal to 10:


$$\frac{R_2}{R_1} = 10 \quad ; \quad R_2 = 10 \times R_1$$

$$R_2 = 10 \mu\Omega$$

$$\text{Hence, } R_1 = 1 \mu\Omega$$

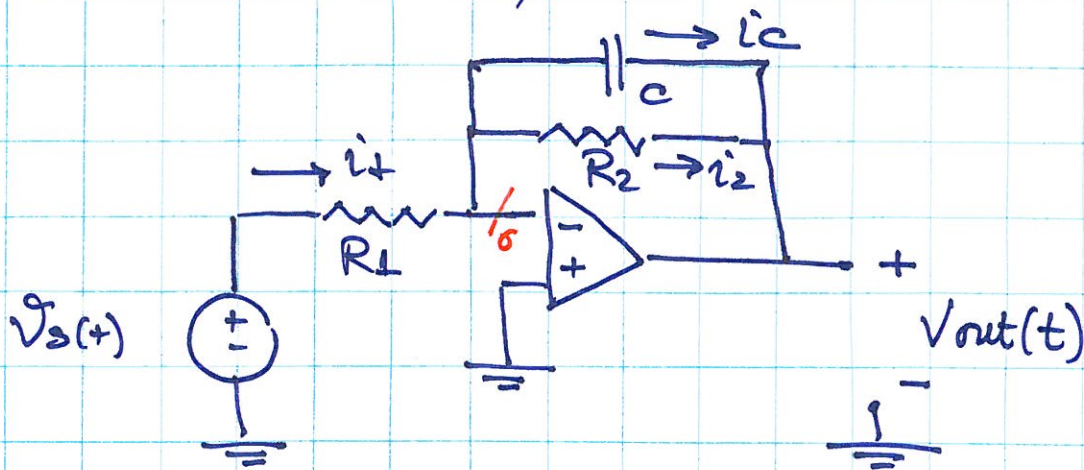(b) Time domain response:

$$V_C(0^-) = 0 \quad ; \quad V_C(0^+) = 0$$



$$V_s(t) - R_1 \cdot i_1 = 0$$

$$i_1 = i_2 + i_c \quad ; \quad i_c = C \frac{dV_C}{dt}$$

$$V_{out}(t) + R_2 \cdot i_2 = 0$$

Hence:

$$i_1 = \frac{V_s}{R_1}$$

$$\frac{V_s}{R_1} = -\frac{V_{out}}{R_2} + C \cdot \frac{dV_C}{dt}$$

$$i_2 = -\frac{V_{out}}{R_2}$$

Since, $V_{out} + V_C = 0$; $V_{out} = -V_C$

$$\text{Hence: } C \frac{dV_C}{dt} + \frac{1}{R_2} \cdot V_C = \frac{1}{R_1} \cdot V_s$$

State equation

(4)

$$\frac{dv_c}{dt} + \frac{1}{R_2 C} v_c = \frac{1}{R_1 C} \cdot v_s \quad (4)$$

$$\text{Recall: } v_s(t) = -5u(t)$$

$$\text{For } t \geq 0: v_s(t) = -5$$

$$v_c(0+) = 0$$

Characteristic equation:

$$s + \frac{1}{R_2 C} = 0 \quad ; \quad s = -\frac{1}{R_2 C}$$

$$v_c(t) = K e^{-t/R_2 C} + v_{cp}(t)$$

$$v_{cp}(t) = A \quad (\text{constant, since } v_s(t) \text{ is a constant})$$

$$\text{From (4): } \frac{d v_{cp}(t)}{dt} + \frac{1}{R_2 C} \cdot v_{cp}(t) = \frac{1}{R_1 C} \cdot v_s(t)$$

$$0 + \frac{1}{R_2 C} \cdot A = \frac{1}{R_1 C} \cdot (-5)$$

$$A = -\frac{R_2}{R_1} \cdot 5 \quad ; \quad A = -50$$

$$R_2 = 10 \text{ M}\Omega$$

$$R_1 = 1 \text{ M}\Omega$$

$$v_c(t) = K e^{-t/R_2 C} - 50$$

$$v_c(0+) = 0 \Rightarrow K - 50 = 0 \quad ; \quad K = 50$$

$$v_c(t) = 50 (1 - e^{-t/R_2 C})$$


$$R_2 C = 10 \times 10^6 \times 10^{-6}$$

$$R_2 C = 10$$

$$1/R_2 C = 0.1$$

$$v_c(t) = 50 (1 - e^{-0.1t}) u(t)$$

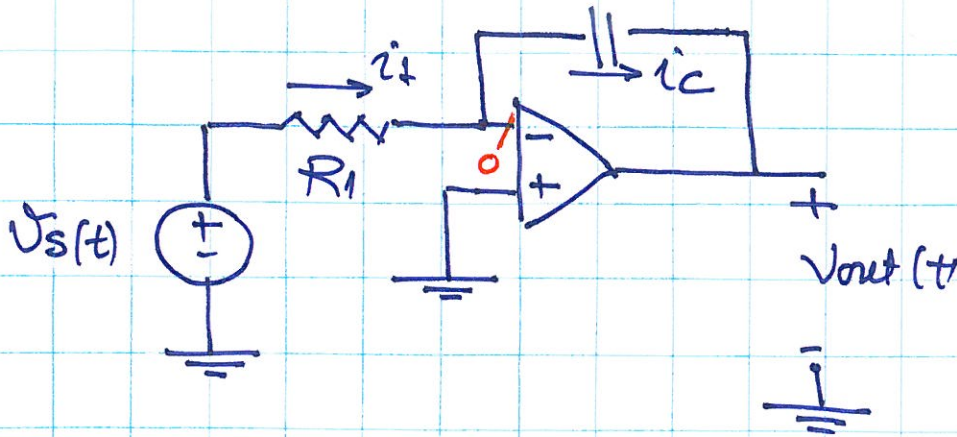(c) Ideal (non-leaky) integrator has ideal capacitor without the leakage represented by R_2 .



$$V_s(t) - R_1 i_1 = 0$$

$$i_1 = \frac{V_s(t)}{R_1}$$

$$i_1 = i_c$$

$$i_1 = C \frac{dV_c}{dt} ; V_{out} = -V_c$$

$$C \frac{dV_c}{dt} = \frac{1}{R_1} \cdot V_s(t)$$

$$\frac{dV_c}{dt} = \frac{1}{R_1 C} \cdot (-5)$$


$$R_1 C = 1 \times 10^6 \times 10^{-6}$$

$$R_1 C = 1$$

$$\frac{dV_c}{dt} = -5 ; V_c = -5t \cdot u(t)$$


$$V_{out} + V_c = 0$$
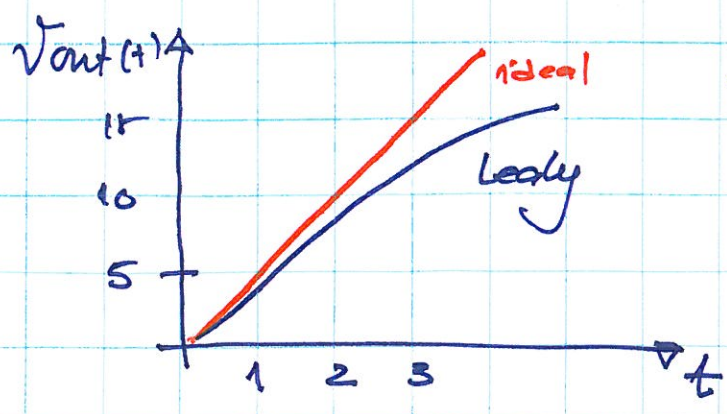
$$V_{out}(t) = 5 \cdot t \cdot u(t) \quad \text{Ideal case}$$




ideal:
 $V_{out}(t) = 5t u(t)$

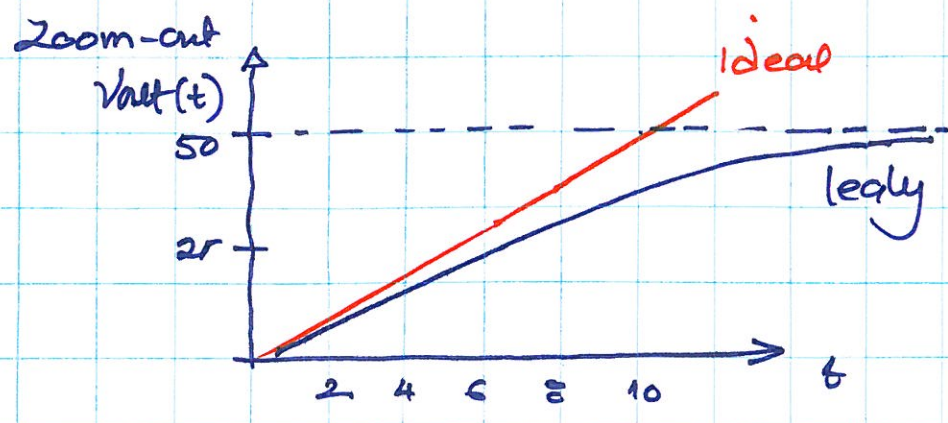leaky:
 $V_{out}(t) = 50(1 - e^{-0.1t})u(t)$



3

10

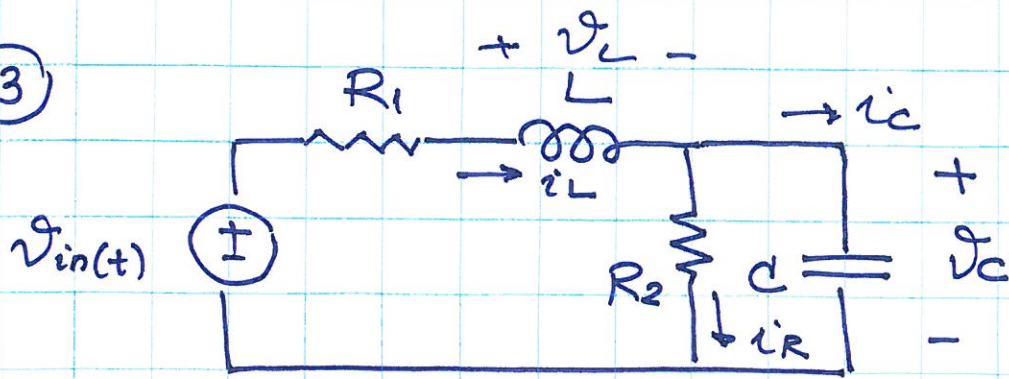

$$R_1 = 1 \Omega; R_2 = 1 \Omega; L = \sqrt{2} \text{ H}; C = \sqrt{2} \text{ F}$$

(a) State equations : state variable $i_L; v_C$

KVL $v_{in} - R_1 \cdot i_L - v_L - v_C = 0$ (1)

KCL $i_L = i_R + i_C$ (2)

$v_L = L \frac{di_L}{dt}$ constitutive relationships

$i_C = C \frac{dv_C}{dt}$

$i_R = \frac{v_C}{R_2}$ Ohm's Law

Hence:

$$R_1 \cdot i_L + L \frac{di_L}{dt} + v_C = v_{in}$$

$$i_L = \frac{v_C}{R_2} + C \frac{dv_C}{dt}$$

> only state variables appear

$$L \frac{di_L}{dt} + v_C + R_1 \cdot i_L = v_{in}$$

$$C \frac{dv_C}{dt} + \frac{1}{R_2} \cdot v_C - i_L = 0$$

} state equations

$$\left. \begin{aligned} \sqrt{2} \cdot \frac{di_L}{dt} + v_C + v_L &= v_{in}(t) & (3) \\ \sqrt{2} \cdot \frac{dv_C}{dt} + v_C - i_L &= 0 & (4) \end{aligned} \right\}$$

(b) Second-order differential equation in terms of v_C :
From (4):

$$i_L = C \frac{dv_C}{dt} + \frac{1}{R_2} v_C$$

Use symbolic form in order to easily check algebra

Substitute into (3) gives:

$$L \cdot \frac{d}{dt} \left\{ C \cdot \frac{dv_C}{dt} + \frac{1}{R_2} v_C \right\} + v_C + R_1 \cdot \left\{ C \cdot \frac{dv_C}{dt} + \frac{1}{R_2} v_C \right\} = v_{in}$$

$$LC \cdot \frac{d^2 v_C}{dt^2} + \frac{L}{R_2} \cdot \frac{dv_C}{dt} + v_C + R_1 C \cdot \frac{dv_C}{dt} + \frac{R_1}{R_2} v_C = v_{in}$$

$$LC \cdot \frac{d^2 v_C}{dt^2} + \left(\frac{L}{R_2} + R_1 C \right) \cdot \frac{dv_C}{dt} + \left(1 + \frac{R_1}{R_2} \right) v_C = v_{in}$$

or:

$$\frac{d^2 v_C}{dt^2} + \left(\frac{1}{R_2 C} + \frac{R_1}{L} \right) \frac{dv_C}{dt} + \frac{1}{LC} \left(1 + \frac{R_1}{R_2} \right) v_C = \frac{1}{LC} v_{in}$$

hence:

$$\frac{d^2 v_C}{dt^2} + \left(\frac{1}{\sqrt{2}} + \frac{1}{\sqrt{2}} \right) \frac{dv_C}{dt} + \frac{1}{\sqrt{2} \cdot \sqrt{2}} \cdot (1 + 1) \cdot v_C = \frac{1}{\sqrt{2} \cdot \sqrt{2}} v_{in}$$

$$\frac{d^2 v_C}{dt^2} + \sqrt{2} \cdot \frac{dv_C}{dt} + v_C = \frac{1}{2} v_{in} \quad (5)$$

(c) Characteristic equation:

$$s^2 + \sqrt{2}s + 1 = 0$$

$$s_{1/2} = -\frac{\sqrt{2}}{2} \pm \sqrt{\left(\frac{\sqrt{2}}{2}\right)^2 - 1}$$

$$s_{1/2} = -\frac{\sqrt{2}}{2} \pm \sqrt{-1/2}$$

$$s_{1/2} = -\frac{\sqrt{2}}{2} \pm \frac{j}{\sqrt{2}} ; \quad 1/\sqrt{2} = \frac{\sqrt{2}}{2}$$

$$s_{1/2} = \frac{-\sqrt{2} \pm j\sqrt{2}}{2}$$

or

$$s_{1/2} = -\frac{1 \pm j}{\sqrt{2}}$$

(d) Two complex-conjugate roots: The system is underdamped

(e) Solutions:

$$v_C(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} + v_{cp}(t)$$

$$i_L(t) = k_3 e^{s_1 t} + k_4 e^{s_2 t} + i_{lp}(t)$$

Since $v_{in}(t) = u(t)$; $v_{in}(t) = 1$ for $t \geq 0$

$$v_{cp}(t) = A ; A = ?$$

From state equation (5):

$$0 + \sqrt{2} \cdot 0 + A = \frac{1}{2} \cdot 1$$

$$A = 1/2$$

$$v_C(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} + \frac{1}{2} \quad ; \quad k_1 + k_2 + \frac{1}{2} = 0 \quad (6)$$

Note: $i_L(0^-) = 0 \quad i_L(0^+) = 0$
 $v_C(0^-) = 0 \quad \Rightarrow \quad v_C(0^+) = 0$

Hence, $\frac{dv_C}{dt} \Big|_{0^+} = k_1 s_1 + k_2 s_2$

From state equations: $\sqrt{2} \cdot \frac{di_L}{dt} + v_C + i_L = 1$
 $\sqrt{2} \cdot \frac{dv_C}{dt} + v_C - i_L = 0$

At $t = 0^+$:

$$\sqrt{2} \times (k_1 s_1 + k_2 s_2) + v_C(0^-) - i_L(0^+) = 0$$

$$k_1 s_1 + k_2 s_2 = 0$$

(7)

Equations: $k_1 + k_2 + \frac{1}{2} = 0$
 $k_1 \cdot \frac{-1+j}{\sqrt{2}} + k_2 \cdot \frac{-1-j}{\sqrt{2}} = 0$ }

$k_1 + k_2 = -\frac{1}{2}$
 $-(k_1 + k_2) + j(k_1 - k_2) = 0$ }

$$k_1 + k_2 = -\frac{1}{2}$$

Hence, $-(-\frac{1}{2}) + j(k_1 - k_2) = 0$

Then: $k_1 + k_2 = -\frac{1}{2}$

$$k_1 - k_2 = \frac{j}{2}$$

$$-\frac{1}{2}j = -\frac{j}{2} \times j^2 = \frac{j}{2}$$

$$k_1 + k_2 = -1/2$$

$$k_1 - k_2 = \frac{1}{2} \times j$$

$$2k_1 = \frac{-1+j}{2} ; k_1 = \frac{-1+j}{4}$$

$$k_2 = -\frac{1}{2} - \left(\frac{-1+j}{4}\right)$$

$$k_2 = \frac{-1-j}{4}$$

Hence,

Recall:
 $S_{1/2} = \frac{-1+j}{\sqrt{2}}$

$$V_C(t) = \frac{-1+j}{4} e^{\frac{-1+j}{\sqrt{2}}t} + \frac{-1-j}{4} e^{\frac{-1-j}{\sqrt{2}}t} + 1/2$$

$$V_C(t) = \frac{1}{4} \cdot (-1+j) e^{-t/\sqrt{2}} \cdot (\cos \frac{t}{\sqrt{2}} + j \sin \frac{t}{\sqrt{2}}) + \frac{1}{4} (-1-j) e^{-t/\sqrt{2}} \cdot (\cos \frac{t}{\sqrt{2}} - j \sin \frac{t}{\sqrt{2}}) + 1/2$$

$$V_C(t) = \frac{1}{4} e^{-t/\sqrt{2}} \cdot (-\cos \frac{t}{\sqrt{2}} - j \sin \frac{t}{\sqrt{2}} + j \cos \frac{t}{\sqrt{2}} - \sin \frac{t}{\sqrt{2}} - \cos \frac{t}{\sqrt{2}} + j \sin \frac{t}{\sqrt{2}} - j \cos \frac{t}{\sqrt{2}} - \sin \frac{t}{\sqrt{2}}) + 1/2$$

$$V_C(t) = \frac{1}{4} e^{-t/\sqrt{2}} \cdot 2 \cdot (-\cos \frac{t}{\sqrt{2}} - \sin \frac{t}{\sqrt{2}}) + \frac{1}{2}$$

$$V_C(t) = \frac{1}{2} \cdot \left(1 - e^{-\frac{t}{\sqrt{2}}} (\cos \frac{t}{\sqrt{2}} + \sin \frac{t}{\sqrt{2}})\right) u(t)$$

Note:

$$\cos t/\sqrt{2} + \sin t/\sqrt{2} = \sin\left(\frac{\pi}{2} - \frac{t}{\sqrt{2}}\right) + \sin \frac{t}{\sqrt{2}}$$

$$= 2 \sin \frac{\pi}{4} \times \cos\left(\frac{\pi}{4} - \frac{t}{\sqrt{2}}\right)$$

$$\sin \alpha + \sin \beta =$$

$$= 2 \sin \frac{\alpha + \beta}{2} \cdot \cos \frac{\alpha - \beta}{2}$$

$$= 2 \times \frac{\sqrt{2}}{2} \cdot \cos\left(\frac{\pi}{4} - \frac{t}{\sqrt{2}}\right)$$

$$= \sqrt{2} \cos\left(\frac{\pi}{4} - \frac{t}{\sqrt{2}}\right)$$

$$= \sqrt{2} \cos\left(\frac{t}{\sqrt{2}} - \frac{\pi}{4}\right)$$

$$\cos(-\alpha) = \cos \alpha$$

$$= \sqrt{2} \cdot \sin\left(\frac{\pi}{2} - \frac{t}{\sqrt{2}} + \frac{\pi}{4}\right)$$

$$= \sqrt{2} \cdot \sin\left(\frac{3\pi}{4} - \frac{t}{\sqrt{2}}\right)$$

$$= \sqrt{2} \cdot \sin\left(\frac{t}{\sqrt{2}} + \frac{\pi}{4}\right)$$

$$\sin \alpha = \sin(\pi - \alpha)$$

Hence,

$$v_c(t) = \frac{1}{2} \left(1 - e^{-t/\sqrt{2}} \times \sqrt{2} \times \cos\left(\frac{t}{\sqrt{2}} - \frac{\pi}{4}\right)\right)$$

$$= \frac{1}{2} \left(1 - e^{-t/\sqrt{2}} \times \sqrt{2} \times \sin\left(\frac{t}{\sqrt{2}} + \frac{\pi}{4}\right)\right)$$

*

Another approach:

$$s = \frac{-1 \pm j}{\sqrt{2}}$$

$$v_c(t) = e^{-t/\sqrt{2}} \cdot \left(A_1 \sin \frac{t}{\sqrt{2}} + A_2 \cos \frac{t}{\sqrt{2}}\right) + \frac{1}{2}$$

$$v_c(0+) = 0 ; v_c'(0+) = A_2 + \frac{1}{2}$$

$$\text{Hence ; } A_2 = -\frac{1}{2}$$

$$\frac{dv_c}{dt} = -\frac{1}{\sqrt{2}} e^{-t/\sqrt{2}} \cdot \left(A_1 \sin \frac{t}{\sqrt{2}} + A_2 \cos \frac{t}{\sqrt{2}}\right) +$$

$$e^{-t/\sqrt{2}} \cdot \left(A_1 \cdot \frac{1}{\sqrt{2}} \cdot \cos \frac{t}{\sqrt{2}} - A_2 \cdot \frac{1}{\sqrt{2}} \cdot \sin \frac{t}{\sqrt{2}}\right)$$

$$\left. \frac{dv_c}{dt} \right|_{0^+} = 0$$

hence:
$$-\frac{1}{\sqrt{2}} A_2 + \frac{A_1}{\sqrt{2}} = 0 \Rightarrow A_1 = A_2$$

$$A_2 = -1/2$$

$$v_c(t) = e^{-t/\sqrt{2}} \cdot \left(-\frac{1}{2} \sin t/\sqrt{2} - \frac{1}{2} \cos t/\sqrt{2} \right) + 1/2$$

As before:
$$v_c(t) = \frac{1}{2} \left(1 - e^{-t/\sqrt{2}} \cdot (\cos t/\sqrt{2} + \sin t/\sqrt{2}) \right) u(t)$$

**

yet another approach:

$$v_c(t) = e^{-t/\sqrt{2}} \cdot A_3 \cdot \cos \left(\frac{t}{\sqrt{2}} - \theta \right) + 1/2$$

$$v_c(0^+) = A_3 \cos(-\theta) + 1/2$$

$$A_3 \cos \theta + 1/2 = 0$$

$$A_3 \cos \theta = -1/2$$

$$\frac{dv_c}{dt} = -\frac{1}{\sqrt{2}} e^{-t/\sqrt{2}} \cdot A_3 \cos \left(\frac{t}{\sqrt{2}} - \theta \right) + e^{-t/\sqrt{2}} \cdot A_3 \cdot \frac{1}{\sqrt{2}} \cdot (-\sin \left(\frac{t}{\sqrt{2}} - \theta \right))$$

$$\left. \frac{dv_c}{dt} \right|_{0^+} = -\frac{1}{\sqrt{2}} \cdot A_3 \cos(-\theta) + \frac{1}{\sqrt{2}} A_3 \cdot \sin \theta$$

$$-\frac{1}{\sqrt{2}} A_3 \cos(-\theta) + \frac{1}{\sqrt{2}} A_3 \sin \theta = 0$$

$$\tan \theta = 1; \quad \theta = \pi/4$$

Then:
$$A_3 \cos \theta = -1/2; \quad A_3 \cos \frac{\pi}{4} = -1/2$$

$$A_3 \cdot \frac{\sqrt{2}}{2} = -1/2; \quad A_3 = -\frac{1}{\sqrt{2}}$$

Hence:


$$V_C(t) = e^{-\frac{t}{\sqrt{2}}} \times \left(-\frac{1}{\sqrt{2}}\right) \cos\left(\frac{t}{\sqrt{2}} - \frac{\pi}{4}\right) + \frac{1}{2}$$

$$V_C(t) = \frac{1}{2} \cdot \left(1 - e^{-t/\sqrt{2}} \times \sqrt{2} \times \cos\left(\frac{t}{\sqrt{2}} - \frac{\pi}{4}\right)\right) u(t)$$

or, equivalently:


$$V_C(t) = \frac{1}{2} \left(1 - e^{-t/\sqrt{2}} \times \sqrt{2} \times \cos\left(\frac{t}{\sqrt{2}} - \frac{\pi}{4}\right)\right) u(t)$$

4

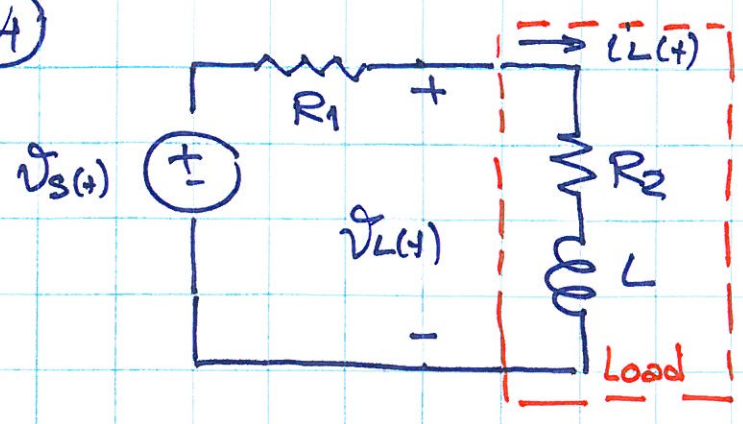

$R_1 = 50 \Omega$
 $R_2 = 350 \Omega$
 $L = 1 \text{ H}$

Steady-state phasors

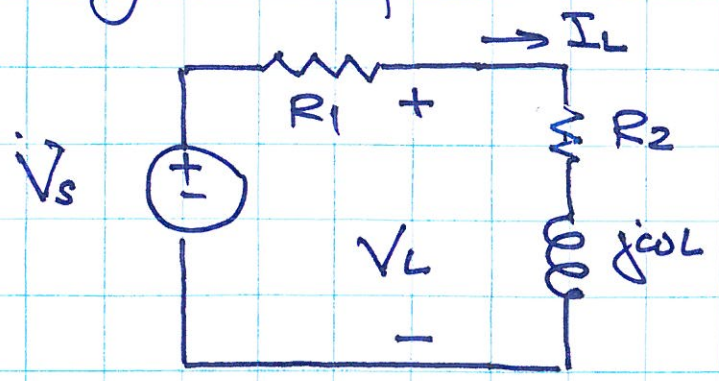

Since $v_s(t) = \sqrt{2} 100 \cos(300t + 30^\circ)$

$\underline{V}_s = 100 e^{j\pi/6}$

$\frac{\pi}{6} = 30^\circ$

$\omega = 300$

$V_{s\text{eff}} = 100$

$V_{s\text{max}} = \sqrt{2} 100$

(a) $\underline{Z}_L = R_2 + j\omega L$

$\underline{Z}_L = 350 + j \cdot 300 \times 1$

$\underline{Z}_L = 350 + j300$

$\underline{Z} = R_1 + \underline{Z}_L \quad ; \quad \underline{Z} = 50 + 350 + j300$

$\underline{Z} = 400 + j300$

$$\underline{I}_L = \frac{V_s}{\underline{Z}}$$

$$\underline{I}_L = \frac{100 e^{j4/6}}{400 + j300}$$

Note that: $\underline{Z} = 400 + j300$

$$\underline{Z} = \sqrt{400^2 + 300^2} \cdot e^{j \arctan \frac{300}{400}}$$

$$\underline{Z} = 500 e^{j \arctan 3/4}$$

$$\underline{Z} = 500 e^{j36.87^\circ}$$

Hence: $\underline{I}_L = \frac{100 e^{j30^\circ}}{500 e^{j36.87^\circ}}$

$$\underline{I}_L = \frac{1}{5} e^{j(-6.87^\circ)}$$

$$i_L(t) = \sqrt{2} \times \frac{1}{5} \cdot \cos(300t - 6.87^\circ)$$

(b): Complex power: $\underline{S}_L = V_L \cdot \underline{I}_L^*$ ← complex-conjugate

$$\underline{S}_L = \underline{Z}_L \cdot \underline{I}_L \cdot \underline{I}_L^*$$

$$\underline{S}_L = (310 + j300) \cdot \frac{1}{5} e^{j(-6.87^\circ)} \cdot \frac{1}{5} e^{j(6.87^\circ)}$$

$$\underline{S}_L = (310 + j300) \times \frac{1}{25} \quad \underline{S}_L = 14 + j12 \text{ (VA)}$$

Average power: $P_L = 14 \text{ (W)}$