
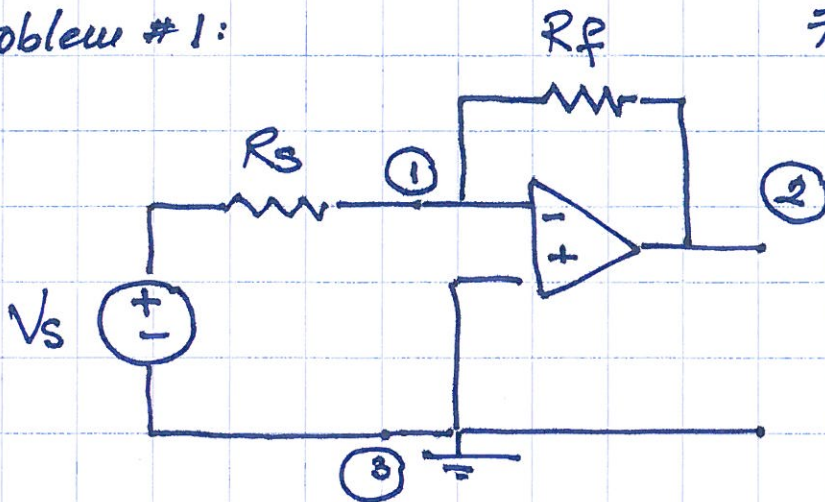



Problem #1:

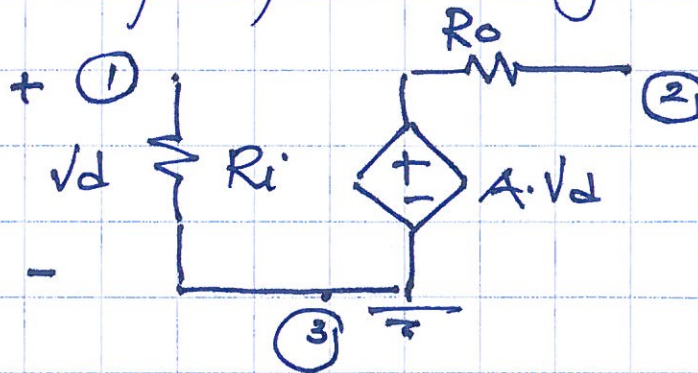


Replace the op-amp with the given model:



The circuit becomes:

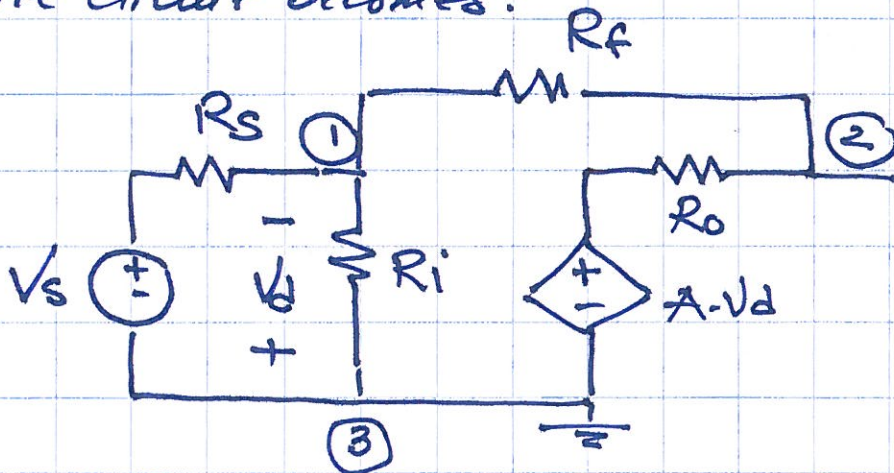


Therstein equivalent:

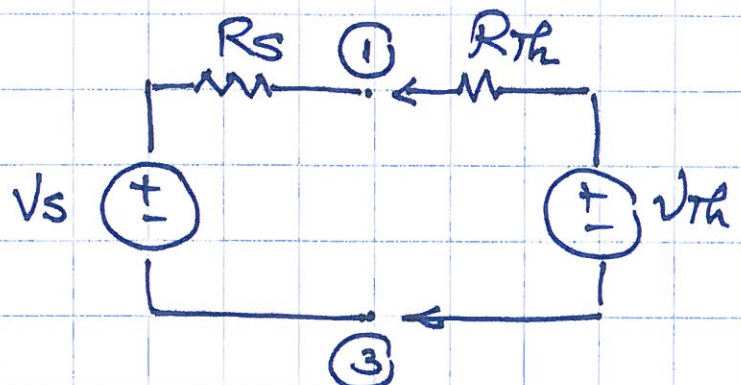

Thevenin equivalent Loading Left to right
between nodes ① and ③.


②

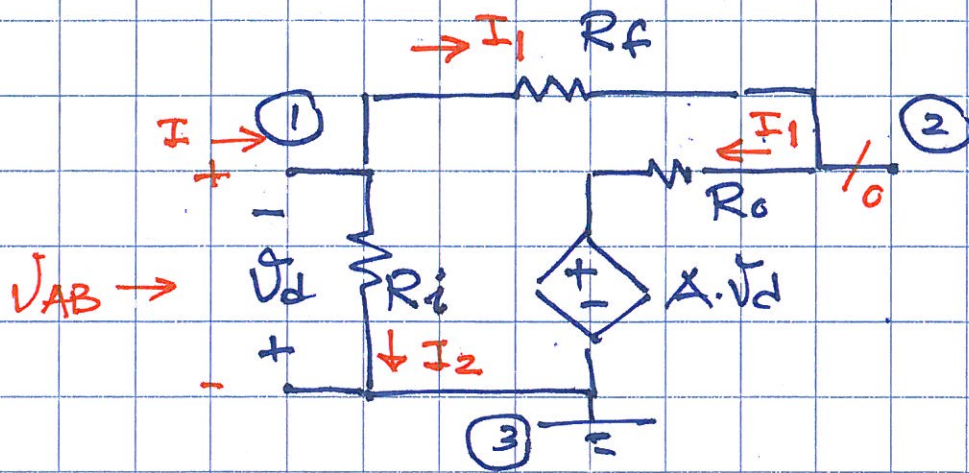

$$R_{th} = ?$$

$$V_{th} = ?$$

KCL ①: $I - I_1 - I_2 = 0$

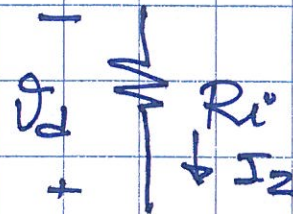

Ohm's Law: $I_2 = -V_d / R_i$

Hence,

$$I_1 - \frac{V_d}{R_i} = I \quad (1)$$


KVL: $V_{AB} - R_f \cdot I_1 - R_o \cdot I_1 - A \cdot V_d = 0$

$$V_{AB} = (R_f + R_o) \cdot I_1 + A \cdot V_d$$

$$V_{AB} = -V_d \quad \text{or} \quad V_d = -V_{AB}$$

Hence,

$$V_{AB} = (R_f + R_o) I_1 - A V_{AB}$$

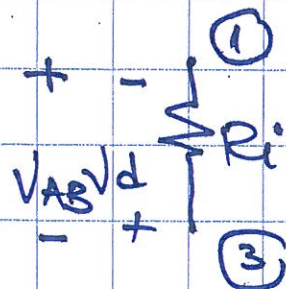

3

$$V_{AB}(1+A) = (R_f + R_o) \cdot I_1$$

$$V_{AB} = \frac{R_f + R_o}{1+A} \cdot I_1 \quad (2)$$

$$R_{Th} = \frac{V_{AB}}{I}$$

From (1): $I = I_1 - \frac{V_d}{R_i}$ Recall that $V_d = -V_{AB}$

$$I = I_1 + \frac{V_{AB}}{R_i}$$

$$I = I_1 + \frac{R_f + R_o}{1+A} \cdot I_1 \cdot \frac{1}{R_i}$$

$$I = \left(1 + \frac{R_f + R_o}{(1+A)R_i}\right) \cdot I_1 \quad (3)$$

From (2) and (3):

$$R_{Th} = \frac{V_{AB}}{I} \Rightarrow R_{Th} = \frac{R_f + R_o}{1+A} \cdot I_1 \cdot \frac{1}{\left(1 + \frac{R_f + R_o}{(1+A)R_i}\right) \cdot I_1}$$

$$R_{Th} = \frac{R_f + R_o}{1+A} \cdot \frac{(1+A) \cdot R_i}{(1+A) \cdot R_i + R_f + R_o}$$

$$R_{Th} = \frac{R_i(R_f + R_o)}{(1+A) \cdot R_i + R_f + R_o}$$


Simplify: $R_{Th} = \frac{1}{\frac{1+A}{R_f + R_o} + 1/R_i}$

$V_{th} = ?$


Note that $V_{th} = 0$

100% seen between ① and ③ is ϕ (no sources are present)

Hence:

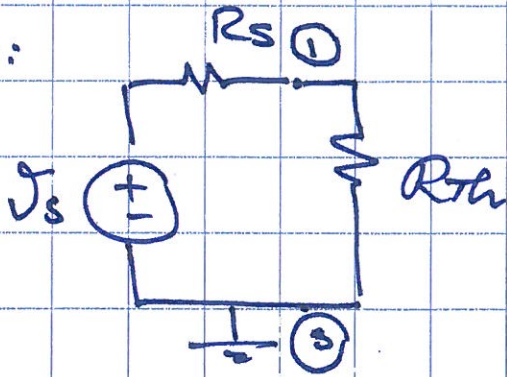


if the op-amp is ideal:

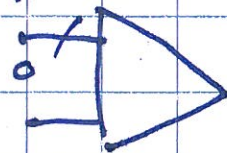

$R_i = \infty$
 $R_o = 0$
 $A = \infty$

$$R_{th} = \frac{1}{\frac{1+\infty}{R_f + 0} + \frac{1}{\infty}}$$


$R_{th} = 0$

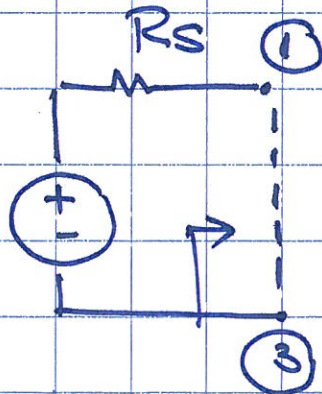

virtual short circuit

5

Problem #2:

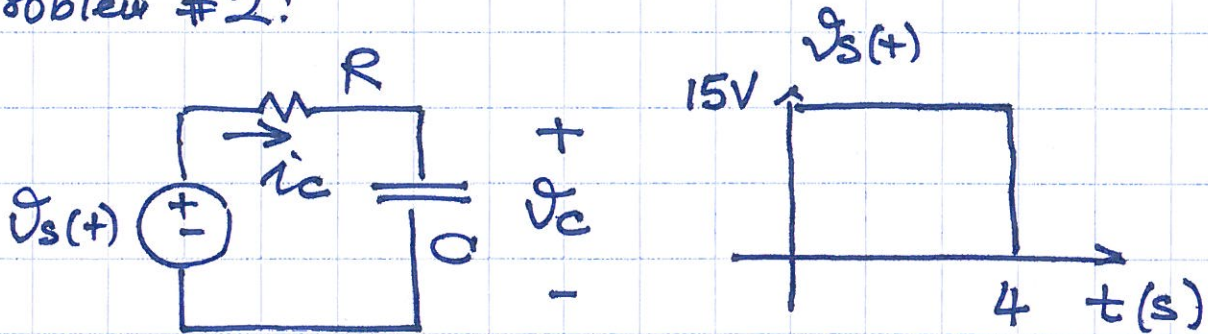

$$v_s(t) = 15(u(t) - u(t-4)) \text{ V}$$

$$R = 200 \text{ k}\Omega$$

$$C = 10 \mu\text{F}$$

$$v_c(0^-) = 0$$

State equations:

$$\text{KVL: } v_s(t) - R \cdot i_c - v_c = 0$$

$$i_c = C \frac{dv_c}{dt}$$

$$R \cdot C \frac{dv_c}{dt} + v_c = v_s$$

$$\frac{dv_c}{dt} + \frac{1}{RC} \cdot v_c = \frac{1}{RC} \cdot v_s$$

$$RC = 200 \times 10^3 \times 10 \times 10^{-6}$$

$$RC = 2$$

$$\frac{dv_c}{dt} + \frac{1}{2} \cdot v_c = \frac{1}{2} \cdot v_s$$

$$\text{State equations: } \frac{dv_c}{dt} + \frac{1}{2} \cdot v_c = \frac{15}{2} \quad 0 < t < 4$$

$$\frac{dv_c}{dt} + \frac{1}{2} \cdot v_c = 0 \quad t > 4$$

$0 < t < 4$:

6

$$\frac{dv_c}{dt} + \frac{1}{2} \cdot v_c = \frac{15}{2}$$

$$v_c = v_{ch} + v_{cp}$$

Homogeneous solutions:

$$\frac{dv_{ch}}{dt} + \frac{1}{2} \cdot v_{ch} = 0$$

$$v_{ch} = k e^{st}$$

k : constant

$$\frac{dv_{ch}}{dt} = k s e^{st}$$

s : constant

$$k \cdot s \cdot e^{st} + \frac{1}{2} \cdot k \cdot e^{st} = 0 \quad ; \quad k \neq 0$$

$$e^{st} \neq 0$$

$$s = -1/2$$

$$v_{ch} = k e^{-t/2}$$

Particular solution:

$$v_{cp} = A \quad (\text{right hand side is a constant})$$

$$\frac{dv_{cp}}{dt} = 0$$

$$0 + \frac{1}{2} \cdot A = \frac{15}{2} \quad A = 15$$

$$\text{Complete solution: } v_c = k e^{-t/2} + 15$$

$$v_c(0^-) = 0 \quad (\text{given})$$

$$v_c(0^+) = 0 \quad \text{Hence: } 0 = k + 15 \quad ; \quad k = -15$$

$$v_c = 15(1 - e^{-t/2}) \quad 0 < t < 4$$

At $t = 4$ s:

(7)

$$V_C(4^-) = 15(1 - e^{-4/2})$$

$$V_C(4^-) = 15(1 - e^{-2})$$

$$V_C(4^+) = 15(1 - e^{-2})$$

For $t > 4$ s

$$\frac{dV_C}{dt} + \frac{1}{2} V_C = 0$$

$$V_C = K_1 \cdot e^{-t/2}$$

the same as the
homogeneous
differential equation
for $0 < t < 4$

Let $t' = t - 4$

$$V_C = K_1 e^{-t'/2}$$

$$V_C(0^+) = K_1 \quad \text{in time } t':$$

$$V_C(0^+) = V_C(0^-)$$

$$\equiv V_C(4^-)$$

$$= 15(1 - e^{-2})$$

$$K_1 = 15(1 - e^{-2})$$


Hence:

$$V_C = 15(1 - e^{-2}) e^{-t'/2}$$

$$V_C = 15(1 - e^{-2}) e^{-\frac{t-4}{2}} \quad t > 4$$

$$V_C = 15 \cdot (1 - e^{-2}) \cdot e^2 \cdot e^{-t/2}$$
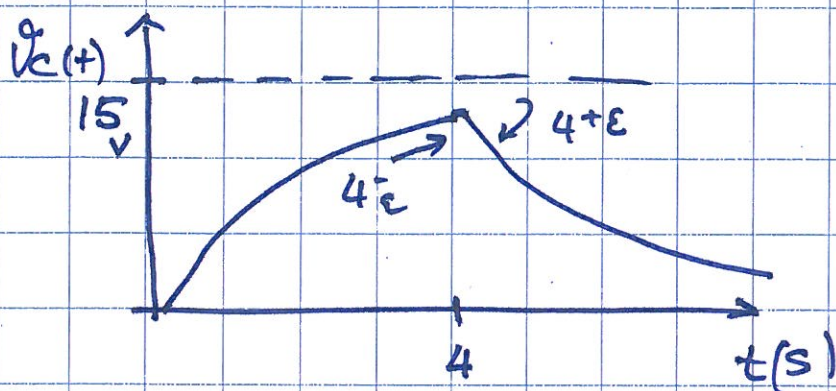
$$V_C = 15(e^2 - 1) e^{-t/2} \quad t > 4$$



$$v_c(t) = \begin{cases} 0 & t < 0 \\ 15(1 - e^{-t/2}) & 0 < t < 4 \\ 15(e^2 - 1)e^{-t/2} & t > 4 \end{cases}$$

Current:

$$i_c = C \frac{dv_c}{dt}$$

$$i_c = 10 \times 10^{-6} \cdot \frac{d}{dt} v_c$$

$$i_c = 0 \quad t < 0$$

$$i_c = 10 \times 10^{-6} \cdot \frac{d}{dt} (15(1 - e^{-t/2})) \quad 0 < t < 4$$

$$i_c = 15 \times 10^{-5} \cdot \left(\frac{1}{2}\right) e^{-t/2}$$

$$i_c = 7.5 \times 10^{-5} e^{-t/2}$$

$$i_c = 75 \times 10^{-6} \cdot e^{-t/2} \quad 0 < t < 4$$

9

$t > 4$

$$i_c = 10 \times 10^{-6} \cdot \frac{d}{dt} (15(e^2 - t)e^{-t/2})$$

$$i_c = 10^{-5} \cdot 15 \cdot (e^2 - 1) \cdot (-1/2) \cdot e^{-t/2}$$


$$i_c = -75(e^2 - 1) \cdot e^{-t/2} \times 10^{-6} \quad t > 4$$

Approximately, at $t = 4$

$$\begin{aligned} i_c(4^+) &= -75 \cdot (e^2 - 1) \cdot e^{-2} \times 10^{-6} \\ &= -75 \cdot (1 - e^{-2}) \times 10^{-6} \end{aligned}$$


$$\text{since } 15(1 - e^{-2}) \approx 13$$
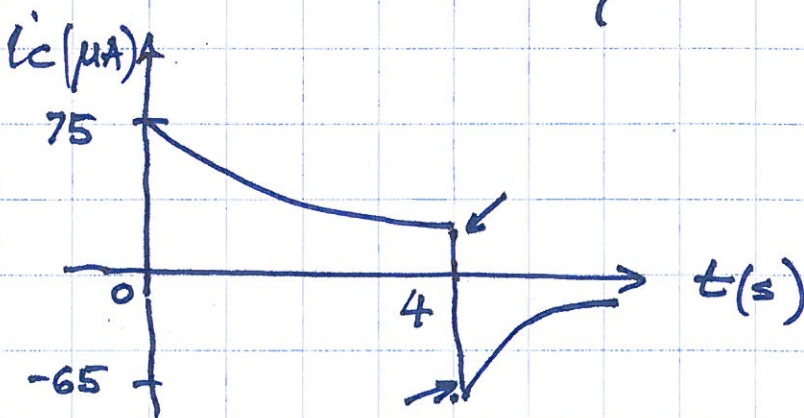
$$\begin{aligned} i_c(4^+) &= -75 \cdot \frac{13}{15} \times 10^{-6} \\ &\approx -65 \mu\text{A} \end{aligned}$$



Problem
#3

10

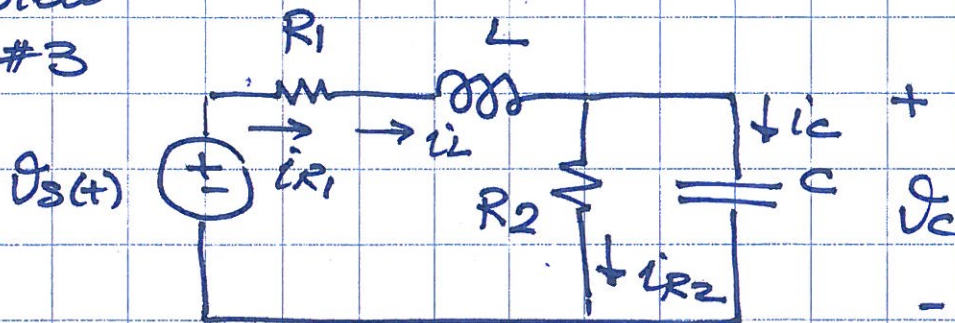

$$R_1 = 1 \Omega$$

$$v_s(t) = u(t)$$

$$R_2 = 1 \Omega$$

$$L = 1 \text{ H}$$

$$C = 1 \text{ F}$$

KCL: $i_{R1} = i_L$

$$i_L = i_{R2} + i_C \quad ; \quad i_{R2} = i_L - i_C$$

KVL: $v_s - R_1 i_L - v_L - v_C = 0$

$$v_C - R_2 i_{R2} = 0$$

$$v_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{dv_C}{dt}$$

Hence: $R_1 i_L + L \frac{di_L}{dt} + v_C = v_s$

$$v_C - R_2 (i_L - i_C) = 0$$

$$L \cdot \frac{di_L}{dt} + R_1 \cdot i_L + v_C = v_S$$

(11)

$$-R_2 \cdot i_L + R_2 \cdot i_C + v_C = 0$$

\uparrow
 $C \frac{dv_C}{dt}$

State equations:

$$L \cdot \frac{di_L}{dt} + R_1 \cdot i_L + v_C = v_S$$

$$R_2 \cdot C \cdot \frac{dv_C}{dt} + v_C - R_2 \cdot i_L = 0$$

or,

$$\frac{di_L}{dt} + \frac{R_1}{L} \cdot i_L + \frac{1}{L} \cdot v_C = \frac{1}{L} \cdot v_S \quad (1)$$

$$\frac{dv_C}{dt} + \frac{1}{R_2 C} \cdot v_C - \frac{1}{C} \cdot i_L = 0 \quad (2)$$

2nd order differential equation:

From (2):

$$i_L = C \frac{dv_C}{dt} + \frac{1}{R_2} \cdot v_C$$

Substitute into (1) gives:

$$\frac{d}{dt} \left(C \cdot \frac{dv_C}{dt} + \frac{1}{R_2} \cdot v_C \right) + \frac{R_1}{L} \left(C \frac{dv_C}{dt} + \frac{1}{R_2} \cdot v_C \right) + \frac{1}{L} \cdot v_C = \frac{1}{L} \cdot v_S$$

$$C \cdot \frac{d^2 v_C}{dt^2} + \frac{1}{R_2} \cdot \frac{dv_C}{dt} + \frac{R_1 C}{L} \cdot \frac{dv_C}{dt} + \frac{R_1}{L R_2} \cdot v_C + \frac{1}{L} \cdot v_C = \frac{1}{L} \cdot v_S$$

$$\frac{d^2 v_c}{dt^2} + \left(\frac{1}{CR_2} + \frac{R_1}{L} \right) \frac{dv_c}{dt} + \left(\frac{R_1}{LCR_2} + \frac{1}{LC} \right) v_c = \frac{1}{LC} v_s \quad (12)$$

Substitute numerical values:

$$\frac{d^2 v_c}{dt^2} + \left(\frac{1}{\sqrt{2}} + \frac{1}{\sqrt{2}} \right) \frac{dv_c}{dt} + \left(\frac{1}{2} + \frac{1}{2} \right) v_c = \frac{1}{2} \cdot 1$$

Recall:

$$v_s(t) = u(t)$$

$$v_s(t) = 1$$

for $t > 0$

$$\frac{d^2 v_c}{dt^2} + \sqrt{2} \cdot \frac{dv_c}{dt} + v_c = \frac{1}{2}$$

characteristic equation:

$$s^2 + \sqrt{2}s + 1 = 0$$

$$s_{1/2} = -\frac{\sqrt{2}}{2} \pm \sqrt{\left(\frac{\sqrt{2}}{2}\right)^2 - 1}$$

$$s_{1/2} = -\frac{\sqrt{2}}{2} \pm \sqrt{\frac{1}{2} - 1}$$

$$s_{1/2} = -\frac{\sqrt{2}}{2} \pm j \cdot \frac{\sqrt{2}}{2} ; s_{1/2} = \frac{-1 \pm j}{\sqrt{2}}$$

$$v_c(t) = v_{ca}(t) + v_{cp}(t)$$

$$v_{ca}(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$\text{or } v_{ca}(t) = k_1 e^{\frac{-1+j}{\sqrt{2}} t} + k_2 e^{\frac{-1-j}{\sqrt{2}} t}$$

$$v_{ca}(t) = e^{-t/\sqrt{2}} \cdot (k_1 e^{jt/\sqrt{2}} + k_2 e^{-jt/\sqrt{2}})$$

$$v_{ca}(t) = e^{-t/\sqrt{2}} \cdot (k_1 \cos t/\sqrt{2} + j \cdot k_1 \sin t/\sqrt{2} + k_2 \cos t/\sqrt{2} - j k_2 \sin t/\sqrt{2})$$

$$v_{ca}(t) = e^{-t/\sqrt{2}} \cdot (A \cos t/\sqrt{2} + B \sin t/\sqrt{2})$$

$$v_p(t) = K \text{ (constant because } v_s(t) = 1 \cdot u(t))$$

$$\frac{d v_p(t)}{dt} = 0; \quad \frac{d^2 v_p(t)}{dt^2} = 0$$

From the 2nd order differential equation:

$$0 + \sqrt{2} \cdot 0 + A = 1/2$$
$$A = 1/2$$

Hence:

$$v_c(t) = e^{-t/\sqrt{2}} \cdot (A \cos t/\sqrt{2} + B \sin t/\sqrt{2}) + 1/2$$

$$v_c(0^-) = 0 \text{ Hence, } A + 1/2 = 0$$

$$v_c(0^+) = 0 \quad A = -1/2$$

From the differential equation:

$$\frac{dv_c}{dt} + \frac{1}{\sqrt{2}L} \cdot v_c - \frac{1}{C} \cdot i_L = 0$$

$$v_c(0^-) = 0$$
$$i_L(0^-) = 0$$

$$v_c(0^+) = 0; \quad i_L(0^+) = 0 \Rightarrow \frac{dv_c}{dt} \Big|_{0^+} = 0$$

$$\frac{dv_c}{dt} = -\frac{1}{\sqrt{2}} e^{-\frac{t}{\sqrt{2}}} \left(A \cos \frac{t}{\sqrt{2}} + B \sin \frac{t}{\sqrt{2}} \right) + e^{-\frac{t}{\sqrt{2}}} \left(A \cdot \frac{1}{\sqrt{2}} \cdot (-\sin \frac{t}{\sqrt{2}}) + B \cdot \frac{1}{\sqrt{2}} \cdot \cos \frac{t}{\sqrt{2}} \right) + 0$$

$$\frac{dv_c}{dt} \Big|_{0^+} = -\frac{1}{\sqrt{2}} A + \frac{1}{\sqrt{2}} B$$

Since $\frac{dv_c}{dt} \Big|_{0^+} = 0 \Rightarrow A = B$; Recall that $A = -1/2$
 Hence, $B = -1/2$

$$v_c(t) = e^{-\frac{t}{\sqrt{2}}} \cdot \left(-\frac{1}{2} \cos \frac{t}{\sqrt{2}} - \frac{1}{2} \sin \frac{t}{\sqrt{2}} \right) + \frac{1}{2} \quad t > 0$$

$$v_c(t) = -\frac{1}{2} e^{-\frac{t}{\sqrt{2}}} \cdot \left(\cos \frac{t}{\sqrt{2}} + \sin \frac{t}{\sqrt{2}} \right) + \frac{1}{2}$$

Another form:

$$\cos \frac{t}{\sqrt{2}} + \sin \frac{t}{\sqrt{2}} = \sqrt{2} \sin \left(\frac{t}{\sqrt{2}} + \theta \right)$$

Find V and θ : $= \sqrt{2} \sin \frac{t}{\sqrt{2}} \cos \theta + \sqrt{2} \cos \frac{t}{\sqrt{2}} \sin \theta$

At $t=0$: $1 = \sqrt{2} \cos \theta$; $1 = \sqrt{2} \sin \theta$

$\tan \theta = 1$; $\theta = \pi/4$


Hence, $\sqrt{2} \cos \theta = 1$; $\sqrt{2} \sin \theta = 1$

$$v_c(t) = -\frac{1}{2} \cdot e^{-\frac{t}{\sqrt{2}}} \cdot \sqrt{2} \cdot \sin \left(\frac{t}{\sqrt{2}} + \frac{\pi}{4} \right) + \frac{1}{2}$$

$$v_c(t) = -\frac{\sqrt{2}}{2} e^{-\frac{t}{\sqrt{2}}} \cdot \sin \left(\frac{t}{\sqrt{2}} + \frac{\pi}{4} \right) + \frac{1}{2}$$

for $t > 0$

Problem #4:

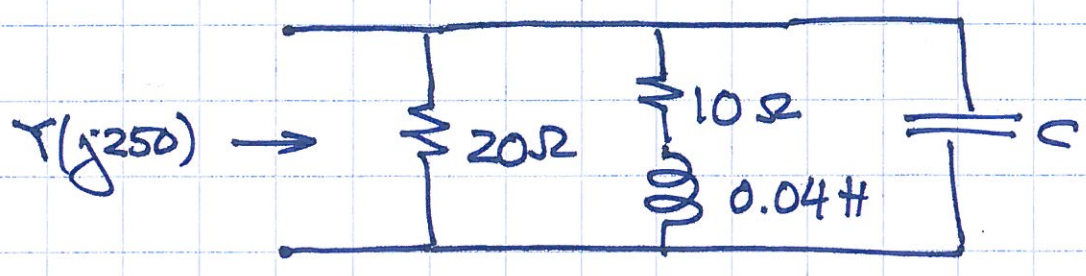

Let $C = 0.6 \mu F$; $Y_{in}(j250) = ?$

$$\omega = 250 \text{ rad/s}$$

$$Y(j\omega) = ?$$

Let:

$$R_1 = 20\Omega$$

$$R_2 = 10\Omega$$

$$L = 0.04 H$$

$$C = 0.6 \times 10^{-3}$$

$$Y(j\omega) = \frac{1}{R_1} + \frac{1}{R_2 + j\omega L} + j\omega C$$

$$Y(j\omega) = \frac{1}{R_1} + \frac{R_2 - j\omega L}{R_2^2 + (\omega L)^2} + j\omega C$$

$$Y(j\omega) = \frac{1}{R_1} + \frac{R_2}{R_2^2 + (\omega L)^2} + j \left(\omega C - \frac{\omega L}{R_2^2 + (\omega L)^2} \right)$$

$$Y(j250) = \frac{1}{20} + \frac{10}{10^2 + (250 \times 0.04)^2} + j \left(250 \times 0.6 \times 10^{-3} - \frac{250 \times 0.04}{10^2 + (250 \times 0.04)^2} \right)$$

$$Y(j250) = \frac{1}{20} + \frac{10}{100 + 100} + j \left(150 \times 10^{-3} - \frac{10}{100 + 100} \right)$$

$$Y(j250) = \frac{1}{20} + \frac{10}{200} + j\left(0.15 - \frac{10}{200}\right)$$

$$Y(j250) = \frac{1}{10} + j\frac{30-10}{200}$$

$$Y(j250) = (0.1 + j0.1) \text{ Siemens}$$

If $Y(j\omega)$ is to be real, then:

$$\omega C - \frac{\omega L}{R_2^2 + (\omega L)^2} = 0 \quad ; \quad \omega = 250 \text{ rad/s}$$

$$\text{or } C = \frac{L}{R_2^2 + (\omega L)^2}$$

$$C = \frac{0.04}{10^2 + (250 \times 0.04)^2}$$

$$C = \frac{0.04}{10^2 + 10^2} \quad ; \quad C = \frac{0.04}{200}$$

$$C = 0.02 \times 10^{-2} \quad ; \quad C = 0.2 \times 10^{-3}$$

$$C = 0.2 \text{ mF}$$