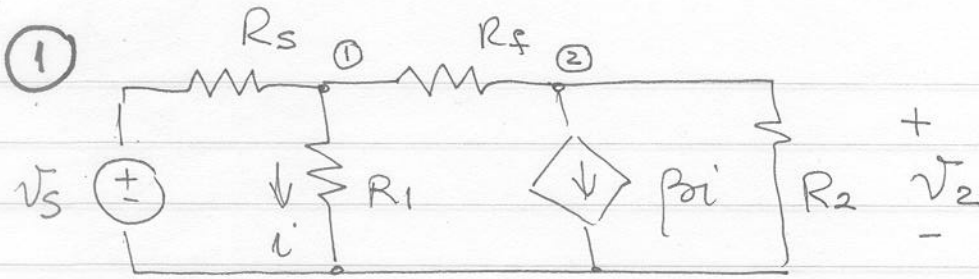


①



$$R_s = 8\Omega$$

$$R_1 = 1\Omega$$

$$R_2 = 5\Omega$$

$$R_f = 30\Omega$$

$$\frac{V_1 - V_s}{R_s} + \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_f} = 0$$

$$\frac{V_2 - V_1}{R_f} + \beta i + \frac{V_2}{R_2} = 0$$

$$V_1 \left( \frac{1}{R_s} + \frac{1}{R_1} + \frac{1}{R_f} \right) - \frac{1}{R_f} \cdot V_2 = \frac{V_s}{R_s}$$

$$-\frac{V_1}{R_f} + V_2 \cdot \left( \frac{1}{R_f} + \frac{1}{R_2} \right) + \beta \cdot \frac{V_1}{R_1} = 0$$

Hence:  $V_1 \cdot \left( -\frac{\beta}{R_1} + \frac{1}{R_f} \right) = V_2 \cdot \left( \frac{1}{R_f} + \frac{1}{R_2} \right)$

$$V_1 = V_2 \cdot \frac{\frac{1}{R_f} + \frac{1}{R_2}}{\frac{1}{R_f} - \beta/R_1}$$

(2)

$$\frac{v_1}{v_2} = \frac{\frac{1}{R_f} + \frac{1}{R_2}}{\frac{1}{R_f} - \beta/R_1}$$

$$v_2 \cdot \frac{\frac{1}{R_f} + \frac{1}{R_2}}{\frac{1}{R_f} - \beta/R_1} \cdot \left( \frac{1}{R_s} + \frac{1}{R_1} + \frac{1}{R_f} \right) - \frac{v_2}{R_f} = \frac{V_s}{R_s}$$

$$\frac{v_2}{R_s} = \frac{1}{\frac{G_f + G_2}{G_f - \beta G_1} \cdot (G_s + G_1 + G_f) - G_f} \cdot \frac{1}{R_s}$$

$$\frac{v_2}{R_s} = \frac{G_f - \beta G_1}{(G_f + G_2)(G_s + G_1 + G_f) - G_f(G_f - \beta G_1)} \cdot G_s$$

$$\frac{v_2}{R_s} = \frac{G_f - \beta G_1}{G_2(G_s + G_1 + G_f) + G_f(G_s + G_1) + \beta G_1 G_f} \times G_s$$

$$G_s = 1/8, G_1 = 1, G_2 = 1/5, G_f = 1/30$$

$$\frac{v_2}{R_s} = \frac{1/30 - \beta}{\frac{1}{5} \cdot \left( \frac{1}{8} + 1 + \frac{1}{30} \right) + \frac{1}{30} \cdot \left( \frac{1}{8} + 1 \right) + \beta \cdot 1 \cdot \frac{1}{30}} \times \frac{1}{8}$$

$$\frac{v_2}{R_s} = \frac{\frac{1}{30} - \beta}{\frac{1}{5} \cdot \frac{45 + 120 + 4}{120} + \frac{1}{30} \cdot \frac{9}{8} + \beta/30} \times \frac{1}{8}$$


$$\frac{V_2}{V_s} = \frac{1/30 - \beta}{\frac{139}{600} + \frac{3}{80} + \frac{\beta}{30}} \cdot \frac{1}{8} / 30$$

$$= \frac{1 - 30\beta}{\frac{139}{20} + \frac{9}{8} + \beta}$$

$$= \frac{40}{8} \cdot \frac{1 - 30\beta}{323 + 40\beta}$$

$$\beta = 0 \Rightarrow \frac{V_2}{V_s} = \frac{5}{323}$$
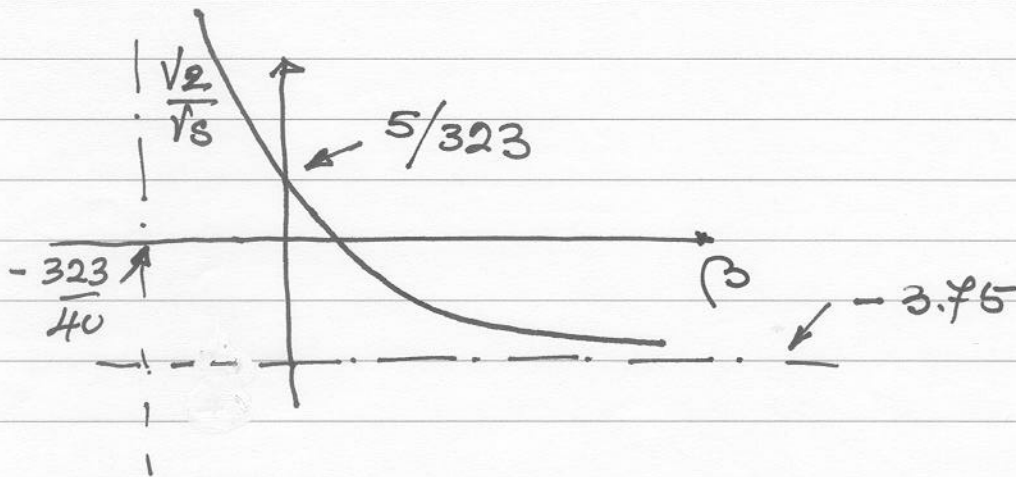
$$\beta \rightarrow \infty \Rightarrow \frac{V_2}{V_s} = -\frac{3}{4} \times 5$$



(4)

$$\frac{V_2}{V_s} = \frac{G_f - \beta \cdot G_1}{G_2(G_s + G_1 + G_f) + G_f \cdot (G_s + G_1) + \beta G_1 \cdot G_f} \cdot G_s$$

$$\frac{V_2}{V_s} = \frac{G_f - \beta}{\frac{1}{5} \cdot \left(\frac{1}{8} + 1 + G_f\right) + G_f \cdot \left(\frac{1}{8} + 1\right) + \beta \cdot G_f} \cdot \frac{1}{8}$$

$G_s = 1/8$   
 $G_1 = 1$   
 $G_2 = 1/5$

Let  $\frac{V_2}{V_s} = 5$

$$5 = \frac{G_f - \beta}{\frac{9}{5} + \frac{8}{5}G_f + 9G_f + 400 \cdot G_f}$$

$$5 = \frac{G_f - \beta}{\frac{9}{5} + \frac{2053G_f}{5}}$$

$$9 + 2053 \cdot G_f = G_f - \beta : \quad \left\{ \begin{array}{l} \beta = 50 \\ \text{Hence:} \end{array} \right.$$

$$2052 \times G_f = -59$$

$$\Rightarrow G_f < 0$$


If:  $\frac{V_2}{V_s} = -5$

Then:  $9 + 2053G_f = \beta - G_f \quad ; \quad \beta = 50$

$$2054 \times G_f = 41 \Rightarrow G_f = \frac{41}{2054}$$

$$R_f = \frac{2054}{41}$$

2

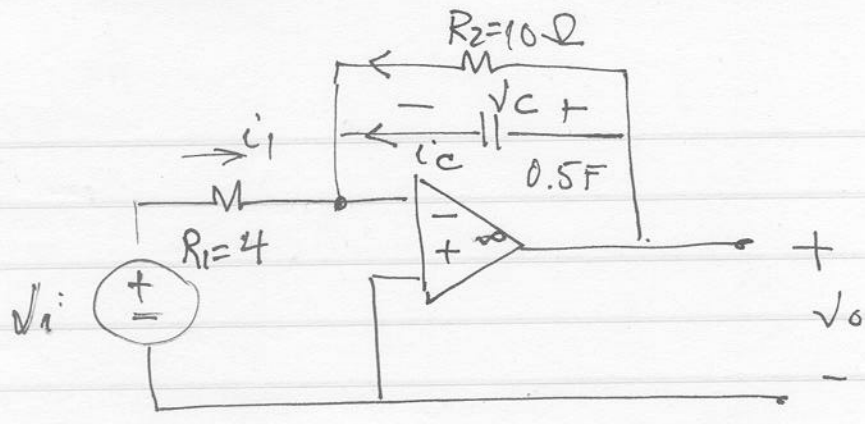

$$i_1 = \frac{v_i}{R_1}$$

$$\frac{v_o}{R_2} + i_c + \frac{v_i}{R_1} = 0$$

$$i_c = C \frac{dv_c}{dt}$$

$$\frac{v_o}{R_2} + C \cdot \frac{dv_c}{dt} + \frac{v_i}{R_1} = 0$$

$$v_c = v_o$$

$$C \cdot \frac{dv_o}{dt} + \frac{v_o}{R_2} + \frac{v_i}{R_1} = 0 \quad \text{Diff. eq.}$$

$$0.5 \cdot \frac{dv_o}{dt} + \frac{v_o}{10} + \frac{v_i}{4} = 0$$

$$\frac{dv_o}{dt} + \frac{v_o}{5} + \frac{v_i}{2} = 0$$

$$\frac{dv_o}{dt} + \frac{v_o}{5} = -\frac{v_i}{2}$$

$$v_{oh} = k e^{-\frac{1}{5}t}$$

$$v_{op} = A$$

$$\frac{A}{5} = -\frac{v_i}{2}$$

$$A = -\frac{5}{2} \cdot v_i$$



$$V_1 = 6 \cdot u(t)$$

$$A = -15 u(t)$$

Hence: 
$$V_0 = \left( K e^{-t/5} - 15 \right) u(t)$$


$$V_0(0^-) = 4$$

$$K e^{-0/5} - 15 = 4 \quad K = 19$$

$$V_0 = \left( 19 e^{-t/5} - 15 \right) u(t)$$

leaky integrator.



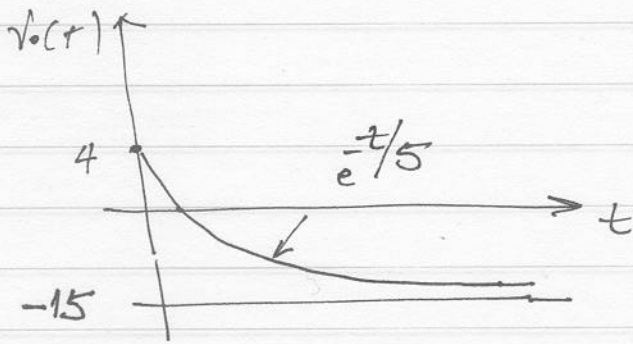
as  $t \rightarrow \infty$   $V_0 = -15 \cdot u(t)$



$$\begin{aligned}
 19 e^{-t/5} &= 15 \\
 e^{-t/5} &= \frac{15}{19} \\
 -t/5 &= \ln \frac{15}{19} \\
 \underline{t_1} &= +5 \ln \frac{19}{15}
 \end{aligned}$$

①

③

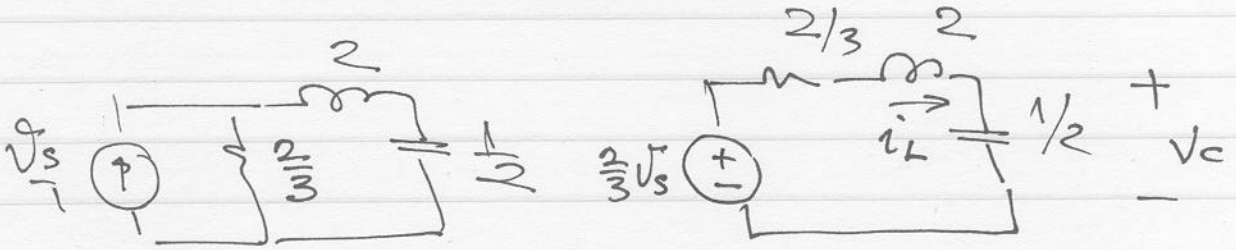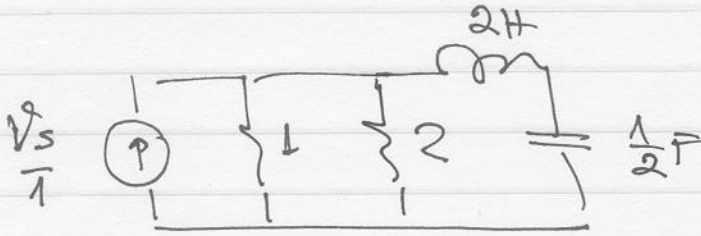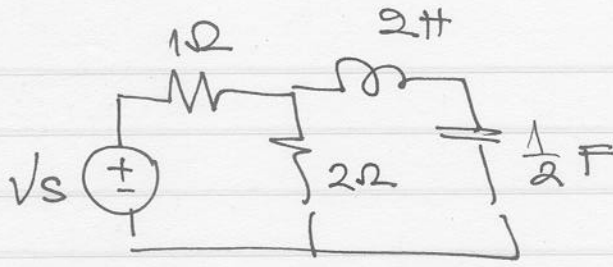

$$\frac{2}{3} V_s - \frac{2}{3} \cdot i_L - 1 \frac{di_L}{dt} - V_C = 0$$

$$2 \frac{di_L}{dt} + \frac{2}{3} i_L + V_C = \frac{2}{3} V_s$$

$$i_C = C \frac{dV_C}{dt}$$

$$\frac{1}{2} \frac{dV_C}{dt} = i_L$$

Hence:  $\frac{2}{3} \frac{di_L}{dt} + \frac{2}{3} i_L + V_C = \frac{2}{3} V_s$

$$\frac{1}{2} \frac{dV_C}{dt} = i_L = 0$$

$$\frac{di_L}{dt} + \frac{1}{3} i_L + \frac{1}{2} V_C = \frac{1}{3} V_s$$

$$\frac{dV_C}{dt} - 2i_L = 0$$

$$\begin{pmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{pmatrix} + \begin{pmatrix} \frac{1}{3} & \frac{1}{2} \\ -2 & 0 \end{pmatrix} \begin{pmatrix} i_L \\ v_C \end{pmatrix} = \begin{pmatrix} \frac{1}{3} \\ 0 \end{pmatrix} v_s$$

$$\begin{pmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{pmatrix} = - \begin{pmatrix} \frac{1}{3} & \frac{1}{2} \\ -2 & 0 \end{pmatrix} \begin{pmatrix} i_L \\ v_C \end{pmatrix} + \begin{pmatrix} \frac{1}{3} \\ 0 \end{pmatrix} v_s$$

$$\dot{x} = Ax + b \cdot v_s$$

$$A = - \begin{pmatrix} \frac{1}{3} & \frac{1}{2} \\ -2 & 0 \end{pmatrix}$$

Then:  $sI - A = \begin{pmatrix} s & 0 \\ 0 & s \end{pmatrix} + \begin{pmatrix} \frac{1}{3} & \frac{1}{2} \\ -2 & 0 \end{pmatrix} = \begin{pmatrix} s + \frac{1}{3} & \frac{1}{2} \\ -2 & s \end{pmatrix}$

$$\det(sI - A) = (s + \frac{1}{3})s + 2 \cdot \frac{1}{2}$$

$$s^2 + \frac{1}{3}s + 1 = 0$$

$$s_{1/2} = -\frac{1}{6} \pm \sqrt{\frac{1}{36} - 1}$$


$$= -\frac{1}{6} \pm \frac{\sqrt{-35}}{6}$$

$$= \frac{-1 \pm j\sqrt{35}}{6}$$


under-damped system.



4

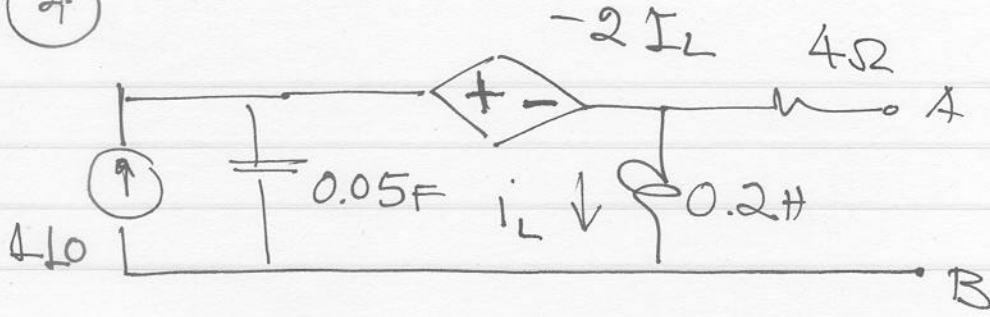

Thevenin's equivalent:

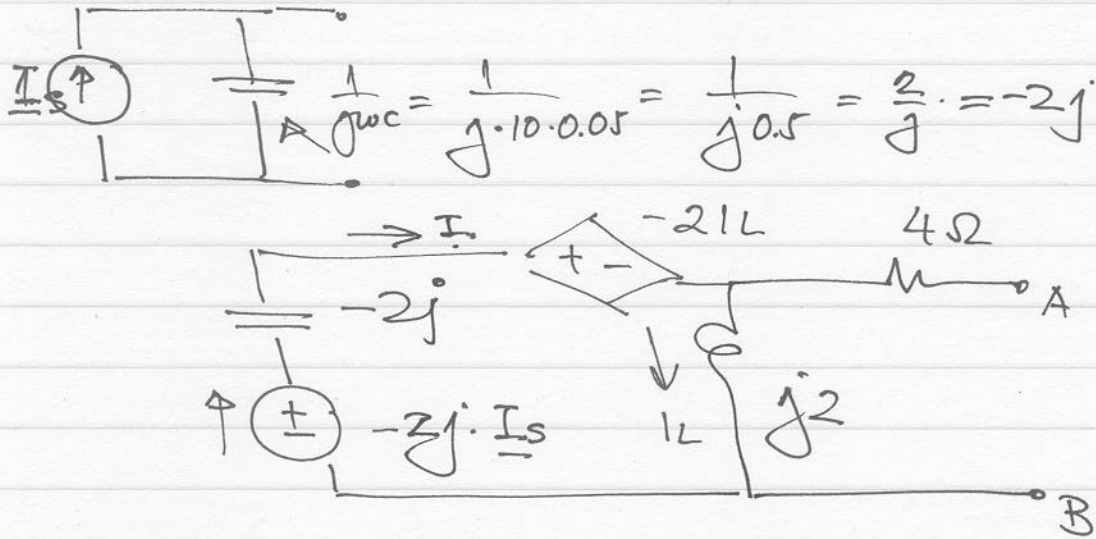

Thevenin's voltage:  $\underline{V_{AB}}$

$$a) \quad (-2j \underline{I_s}) - (-2j \cdot \underline{I}) - (-2 \cdot \underline{I}) - j2 \cdot \underline{I} = 0$$

↑  
 $\underline{I_L} = \underline{I}$


$$-2j \cdot \underline{I_s} + 2j \cdot \underline{I} + 2 \cdot \underline{I} + j2 \cdot \underline{I} = 0$$

$$\underline{I} = j \underline{I_s} \quad \underline{I} = j$$

$$V_{th} = j2 \cdot 5$$

$$V_{oh} = \underline{\underline{-2V}}$$

(6)

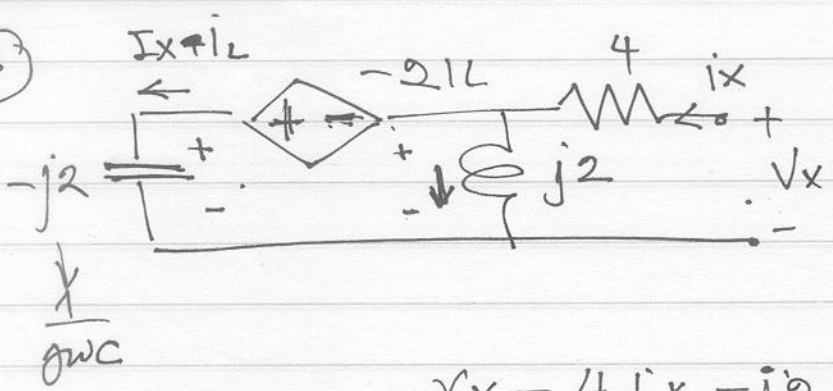

w=10  
C=0.05

$$V_x - 4 \cdot i_x - j2 \cdot i_L = 0$$

$$V_x = 4 \cdot i_x + j2 \cdot i_L$$

$$j2 \cdot i_L - 2 \cdot i_L - (-j2) \cdot (i_x - i_L) = 0$$

$$j2 \cdot i_L - 2 \cdot i_L + j2 \cdot (i_x - i_L) = 0$$

$$-2i_L = -j2i_x$$

$$+j i_x = i_L$$

$$V_x = 4 \cdot i_x + j2 \cdot (j \cdot i_x)$$

$$V_x = 2 \cdot i_x \quad \underline{\underline{Z_{th} = 2}}$$