

$v_{in} = u(t)$  : unit step function

Ideal op-amp:  $v_+ = v_-$   
input current = 0

let  $R_1 = 1\text{k}\Omega$   
 $C_1 = 1\mu\text{F}$

Then:  $v_{in} = R_1 i_1 + v_+$

$v_+ = v_{C_1}$

$i_1 = C_1 \frac{dv_{C_1}}{dt}$

$v_{in} = R_1 \cdot C_1 \cdot \frac{dv_{C_1}}{dt} + v_{C_1}$

$R_1 C_1 \cdot \frac{dv_{C_1}}{dt} + v_{C_1} = v_{in}$

Solution:  $R_1 C_1 \frac{dv_{C_1}}{dt} + v_{C_1} = 0$  ;  $\frac{dv_{C_1}}{dt} = -\frac{1}{R_1 C_1} v_{C_1}$

$v_{C_1} = K_1 e^{-t/R_1 C_1}$

$$V_d^p = A$$

$$A = 1 \quad (\text{unit step function})$$

$$V_{c1} = K_1 e^{-t/R_1 C_1} + 1$$

$$V_{c1}(0^-) = V_{c1}(0^+)$$

$$V_{c1}(0^-) = 0$$

$$K_1 = -1$$

$$V_{c1} = 1 - e^{-t/R_1 C_1}$$

Then:  $V_{out} = R(1+k) \cdot i_2$


$$V_- = R \cdot i_2$$

$$V_- = V_{c1}$$

$$i_2 = \frac{1}{R} \cdot V_{c1}$$


$$R_1 C_1 = 10^{-3}$$

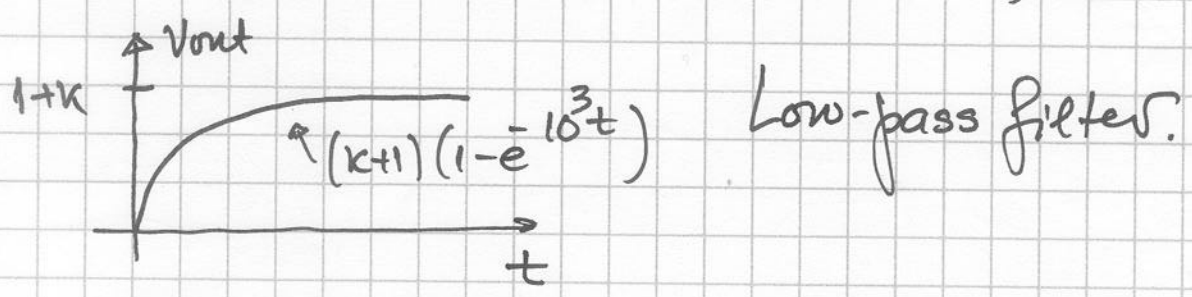Hence:  $V_{out} = (1+k) \cdot (1 - e^{-t/R_1 C_1})$



1

b)

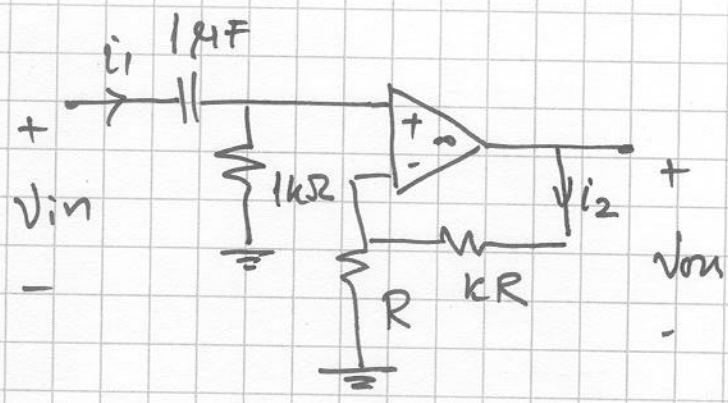

Agarv, as in 1 a):

$$V_{in} = V_{c1} + R_1 \cdot i_1$$

and

$$V_{c1} = 1 - e^{-t/R_1 C_1}$$

In this case:

$$V_{out} = (k+1) R \cdot i_2$$

$$R \cdot i_2 = V_-$$

$$V_- = V_+$$


$$V_+ = R_1 \cdot i_1 \quad ; \quad i_1 = C_1 \frac{dV_{c1}}{dt}$$

$$R \cdot i_2 = R_1 \cdot C_1 \cdot \frac{dV_{c1}}{dt}$$

$$V_{out} = (k+1) \cdot R_1 \cdot C_1 \cdot \frac{dV_{c1}}{dt}$$

$$V_{out} = (k+1) \cdot e^{-t/R_1 C_1}$$


4

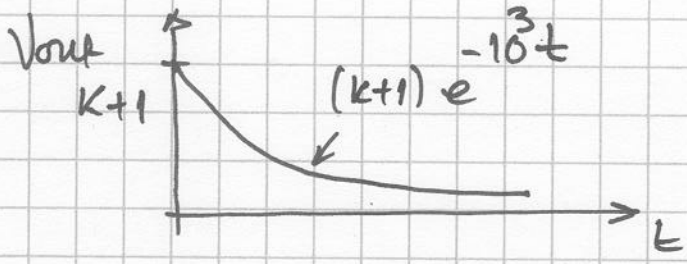

$$R_1 C_1 = 10^{-3}$$

High-pass filter

(2)

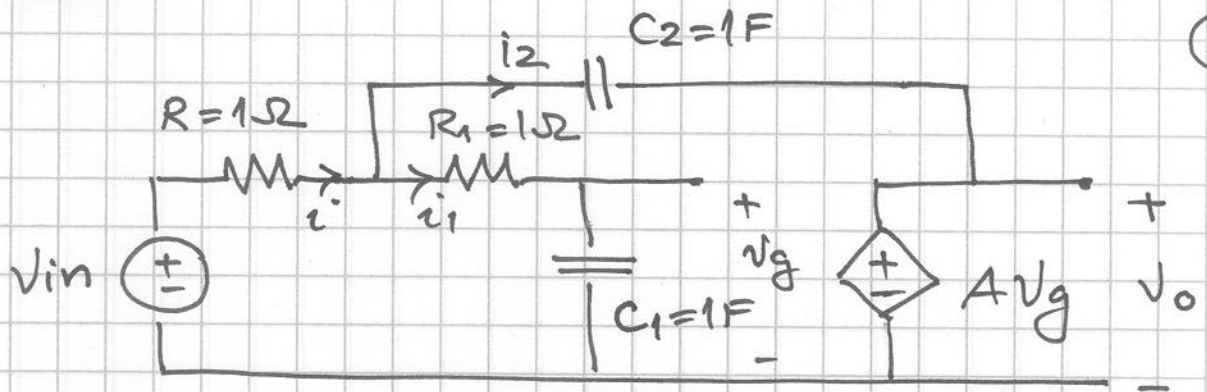

State variables:  $v_{c1}$   
 $v_{c2}$

$$R \cdot i + R_1 \cdot i_1 + v_{c1} = v_{in}$$

$$R \cdot i + v_{c2} + A \cdot v_g = v_{in}$$

$$v_g = v_{c1}$$

$$i = i_1 + i_2$$

$$i_1 = C_1 \cdot \frac{dv_{c1}}{dt} ; i_2 = C_2 \cdot \frac{dv_{c2}}{dt}$$

hence:

$$R \cdot \left( C_1 \cdot \frac{dv_{c1}}{dt} + C_2 \cdot \frac{dv_{c2}}{dt} \right) + R_1 \cdot C_1 \cdot \frac{dv_{c1}}{dt} + v_{c1} = v_{in}$$

$$R \cdot \left( C_1 \cdot \frac{dv_{c1}}{dt} + C_2 \cdot \frac{dv_{c2}}{dt} \right) + v_{c2} + A \cdot v_{c1} = v_{in}$$

$$(R + R_1) \cdot C_1 \cdot \frac{dv_{c1}}{dt} + R \cdot C_2 \cdot \frac{dv_{c2}}{dt} + v_{c1} = v_{in}$$

$$R C_1 \cdot \frac{dv_{c1}}{dt} + R C_2 \cdot \frac{dv_{c2}}{dt} + A v_{c1} + v_{c2} = v_{in}$$

Let  $R = R_1 = 1 \Omega$

$C_1 = C_2 = 1 F$

$$2 \frac{dv_{c1}}{dt} + \frac{dv_{c2}}{dt} + v_{c1} = v_{in}$$

$$\frac{dv_{c1}}{dt} + \frac{dv_{c2}}{dt} + A v_{c1} + v_{c2} = v_{in}$$

State equation:

$$\begin{pmatrix} 2 & 1 \\ 1 & 1 \end{pmatrix} \cdot \begin{pmatrix} \frac{dv_{c1}}{dt} \\ \frac{dv_{c2}}{dt} \end{pmatrix} + \begin{pmatrix} 1 & 0 \\ A & 1 \end{pmatrix} \begin{pmatrix} v_{c1} \\ v_{c2} \end{pmatrix} = \begin{pmatrix} 1 \\ 1 \end{pmatrix} v_{in}$$

or:

$$\begin{pmatrix} 2 & 1 \\ 1 & 1 \end{pmatrix}^{-1} = \begin{pmatrix} 1 & -1 \\ -1 & 2 \end{pmatrix}; \begin{pmatrix} 1 & -1 \\ -1 & 2 \end{pmatrix} \cdot \begin{pmatrix} 1 & 0 \\ A & 1 \end{pmatrix} = \begin{pmatrix} 1-A & -1 \\ 2A-1 & 2 \end{pmatrix}$$

$$\begin{pmatrix} \frac{dv_{c1}}{dt} \\ \frac{dv_{c2}}{dt} \end{pmatrix} + \begin{pmatrix} 1-A & -1 \\ 2A-1 & 2 \end{pmatrix} \cdot \begin{pmatrix} v_{c1} \\ v_{c2} \end{pmatrix} = \begin{pmatrix} 0 \\ 1 \end{pmatrix} v_{in}$$

Characteristic equation:  $v = k e^{st}$

$$\det(sI + A) = 0$$

$$\det \begin{pmatrix} s+1-A & -1 \\ 2A-1 & s+2 \end{pmatrix} = 0$$

$$(s+1-A)(s+2) + 2A - 1 = 0$$

$$s^2 + s - As + 2s + 2 - 2A + 2A - 1 = 0$$

$$s^2 + 3s - As + 1 = 0$$

$$s^2 + (3-A)s + 1 = 0$$

$$s_{1/2} = -\frac{3-A}{2} \pm \sqrt{\left(\frac{3-A}{2}\right)^2 - 1}$$

System analysis:

a) over-damped system:

$s_{1/2}$  both real, distinct:

$$\left(\frac{3-A}{2}\right)^2 - 1 > 0 \quad \text{or} \quad \left(\frac{3-A}{2} + 1\right)\left(\frac{3-A}{2} - 1\right) > 0$$

$$(5-A)(1-A) > 0$$

$$(A-5)(A-1) > 0$$

or:  $A > 5$   
 $A < 1$

Note:  $A < 3$  requires for  $s_{1/2}$  to be negative.

Hence if  $A < 1$  system is over-damped

6) under-damped system:

$$(A-5)(A-1) < 0$$

$$1 < A < 5$$

and  $A < 3$  (real part negative)

Hence:  $1 < A < 3 \Rightarrow$  under-damped system

c) critically damped:  $A = 1$   
 $A = 5$

and  $A < 3 \Rightarrow$

$A = 1$ : critically damped system

d) undamped system:  $A = 3$



Output voltages:

$$V_o = A \cdot V_g$$

$$V_g = V_{c1}$$

$$V_o = A \cdot V_{c1}$$

From our state equations:

$$\left. \begin{aligned} \frac{dV_{c1}}{dt} + (1-A) \cdot V_{c1} - V_{c2} &= 0 \\ \frac{dV_{c2}}{dt} + (2A-1) \cdot V_{c1} + 2V_{c2} &= V_{in} \end{aligned} \right\}$$

Solution for  $V_{c1} = \underbrace{k_1 e^{s_1 t} + k_2 e^{s_2 t}}_{\text{homogeneous soluh.}} + \underbrace{V_1}_{\text{particular solut}}$

But, for  $A=1$

$$s^2 + 2s + 1 = 0 \quad s_{1/2} = -1$$

Critical case

Hence:

$$V_{c1} = k_1 e^{-t} + k_2 t e^{-t} + V$$

let us find  $V$  first :

$V = \text{constant}$  , because  $V_{in} = \text{constant}$

$$(1-A) \cdot V_1 - V_2 = 0$$

↑ particular soluti. for  $V_{C2}$

$$(2A-1) \cdot V_1 + 2V_2 = V_{in}$$

$$A=1 \Rightarrow V_2=0$$

$$\Rightarrow V_1 = V_{in} \text{ (constant)}$$

Hence:

$$V_{C1} = (k_1 + k_2 t) e^{-t} + V_{in}$$

$$V_{C1}(0^-) = 0 \Rightarrow k_1 + V_{in} = 0 \quad k_1 = -V_{in}$$

$$V_{C1}(0^+) = 0 \quad \nearrow$$

Then:

$$\frac{dV_{C1}}{dt} = k_2 e^{-t} - (k_1 + k_2 t) e^{-t}$$

From:

$$\frac{dV_{C1}}{dt} + (1-A) \cdot V_{C1} - V_{C2} = 0 \quad ; \quad A=1$$

$$\left(\frac{dV_{C1}}{dt}\right)_{0^+} - V_{C2}(0^+) = 0 \Rightarrow \left(\frac{dV_{C1}}{dt}\right)_{0^+} = 0$$

or:

$$k_2 - k_1 = 0 \Rightarrow k_2 = k_1$$
$$k_2 = -V_{in}$$

Hence:


11

$$V_{C1} = (-V_{in} - V_{in} \cdot t) e^{-t} + V_{in}$$

$$V_{C1} = V_{in} (1 - (1+t)e^{-t})$$

$$V_o = A \cdot V_{in} (1 - (1+t)e^{-t})$$

3

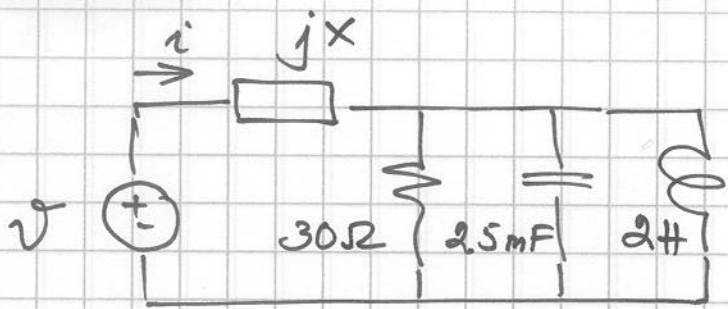

$$\omega = 10$$

$$v = 96 \cos(10t + \pi/9)$$

input impedance:  $R = 30\Omega$ ;  $X_C = \frac{1}{\omega C}$ ;  $X_L = \omega L$

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$Y = \frac{1}{30} + j \cdot 10 \cdot 2.5 \times 10^{-3} + \frac{1}{j \cdot 10 \cdot 2}$$

$$Y = \frac{1}{30} + 25 \times 10^{-3} j + \frac{1}{20j}$$

$$Z = \frac{1}{Y}$$

$$Z = \frac{1}{\frac{1}{30} + j(25 \times 10^{-3} - \frac{1}{20})}$$

$$Z = \frac{1}{\frac{1}{30} + j \cdot \frac{500 \times 10^{-3} - 1}{20}}$$

$$Z = \frac{1}{\frac{1}{30} + j \cdot \frac{-0.5}{20}}$$

$$Z = \frac{1}{\frac{1}{30} - \frac{j}{40}}$$

$$Z = \frac{1}{\frac{4 - j3}{120}}$$

$$Z = \frac{120}{4 - j3} ; \frac{120(4 + j3)}{16 + 9}$$

$$Z = \frac{120}{25} \cdot (4 + j3)$$

Hence:  $Z_{total} = jX + \frac{120}{25} \cdot (4 + j3)$

Ques  $X + \frac{120}{25} \times 3 = 0 ; X = -\frac{360}{25}$

$$X = -\frac{72}{5}$$

$$X = -14.4 \text{ (reactance)}$$

$\frac{j}{\omega C} = 14.4$   
↑  
Capacitor

(otherwise inductor would have negative inductance)

$$C = \frac{1}{144} \text{ F}$$

$$\underline{V} = 96 e^{j\pi/3}$$

$$\underline{I} = \frac{V}{Z_{\text{total}}}$$

$$\text{where } Z_{\text{total}} = \frac{120 \times 4}{25}$$


$$Z_{\text{total}} = \frac{96}{5}$$

$$\underline{I} = \frac{96}{96/5} \cdot e^{j\pi/3}$$

$$\underline{I} = 5 e^{j\pi/3}$$

$$i(t) = 5 \cos(10t + \pi/3)$$

4

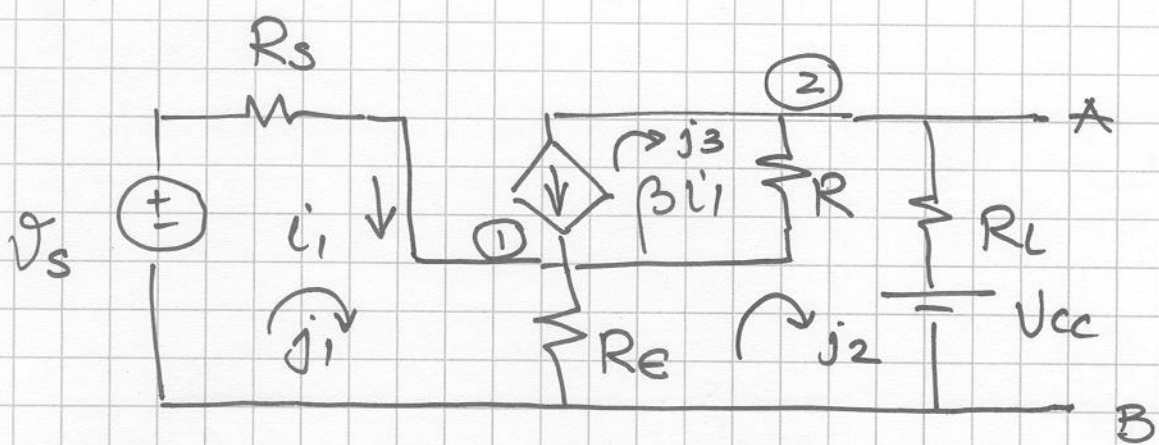

a)

Nodal equations:

$$\frac{v_1 - v_s}{R_s} + \frac{v_1}{R_e} + \frac{v_1 - v_2}{R} - \beta i_1 = 0$$

$$\beta i_1 + \frac{v_2 - v_1}{R} + \frac{v_2 - v_{cc}}{R_L} = 0$$

$$i_1 = \frac{v_s - v_1}{R_s}$$

Hence:

$$\frac{v_1 - v_s}{R_s} + \frac{v_1}{R_e} + \frac{v_1 - v_2}{R} - \beta \cdot \frac{v_s - v_1}{R_s} = 0$$

$$\beta \cdot \frac{v_s - v_1}{R_s} + \frac{v_2 - v_1}{R} + \frac{v_2 - v_{cc}}{R_L} = 0$$

$$v_1 \cdot \left( \frac{1 + \beta}{R_s} + \frac{1}{R_e} + \frac{1}{R} \right) - v_2 \cdot \frac{1}{R} = \frac{1 + \beta}{R_s} \cdot v_s$$

$$- \frac{1 + \beta}{R} \cdot v_1 + v_2 \cdot \left( \frac{1}{R} + \frac{1}{R_L} \right) = - \frac{\beta}{R_s} \cdot v_s + \frac{1}{R_L} \cdot v_{cc}$$

Validity can be checked by setting  $\beta=0$   
Nodal equations should be symmetric:

$$\left(\frac{1}{R_S} + \frac{1}{R_E} + \frac{1}{R}\right)v_1 - \frac{1}{R}v_2 = \frac{1}{R_S}v_S$$

$$-\frac{1}{R}v_1 + \left(\frac{1}{R} + \frac{1}{R_L}\right)v_2 = \frac{1}{R_L}v_{CC}$$



b) Mesh equations:

$$v_S - (R_S + R_E)j_1 + R_E j_2 = 0$$

$$j_3 = -\beta i_1$$

$$v_{CC} + (R_L + R + R_E)j_2 - R_E j_1 - R j_3 = 0$$

Since  $i_1 = j_1$   
 $\Rightarrow j_3 = -\beta j_1$

and

$$(R_S + R_E)j_1 - R_E j_2 = v_S$$

$$-R_E j_1 - R(-\beta j_1) + (R_L + R + R_E)j_2 = -v_{CC}$$

or:

$$(R_S + R_E)j_1 - R_E j_2 = v_S$$

$$-(R_E + \beta R)j_1 + (R + R_E + R_L)j_2 = -v_{CC}$$



Validity check:  $\beta = 0$

$$(R_s + R_e) j_1 - R_e j_2 = V_s$$

$$-R_e j_1 + (R + R_e + R_L) j_2 = -V_{cc}$$

symmetric.

Let  $R = R_s = R_e = R_L$

Thevenin's voltage: (AB open circuited)

From nodal equations:

$$\frac{1}{R} \cdot (3 + \beta) v_1 - v_2 \cdot \frac{1}{R} = \frac{1 + \beta}{R} \cdot V_s$$

$$-\frac{1 + \beta}{R} \cdot v_1 + \frac{2}{R} \cdot v_2 = -\frac{\beta}{R} \cdot V_s + \frac{1}{R} V_{cc}$$

$$V_{AB} = v_2$$

$$(3 + \beta) v_1 - v_2 = (1 + \beta) V_s$$

$$-(1 + \beta) v_1 + 2v_2 = -\beta V_s + V_{cc}$$

Solving:

$$\frac{v_2 + (1 + \beta) V_s}{3 + \beta} \cdot (1 + \beta) + 2v_2 = -\beta V_s + V_{cc}$$

$$V_2 \cdot \left(2 - \frac{1+\beta}{3+\beta}\right) = -\beta V_s + \frac{(1+\beta)^2}{3+\beta} \cdot V_s + V_{cc}$$


$$V_2 \cdot (6 + 2\beta - 1 - \beta) = \left(-\beta(3+\beta) + (1+\beta)^2\right) V_s + (3+\beta) \cdot V_{cc}$$

$$V_2 = \frac{(1-\beta) V_s + (3+\beta) V_{cc}}{5+\beta}$$

Thevenin's voltage

Thevenin's resistance

All independent sources removed

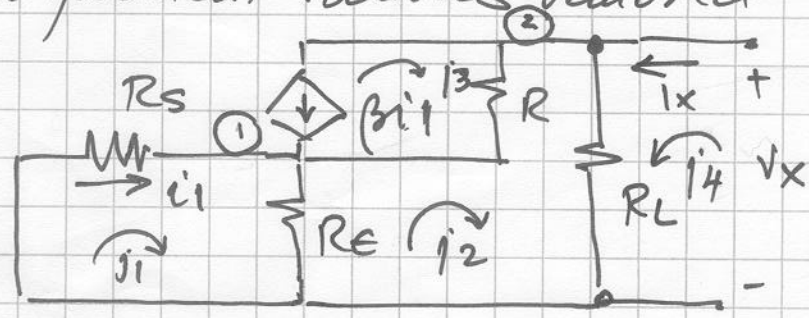

$$R_{th} = V_x / I_x$$

$$j_1 \cdot (R_s + R_e) - R_e j_2 = 0$$

$$j_3 = -\beta \cdot i_1$$

$$-R_e \cdot j_1 + (R_e + R + R_c) j_2 - R j_3 - R_L \cdot j_4 = 0$$

$$V_x - R_L \cdot j_4 + R_L \cdot j_2 = 0$$

Also:  $i_1 = j_1$

Then:  $(R_s + R_e) j_1 - R_e j_2 = 0$

$$j_3 = -\beta \cdot j_1$$

$$-R_e j_1 + (R_e + R + R_L) j_2 - R \cdot j_3 - R_L j_4 = 0$$

$$R_L(j_4 - j_2) = V_x$$

Let  $R = R_s = R_e = R_L$

Then:  $2j_1 - j_2 = 0$

$$j_3 = -\beta \cdot j_1$$

$$-j_1 + 3j_2 - j_3 - j_4 = 0$$

$$R(j_4 - j_2) = V_x$$

We only need  $V_x / j_4$  (since  $I_x = j_4$ )

$$j_2 = 2j_1$$

Then:  $-j_1 + 6j_1 - j_3 - j_4 = 0$

$$5j_1 + \beta j_1 = j_4 \Rightarrow j_1 = \frac{j_4}{5 + \beta}$$

$$j_2 = \frac{2}{5 + \beta} \cdot j_4$$

Then:  $V_x = R \cdot (j_4 - \frac{2j_4}{5 + \beta})$

$$R_{th} = \frac{V_x}{j_4}; R_{th} = \frac{3 + \beta}{5 + \beta} R$$

Test: let  $\beta = 0$



$$\begin{aligned} \left( \frac{R \cdot R}{R+R} + R \right) R &= \frac{\frac{3R}{2} \cdot R}{\frac{3R}{2} + R} \\ &= \frac{3R \cdot R}{3R + 2R} \\ &= \frac{3R}{5} R \end{aligned}$$