

$$100 \times 10^{-3} - 50 \times I_1 - 150 \cdot I_1 = 0$$

$$I_1 = \frac{100 \times 10^{-3}}{200}$$

$$I_1 = 0.5 \times 10^{-3} \text{ A}, \quad I_1 = 0.5 \text{ mA}$$

KCL for node A: $150I_1 = I_2 + I_L$

$$R_L \cdot I_L - 20 \times 10^3 I_2 = 0$$

Hence,

$$I_2 + I_L = 150 \times 0.5 \times 10^{-3}$$

$$200 I_L = 20 \times 10^3 I_2 \quad ; \quad I_2 = 0.01 I_L$$

And $0.01 I_L + I_L = 150 \times 0.5 \times 10^{-3}$

$$I_L = \frac{75 \times 10^{-3}}{1.01} \text{ A}; \quad I_L = \frac{75}{1.01} \times 10^{-3} \text{ A}$$

$$I_L = \frac{75}{1.01} \text{ mA}$$


Power absorbed by the load is:

$$P_L = V_L \cdot I_L; \quad P_L = R_L I_L^2$$

$$P_L = 200 \times \left(\frac{75}{1.01} \times 10^{-3} \right)^2; \quad P_L = \frac{2 \times 5625 \times 10^{-4}}{(1.01)^2}$$

$$P_L = \frac{11250}{(1.01)^2} \times 10^{-4}; \quad P_L = \frac{1125}{(1.01)^2} \times 10^{-3}; \quad P_L = \frac{1.125}{(1.01)^2} \text{ W}$$

$$P_L = 1.103 \text{ mW}$$

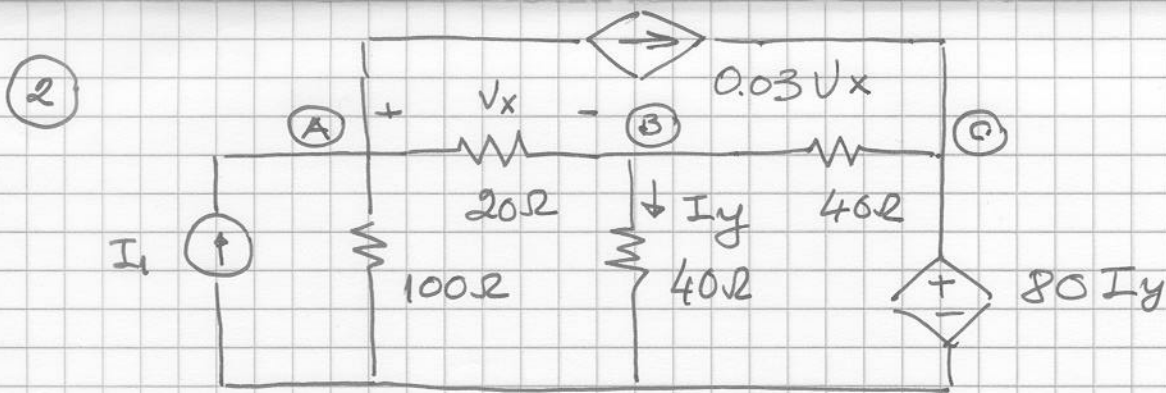

$$I_1 = 0.4 \text{ A}$$

Node equations:

$$\frac{V_A}{100} + \frac{V_A - V_B}{20} + 0.03V_x = I_1$$

$$\frac{V_B - V_A}{20} + \frac{V_B}{40} + \frac{V_B - V_C}{40} = 0$$

$$V_C = 80 \cdot I_y$$

Note that $V_x = V_A - V_B$

$$I_y = \frac{V_B}{40}$$

Hence:

$$V_A \cdot \left(\frac{1}{100} + \frac{1}{20} \right) - \frac{1}{20} \cdot V_B + 0.03 \cdot (V_A - V_B) = 0.4$$

$$V_B \cdot \left(\frac{1}{20} + \frac{1}{40} + \frac{1}{40} \right) - \frac{1}{20} V_A - \frac{1}{40} V_C = 0$$

$$V_C = 80 \times \frac{V_B}{40} \Rightarrow V_C = 2V_B$$

$$\text{Hence: } V_A \left(\frac{1}{100} + \frac{1}{20} + \frac{3}{100} \right) - \left(\frac{1}{20} + \frac{3}{100} \right) V_B = 0.4$$

$$V_B \cdot \left(\frac{1}{20} + \frac{1}{40} + \frac{1}{40} \right) - \frac{1}{20} V_A - \frac{1}{40} \cdot 2V_B = 0$$

After arranging the terms:

$$V_A \cdot \frac{3}{100} - \frac{8}{100} \cdot V_B = 0.4$$

$$V_B \times \frac{1}{20} - V_A \cdot \frac{1}{20} = 0$$

From the second equation:

$$V_B = V_A$$

Substituting in the first equation gives:

$$V_A \cdot \frac{3}{100} - V_A \cdot \frac{8}{100} = 0.4$$


$$\text{or } V_A = 40V$$

and $V_B = 40V$

Since $V_X = V_A - V_B \Rightarrow V_X = 0$

(4)

(3)

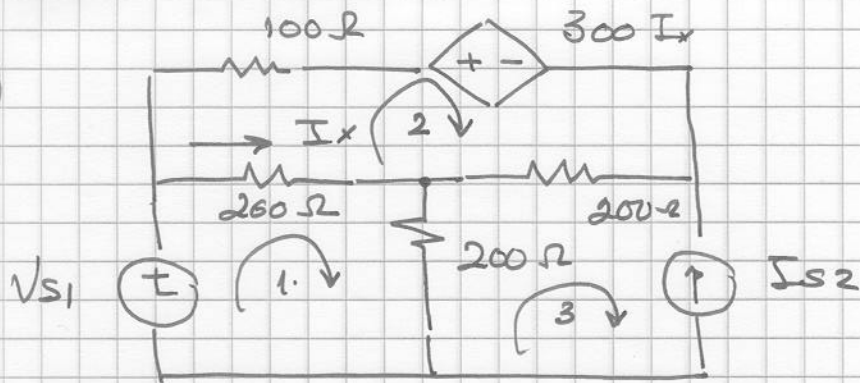

$$V_{S1} = 250V$$

$$I_{S2} = 0.75A$$

Let us denote mesh currents as I_1 , I_2 , and I_3 .

Mesh equations are:

$$V_{S1} - 200(I_1 - I_2) - 200(I_1 - I_3) = 0$$

$$100 \cdot I_2 + 300 \cdot I_x + 200 \cdot (I_2 - I_3) + 200(I_2 - I_1) = 0$$

$$I_3 = -I_{S2}$$

Hence $400I_1 - 200I_2 - 200I_3 = 250$

$$500I_2 - 200I_1 - 200I_3 + 300I_x = 0$$

$$I_3 = -0.75$$

Note: $I_x = I_1 - I_2$

Hence, $400I_1 - 200I_2 - 200I_3 = 250$

$$500I_2 - 200I_1 - 200I_3 + 300 \cdot (I_1 - I_2) = 0$$

Since $I_3 = -0.75$

$$400 \cdot I_1 - 200I_2 - 200 \times (-0.75) = 250$$

$$500I_2 - 200I_1 - 200 \cdot (-0.75) + 300I_1 - 300I_2 = 0$$

$$400I_1 - 200I_2 = 100$$

$$200I_2 + 100I_1 = -150$$

After simplification:

$$4I_1 - 2I_2 = 1$$

$$10I_1 + 20I_2 = -15$$

$$\begin{pmatrix} 4 & -2 \\ 10 & 20 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 1 \\ -15 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 4 & -2 \\ 10 & 20 \end{pmatrix}^{-1} \cdot \begin{pmatrix} 1 \\ -15 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \frac{1}{100} \begin{pmatrix} 20 & 2 \\ -10 & 4 \end{pmatrix} \cdot \begin{pmatrix} 1 \\ -15 \end{pmatrix}$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \frac{1}{100} \begin{pmatrix} -10 \\ -70 \end{pmatrix} \quad I_1 = -1/10 \text{ A} ; I_1 = -0.1 \text{ A}$$


$$I_2 = -7/10 \text{ A} ; I_2 = -0.7 \text{ A}$$

Since $I_x = I_1 - I_2$
 $I_x = 0.6 \text{ A}$

Power delivered by the voltage source V_{s1} is:

$$P_{s1} = V_{s1} \cdot I_1$$

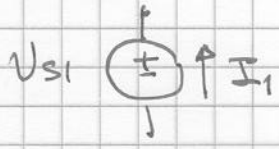
$$P_{s1} = 210 \times (-0.1) ; P_{s1} = -21 \text{ W}$$



$$P_{s2} = V_{s2} \cdot I_{s2}$$

$$V_{s2} = -200 \cdot (I_3 - I_1) - 200 \cdot (I_3 - I_2)$$
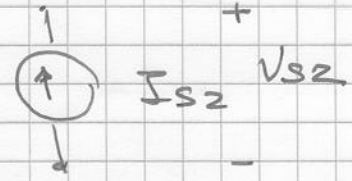
$$V_{s2} = -400 \cdot I_3 + 200I_1 + 200I_2$$




Note that $I_3 = -0.4 \text{ A}$
 $I_1 = -0.1 \text{ A}$
 $I_2 = -0.7 \text{ A}$

Hence: $V_{s2} = -400 \times (-0.4) + 200 \times (-0.1) + 200 \times (-0.7)$
 $V_{s2} = 140 \text{ V}$

$$P_{s1} = 110 \times 0.4 \text{ W} ; P_{s2} = 105 \text{ W}$$

Power delivered by the dependent source:

6

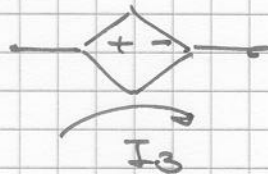

$$P_3 = (300 \times I_x) \times (-I_2)$$

$$P_3 = 300 \times 0.6 \times (+0.4)$$

$$P_3 = 126 \text{ W}$$


Total power delivered by all the sources is:

$$P = \sum P_i$$

$$P = -25 + 105 + 126$$

$$P = 206 \text{ W}$$

4

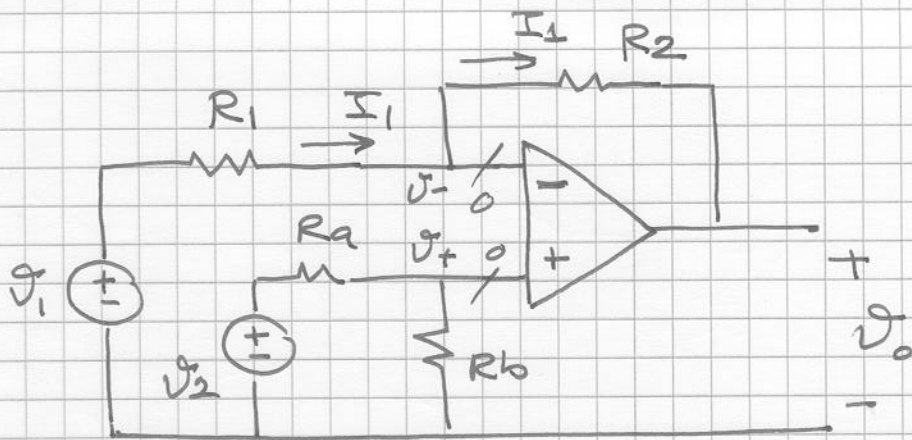

The opamp is ideal. Hence, the input current to the opamp is zero and:

$$v_+ = v_-$$

$$v_+ = \frac{R_b}{R_a + R_b} \cdot v_2$$

$$v_- = \frac{R_b}{R_a + R_b} \cdot v_2$$

$$I_1 = \frac{v_1 - v_-}{R_1} \quad ; \quad I_1 = \frac{v_1}{R_1} - \frac{R_b}{R_1(R_a + R_b)} v_2$$

$$v_o = -R_2 \cdot I_1 + v_-$$

$$v_o = -R_2 \cdot \left(\frac{v_1}{R_1} - \frac{R_b}{R_1(R_a + R_b)} v_2 \right) + \frac{R_b}{R_a + R_b} v_2$$

Hence,

$$v_o = -\frac{R_2}{R_1} \cdot v_1 + \frac{R_2}{R_1} \cdot \frac{R_b}{R_a + R_b} v_2 + \frac{R_b}{R_a + R_b} v_2$$

or

$$v_o = -\frac{R_2}{R_1} v_1 + \left(\frac{R_2}{R_1} + 1 \right) \cdot \frac{R_b}{R_a + R_b} v_2$$

Conditions: $\left| -\frac{R_2}{R_1} v_1 + \left(\frac{R_2}{R_1} + 1 \right) \cdot \frac{R_b}{R_a + R_b} v_2 \right| < V_{sat}$

If the circuit is to be used as a differential amplifier,

$$V_o = -\frac{R_2}{R_1} \cdot V_1 + \left(\frac{R_2}{R_1} + 1\right) \frac{R_b}{R_a + R_b} \cdot V_2$$


$$V_o = -\frac{R_2}{R_1} (V_1 - V_2)$$

Then: $\left(\frac{R_2}{R_1} + 1\right) \frac{R_b}{R_a + R_b} = \frac{R_2}{R_1}$

$$(R_2 + R_1) R_b = R_2 (R_a + R_b)$$

$$\frac{R_1 + R_2}{R_2} = \frac{R_a + R_b}{R_b}$$


$$\frac{R_1}{R_2} = \frac{R_a}{R_b}$$

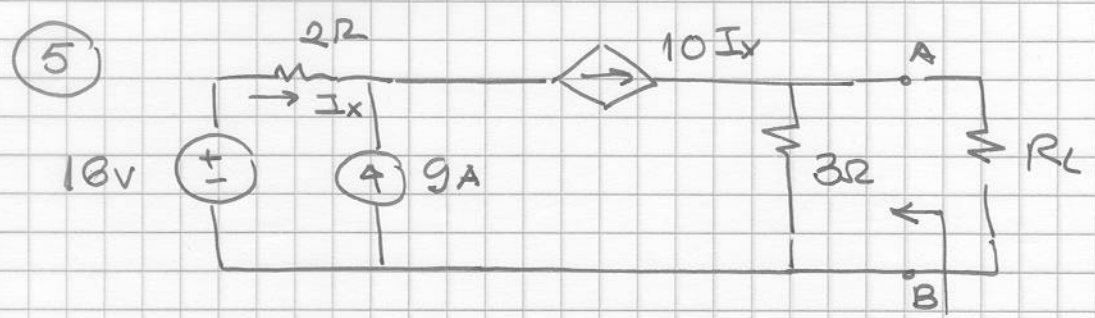

V_{th}
 R_{th}

Let us find Thevenin voltage:

$$I_x + 9 = 10I_x \Rightarrow I_x = 1A$$

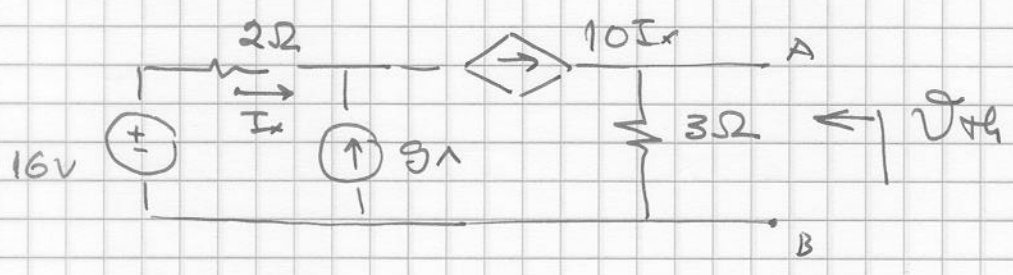


open-circuit

$$V_{th} = 10I_x \times 3$$

$$V_{th} = 30I_x$$

$$V_{th} = 30V$$

Thevenin resistance:

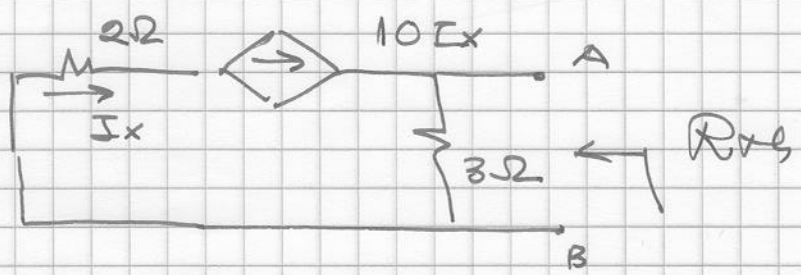

Note that $I_x = 10I_x \Rightarrow I_x = 0$

$$R_{th} = 3\Omega$$

$R_L = 3\Omega$. maximum power transfer

Proof of $R_L = R_{Th}$ for maximum power transfer.

$$P_L = R_L \cdot \left(\frac{V_{Th}}{R_L + R_{Th}} \right)^2$$


$$P_L = V_{Th}^2 \cdot \frac{R_L}{(R_L + R_{Th})^2}$$

$$\frac{\partial P_L}{\partial R_L} = \frac{(R_L + R_{Th})^2 - R_L \cdot 2(R_L + R_{Th})}{(R_L + R_{Th})^3} \cdot V_{Th}$$

$$\frac{\partial P_L}{\partial R_L} = 0 \text{ for } (R_L + R_{Th})(R_{Th} - R_L) = 0$$

i.e., $R_L = R_{Th}$

Maximum power transferred.

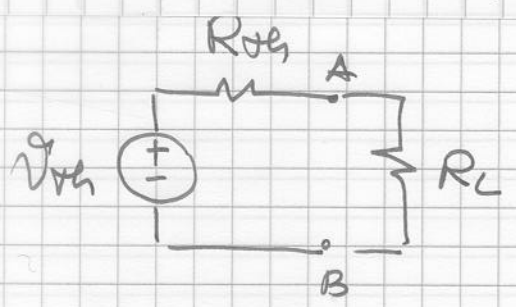

$$V_{Th} = 30V$$
$$R_{Th} = 3\Omega$$

$$P_L = R_L \cdot I^2$$
$$= R_L \cdot \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2$$

if $R_L = R_{Th}$

$$P_L = \frac{V_{Th}^2}{4R_{Th}} \quad ; \quad P_L = \frac{30^2}{4 \times 3}$$
$$= \frac{900}{12}$$
$$= 75W$$