

**SIMON FRASER UNIVERSITY
SCHOOL OF ENGINEERING SCIENCE**

Fall 1999

ENSC 220

ELECTRIC CIRCUITS I

Midterm Examination

October 21, 1999

*Attempt all six problems.
Problems are equally weighted.*

1. For the device shown in Figure 1, the power (in Watts) absorbed by a circuit element is:

$$p(t) = \begin{cases} P_0 & \text{for } t \geq 0 \\ 0 & \text{for } t < 0 \end{cases}$$

and the charge delivered to the device is $q(t) = e^{-2t}$ coulombs for $t \geq 0$ and zero otherwise.

- Find the energy $W(t)$ expended in time t to move charge $q(t)$.
 - Find the current $i(t)$ and the voltage $v(t)$.
 - Find a general expression for $v(t)$ in terms of $W(t)$.
2. Determine the value of the voltage V_x for the circuit of Figure 2.
3. For the circuit of Figure 3:
- Find the Thévenin's equivalent for the circuit left of R_L .
 - Determine the value of R_L required for maximum power transfer.
 - Determine maximum power that can be absorbed by R_L .
4. Find the output voltage V_o for the circuit shown in Figure 4.
5. The op-amp in circuit shown in Figure 5(a) is non-ideal. Its model is given in Figure 5(b). Assuming this non-ideal model:
- Find the Thévenin's equivalent for the circuit to the right of nodes 1 and 3.
 - What is the Thévenin's equivalent if the op-amp is ideal with infinite open-loop gain?
 - Explain your result.
6. Use nodal equations to find $\frac{V_o}{I_{in}}$ for the circuit of Figure 6.

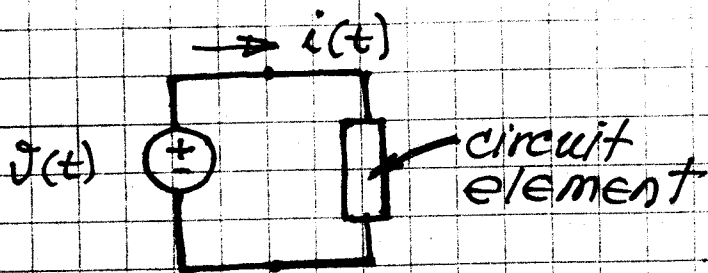


Fig. 1

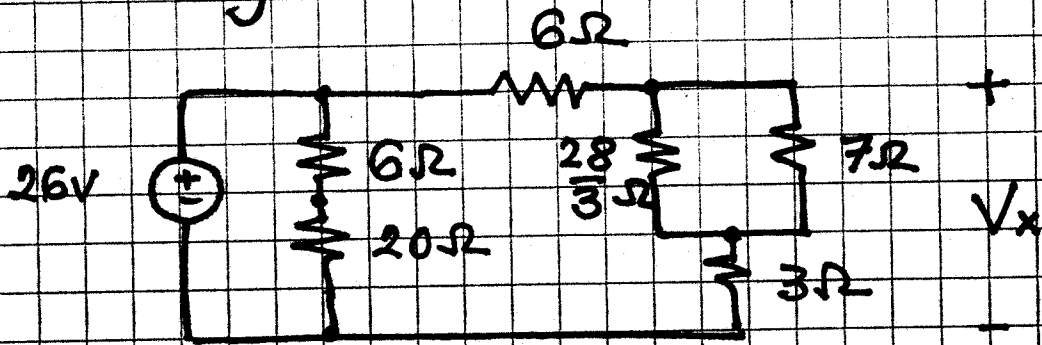


Fig. 2

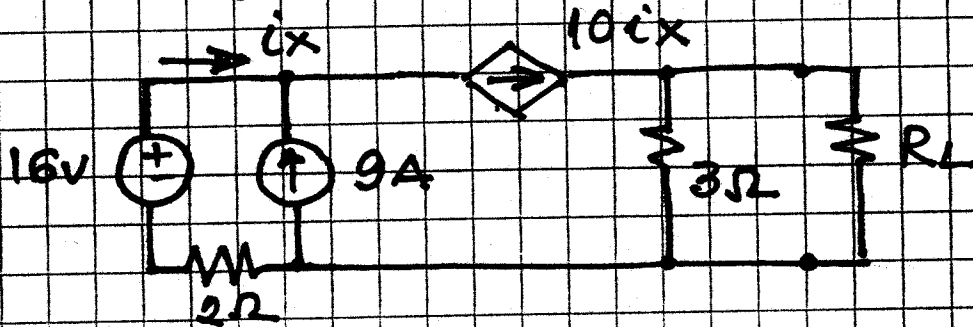


Fig. 3

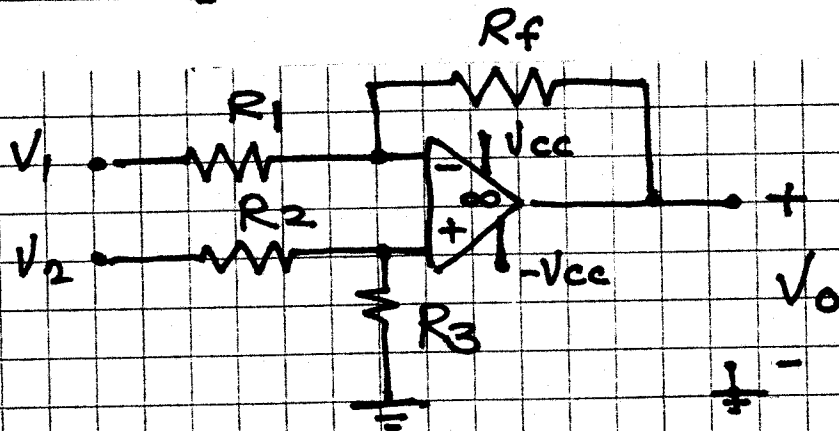


Fig. 4

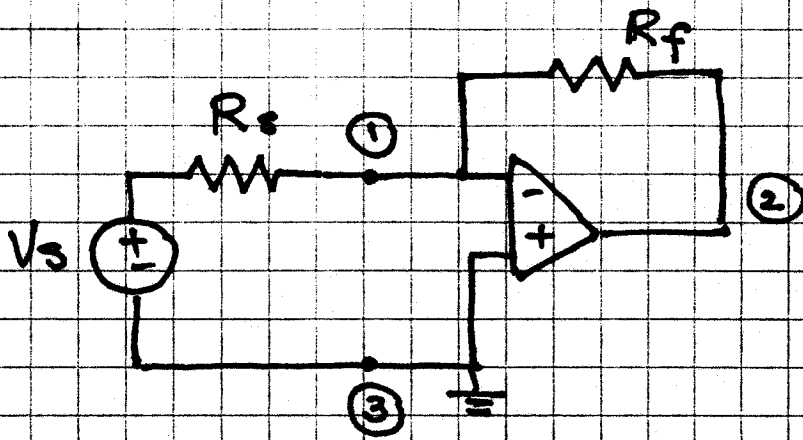


Fig. 5(a)

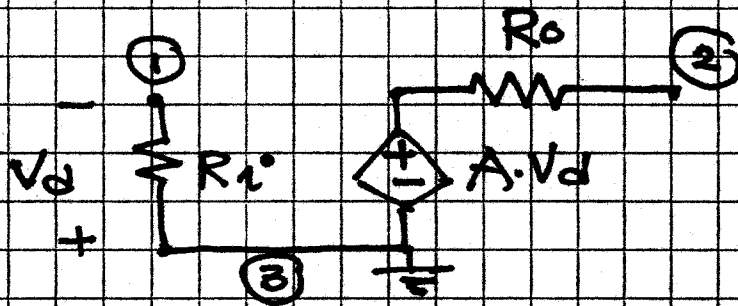


Fig. 5(b)

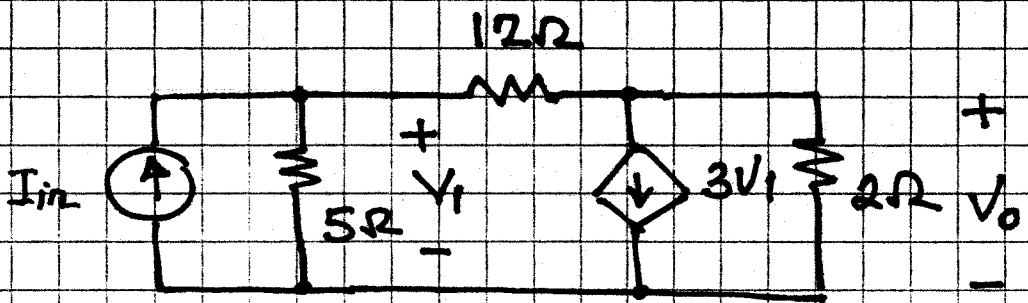


Fig. 6