

$$V_{in} = R_1 \cdot I_{in}$$

$$\mu \cdot V_{in} - R_2 \cdot I_{out} = 0; \quad I_{out} = \frac{\mu}{R_2} \cdot V_{in}$$

$$I_{out} = \mu \cdot \frac{R_1}{R_2} \cdot I_{in}$$

Power absorbed by R_2 :

$$P_{R_2} = V_{R_2} \times I_{R_2}$$


$$P_{R_2} = R_2 \cdot (I_{R_2})^2$$

$$P_{R_2} = R_2 \cdot (I_{out})^2$$

$$P_{R_2} = R_2 \cdot \left(\mu \cdot \frac{R_1}{R_2} \right)^2 \cdot I_{in}^2$$

$$P_{R_2} = \mu \cdot \frac{R_1^2}{R_2} \cdot I_{in}^2 \text{ (Watts)}$$

(2)

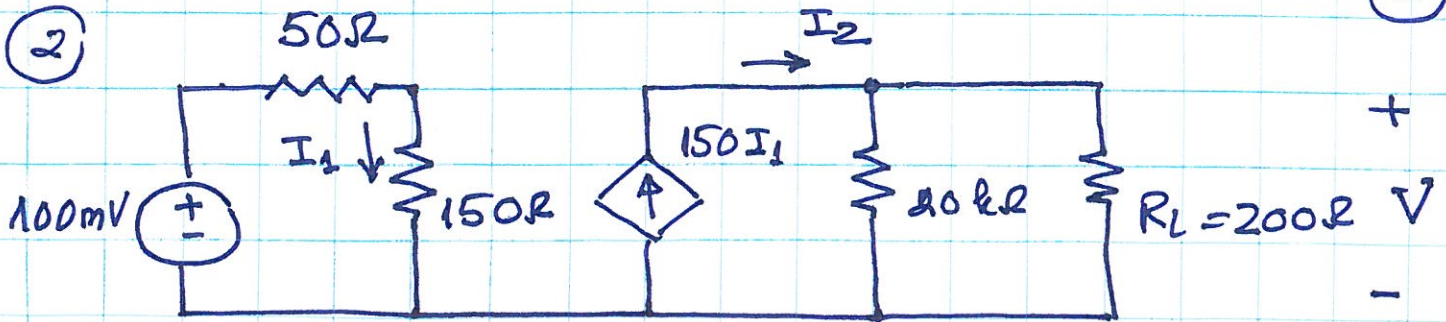

(2)

Power absorbed by $R_L = ?$ R_e

$$I_1 = \frac{100 \times 10^{-3}}{50 + 150} \quad ; \quad I_1 = \frac{100}{200} \times 10^{-3}$$

$$I_1 = 0.5 \times 10^{-3}$$

$$I_1 = 0.5 \text{ mA}$$

$$R_e = \frac{20 \times 10^3 \times 200}{20 \times 10^3 + 200}$$

$$R_e = \frac{4000 \times 10^3}{20.2 \times 10^3} \quad ; \quad R_e = \frac{4000}{20.2}$$


$$V = I_2 \times R_e \quad ; \quad I_2 = 150 I_1$$

$$V = 150 \times I_1 \times R_e$$

$$V = 150 \times 0.5 \times 10^{-3} \times \frac{4000}{20.2} \quad ; \quad V = \frac{300}{20.2}$$

$$P = I_L \cdot V_L \quad ; \quad V_L = V \quad ; \quad I_L = \frac{V}{R_L} \quad V = \frac{1500}{101} \text{ (V)}$$
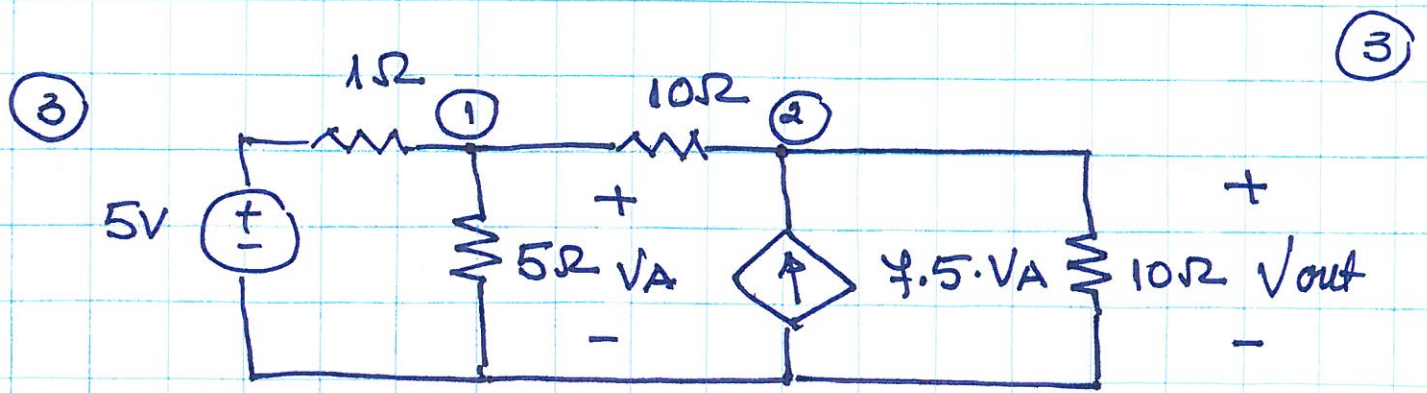
$$P = \frac{V^2}{R_L} \quad ; \quad P = \left(\frac{1500}{101} \right)^2 \times \frac{1}{200} \quad ; \quad P = \frac{450 \times 10^2}{(202)^2} \text{ (W)}$$



Nodal equations:

$$V_1 - 5 + \frac{V_1}{5} + \frac{V_1 - V_2}{10} = 0$$

$$\frac{V_2 - V_1}{10} - 4.5 \cdot V_A + \frac{V_2}{10} = 0$$

Note: $V_A = V_1$

Hence:

$$V_1 \left(\frac{1}{1} + \frac{1}{5} + \frac{1}{10} \right) - V_2 \times \frac{1}{10} = 5$$

$$V_1 \left(-\frac{1}{10} - 4.5 \right) + V_2 \left(\frac{1}{10} + \frac{1}{10} \right) = 0$$

or:

$$1.3V_1 - 0.1V_2 = 5$$

$$-7.6V_1 + 0.2V_2 = 0 \quad ; \quad V_1 = \frac{1}{38} \cdot V_2$$

Then:

$$1.3 \times \frac{1}{38} \cdot V_2 - 0.1V_2 = 5$$


$$V_2 \cdot \left(\frac{1.3}{38} - 0.1 \right) = 5; \quad V_2 = \frac{5 \times 38}{1.3 - 3.8}$$

$$V_2 = -\frac{5 \times 38}{2.5}; \quad V_2 = -76(V)$$

Then: $V_1 = \frac{1}{38} \cdot (-76); \quad V_1 = -2(V)$

$$V_A = -2V; \quad \frac{V_{out}}{5} = \text{gain}; \quad \text{Gain} = -\frac{76}{5}; \quad \text{gain} = -15.2$$

4

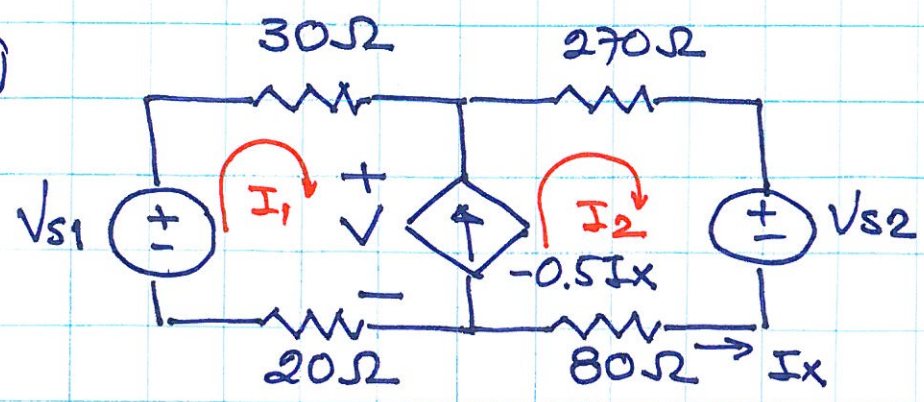

$V_{s1} = 22\text{V}$
 $V_{s2} = 15\text{V}$

Mesh equations:

$V_{s1} - 30 \cdot I_1 - V - 20 \cdot I_1 = 0$
 $V_{s2} + 270 I_2 + 80 \cdot I_2 - V = 0$

Hence:

$(20 + 30) I_1 + V = V_{s1}$
 $(270 + 80) I_2 - V = -V_{s2}$

or:

$50 I_1 + V = V_{s1}$
 $350 I_2 - V = -V_{s2}$

Note that: $-0.5 I_x = I_2 - I_1$

while: $I_x = -I_2$

Hence: $0.5 I_2 = I_2 - I_1$

or: $I_2 = 2 I_1$

From mesh equation; by adding the two equations:

$50 I_1 + 350 I_2 = V_{s1} - V_{s2}$

or: $10 I_1 + 35 I_2 = 22 - 15$

and: $50 I_1 + 350 I_2 = 210$

$10 I_1 + 350 \cdot (2 I_1) = 210$; $I_1 = \frac{210}{710}$; $I_1 = \frac{7}{24} \text{ A}$

Ans: $I_2 = 2 \times \frac{7}{25}$; $I_2 = \frac{14}{25} \text{ A}$

5

Power delivered by the dependent current source:

$$P = V \times (-0.5 I_x)$$

where: $V = 225 - 50 \cdot I_1$

$$I_x = -I_2$$

Hence, $V = 225 - 50 \times \frac{7}{25}$; $V = 211 \text{ (V)}$

$$I_x = -\frac{14}{25} \text{ (A)}$$

$$P = 211 \times (-0.5) \times \left(-\frac{14}{25}\right)$$

$$P = 211 \times \frac{7}{25}$$
 ; $P = \frac{1477}{25}$; $P = 59.08 \text{ W}$