

SIMON FRASER UNIVERSITY  
SCHOOL OF ENGINEERING SCIENCE

Summer 2007  
ENSC 320: ELECTRIC CIRCUITS II

Final Examination

August 16, 2007

*Duration: 3 hours. Attempt all problems. Questions are **not** equally weighted. Closed book and closed notes. Calculators, PDAs, laptops, and wireless phones are not permitted.*

1. **(20 points)** For the ideal op amp circuit shown in Figure 1:
  - Find the transfer function and the poles and the zeros in terms of  $R_1$ ,  $R_2$ ,  $C_1$ , and  $C_2$ .
  - Find the impulse response.

2. **(20 points)**

For the circuit shown in Figure 2:

- Find the value of  $C$  that makes the circuit resonant at  $\omega = 3 \text{ rad/s}$ .
- Find the value of  $Y_{in}$  at the resonant frequency.
- Is the circuit stable? Please justify your answer.

3. **(40 points)**

Consider the Sallen and Key circuit shown in Figure 3. Assume that the op-amp is ideal.

- Find transfer function  $H(s) = V_{out}/V_{in}$ .
- Find the zeros and the poles of  $H(s)$ .
- Find the magnitude and the phase of the frequency response.
- Identify the type of this circuit.

4. **(20 points)**

Consider the circuit shown in Figure 4.

- Compute the  $y$ -parameters of the boxed two-port.
- Compute the input admittance  $Y_{in}(s)$  of the complete circuit.

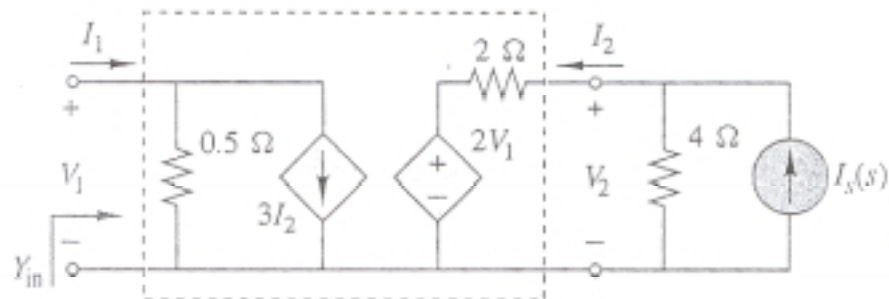
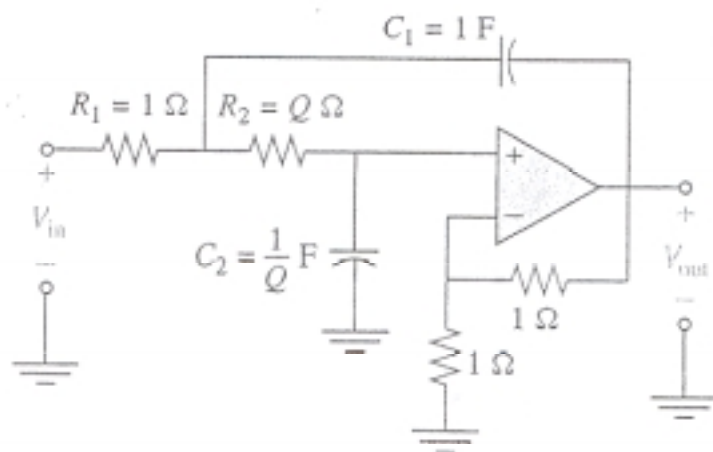
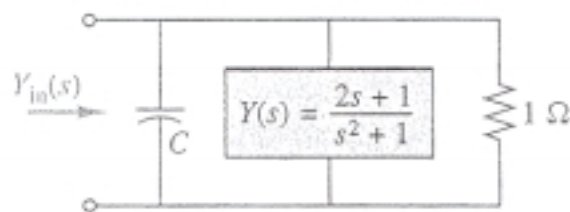
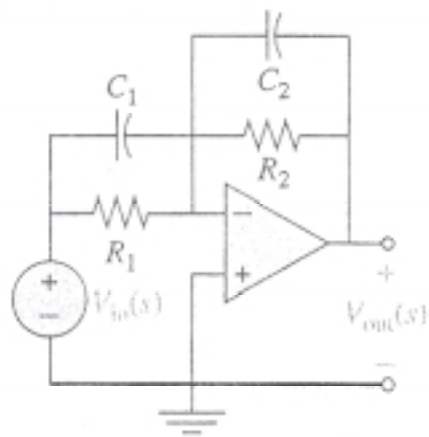


TABLE 13.1 Laplace Transform Pairs

Item number	$f(t)$	$\mathcal{L}[f(t)] = F(s)$
1	$K\delta(t)$	$K$
2	$Ku(t)$ or $K$	$\frac{K}{s}$
3	$t$	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at} u(t)$	$\frac{1}{s+a}$
6	$te^{-at} u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at} u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t) u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t) u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t) u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t) u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t) u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t) u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \phi) u(t)$	$\frac{s \sin(\phi) + \omega \cos(\phi)}{s^2 + \omega^2}$
15	$\cos(\omega t + \phi) u(t)$	$\frac{s \cos(\phi) - \omega \sin(\phi)}{s^2 + \omega^2}$
16	$e^{-at} [\sin(\omega t) - \omega t \cos(\omega t)] u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t) u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[ C_1 \cos(\omega t) + \left( \frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[ \omega t - \tan^{-1} \left( \frac{B}{A} \right) \right]$	$\frac{A + jB}{s+a+j\omega} + \frac{A - jB}{s+a-j\omega}$
20	$2\sqrt{A^2 + B^2} te^{-at} \cos \left[ \omega t - \tan^{-1} \left( \frac{B}{A} \right) \right]$	$\frac{A + jB}{(s+a+j\omega)^2} + \frac{A - jB}{(s+a-j\omega)^2}$