

SIMON FRASER UNIVERSITY
SCHOOL OF ENGINEERING SCIENCE

Spring 2008
ENSC 320: ELECTRIC CIRCUITS II

Final Examination

April 15, 2008

*Duration: 3 hours. Attempt all four problems. Questions are **not** equally weighted. Closed book and closed notes. Calculators, PDAs, laptops, and wireless phones are not permitted.*

1. **(30 points)** The ideal op amp circuit shown in Figure 1 has initial capacitor voltages $v_{c1}(0_-) = 2\text{ V}$ and $v_{c2}(0_-) = 0\text{ V}$. Circuit parameters are: $R_1 = 2.5\text{ k}\Omega$, $R_2 = 5\text{ k}\Omega$, $C_1 = 0.2\text{ mF}$, and $C_2 = 0.2\text{ mF}$.
 - Construct the Laplace transform domain equivalent circuits, accounting for these initial conditions.
 - Find $V_{out}(s)$.
 - Find $v_{out}(t)$ for $t \geq 0$.
 - Make a rough sketch of the response.

2. **(30 points)** For the circuit shown in Figure 2:
 - Find the transfer function $H(s) = I_L(s)/V_{in}(s)$.
 - Find ω_m , H_m , and B_w .

3. **(20 points)** For the circuit shown in Figure 3, $R = 1\ \Omega$, $L_1 = 2\text{ H}$, $L_2 = 10\text{ H}$, $M = 2\text{ H}$, and $C = 0.8\text{ mF}$.
 - Find $Z_{in}(s)$
 - Find the value of ω at which resonance occurs.

4. **(20 points)** Consider the circuit shown in Figure 4.
 - Find the z -parameters.
 - Compute $Z_{in}(s)$.
 - If $v_1(t) = 10u(t)\text{ V}$, find $i_1(t)$.

Figure 1.

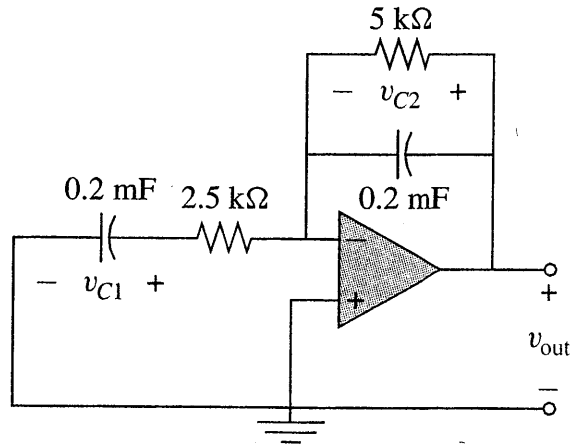


Figure 2.

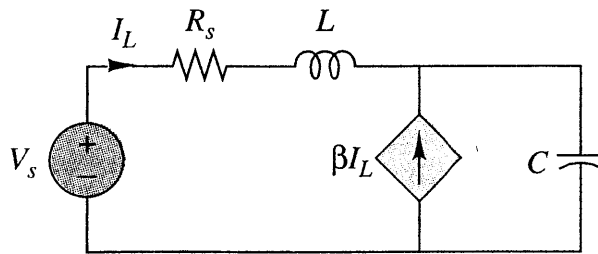


Figure 3.

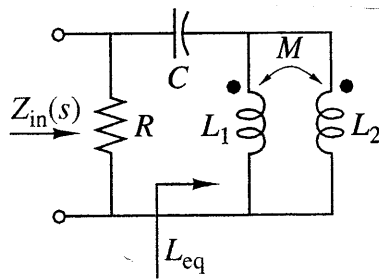


Figure 4.

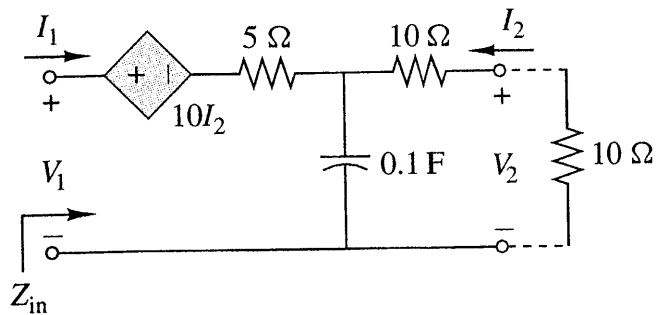


TABLE 13.1 Laplace Transform Pairs

Item number	$f(t)$	$\mathcal{L}[f(t)] = F(s)$
1	$K\delta(t)$	K
2	$Ku(t)$ or K	$\frac{K}{s}$
3	$r(t)$	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at} u(t)$	$\frac{1}{s+a}$
6	$te^{-at} u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at} u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t) u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t) u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t) u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t) u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t) u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t) u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \phi) u(t)$	$\frac{s \sin(\phi) + \omega \cos(\phi)}{s^2 + \omega^2}$
15	$\cos(\omega t + \phi) u(t)$	$\frac{s \cos(\phi) - \omega \sin(\phi)}{s^2 + \omega^2}$
16	$e^{-at} [\sin(\omega t) - \omega t \cos(\omega t)] u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t) u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[C_1 \cos(\omega t) + \left(\frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right]$	$\frac{A + jB}{s+a+j\omega} + \frac{A - jB}{s+a-j\omega}$
20	$2\sqrt{A^2 + B^2} te^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right]$	$\frac{A + jB}{(s+a+j\omega)^2} + \frac{A - jB}{(s+a-j\omega)^2}$