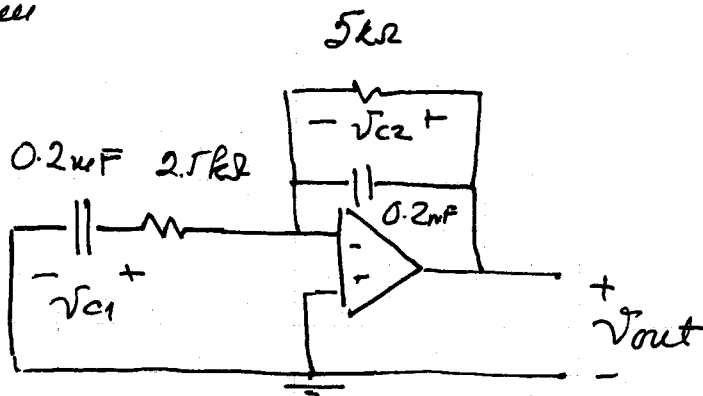



# 1



$$v_{c1}(0^-) = 2V \quad R_1 = 2.5k\Omega \quad C_1 = 0.2\mu F$$

$$v_{c2}(0^-) = 0V \quad R_2 = 5k\Omega \quad C_2 = 0.2\mu F$$

Laplace transform domain circuit:

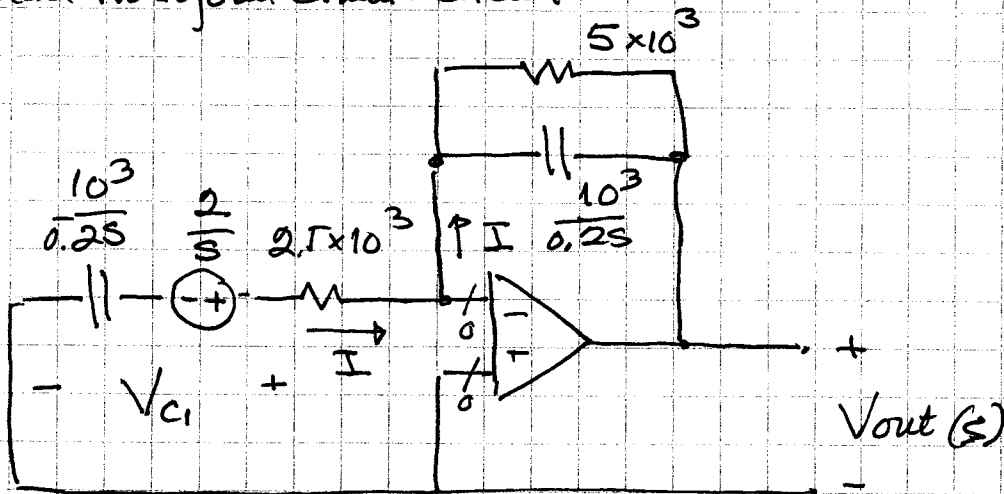

Node equations:

$$I(s) = \frac{\frac{2}{s}}{2.5 \times 10^3 + \frac{10^3}{0.2s}}$$

$$= \frac{-2 \times 10^{-3}}{2.5s + 0.5 \times 10^{-3}}$$

$$= \frac{-8 \times 10^{-4}}{s + 2}$$

$$V_{out}(s) = I(s) \times \frac{5 \times 10^3 \times \frac{10^3}{0.2s}}{5 \times 10^3 + \frac{10^3}{0.2s}}$$

$$V_{out}(s) = \frac{-8 \times 10^{-4}}{s+2} \times \frac{5 \times \frac{10^4}{2s}}{5 + \frac{10^4}{2s}}$$

$$= -8 \times \frac{10^{-4}}{s+2} \times \frac{5 \times 10^4}{10s+10}$$

$$= -8 \cdot \frac{5}{10 \cdot (s+1)(s+2)}$$

$$= \frac{-4}{(s+1)(s+2)}$$

Partial frach expansion zu:

$$-\frac{4}{(s+1)(s+2)} = \frac{A}{s+1} + \frac{B}{s+2}$$

$$A = \lim_{s \rightarrow -1} (s+1) \times \frac{-4}{(s+1)(s+2)}$$

$$s \rightarrow -1$$

$$= \frac{-4}{-1+2} ; A = -4$$

$$B = \lim_{s \rightarrow -2} (s+2) \times \frac{-4}{(s+1)(s+2)}$$


$$s \rightarrow -2$$

$$= \frac{-4}{-2+1} ; B = 4$$

$$\text{Also: } V_{out}(s) = \frac{-4}{s+1} + \frac{4}{s+2} ; V_{out}(t) = 4(e^{-2t} - e^{-t})u(t) \checkmark$$

# 2

3

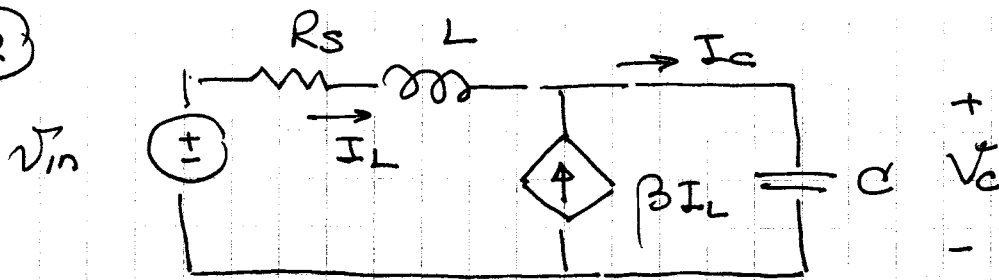

In "s"-domain:

$$V_{in}(s) = (R_s + sL) \cdot I_L + V_C \quad (1)$$

$$I_C = Cs \cdot V_C$$

$$I_L = -\beta \cdot I_L + I_C \Rightarrow (1 + \beta) I_L = I_C$$

$$V_C = \frac{1}{Cs} \cdot I_C$$

$$V_C = \frac{1}{Cs} \cdot (1 + \beta) \cdot I_L$$

Then (1) becomes:

$$V_{in}(s) = (R_s + sL) \cdot I_L + \frac{1}{Cs} (1 + \beta) \cdot I_L$$

$$H(s) = \frac{I_L(s)}{V_{in}(s)}$$

Hence:

$$H(s) = \frac{1}{R_s + sL + \frac{1}{Cs} (1 + \beta)}$$

$$H(s) = \frac{Cs}{Lcs^2 + R_s Cs + (1 + \beta)}$$

Frequency response:

4

$$H(j\omega) = \frac{j\omega C}{1 + \beta - LC\omega^2 + j\omega R_s C}$$

Amplitude:

$$|H(j\omega)|^2 = \frac{\omega^2 C^2}{(1 + \beta - LC\omega^2)^2 + (\omega R_s C)^2}$$

Finding  $\omega_m$ :  $1 + \beta - LC\omega^2 = 0$

$$\omega_m = \sqrt{\frac{1 + \beta}{LC}}$$

Then:  $|H_m|^2 = |H(j\omega)|^2 \Big|_{\omega = \omega_m}$

$$|H_m|^2 = \frac{\omega_m^2 C^2}{(\omega_m R_s C)^2} \Big|_{\omega = \omega_m}$$

$$H_m = \frac{1}{R_s}$$

Bandwidth:


$$\frac{|H(j\omega)|^2}{H_m^2} = \frac{1}{2}$$

$$(1 + \beta - LC\omega^2)^2 = (\omega R_s C)^2$$

$$1 + \beta - LC\omega^2 = \pm \omega R_s C$$

$$LC\omega^2 \pm \omega R_s C - (1 + \beta) = 0$$
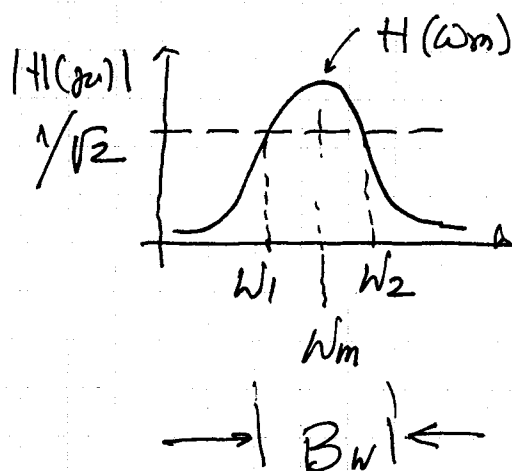
$$\omega^2 \pm \frac{\omega R_s}{L} - \frac{1 + \beta}{LC} = 0$$



5

$$W_{1/2} = -\frac{R_S}{2L} \pm \sqrt{\left(\frac{R_S}{2L}\right)^2 + \frac{1+B}{LC}}$$

$$W_{3/4} = \frac{R_S}{2L} \pm \sqrt{\left(\frac{R_S}{2L}\right)^2 + \frac{1+B}{LC}}$$

positive solutions  
for  $\omega$  only.  
(choose +)

$$B_{BW} = W_3 - W_4 = \frac{R_S}{L} \quad \text{Bandwidth}$$

Hence

$$I = I_1 + I_2$$


$$I = \frac{L_1 + L_2 - 2M}{s(L_1 L_2 - M^2)} \cdot V$$

OR, equivalently:  $V = s \cdot \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \cdot I$

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

$$L_{eq} = \frac{2 \times 10 - 2^2}{2 + 10 - 2 \times 2} \quad ; \quad L_{eq} = \frac{16}{8} \quad ; \quad L_{eq} = 2H$$

The circuit can be viewed as:

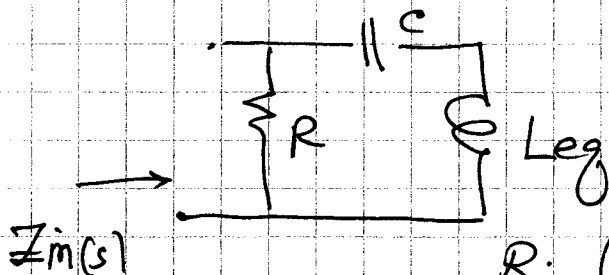

$$Z_{in}(s) = R \cdot \left( s \cdot L_{eq} + \frac{1}{Cs} \right)$$


$$Z_{in}(s) = \frac{R \cdot (1 + C L_{eq} \cdot s^2)}{1 + R C s + C L_{eq} \cdot s^2}$$

$$Z_{in}(s) = \frac{1 \times (1 + 0.8 \times 10^{-3} \times 2 s^2)}{1 + 1 \times 0.8 \times 10^{-3} s + 0.8 \times 10^{-3} \times 2 s^2}$$


$$Z_{in}(s) = \frac{1 + 1.6 \times 10^{-3} s^2}{1 + 0.8 \times 10^{-3} s + 1.6 \times 10^{-3} s^2}$$

# 3

6

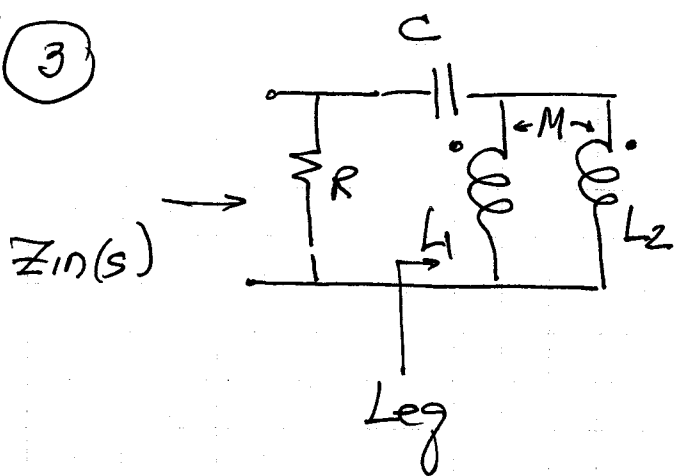
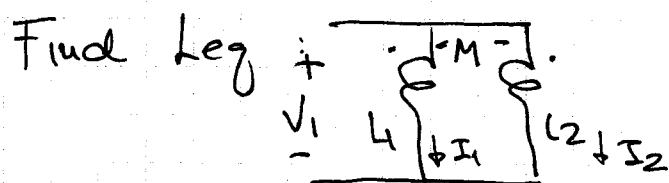
$$\begin{aligned}
 R &= 1\Omega \\
 L_1 &= 2H \\
 L_2 &= 10H \\
 M &= 2H \\
 C &= 0.8mF
 \end{aligned}$$



$$I = I_1 + I_2$$

$$V = L_1 s \cdot I_1 + M s \cdot I_2$$

$$V = L_2 s \cdot I_2 + M s \cdot I_1$$

$$L_1 I_1 + M I_2 = L_2 I_2 + M I_1$$

$$(L_1 - M) I_1 = (L_2 - M) I_2 ; I_2 = \frac{L_1 - M}{L_2 - M} I_1$$

Hence,

$$V = L_1 s \cdot I_1 + M s \cdot \frac{L_1 - M}{L_2 - M} I_1$$

$$I_1 = \frac{V}{L_1 s + M s \cdot \frac{L_1 - M}{L_2 - M}} ; I_2 = \frac{(L_2 - M) \cdot V}{s \cdot (L_1 L_2 - L_1 M + L_2 M - M^2)}$$

$$I_1 = \frac{L_2 - M}{s \cdot (L_1 L_2 - M^2)} \cdot V$$

$$I_2 = \frac{L_1 - M}{s \cdot (L_1 L_2 - M^2)} \cdot V$$

$$Z_{in}(s) = \frac{s^2 + \frac{1}{16 \times 10^{-3}}}{s^2 + \frac{0.8 \times 10^{-3}}{16 \times 10^{-3}} s + \frac{1}{16 \times 10^{-3}}}$$

$$Z_{in}(s) = \frac{s^2 + 625}{s^2 + 0.5s + 625}$$

By definition, resonance occurs at:

$$\text{Im} \{ Z_{in}(j\omega) \} = 0$$

$$Z(j\omega) = \frac{625 - \omega^2}{(625 - \omega^2) + 0.5j\omega}$$

$$= (625 - \omega^2) \times \frac{625 - \omega^2 - 0.5j\omega}{(625 - \omega^2)^2 + (0.5\omega)^2}$$

$$\text{Im} \{ Z(j\omega) \} = 0 \text{ at } (625 - \omega^2) \times (-0.5\omega) = 0$$

Trivial solution:  $\omega = 0$

Non-trivial solution:  $625 - \omega^2 = 0$


$$\omega = 25 \text{ rad/s}$$

$$\text{At resonance: } Z(j\omega) \Big|_{\omega=25} = 0$$



#4

9

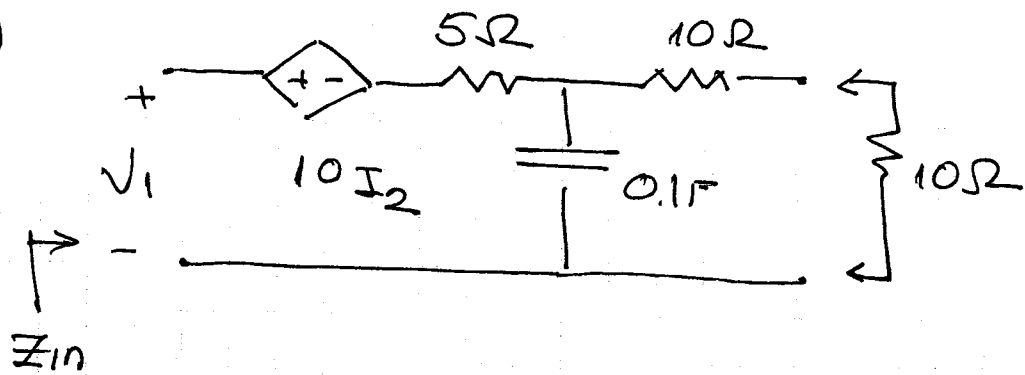

Consider the two-port without the resistor load.

KVL and KCL equations:

$$V_1 - 10 \times I_2 - 5 \times I_1 - \frac{1}{0.1s} \cdot (I_1 + I_2) = 0$$

$$V_2 - 10 \times I_2 + \frac{1}{0.1s} \cdot (I_1 + I_2) = 0$$

OR

$$V_1 = 10 \times I_2 + 5 \times I_1 + \frac{10}{s} \cdot (I_1 + I_2)$$

$$V_2 = 10 \times I_2 + \frac{10}{s} \cdot (I_1 + I_2)$$

Hence,

$$V_1 = \left(5 + \frac{10}{s}\right) I_1 + 10 \left(1 + \frac{1}{s}\right) \cdot I_2$$

$$V_2 = \frac{10}{s} \times I_1 + 10 \cdot \left(1 + \frac{1}{s}\right) I_2$$

$$\underline{Z} = \begin{pmatrix} 5 + \frac{10}{s} & 10 \left(1 + \frac{1}{s}\right) \\ \frac{10}{s} & 10 \left(1 + \frac{1}{s}\right) \end{pmatrix}$$

$$Z_{in} = ?$$

The two port is now terminated by the resistive load:

$$V_2 = -10 \times I_2$$

$$\text{From: } \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_2 = -10 I_2$$

$$\text{Then: } -10 \times I_2 = \frac{10}{s} \times I_1 + 10 \left(1 + \frac{1}{s}\right) \cdot I_2$$

$$\left(-20 - \frac{10}{s}\right) I_2 = \frac{10}{s} \cdot I_1$$

$$\text{Hence, } I_2 = \frac{-10}{20s + 10} \times I_1$$

$$I_2 = -\frac{1}{1 + 2s} \cdot I_1$$

$$\text{From: } V_1 = Z_{11} \cdot I_1 + Z_{12} \cdot I_2$$

$$V_1 = \left(5 + \frac{10}{s}\right) I_1 + 10 \cdot \left(1 + \frac{1}{s}\right) \cdot \frac{-1}{1 + 2s} \cdot I_1$$

$$Z_{in} = \frac{V_1}{I_1}$$

$$\begin{aligned} \text{So } Z_{in} &= 5 + \frac{10}{s} - \frac{10(1+s)}{s(1+2s)} \\ &= 5 + \frac{2s+1 - (1+s)}{s(1+2s)} \times 10 \end{aligned}$$

$$Z_{in} = 5 + \frac{s}{s(1+2s)} \times 10$$

$$= 5 + \frac{1}{1+2s} \times 10$$

$$Z_{in} = \frac{10s+5}{1+2s} \quad ; \quad Z_{in} = \frac{5s+7.5}{s+0.5}$$

17  $V_1(t) = 10u(t)$ ;  $V_1(s) = 10/s$

The easiest way to find  $i_1(t)$  is from:

$$I_1 = V_1 / Z_{in}$$

$$I_1 = \frac{10}{s} \times \frac{s+0.5}{5s+7.5}$$

$$I_1 = \frac{10s+5}{s(5s+7.5)} \quad ; \quad I_1 = \frac{2s+1}{s(s+1.5)}$$

Partial fraction expansion leads to:

$$\frac{2s+1}{s(s+1.5)} = \frac{A}{s} + \frac{B}{s+1.5} \quad A = \lim_{s \rightarrow 0} s \times \frac{2s+1}{s(s+1.5)}$$

$$A = \frac{1}{1.5}$$

$$A = 2/3$$

$$B = \lim_{s \rightarrow -1.5} (s+1.5) \times \frac{2s+1}{s(s+1.5)}$$

$$= \frac{2 \times (-1.5) + 1}{-1.5}$$

$$= +2/1.5 \quad ; \quad B = +4/3$$

Hence, Laplace transform of current  $i_1(t)$  is:

(12)

$$I_1 = \frac{2}{3s} + \frac{4}{3} \cdot \frac{1}{s+1.5}$$

Hence;

$$i_1(t) = \frac{2}{3} \cdot u(t) + \frac{4}{3} \cdot e^{-1.5t} u(t)$$

or

$$i_1(t) = \frac{2}{3} (1 + 2e^{-1.5t}) \cdot u(t)$$