

SIMON FRASER UNIVERSITY
SCHOOL OF ENGINEERING SCIENCE

Summer 2007
ENSC 320: ELECTRIC CIRCUITS II

Midterm Examination No. 1

June 15, 2007

*Duration: 110 minutes. Attempt all five problems. Questions are **not** equally weighted.
Closed book and closed notes. Calculators, PDAs, laptops, and wireless phones are not permitted.*

1. **(20 points)**

Find the response $v_{out}(t)$ for the ideal op amp circuit shown in Fig. 1 in terms of $v_{in}(t)$, R , and C . Based on your response, state the function that this circuit realizes. Suppose that $v_{in}(t) = \cos(250t)$, $R = 4k\Omega$, and $C = 1\mu F$. The circuit is initially relaxed. Find $v_{out}(t)$.

2. **(30 points)**

The switch in the circuit shown in Fig. 2 has been closed for a long time when it opens at $t = 0$. Circuit parameters are: $V_0 = 10V$, $R_1 = 20\Omega$, $R_2 = 0.5\Omega$, $L = 1H$, and $C = 0.25F$.

- Specify the $t = 0+$ values of v and i (shown on the diagram).
- Write two state equations describing the circuit.
- Write the state equations in the matrix form.
- Convert the two first order equations into a second order equation in terms of i .
- Find the natural frequencies (characteristic values) of the circuit.
- Find the solution $i(t)$.

3. **(10 points)**

Find Laplace transform of the signals sketched in Fig. 3 and the following functions of t :

- $f(t) = te^{-at}$
- $f(t) = e^{-at} \sin(\omega t)$.

4. **(10 points)**

Find the inverse Laplace transform of the following functions of s : (Use simplifications and the transform properties to simplify calculations.)

- $F(s) = \frac{3s+1}{(s+2)(s^2+4s+8)}$
- $F(s) = \frac{s(s+2)e^{-3s}}{(s+1)^2(s+4)}$

5. (30 points)

A series RLC circuit is shown in Fig. 4. Circuit parameters are: $R = 4\Omega$, $L = 1H$, and $C = 0.2F$. Use Laplace transform to find the circuit's:

- impulse response
- step response.

Figure 1:

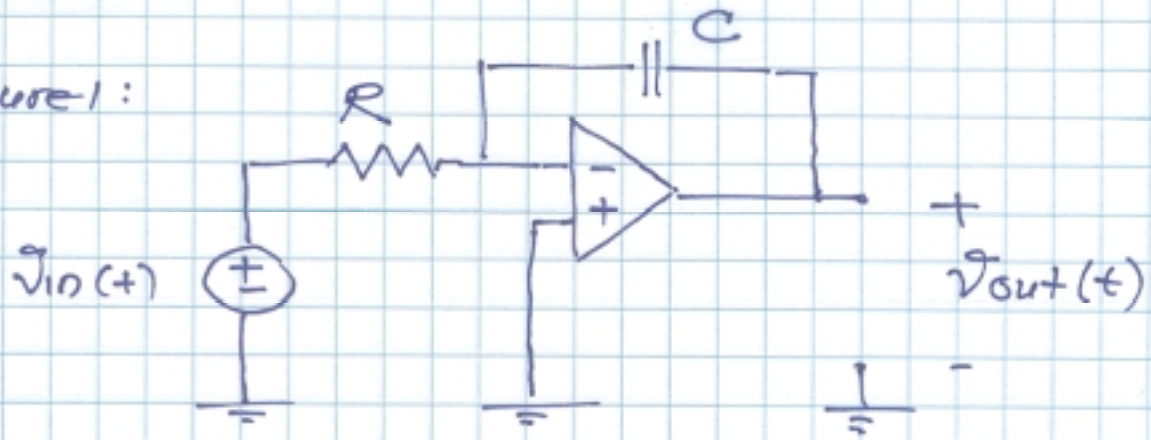


Figure 2:

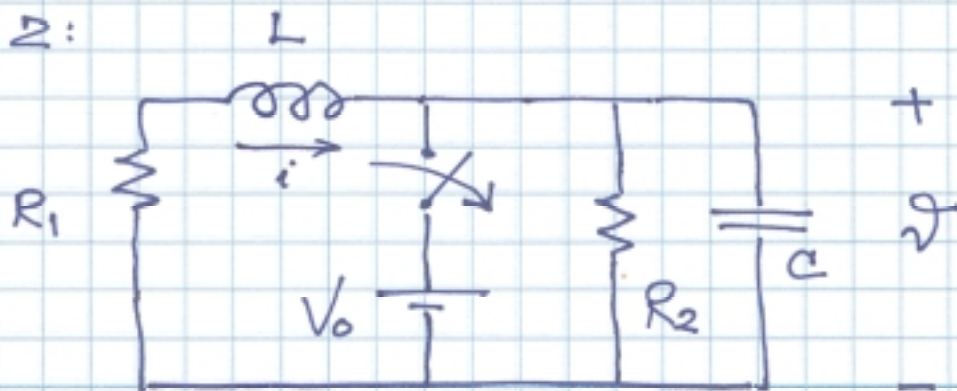


Figure 3:

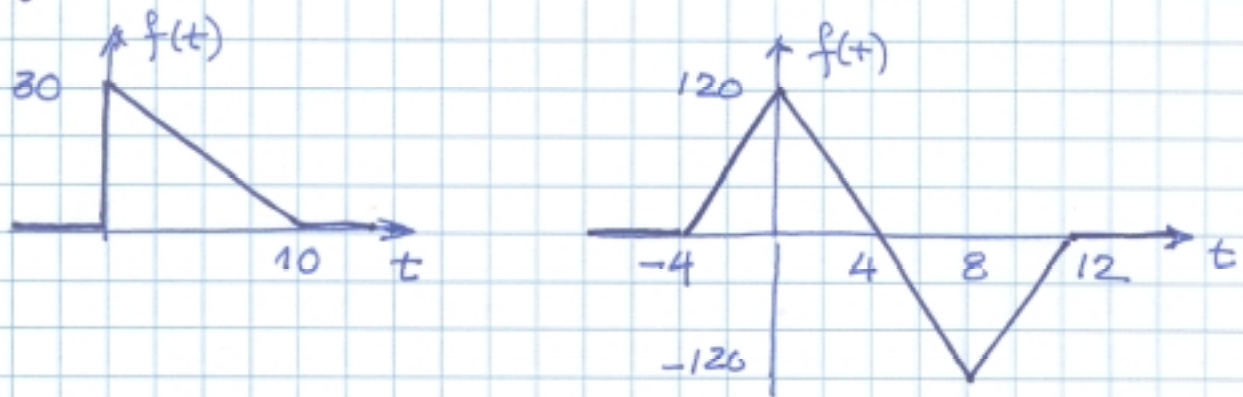


Figure 4:

