

$$V_{out} = - \sin(207t)$$

$$V_{out} = - \frac{1}{4 \times 10^{-3}} \cdot \frac{1}{207} \cdot \sin(207t)$$

$$V_{out} = - \frac{1}{4 \times 10^{-3}} \cdot \int_0^t (\cos(207t)) dt$$

$$R = 4 \text{ k}\Omega \quad C = 1 \mu\text{F}$$

$$RC = 4 \times 10^{-3} \cdot 10^{-6} \text{ s}$$

$$\text{if } \sin(t) = \cos(207t)$$


This is an integrator circuit

$$V_{out} = - \frac{1}{RC} \int V_{in} dt$$

$$V_{in} = -RC \cdot \frac{dV_{out}}{dt}$$

$$i = -C \cdot \frac{dV_{out}}{dt}$$


$$V_{in} = R \cdot i$$

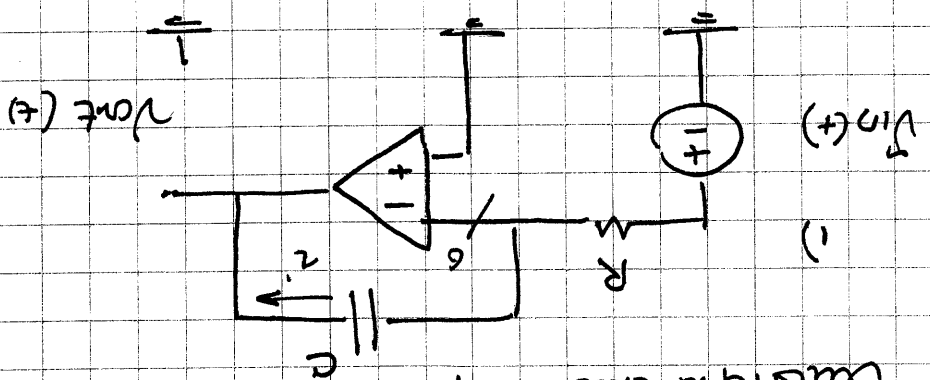

Wustern exam: #1

2.

Switch closed

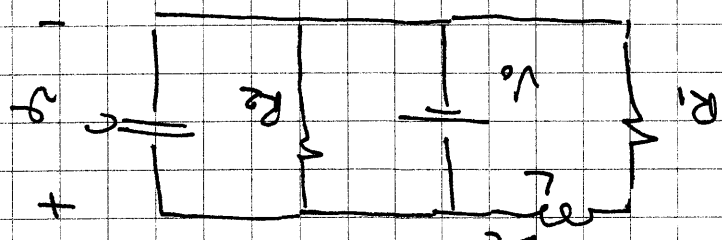

- $V_0 = 10V$
 - $R_1 = 20\Omega$
 - $R_2 = 0.5\Omega$
 - $L = 1H$
 - $C = 0.25F$
- All units in SI

at $t=0^-$:


$$V_c(0^-) = 10V$$

$$i_c(0^-) = -\frac{V_0}{R_1}$$

$$i_L(0^-) = -\frac{10}{20} ; i(0^-) = -0.5A$$

$$V_c(0^+) = 10V$$

$$i(0^+) = -0.5A$$

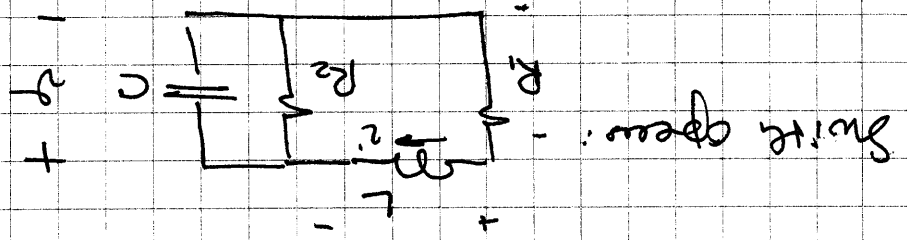

$$i + L \frac{di}{dt} + R_2 i = 0$$

$$i = \frac{V_0}{R_2} + C \cdot \frac{dV}{dt}$$

$$\left. \begin{aligned} L \frac{di}{dt} + R_1 i + R_2 i = 0 \\ C \frac{dV}{dt} - i = 0 \end{aligned} \right\}$$

$$\frac{di}{dt} + \frac{1}{R_1} i + \frac{1}{L} v = 0$$

$$\frac{dv}{dt} - \frac{1}{L} i + \frac{1}{R_2 C} v = 0$$

$$\begin{pmatrix} di/dt \\ dv/dt \end{pmatrix} + \begin{pmatrix} R_1/L & 1/C \\ 1/L & R_2/C \end{pmatrix} \begin{pmatrix} i \\ v \end{pmatrix} = 0$$

or

$$\frac{d}{dt} \begin{pmatrix} i \\ v \end{pmatrix} + \begin{pmatrix} R_1/L & 1/C \\ 1/L & R_2/C \end{pmatrix} \begin{pmatrix} i \\ v \end{pmatrix} = 0$$

Convert it into a 2nd order differential equation.

$$v = -L \frac{di}{dt} - R_1 i$$

From

$$\frac{dv}{dt} - \frac{1}{L} i + \frac{1}{R_2 C} v = 0$$

we obtain:

$$\frac{d}{dt} \left(-L \frac{di}{dt} - R_1 i \right) - \frac{1}{L} i + \frac{1}{R_2 C} \left(-L \frac{di}{dt} - R_1 i \right) = 0$$

$$L \frac{d^2 i}{dt^2} + R_1 \frac{di}{dt} + \frac{1}{R_2 C} i + \frac{R_1}{R_2 C} i = 0$$

$$\frac{d^2 i}{dt^2} + \left(\frac{1}{R_1} + \frac{1}{R_2 C} \right) \frac{di}{dt} + \left(\frac{1}{L} + \frac{R_1}{R_2 LC} \right) i = 0$$

or finally

$$\frac{d^2z}{dt^2} + \left(\frac{1}{R_1} + \frac{1}{CR_2} \right) \frac{dz}{dt} + \frac{1}{R_1} \left(1 + \frac{R_1}{R_2} \right) z = 0$$

$$s^2 + \left(\frac{1}{R_1} + \frac{1}{CR_2} \right) s + \frac{1}{R_1} \left(1 + \frac{R_1}{R_2} \right) = 0$$

$$R_1 = 20 \quad R_2 = 0.5 \\ L = 1 \\ C = 0.25$$

$$s^2 + \left(\frac{1}{20} + \frac{0.25 \times 0.5}{1} \right) s + \frac{1}{20} \left(1 + \frac{20}{0.5} \right) = 0$$

$$s^2 + 28s + 164 = 0$$

$$s_{1/2} = -14 \pm \sqrt{196 - 164}$$

$$s_{1/2} = -14 \pm \sqrt{32}$$

$$s_{1/2} = -14 \pm 4\sqrt{2}$$

Two real roots

$$x(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$x'(0+) = -0.5 \rightarrow k_1 + k_2 = -0.5$$

$$\left(\frac{dx}{dt} \right)_{0+} = k_1 s_1 + k_2 s_2$$

$$\text{Note from: } \left(\frac{dx}{dt} \right) + 20x + V = 0$$

$$\frac{dx}{dt} \Big|_{0+} = -20 \cdot x(0+) - V(0+) \quad ; \quad \frac{dx}{dt} \Big|_{0+} = -20 \cdot (-0.5) - 10 \\ \left(\frac{dx}{dt} \right)_{0+} = 0$$

5

$$K_2 = -K_1 \cdot \frac{s_2}{s_1}$$

$$K_1 s_1 + K_2 s_2 = 0$$

$$K_1 + K_2 = -0.5$$

$$K_1 \left(1 - \frac{s_1}{s_2}\right) = -\frac{1}{2}$$

$$K_1 = -\frac{1}{2} \cdot \frac{s_2}{s_2 - s_1}$$

$$s_{1/2} = -1.4 \pm 4j\sqrt{2}$$
$$s_1 = -1.4 + 4j\sqrt{2}$$
$$s_2 = -1.4 - 4j\sqrt{2}$$

$$K_2 = \frac{1}{2} \cdot \frac{s_2}{s_2 - s_1} \cdot \frac{s_1}{s_2}$$

$$K_2 = \frac{1}{2} \cdot \frac{s_2 - s_1}{s_1}$$

Hence, $s_2 - s_1 = -8j\sqrt{2}$

$$K_1 = -\frac{1}{2} \cdot \frac{-1.4 - 4j\sqrt{2}}{-8j\sqrt{2}} \quad ; \quad K_1 = -\frac{j+2j\sqrt{2}}{8j\sqrt{2}}$$

$$K_2 = \frac{1}{2} \cdot \frac{-1.4 + 4j\sqrt{2}}{-8j\sqrt{2}} \quad ; \quad K_2 = \frac{j-2j\sqrt{2}}{8j\sqrt{2}}$$

Alternativ: $K_1 = -\frac{j\sqrt{2}+4}{8j\sqrt{2}} \quad ; \quad K_1 = -\frac{j\sqrt{2}+4}{16}$

$$K_2 = \frac{j\sqrt{2}-4}{8j\sqrt{2}} \quad ; \quad K_2 = \frac{j\sqrt{2}-4}{16}$$

$$3. \quad f(t) = t e^{-at}$$

Alors on fera nous de ce que l'on trouve.

$$f_1(t) = e^{-at}$$

$$f_2(t) = t$$

$$f_3(t) = 1$$

then:

$$F_3(s) = \frac{1}{s}$$

$$F_2(s) = \frac{1}{s^2}$$

$$F_1(s) = \frac{1}{s+a}$$

$$F(s) = \frac{(s+a)^2}{1}$$

$$6) \quad f(t) = e^{-at} \sin at$$


$$f_1(t) = \sin at$$

$$F_1(s) = \frac{a}{s^2 + a^2}$$

$$F(s) = \frac{M}{(s+a)^2 + M^2}$$

$$f(t) = 30 \cdot u(t+4) - 30 \cdot u(t+4) + 30 \cdot u(t-4) - 30 \cdot u(t-4) + 30 \cdot u(t-12) - 30 \cdot u(t-12)$$
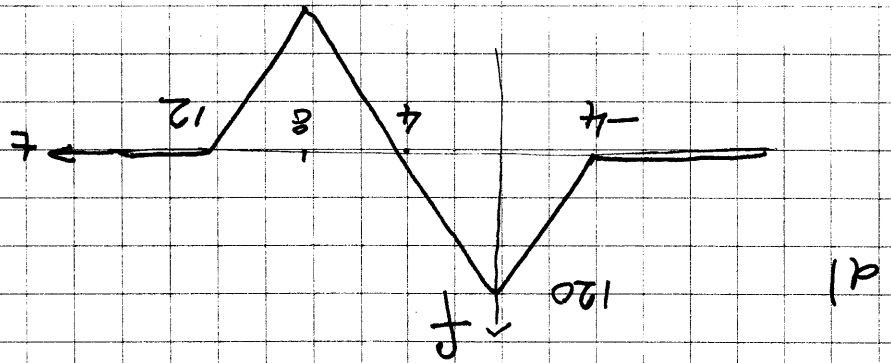
$$f(t) = 30 \cdot (t+4) \cdot [u(t+4) - u(t+)] - 30 \cdot (t-4) \cdot [u(t-4) - u(t-8)] + 30 \cdot (t-12) \cdot [u(t-12) - u(t-12)]$$




$$F(s) = -\frac{30}{s^2} + \frac{3}{s} e^{-10s} + \frac{30}{s} e^{-10s}$$

$$f(t) = -3t u(t) + 3(t-10) \cdot u(t-10) + 30 u(t-10)$$

$$f(t) = -3t u(t) + 3t u(t-10)$$
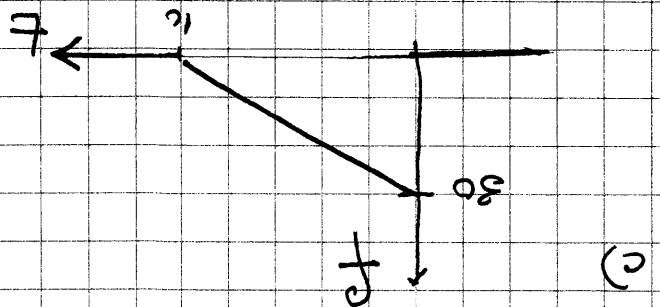
$$f(t) = -\frac{30}{s} \cdot t \cdot (u(t) - u(t-10))$$



$$f(s) = \frac{30}{s^2} e^{4s} - \frac{60}{s^2} + \frac{60}{s^2} e^{-8s} - \frac{80}{s^2} e^{-12s}$$

$$f(t) = 30/t+4) u(t+4) - 60t u(t) + 60/t-8) u(t-8) - 30/t-12) u(t-12)$$

$$f(t) = 30/t+4) u(t+4) - 30t u(t) - 120/t-8) + 30/t-8) u(t-8) + 120/t-8) - 30t u(t) + 120/t-12) - 30/t-12) u(t-12) + 30/t-8) u(t-8) - 120/t-8) - 30/t-12) u(t-12)$$

5

$$4. F(s) = \frac{(s+2)(s^2+4s+8)}{3s+1}$$

$$6. F(s) = \frac{(s+1)^2(s+4)}{s(s+2)e^{-3s}}$$

$$a) F(s) = \frac{(s+2)(s^2+4s+8)}{3s+1}$$

$$= \frac{A}{3s+2} + \frac{Bs+C}{s^2+4s+8}$$

$$A = \lim_{s \rightarrow -2} (s+2) \cdot F(s)$$

$$A = \lim_{s \rightarrow -2} \frac{Bs+C}{s^2+4s+8}$$

$$A = \frac{-6+C}{4-8+8}$$

$$A = -\frac{4}{5}$$

$$\text{Hence: } F(s) = -\frac{4}{5} \cdot \frac{1}{s+2} + \frac{Bs+C}{s^2+4s+8}$$

$$\text{Hence: } \frac{Bs+C}{s^2+4s+8} = \frac{(s+2)(s^2+4s+8)}{3s+1} + \frac{4}{5} \cdot \frac{1}{s+2}$$

$$F(s) = \frac{3s+1}{(s+2)(s^2+4s+8)} + \frac{4}{5(s+2)}$$

$$= \frac{4(3s+1) + 5(s^2+4s+8)}{4(s+2)(s^2+4s+8)}$$

$$= \frac{5s^2 + 32s + 44}{4(s+2)(s^2+4s+8)}$$

$$= \frac{5s(s+2) + 22(s+2)}{4(s+2)(s^2+4s+8)}$$

$$= \frac{5s+22}{4(s^2+4s+8)}$$

$$= \frac{5s+22}{4[(s+2)^2+4]}$$

$$= \frac{5(s+2)}{4[(s+2)^2+4]} + \frac{12}{4[(s+2)^2+4]}$$

$$F(s) = \frac{4(s+2)}{5} + \frac{4[(s+2)^2+4]}{5(s+2)} + \frac{3}{(s+2)^2+4}$$

$$f(t) = \left\{ -\frac{4}{5} e^{-2t} + \frac{4}{5} \cos 2t e^{-2t} + 3 \sin 2t e^{-2t} \right\} u(t)$$

$$f(t) = \frac{1}{4} \left\{ -5 + 5 \cos 2t + 6 \sin 2t \right\} e^{-2t} u(t)$$

6)

$$F(s) = \frac{S(s+2)e^{-3s}}{(s+1)^2(s+4)}$$

$$F(s) = \frac{S(s+2)}{(s+1)^2(s+4)}$$

$$= \frac{A}{s+1} + \frac{B}{(s+1)^2} + \frac{C}{s+4}$$

$$C = \lim_{s \rightarrow -4} F(s)$$

$$= \frac{-4 \cdot (-4+2)}{(-4+1)^2}$$

$$C = \frac{8}{9}$$

$$B = \lim_{s \rightarrow -1} (s+1)^2 F(s)$$

$$= \frac{-1 \cdot (-1+2)}{-1+4}$$

$$B = -\frac{1}{3}$$

$$A = \lim_{s \rightarrow -1} \frac{d}{ds} (s+1)^2 F(s)$$

$$= \lim_{s \rightarrow -1} \frac{d}{ds} \frac{S(s+2)}{s(s+4)}$$

$$= \lim_{s \rightarrow -1} \frac{(s+2)(s+4)^2 - S(s+4)^2}{(s(s+4))^2}$$

$$A = \frac{-2+2+1(-1+2)}{(-1+4)^2}$$

$$A = \frac{1}{9}$$


11

$$f(t) = \left\{ \frac{1}{3} e^{-(t-3)} - \frac{1}{3} (t-3) e^{-(t-3)} + \frac{9}{8} e^{-4(t-3)} \right\} u(t-3)$$

$$F(s) = e^{-3s} \cdot F_1(s)$$

$$f(t) = \left\{ \frac{1}{3} e^{-t} - \frac{1}{3} t e^{-t} + \frac{9}{8} e^{-4t} \right\} u(t)$$
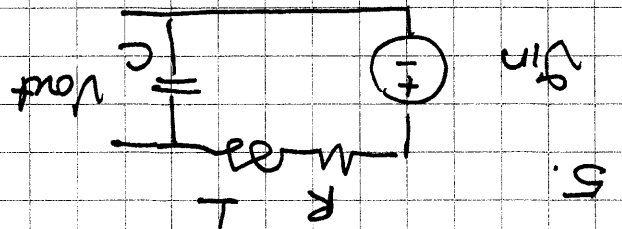
$$F_1(s) = \frac{1}{s} \cdot \frac{1}{s+1} - \frac{1}{s} \cdot \frac{1}{(s+1)^2} + \frac{9}{8} \cdot \frac{1}{s+4}$$



$R = 4 \Omega$
 $L = 1 \text{ H}$
 $C = 0.2 \text{ F}$

$$V_{out} = \frac{1}{CS} \cdot (R + LS + \frac{1}{C}) V_{in}$$

$$H(s) = \frac{1}{LCs^2 + RCs + 1}$$

$$H(s) = \frac{1}{0.25s^2 + 0.8s + 1}$$

$$H(s) = \frac{1}{s^2 + 4s + 5}$$

Impulse response: $V_{out}(s) = H(s)$

$V_{in}(t) = \delta(t)$
 $V_{in}(s) = 1$

$$V_{out}(s) = \frac{1}{(s+2)^2 + 1}$$

$$V_{out}(t) = 5 \sin t \cdot e^{-2t} u(t)$$

Step response: $V_{out}(s) = \frac{1}{s} \cdot \frac{1}{s^2 + 4s + 5}$

$$V_{out}(s) = \frac{1}{s} + \frac{1}{s+2} + \frac{1}{(s+2)^2 + 1}$$

$$A = \lim_{s \rightarrow 0} s \cdot \frac{1}{s(s^2 + 4s + 5)} = \frac{1}{5} \quad ; \quad A = 1$$

$$\frac{s[(s+2)^2 + 1]}{s} = \frac{1}{s} - \frac{1}{s-1} = \frac{s[(s+2)^2 + 1]}{s^2 - (s+2)^2 - 1} = \frac{s[(s+2)^2 + 1]}{4 - s^2 - 4s - 4} = \frac{s[(s+2)^2 + 1]}{s^2 + 4s}$$

→ erwarten

$$\frac{d \text{Voll}}{dt} = \text{Erlöse} - \text{Kosten}$$

$$\frac{d \text{Voll}}{dt} = (\text{Erlöse} + \text{Kosten} - \text{Kosten} + \text{Kosten}) \cdot u(t)$$

Impulsantwort = $\frac{d}{dt}$ (step response)

Check: $f(t) = \mathcal{L}^{-1}(u(t))$

$$f(t) = (1 - \cos t) - 2 \sin t \cdot u(t)$$

$$F(s) = \frac{1}{s} - \frac{s}{s^2+1} - \frac{2}{s^2+1}$$

Heur:

$$F(s) = \frac{s+4}{s^2+1} - \frac{s+2}{s^2+1} - \frac{2}{s^2+1}$$

Note that