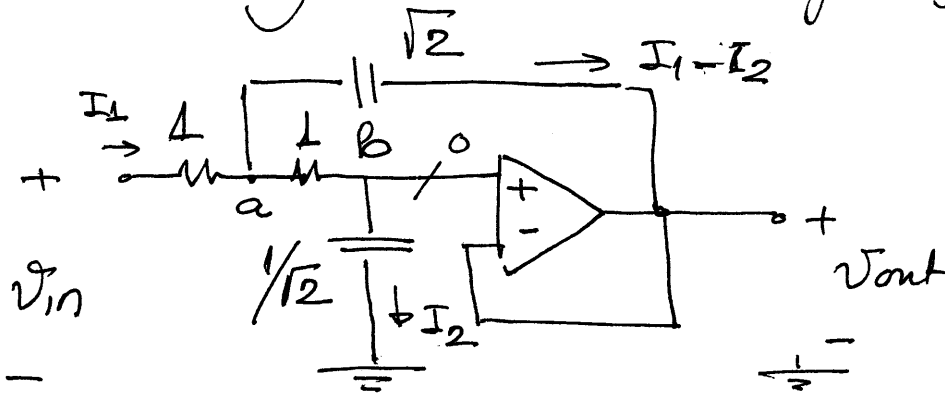


Sallen-key normalized low-pass filter



$$R_1 = R_2 = 1$$

$$C_1 = \sqrt{2}$$

$$C_2 = 1/\sqrt{2}$$

ideal op-amp

$$V_{out} = V_b$$

$$I_2 = \frac{1}{\sqrt{2}} s \cdot V_{out} \quad (1)$$

$$V_{in} - 1 \times I_1 - (1 + \frac{\sqrt{2}}{s}) I_2 = 0$$

KVL:

$$V_{in} = I_1 + (1 + \frac{\sqrt{2}}{s}) \cdot I_2 \quad (2)$$

$$V_{in} = I_1 + (1 + \frac{\sqrt{2}}{s}) \cdot \frac{1}{\sqrt{2}} s \cdot V_{out}$$

$$V_{in} = I_1 + \frac{s + \sqrt{2}}{\sqrt{2}} \cdot V_{out}$$

$$I_1 = V_{in} - \frac{s + \sqrt{2}}{\sqrt{2}} \cdot V_{out}$$

KVL:

2

$$V_{in} - 1 \times I_1 - \frac{1}{\sqrt{2}S} (I_1 - I_2) - V_{out} = 0$$

$$V_{in} = \left(1 + \frac{1}{\sqrt{2}S}\right) I_1 - \frac{1}{\sqrt{2}S} \cdot I_2 + V_{out}$$

Hence,

$$V_{in} = \left(1 + \frac{1}{\sqrt{2}S}\right) \cdot \left(V_{in} - \frac{S + \sqrt{2}}{\sqrt{2}} V_{out}\right) - \frac{1}{\sqrt{2}S} \cdot \frac{1}{\sqrt{2}} S V_{out} + V_{out}$$

$$V_{in} \left(1 - 1 - \frac{1}{\sqrt{2}S}\right) = - \left(1 + \frac{1}{\sqrt{2}S}\right) \cdot \frac{S + \sqrt{2}}{\sqrt{2}} V_{out} + \frac{1}{2} V_{out}$$

$$- \frac{1}{\sqrt{2}S} \cdot V_{in} = - \frac{(\sqrt{2}S + 1)(S + \sqrt{2})}{2S} V_{out} + \frac{1}{2} V_{out}$$

$$V_{in} = \left(\frac{(\sqrt{2}S^2 + S + 2S + \sqrt{2})}{\sqrt{2}} - \frac{S}{\sqrt{2}} \right) V_{out}$$

$$V_{in} = \frac{\sqrt{2}S^2 + 2S + \sqrt{2}}{\sqrt{2}} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{S^2 + \sqrt{2}S + 1}$$

Zeros: 2 at infinity

Poles: 2 finite poles at $S^2 + \sqrt{2}S + 1 = 0$

$$S_{1/2} = -\frac{\sqrt{2}}{2} \pm \sqrt{\left(\frac{\sqrt{2}}{2}\right)^2 - 1}$$

$$= -\frac{\sqrt{2}}{2} \pm \sqrt{-\frac{1}{2}}$$

$$= -\frac{\sqrt{2}}{2} \pm j \frac{\sqrt{2}}{2}$$

$$H(j\omega) = \frac{1}{(1-\omega^2) + j\sqrt{2}\omega}$$

$$|H(j\omega)|^2 = \frac{1}{(1-\omega^2)^2 + 2\omega^2}$$

or $|H(j\omega)| = \frac{1}{\sqrt{(1-\omega^2)^2 + 2\omega^2}}$


$$|H(j\omega)| = \frac{1}{\sqrt{1+\omega^4}}$$

$$\angle H(j\omega) = -\arctan \frac{\sqrt{2}\omega}{1-\omega^2}$$


Amplitude frequency response:



Low pass filter
(Butterworth design)

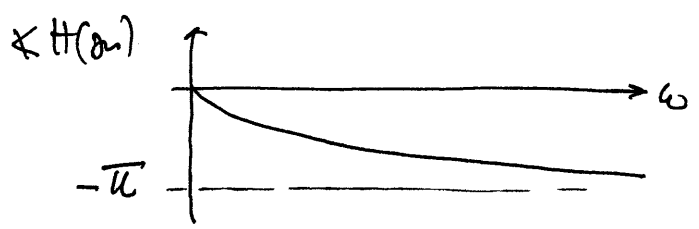

(2)

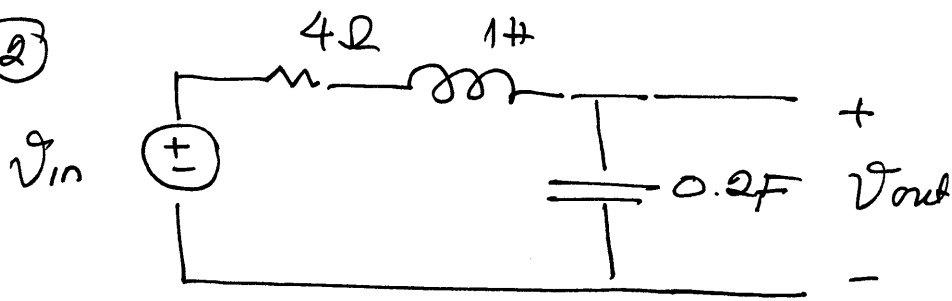

(4)

$$V_{out}(s) = \frac{1/cs}{R + Ls + \frac{1}{Cs}}$$

$$H(s) = \frac{1}{LC} \cdot \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$H(s) = \frac{1}{0.2} \cdot \frac{1}{s^2 + 4s + 5}$$

$$H(s) = \frac{5}{s^2 + 4s + 5} \quad ; \quad H(s) = \frac{5}{(s+2)^2 + 1}$$

Impulse response:

$$h(t) = \mathcal{L}^{-1}\{H(s)\}$$

$$h(t) = \mathcal{L}^{-1}\left\{\frac{5}{(s+2)^2 + 1}\right\}$$

$$h(t) = 5e^{-2t} \cdot \sin t \cdot u(t)$$

complete response
particular solution
natural response
transient response

Step response:

$$V_{out}(s) = \frac{5}{(s+2)^2 + 1} \cdot V_{in}(s) \quad ; \quad V_{in}(s) = \frac{1}{s}$$

(step function)

$$V_{out}(s) = \frac{5}{(s+2)^2 + 1} \times \frac{1}{s}$$

$$V_{out}(s) = \frac{A}{s} + \frac{Bs+C}{(s+2)^2+1}$$

$$\Delta = \lim_{s \rightarrow 0} s \cdot V_{out}(s)$$

$$s \rightarrow 0 \\ = \lim_{s \rightarrow 0} \frac{5}{(s+2)^2+1}$$

$$\Delta = 1$$

$$V_{out}(s) = \frac{1}{s} + \frac{Bs+C}{(s+2)^2+1}$$

$$\frac{Bs+C}{(s+2)^2+1} = -\frac{1}{s} + \frac{5}{s[(s+2)^2+1]}$$

$$\frac{Bs+C}{(s+2)^2+1} = \frac{-(s+2)^2-1+5}{s[(s+2)^2+1]} \\ = \frac{-s^2-4s-1+5}{s[(s+2)^2+1]}$$

$$Bs+C = -s-4$$

$$B = -1; C = -4$$

$$\text{Hence: } V_{out}(s) = \frac{1}{s} - \frac{s+4}{(s+2)^2+1}$$

$$V_{out}(s) = \frac{1}{s} - \frac{s+2}{(s+2)^2+1} - \frac{2}{(s+2)^2+1}$$

$$V_{out}(t) = (1 - e^{-2t} \cos t - 2e^{-2t} \sin t) u(t)$$


forced steady state

transient

Complete response

3

6

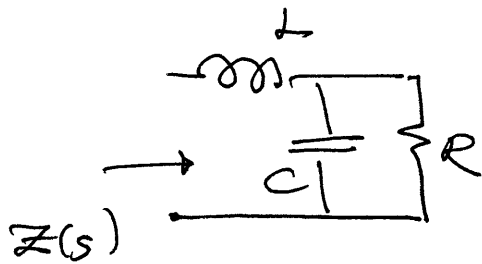

$$Z(s) = Ls + \frac{R \cdot \frac{1}{Cs}}{R + \frac{1}{Cs}}$$

$$Z(s) = Ls + \frac{R}{1 + RCs}$$

$$Z(j\omega) = j\omega L + \frac{R}{1 + j\omega RC}$$

$$Z(j\omega) = j\omega L + \frac{R(1 - j\omega RC)}{(1 + j\omega RC)(1 - j\omega RC)}$$

$$Z(j\omega) = \frac{R}{1 + (\omega RC)^2} + j\omega \left(L - \frac{R^2 C}{1 + (\omega RC)^2} \right)$$

Resonance:

$$Z(j\omega) = \text{Real}$$

$$X(\omega) = 0$$

$$\omega \left(L - \frac{R^2 C}{1 + (\omega RC)^2} \right) = 0$$

$\omega = 0$: Trivial solution

$$L - \frac{R^2 C}{1 + (\omega RC)^2} = 0 ; \quad \omega_r = \frac{1}{RC} \sqrt{\frac{R^2 C}{L} - 1}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{1}{R^2 C^2}}$$

$$\omega_r = \omega_0 \sqrt{1 - \frac{L}{CR^2}} ; \quad \omega_0 = \frac{1}{\sqrt{LC}}$$