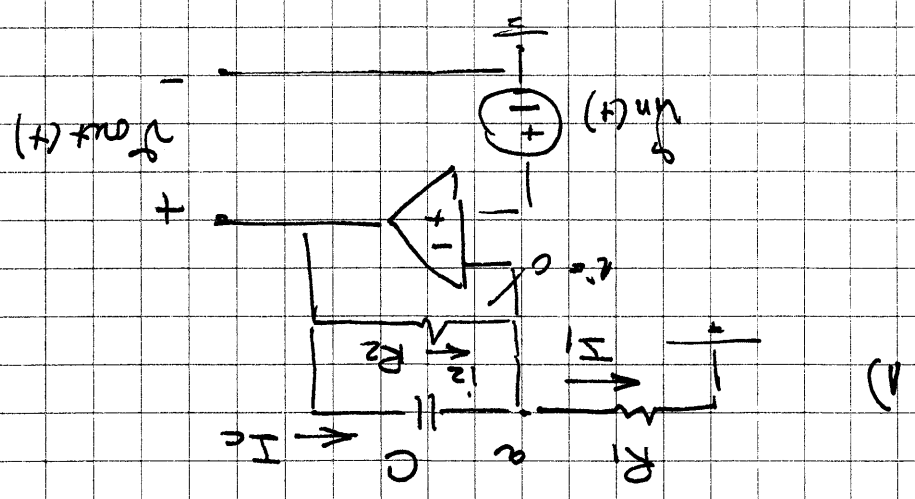


Wiederholung #2:

ausgabe #2:



$$G = \frac{R_2}{R_1 + R_2}$$

$V_a = V_{in}$ ; input current = 0 ideal op amp

in-s-dennar.

$$I_1 = \frac{V_{in}}{R_1}$$

$$V_a = V_{in}$$

$$I_1 + I_2 = I_c$$

$$\frac{1}{C} I_c = R_2 \cdot I_2$$

$$V_{out} - R_2 \cdot I_2 - V_{in} = 0$$

hierzu:

$$I_1 + I_2 = \frac{V_{in}}{R_1}$$

$$I_c = R_2 \cdot I_2$$

$$I_2 = \frac{1}{1 + R_2 \cdot C} \cdot \frac{V_{in}}{R_1}$$

Hence, 
$$V_{out} = R_2 \cdot \frac{1}{1 + R_2 C s} \cdot \frac{V_{in}}{R_1} + V_{in}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)}$$

$$H(s) = \frac{R_2}{R_1} \cdot \frac{1}{1 + R_2 C s} + 1$$

$$H(s) = \frac{\frac{R_2}{R_1} + 1 + R_2 C s}{1 + R_2 C s}$$

$$H(s) = \frac{\frac{R_2}{R_1} + C s}{\frac{R_2 + R_1}{R_1 R_2} + C s}$$

$$H(s) = \frac{s + \frac{1}{R_2 C}}{s + \frac{1}{C} \cdot \left( \frac{1}{R_1} + \frac{1}{R_2} \right)}$$

$$C = 1 \mu F$$

$$H(s) = \frac{s + 4}{s + 2}$$

Hence:

$$\frac{1}{R_2 C} = 2$$

$$R_2 C = \frac{1}{2}$$

$$C = 1 \mu F$$

$$R_2 = 0.5 \times 10^6$$

$$R_2 = 500 \text{ k}\Omega$$

$$\frac{1}{R_1} + \frac{1}{R_2} = 4 \times 10^{-6}$$

$$\frac{1}{R_1} = 4 \times 10^{-6} - 2 \times 10^{-6} \quad ; \quad R_1 = 500 \text{ k}\Omega$$

def. oper.  $H(s) = \frac{s+4}{s+2}$

$$V_{out}(s) = \frac{1}{s} \times H(s)$$

$$= \frac{s+4}{s+2}$$

$$= \frac{s+4}{s} + \frac{B}{s+2}$$

$$A+B=1$$


$$2A=4 \Rightarrow A=2$$

$$B=-1$$

$$V_{out}(s) = \frac{s}{s} - \frac{1}{s+2}$$

$$V_{out}(t) = 2u(t) - e^{-2t}u(t)$$

2)

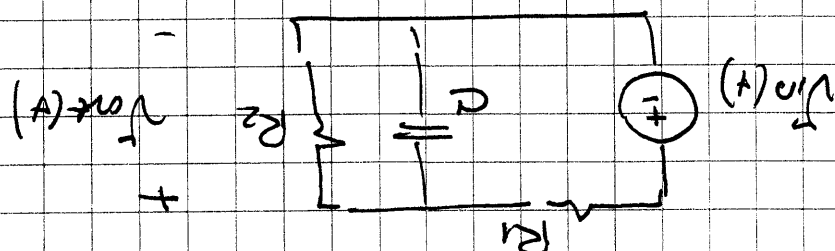

$R_1 = 50\Omega$   
 $R_2 = 200\Omega$   
 $C = 2.5\text{mF}$

at  
 $u_{in}(t) = 10e u(t)$   
 $u_{e(0-)} = 4V$

$$H(s) = \frac{R_2 \cdot Cs}{R_2 + \frac{1}{Cs}}$$

$$\frac{R_2 \cdot Cs}{R_2 + \frac{1}{Cs}}$$

$$H(s) = \frac{R_2}{R_2 + R_2Cs}$$

$$\frac{R_2}{R_2 + R_2Cs}$$

$$H(s) = \frac{R_2}{R_1 + R_2 + R_1R_2Cs}$$

$$\frac{R_2}{R_1 + R_2 + R_1R_2Cs}$$

$$H(s) = \frac{\frac{R_1R_2}{R_1+R_2}}{CR_1 + s}$$

$$Reg = \frac{R_1R_2}{R_1+R_2}$$

$$H(s) = \frac{\frac{1}{CR_1}}{s + Reg \cdot C}$$


$$\frac{1}{CR_1}$$

$$H(s) = \frac{s + \frac{1}{2.5 \times 10^{-3}}}{s + \frac{1}{140 \times 2.5 \times 10^{-3}}}$$

$$Reg = \frac{50 \times 200}{250} = 40\Omega$$

$$Reg = 40\Omega$$

4

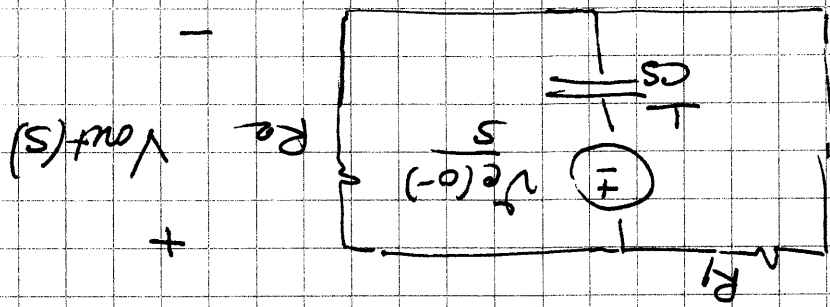

- zero-input respon.

Zero-state (+) =  $(-10e^{-10t} + 10e^{-2t})u(t)$

$$V_{out}(s) = -\frac{10}{s+10} + \frac{10}{s+2}$$

$$\begin{aligned} 2A - 10A &= 80 \\ A &= -10 \\ B &= 10 \end{aligned}$$

$$\begin{aligned} 2A + 10B &= 80 \\ A + B &= 0 \end{aligned}$$

$$= \frac{A}{s+10} + \frac{B}{s+2}$$

$$V_{out}(s) = \frac{8}{s+10} - \frac{10}{s+2}$$

$$V_{in}(s) = \frac{10}{s+2}$$

Zero state respon:

$$V_{in}(+) = 10e^{-2t}u(t)$$

$$H(s) = \frac{8}{s+10}$$

$$H(s) = \frac{1000}{2.5 \times 50} = s + \frac{1000}{40 \times 2.5}$$

$$V_{out}(t) = (-6e^{-10t} + 10e^{-2t}) u(t)$$

$$V_{out}(t) = (-10e^{-10t} + 10e^{-2t} + 4e^{-2t}) u(t)$$

- complete response:

$$V_{out}^{zero-input} = 4e^{-10t} u(t)$$

$$= \frac{4}{s+10}$$

$$V_{out} = \frac{1}{s+10} + \frac{4 \times 2.5 \times 10^{-3}}{s+10} = \frac{1}{s+10}$$

$$= \frac{1}{s + \frac{1}{RC}} \cdot V_c(-)$$

$$= \frac{RC \cdot C}{RCs + 1} \cdot V_c(-)$$

$$V_{out} = \frac{RC}{RCs + 1} \times \frac{V_c(-)}{s}$$

$$V_{out}(s) = \frac{R_1 R_2}{(R_1 + R_2) \left( \frac{R_1 R_2}{s} + 1 \right)} \times V_c(-)$$

-10 is the natural frequency of the circuit.

Note that  $V_{in}(t) = 10e^{-10t}$  is not well defined.

$$V_{out}(t) = 807e^{-10t} u(t) = \frac{80}{s+10} = \frac{8}{s+10} \times \frac{10}{s+10}$$

Then  $V_{out}(s) = \frac{8}{s+10} \times V_{in}(s)$

Let  $V_{in}(t) = 10e^{-10t} u(t) ; V_{in}(s) = 0$

denominator:  $(-6e^{-10t} + 10e^{-10t}) u(t)$

- Steady-state:  $\phi$

Natural response:  $-6e^{-10t} u(t)$

Forced response:  $10e^{-10t} u(t)$

$$V_{out}(t) = -e^{-t} (e^{-3t} - 1) u(t); \quad V_{out}(t) = (e^{-t} - e^{-4t}) u(t)$$

$$t > 0 \quad V_{out}(t) = \int_t^{\infty} 3e^{-\tau} \cdot e^{-3\tau} d\tau = 3e^{-t} \int_t^{\infty} e^{-4\tau} d\tau = 3e^{-t} \left[ -\frac{1}{4} e^{-4\tau} \right]_t^{\infty} = \frac{3}{4} e^{-t}$$

$$t < 0 \quad V_{out}(t) = 0$$

$$V_{out}(t) = \int_{-\infty}^t e^{-4\tau} \cdot 3e^{-3\tau} u(\tau) d\tau = \int_{-\infty}^t 3e^{-7\tau} u(\tau) d\tau = \int_0^t 3e^{-7\tau} d\tau = -\frac{3}{7} e^{-7\tau} \Big|_0^t = \frac{3}{7} (1 - e^{-7t}) u(t)$$

$$V_{out}(t) = h(t) * \delta'(t)$$

$$h(t) = e^{-4t} u(t)$$

$$e'u(t) = 3e^{-t} u(t)$$

$$H(s) = \frac{1}{s + \frac{1}{0.25}} = \frac{1}{s + 4}$$

$$h(t) = \frac{1}{s + 4}$$

$$H(s) = \frac{1/C}{s + 1/RC}$$

$$H(s) = \frac{\frac{1}{Cs} \times R}{R + \frac{1}{Cs}} = \frac{R}{1 + RCs}$$

$$R = 0.25 \Omega$$

$$C = 1 F$$

