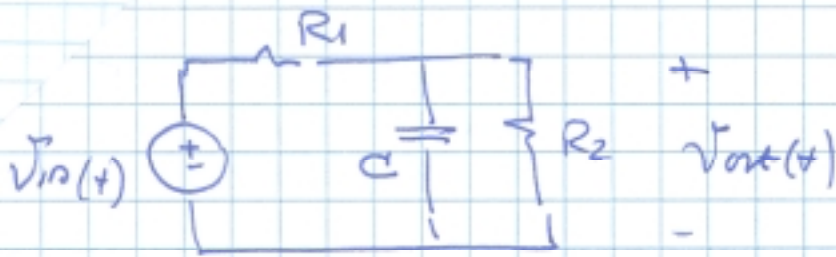


①



$$R_1 = 50 \Omega$$

$$R_2 = 200 \Omega$$

$$C = 2.5 \text{ mF}$$

$$V_{in}(t) = 10e^{-2t} u(t)$$

$$V_c(0^-) = 4 \text{ V}$$

$$H(s) = \frac{R_2 \cdot \frac{1}{Cs}}{R_2 + \frac{1}{Cs}} \cdot \frac{1}{R_1 + \frac{R_2 \cdot \sqrt{Cs}}{R_2 + \frac{1}{Cs}}}$$

$$H(s) = \frac{R_2}{1 + R_2 Cs} \cdot \frac{1}{R_1 + \frac{R_2}{1 + R_2 Cs}}$$

$$H(s) = \frac{R_2}{R_1 + R_2 + R_1 R_2 Cs}$$

$$H(s) = \frac{\frac{1}{CR_1}}{\frac{R_1 + R_2}{R_1 R_2 C} + s}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$H(s) = \frac{\frac{1}{CR_1}}{s + \frac{1}{R_{eq} \cdot C}}$$

$$H(s) = \frac{\frac{1}{2.5 \times 10^{-3}} \cdot \frac{1}{50}}{s + \frac{1}{40 \times 2.5 \times 10^{-3}}}$$

$$R_{eq} = \frac{50 \times 200}{250}$$

$$R_{eq} = 40 \Omega$$

$$H(s) = \frac{\frac{100\phi}{2.5 \times 5\phi}}{s + \frac{1000}{40 \times 2.5}}$$

$$H(s) = \frac{8}{s+10}$$

- Zero state response:

$$V_{in}(t) = 10e^{-2t} u(t)$$

$$V_{in}(s) = \frac{10}{s+2}$$

$$V_{out}(s) = \frac{8}{s+10} \cdot \frac{10}{s+2}$$

$$= \frac{A}{s+10} + \frac{B}{s+2}$$


$$\begin{aligned} A+B &= 0 \\ 2A+10B &= 80 \end{aligned}$$

$$\begin{aligned} 2A-10A &= 80 \\ A &= -10 \\ B &= 10 \end{aligned}$$

$$V_{out}(s) = -\frac{10}{s+10} + \frac{10}{s+2}$$

$$V_{zero-state}(t) = (-10e^{-10t} + 10e^{-2t}) u(t)$$

- Zero-input response:

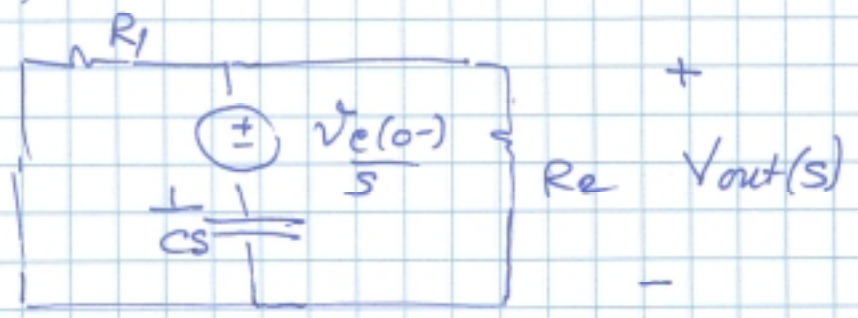

(3)

$$\tilde{V}_{out}(s) = \frac{R_1 R_2}{R_1 + R_2} \times \frac{V_C(0^-)}{s}$$

$$\frac{R_1 R_2}{R_1 + R_2} + \frac{1}{Cs}$$

$$\tilde{V}_{out} = \frac{R_{eq}}{R_{eq} + \frac{1}{Cs}} \times \frac{V_C(0^-)}{s}$$

$$= \frac{R_{eq} \cdot C}{R_{eq} \cdot Cs + 1} \cdot V_C(0^-)$$

$$= \frac{1}{s + \frac{1}{R_{eq} \cdot C}} \cdot V_C(0^-)$$

$$\tilde{V}_{out} = \frac{1}{s + \frac{1}{40 \times 2.5 \times 10^{-3}}} \cdot 4$$

$$= \frac{4}{s + 10}$$

$$\underset{\text{zero-input}}{V_{out}} = 4e^{-10t} u(t)$$

- complete response:

$$\tilde{V}_{out}(s) = (-10e^{-10t} + 10e^{-2t} + 4e^{-10t}) u(t)$$

$$\tilde{V}_{out}(s) = (-6e^{-10t} + 10e^{-2t}) u(t)$$

Forced response: $10e^{-2t} u(t)$

Natural response: $-6e^{-10t} u(t)$

- Steady-state: ϕ
transient: $(-6e^{-10t} + 10e^{-2t}) u(t)$

Let $V_{in}(t) = 10e^{-10t} u(t)$; $V_C(0^-) = 0$

Then $V_{out}(s) = \frac{8}{s+10} \times V_{in}(s)$

$$= \frac{8}{s+10} \times \frac{10}{s+10}$$

$$= \frac{80}{(s+10)^2}$$


$$V_{out}(t) = 80t e^{-10t} u(t)$$

! not well defn.

Note that $V_{in}(t) = 10e^{-10t} u(t)$

-10 is the natural frequency of the circuit.

(2)

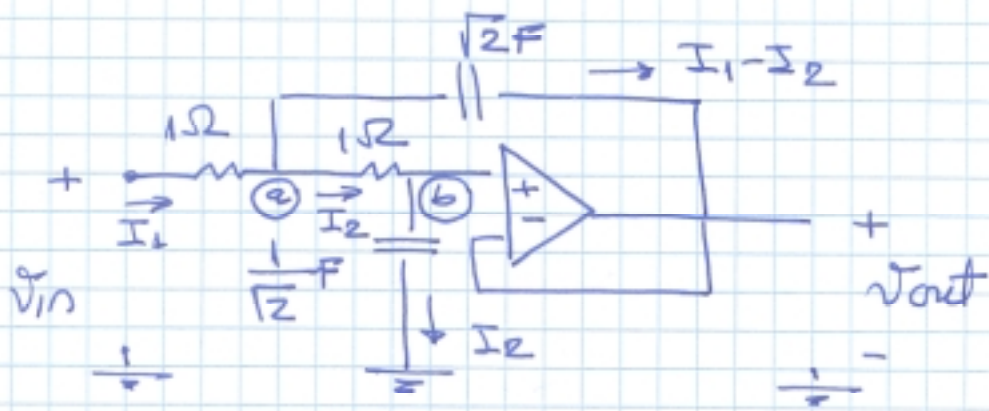

(5)

Sallen-key filter:

$$V_{out} = V_b \quad (1)$$

$$I_2 = \frac{1}{\sqrt{2}} s \cdot V_{out} \quad (2)$$

$$\text{KVL: } V_a = \left(1 + \frac{\sqrt{2}}{s}\right) I_2 \quad (3)$$

$$\text{using (2): } = \left(1 + \frac{\sqrt{2}}{s}\right) \times \frac{s}{\sqrt{2}} \cdot V_{out}$$

$$= \left(\frac{s}{\sqrt{2}} + 1\right) \cdot V_{out} \quad (4)$$

$$\text{KVL: } V_{in} - V_a = 1 \times I_1$$

$$V_{in} = V_a + I_1$$

$$\text{Hence: } I_1 = V_{in} - V_a$$

$$\text{From (4): } I_1 = V_{in} - \left(\frac{s}{\sqrt{2}} + 1\right) \cdot V_{out} \quad (5)$$

Voltage across capacitor of $\sqrt{2} F$ is:

$$V_a - V_{out} = \frac{1}{\sqrt{2}S} \cdot (I_1 - I_2) \quad (6)$$

Substituting (2), (4), and (5) into (6) gives:

$$\left(\frac{S}{\sqrt{2}} + 1\right) \cdot V_{out} - V_{out} = \frac{1}{\sqrt{2}S} \times \left(V_{in} - \left(\frac{S}{\sqrt{2}} + 1\right) V_{out} - \frac{1}{\sqrt{2}} S V_{out}\right)$$

Hence,

$$\frac{S}{\sqrt{2}} \cdot V_{out} = \frac{1}{\sqrt{2}S} \cdot V_{in} - \frac{1}{\sqrt{2}S} \cdot \left(\frac{S}{\sqrt{2}} + 1 + \frac{S}{\sqrt{2}}\right) V_{out}$$

$$\frac{S}{\sqrt{2}} \cdot V_{out} = \frac{1}{\sqrt{2}S} \cdot V_{in} - \frac{1}{\sqrt{2}S} \cdot (S\sqrt{2} + 1) \cdot V_{out} / \sqrt{2}S$$

$$S^2 V_{out} = V_{in} - (S\sqrt{2} + 1) V_{out}$$

$$\text{rr: } \frac{V_{out}}{V_{in}} = \frac{1}{S^2 + \sqrt{2}S + 1}$$

Zeros: Two at infinity.

Poles: Two finite poles: $S^2 + \sqrt{2}S + 1 = 0$

$$S/2 = -\frac{\sqrt{2}}{2} \pm \sqrt{\left(\frac{\sqrt{2}}{2}\right)^2 - 1}$$

$$S/2 = -\frac{\sqrt{2}}{2} \pm j\frac{\sqrt{2}}{2}$$

$$S/2 = \frac{1}{\sqrt{2}}(-1 \pm j) \quad (\text{on a circle})$$



Frequency respons:

$$H(s) = \frac{1}{s^2 + \sqrt{2}s + 1}$$

$$H(j\omega) = \frac{1}{1 - \omega^2 + j\sqrt{2}\omega}$$

$$|H(j\omega)| = \frac{1}{\sqrt{(1 - \omega^2)^2 + 2\omega^2}}$$
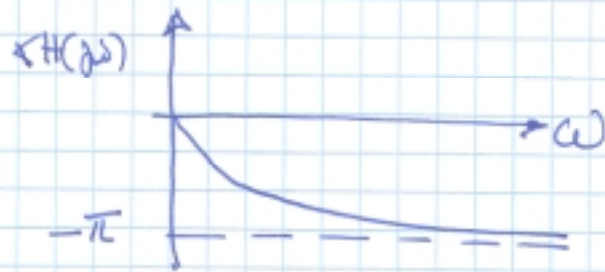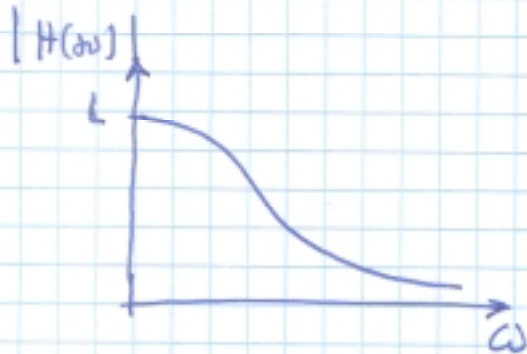
$$\angle H(j\omega) = -\arctg \frac{\sqrt{2}\omega}{1 - \omega^2}$$



This is a low-pass filter.

3)



$R = 0.25 \Omega$
 $C = 1 F$

$$H(s) = \frac{\frac{1}{Cs} \times R}{R + \frac{1}{Cs}} \quad ; \quad H(s) = \frac{R}{1 + RCs}$$

$$H(s) = \frac{1/C}{s + 1/RC}$$

$$H(s) = \frac{1}{s + \frac{1}{0.25}} \quad ; \quad H(s) = \frac{1}{s + 4}$$

$$h(t) = e^{-4t} u(t)$$

$$i_{in}(t) = 3e^{-t} u(t)$$

$$v_{out}(t) = h(t) * i_{in}(t)$$

$$v_{out}(t) = \int_{-\infty}^{\infty} e^{-4\tau} u(\tau) \cdot 3e^{-(t-\tau)} u(t-\tau) d\tau$$

$$= \int_{-\infty}^{\infty} 3e^{-t} \cdot e^{-3\tau} u(\tau) u(t-\tau) d\tau$$


$t < 0 \quad v_{out}(t) = 0$

$t \geq 0 \quad v_{out}(t) = \int_0^t 3e^{-t} \cdot e^{-3\tau} d\tau$

$$= 3e^{-t} \cdot \int_0^t e^{-3\tau} d\tau = 3e^{-t} \cdot \left. \frac{e^{-3\tau}}{-3} \right|_0^t$$

$$v_{out}(t) = -e^{-t} (e^{-3t} - 1) u(t) \quad ; \quad v_{out}(t) = (e^{-t} - e^{-4t}) u(t)$$

(4)

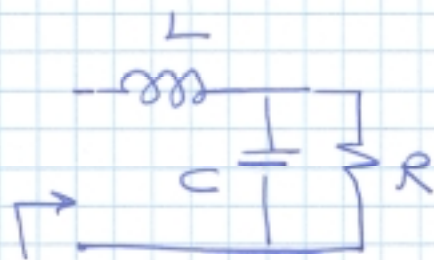 $Z(s)$

$$Z(s) = Ls + \frac{R \cdot \frac{1}{Cs}}{R + \frac{1}{Cs}}$$

$$Z(s) = Ls + \frac{R}{1 + RCs}$$

$$Z(j\omega) = j\omega L + \frac{R}{1 + j\omega RC}$$

$$Z(j\omega) = j\omega L + \frac{R(1 - j\omega RC)}{1 + (\omega RC)^2}$$

$$Z(j\omega) = \frac{R}{1 + (\omega RC)^2} + j\left(\omega L - \frac{\omega R^2 C}{1 + (\omega RC)^2}\right)$$

Resonance condition:

$$\text{Im}(Z(j\omega)) = 0$$

$$\omega L - \frac{\omega R^2 C}{1 + (\omega RC)^2} = 0$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{1}{(RC)^2}}$$

 $\omega = 0$: trivial solution

$$1 - \frac{R^2 C}{1 + (\omega RC)^2} = 0$$

$$\omega = \frac{1}{RC} \cdot \sqrt{\frac{R^2 C}{L} - 1}$$

(9)

$$\text{Let } \omega_0 = \frac{1}{\sqrt{LC}}$$

Then

$$\omega_r = \frac{1}{\sqrt{LC}} \cdot \sqrt{1 - \frac{L}{R^2C}}$$

$$\omega_r = \omega_0 \sqrt{1 - \frac{L}{R^2C}}$$