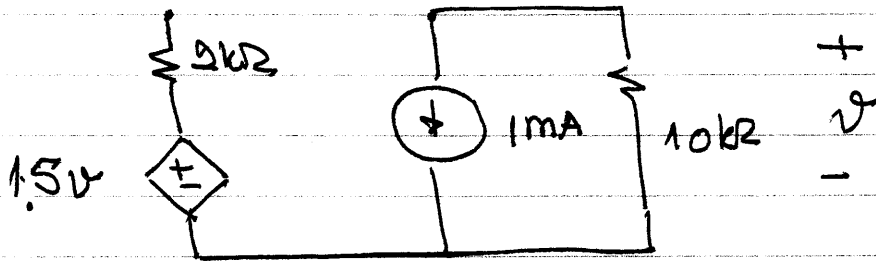


1) Switch open: $+ V_c -$



$$V = -10 \times 10^3 \times 10^{-3}$$

$$V = -10$$


$$V_c - 1.5V + V = 0$$

$$V_c = 0.5V$$


$$V_c = -5V$$

Switch closed

Note the initial conditions

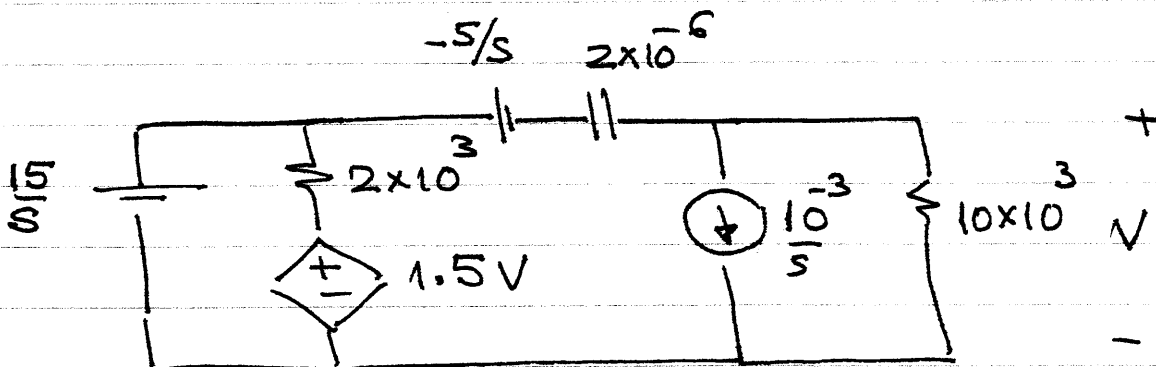

Thevenin's equivalent

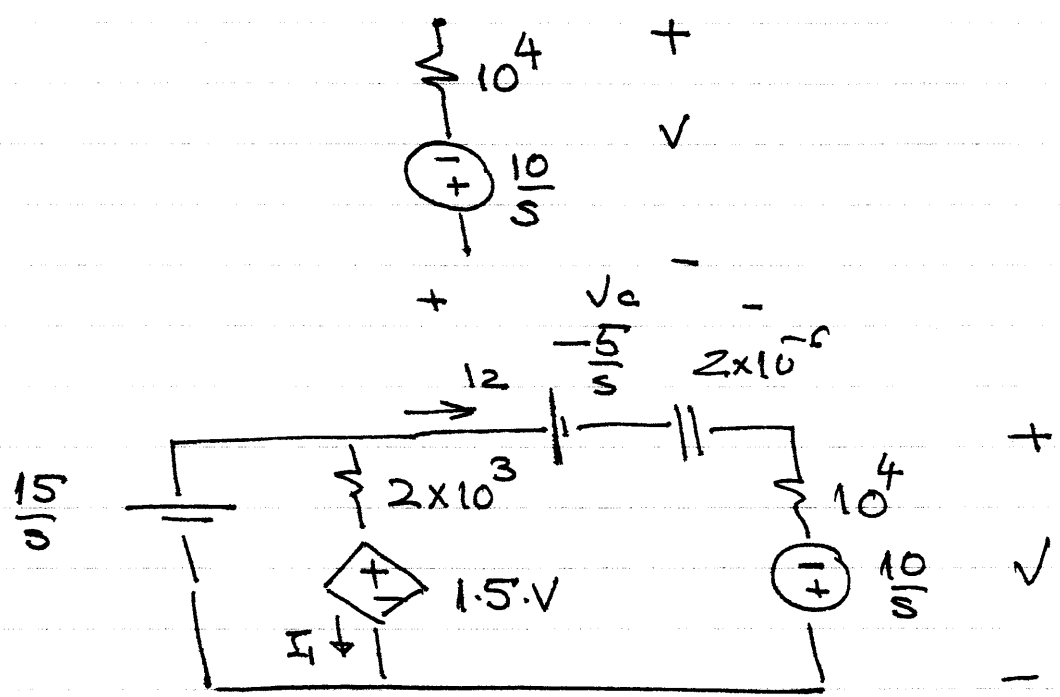

$$\frac{15}{s} - 2 \times 10^3 I_1 - 1.5V = 0 \quad (1)$$

$$\frac{15}{s} - \left(-\frac{5}{s}\right) - \frac{1}{2 \times 10^{-6} s} \cdot I_2 - V = 0 \quad (2)$$

$$V - 10^4 \cdot I_2 + \frac{10}{s} = 0 \quad (3)$$

Hence $\frac{15}{s} = 2 \times 10^3 I_1 + 1.5V \quad (1)$

$$\frac{20}{s} = \frac{1}{2 \times 10^{-6} s} \cdot I_2 + V \quad (2)$$

$$V = 10^4 I_2 + \frac{10}{s} \quad (3)$$

$$\frac{15}{s} = 2 \times 10^3 I_1 + 1.5 \cdot \left(10^4 I_2 - \frac{10}{s} \right) \quad (1)$$

$$\frac{20}{s} = \frac{1}{2 \times 10^{-6} s} \cdot I_2 + 10^4 I_2 - \frac{10}{s} \quad (2)$$

From (2): $\frac{30}{s} = \left(10^4 + \frac{1}{2 \times 10^{-6} s} \right) I_2$

$$I_2 = \frac{30}{s} \cdot \frac{1}{10^4 + \frac{10^6}{2} \frac{1}{s}}$$

$$I_2 = \frac{30}{s} \cdot \frac{1}{10^4 \left(1 + \frac{50}{s} \right)}$$

$$I_2 = 10^{-3} \cdot \frac{3}{s+50}$$

Hence: $V = 10^4 \cdot I_2 - \frac{10}{s}$

$$V = 10^4 \cdot \left(10^{-3} \cdot \frac{3}{s+50} \right) - \frac{10}{s}$$

$$V = \frac{30}{s+50} - \frac{10}{s}$$

$$V = \frac{3s + s + 50}{s(s+50)} \cdot 10$$

$$V = 10 \cdot \frac{2s+50}{s(s+50)}$$

$$V = 10 \cdot \frac{s + s + \sqrt{6}}{s(s + \sqrt{6})}$$

or/

$$\sigma = 10 \cdot \frac{3}{s + \sqrt{6}} - 10 \cdot \frac{1}{s}$$

$$V(t) = 10 e^{-\sqrt{6}t} u(t) - 10 u(t)$$

$$\frac{A}{s} + \frac{B}{s + \sqrt{6}}$$

$$A + B = 2$$

$$\sqrt{6}A = -\sqrt{6}$$

$$A = -1$$

$$B = 3$$

Find $V_c(t)$:

$$V_c = -\frac{5}{s} + \frac{1}{2 \times 10^{-6} s} \cdot 12$$

$$V_c = -\frac{5}{s} + \frac{10^6}{2s} \cdot 10^{-3} \cdot \frac{3}{s + \sqrt{6}}$$

$$V_c = -\frac{5}{s} + \frac{10^3}{2s} \cdot \frac{3}{s + \sqrt{6}}$$

$$V_c = -\frac{5}{s} + \frac{500 \times 3}{s(s + \sqrt{6})} ; V_c = \frac{-5(s + \sqrt{6}) + 1500}{s(s + \sqrt{6})}$$

$$V_c = \frac{1250 - 5s}{s(s + \sqrt{6})}$$

$$\text{Since: } \frac{1250 - 5s}{s(s + \sqrt{6})} = \frac{A}{s} + \frac{B}{s + \sqrt{6}}$$

$$1250 = \sqrt{6}A \quad A = 25$$

$$A + B = -5 \quad B = -30$$

$$V_c = \frac{25}{s} - \frac{30}{s+50}$$

$$V_c(t) = 25u(t) - 30e^{-50t}u(t)$$

Check: $V_c(t) = 25u(t) - 30e^{-50t}u(t)$

$$V_c(t) = 5(5 - 6e^{-50t})u(t)$$

$$V_c(0) = -5 \quad \checkmark$$

$$V_c(\infty) = 25$$


$$V_c(s) = \frac{1250 - 15}{s(s+10)}$$

$$\lim_{s \rightarrow \infty} s \cdot V_c(s) = -5 \quad \checkmark$$


$$\lim_{s \rightarrow \infty} s \cdot V_c(s) = V_c(0)$$

$$\lim_{s \rightarrow 0} s \cdot V_c(s) = 25$$
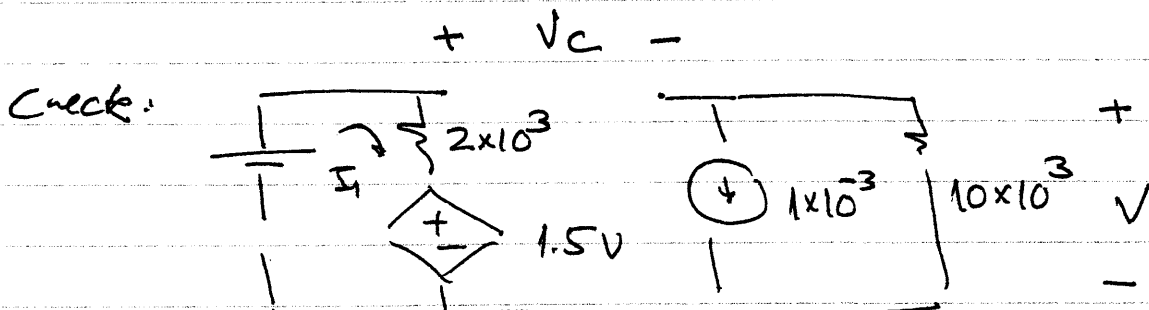
$$\lim_{s \rightarrow 0} s \cdot V_c(s) = V_c(\infty)$$


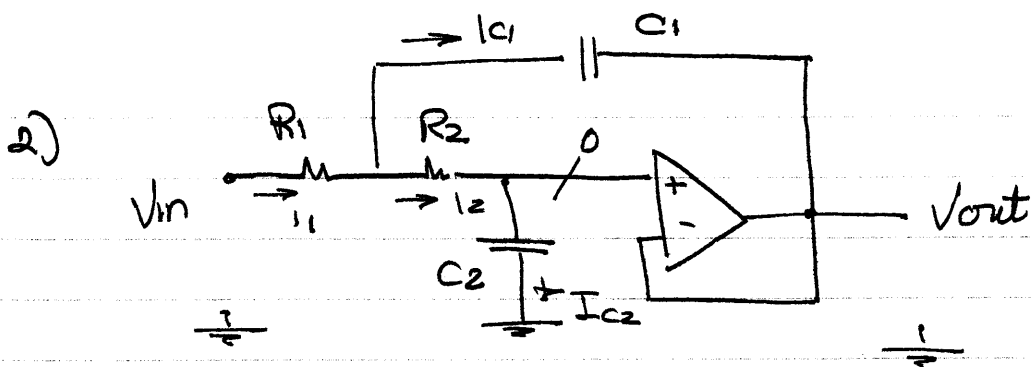
$$V = -10^4 \times 10^{-3}; V = -10V; V_c = V + 15; V_c = 25V \quad \checkmark$$



$$C_1 = 2Q$$

$$C_2 = \frac{1}{2Q}$$

Ideal op-amp:

KVL+

$$\text{KCL: } V_{in} = R_1 I_1 + R_2 I_2 + V_{out} \quad (1)$$

$$V_{in} = R_1 I_1 + \frac{1}{C_1 s} \cdot I_{C1} + V_{out} \quad (2)$$

$$\text{KCL: } I_1 = I_2 + I_{C1} \quad (3)$$

$$I_{C2} = C_2 s V_{out}$$

$$I_2 = I_{C2}$$

$$\text{From (1) and (2): } R_2 I_2 = \frac{1}{C_1 s} I_{C1} \Rightarrow I_{C1} = R_2 C_1 s I_2$$

Then: ~~$I_1 = I_2 + I_{C1}$~~

$$I_1 = I_2 + I_{C1}$$

$$I_1 = I_2 + R_2 C_1 s I_2 \quad ; \quad I_1 = (1 + R_2 C_1 s) I_2$$

$$\text{From (1)} \quad V_{in} = R_1 \cdot (1 + R_2 C_1 s) I_2 + R_2 I_2 + V_{out}$$

$$I_2 = C_2 s V_{out}$$

$$V_{in} = (R_1 (1 + R_2 C_1 s) + R_2) C_2 s V_{out} + V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + C_2 s (R_1 + R_1 R_2 C_1 s + R_2)}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + (C_2 R_1 + C_2 R_2) s + R_1 R_2 C_1 C_2 s^2}$$

$$R_1 = 1$$

$$R_2 = 1$$

$$C_1 = 2Q$$

$$C_2 = \frac{1}{2Q}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{1}{Q} s + s^2}$$

zeros: 2 at infinity.

poles: $s^2 + \frac{1}{Q}s + 1 = 0$ $s_{1/2} = -\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 - 1}$

let $Q = 1/\sqrt{2}$

$$H(s) = \frac{1}{1 + \sqrt{2}s + s^2} \quad ; \quad s_{1/2} = -\frac{1}{\sqrt{2}} \pm \sqrt{\frac{1}{2} - 1}$$



$$s_{1/2} = -\frac{1}{\sqrt{2}} \pm j \frac{1}{\sqrt{2}}$$

$$s_{1/2} = \frac{-1 \pm j}{\sqrt{2}}$$


$$H(j\omega) = \frac{1}{1 + \sqrt{2}j\omega - \omega^2}$$

$$|H(j\omega)|^2 = \frac{1}{(1 - \omega^2)^2 + 2\omega^2}$$
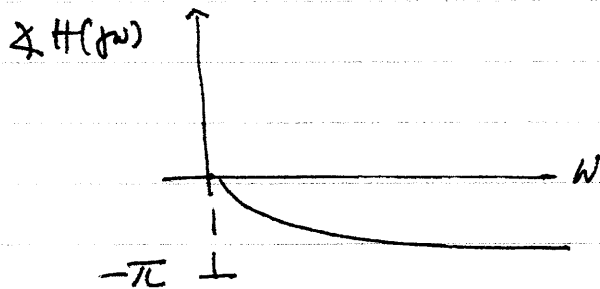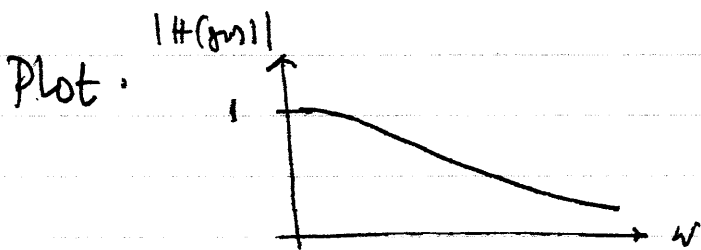
$$\angle H(j\omega) = -\arctan \frac{\sqrt{2}\omega}{1 - \omega^2}$$



Low pass filter or key filter

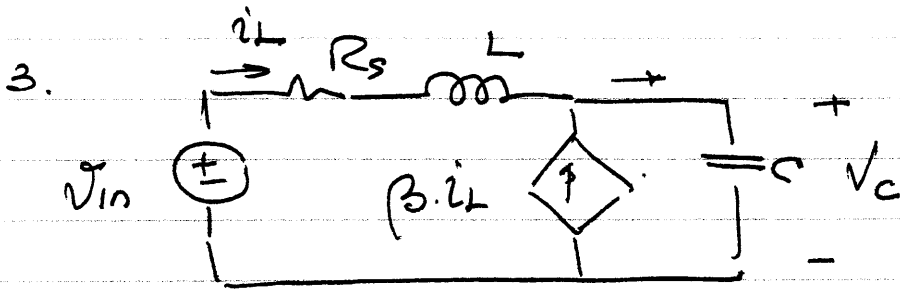

$$V_{in} = (R_s + sL) \cdot I_L + V_C$$

$$I_C = Cs \cdot V_C$$

$$I_L = \beta I_L + I_C \Rightarrow (1 + \beta) I_L = I_C$$

$$V_C = \frac{1}{Cs} \cdot I_C$$

$$V_C = \frac{1}{Cs} \cdot (1 + \beta) I_L$$

$$V_{in} = (R_s + sL) \cdot I_L + \frac{1}{Cs} \cdot (1 + \beta) \cdot I_L$$

$$H(s) = \frac{I_L}{V_{in}}$$

$$H(s) = \frac{1}{R_s + sL + \frac{1}{Cs} \cdot (1 + \beta)}$$

$$H(s) = \frac{Cs}{Lcs^2 + R_sCs + (1 + \beta)}$$

$$H(j\omega) = \frac{j\omega C}{1 + \beta - L\omega^2 + j\omega R_s C}$$


$$|H(j\omega)|^2 = \frac{\omega^2 C^2}{(1+\beta - LC\omega^2)^2 + (\omega R_s C)^2}$$

$$\omega_m: 1+\beta - LC\omega^2 = 0$$

$$\omega = \sqrt{\frac{1+\beta}{LC}}$$

$$|H_m|^2 = \frac{\omega^2 C^2}{(\omega R_s C)^2}$$

$$H_m = \frac{1}{R_s}$$

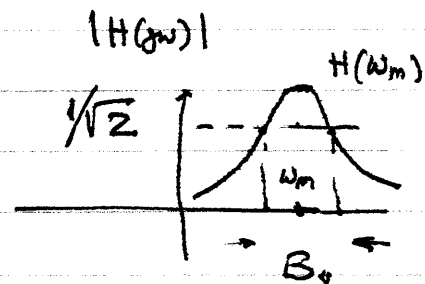

Bandwidth:

$$\frac{|H(j\omega)|^2}{H_m^2} = \frac{1}{2}$$

$$(1+\beta - LC\omega^2)^2 = (\omega R_s C)^2$$

$$1+\beta - LC\omega^2 = \pm \omega R_s C$$

$$LC\omega^2 \pm \omega R_s C - (1+\beta) = 0$$

$$\omega^2 \pm \frac{\omega R_s}{L} - \frac{1+\beta}{LC} = 0$$


~~$$\omega_{1/2} = \frac{R_s}{2L} \pm \sqrt{\left(\frac{R_s}{2L}\right)^2 + \frac{1+\beta}{LC}}$$~~

$$\omega_{1/2} = \frac{R_s}{2L} \pm \sqrt{\left(\frac{R_s}{2L}\right)^2 + \frac{1+\beta}{LC}}$$

⊕

$$\omega_{3/4} = \frac{R_s}{2L} \pm \sqrt{\left(\frac{R_s}{2L}\right)^2 + \frac{1+\beta}{LC}}$$
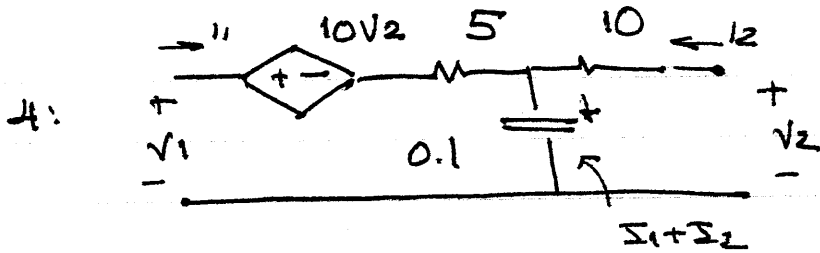
$$\omega_3 - \omega_1 = \frac{R_s}{L} : BW \oplus$$



$$V_1 - 10V_2 = 5 \cdot I_1 + \frac{1}{0.1s} (I_1 + I_2)$$

$$V_2 = 10 \cdot I_2 + \frac{1}{0.1s} (I_1 + I_2)$$

$$V_1 - 10V_2 = \left(5 + \frac{10}{s}\right) I_1 + \frac{10}{s} I_2$$

$$V_2 = \frac{10}{s} I_1 + \left(10 + \frac{10}{s}\right) I_2$$

$$V_1 = 10 \cdot \left\{ \frac{10}{s} I_1 + \left(10 + \frac{10}{s}\right) I_2 \right\} + \left(5 + \frac{10}{s}\right) I_1 + \frac{10}{s} I_2$$

$$V_2 = \frac{10}{s} I_1 + \left(10 + \frac{10}{s}\right) I_2$$

$$V_1 = \left(\frac{100}{s} + 5 + \frac{10}{s}\right) I_1 + \left(100 \cdot \frac{1+s}{s} + \frac{10}{s}\right) I_2$$

$$V_2 = \frac{10}{s} I_1 + 10 \cdot \frac{1+s}{s} I_2$$

$$V_1 = \frac{110+5s}{s} I_1 + \frac{110+s}{s} I_2$$

$$V_2 = \frac{10}{s} I_1 + 10 \cdot \frac{1+s}{s} I_2$$

$$\mathcal{Z} = \begin{pmatrix} \frac{110+5s}{s} & \frac{110+100s}{s} \\ \frac{10}{s} & 10 \frac{1+s}{s} \end{pmatrix}$$

$$V_1 = \frac{110+5s}{s} I_1 + \frac{110+100s}{s} I_2$$

$$V_2 = \frac{10}{s} I_1 + 10 \cdot \frac{1+s}{s} I_2$$

$Z_{in} = ?$

$$V_2 = -10 \cdot I_2$$

$$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

$$V_2 = z_{21} I_1 + z_{22} I_2$$

$$V_2 = -10 I_2$$

$$-10 I_2 = \frac{10}{s} I_1 + 10 \cdot \frac{1+s}{s} I_2$$

$$\left(-10 - 10 \cdot \frac{1+s}{s} \right) I_2 = \frac{10}{s} I_1$$

$$\frac{-20s-10}{s} I_2 = \frac{10}{s} I_1$$

$$I_2 = -\frac{10}{20s+10} I_1$$

$$I_2 = -\frac{1}{2s+1} I_1$$

$$V_1 = \frac{110+5s}{s} I_1 + \frac{110+100s}{s} I_2$$

$$V_1 = \frac{110+5s}{s} I_1 + \frac{110+100s}{s} \cdot \left(\frac{-1}{2s+1} \right) I_1$$

$$V_i = \left(\frac{110 + 5s}{s} - \frac{110 + 100s}{s(2s+1)} \right) I_1$$

$$Z_{in} = \frac{(110 + 5s)(2s+1) - (110 + 100s)}{s(2s+1)}$$

$$Z_{in} = \frac{220s + 10s^2 + 110 + 5s - 110 - 100s}{s(2s+1)}$$

$$Z_{in} = \frac{125s + 10s^2}{s(2s+1)}$$

$$Z_{in} = 5 \frac{25 + 2s}{2s+1} ; Z_{in} = 5 \cdot \frac{25 + 2s}{1 + 2s}$$

$$v_i(t) = 10u(t)$$

$$V_i(s) = \frac{10}{s}$$

$$I_1 = \frac{V_i}{Z_{in}}$$

$$I_1(s) = \frac{10}{s} \cdot \frac{1+2s}{5(2s+25)}$$

$$I_1 = \frac{2}{s} \cdot \frac{1+2s}{2s+25} ; I_1 = \frac{A}{s} + \frac{B}{2s+25}$$

$$I_1 = \frac{A}{s} + \frac{B}{2s+25} ; A = \lim_{s \rightarrow 0} s I_1 = 2 \cdot \frac{1+2s}{2s+25} = 2/25$$

$$B = \text{Res}(2s+28) \cdot \frac{2}{s} \cdot \frac{1+2s}{2s+28}$$

$$s \Rightarrow -\frac{2s}{2}$$

$$B = \frac{2}{-2s} \cdot 2 \cdot \left(1 + 2 \times \frac{-2s}{2}\right)$$

$$B = -\frac{4}{2s} \cdot (1 - 2s)$$

$$B = \frac{4 \times 24}{2s}$$

$$I_1(s) = \frac{2}{2s} \cdot \frac{1}{s} + \frac{96}{2s} \cdot \frac{1}{2s+28}$$

$$v_1(t) = \frac{2}{2s} \cdot u(t) + \frac{48}{2s} \cdot e^{-\frac{2s}{2}t}$$