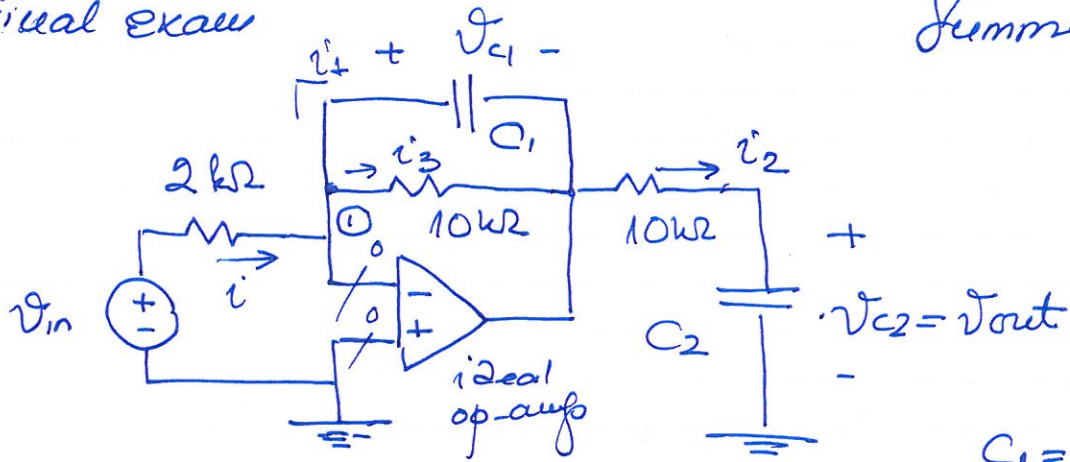


①



$$C_1 = 0.2 \text{ mF}$$

$$C_2 = 0.5 \text{ mF}$$

$$v_{c1}(0^-) = 80 \text{ mV}$$

$$v_{c2}(0^-) = 0 \text{ V}$$

$$v_{in} = 400 \mu(t) \text{ mV}$$

• Zero-state response:

Assume all initial conditions are 0.

Apply Laplace transform.

$$(1) \quad v_{in} - 2 \times 10^3 \cdot I = 0 \quad \text{then } I = \frac{400 \times \frac{1}{s} \times 10^{-3}}{2 \times 10^3}$$

$$(2) \quad I_3 \times 10 \times 10^3 = \frac{1}{C_1 s} \times I_4 \quad I = \frac{200}{s} \times 10^{-6}$$

$$I_3 \times 10^4 = \frac{1}{0.2 \times 10^{-3} \cdot s} \cdot I_4$$

$$I_3 = \frac{1}{2s} \cdot I_4$$

KCL for node ① gives:

$$(3) \quad I = I_3 + I_4$$

$$I = \frac{1}{2s} \cdot I_4 + I_4 \quad I_4 = \frac{2s}{1+2s} \cdot I$$

$$I_4 = \frac{400}{1+2s} \times 10^{-6}$$

Then:

$$I_3 = \frac{1}{2S} \times \frac{400}{1+2S} \times 10^{-6}$$

(2)

$$I_3 = \frac{200}{S(1+2S)} \times 10^{-6}$$

KVL around the outer loop across the output to the op-amp:

$$(4) \quad 10 \times 10^3 \cdot I_3 + 10 \times 10^3 \cdot I_2 + V_{C2} = 0$$

$$(5) \quad I_2 = C_2 S \cdot V_{C2} \quad ; \quad I_2 = 0.5 \times 10^{-3} \cdot S \cdot V_{C2}$$

Then:

$$10^4 \cdot I_3 + 10^4 \cdot 0.5 \times 10^{-3} \cdot S \cdot V_{C2} + V_{C2} = 0$$

$$V_{C2} = - \frac{10^4}{5S + 1} \times I_3$$

$$V_{C2} = - \frac{10^4}{1+5S} \times \frac{200 \times 10^{-6}}{S(1+2S)}$$

$$V_{C2} = - \frac{2}{S(1+2S)(1+5S)}$$

$$V_{C2} = - \frac{0.2}{S(S+0.2)(S+0.5)}$$

$$V_{out} = V_{C2}$$

$$\text{Hence: } V_{out} = - \frac{0.2}{S(S+0.2)(S+0.5)}$$

Inverse Laplace transform:

$$V_{out} = \frac{k_0}{s} + \frac{k_1}{s+0.2} + \frac{k_2}{s+0.5}$$

$$k_0 = \lim_{s \rightarrow 0} s \times V_{out} ; k_0 = \lim_{s \rightarrow 0} s \times \left(-\frac{0.2}{s(s+0.2)(s+0.5)} \right)$$

$$k_0 = \frac{-0.2}{0.2 \times 0.5} ; k_0 = -2$$

$$k_1 = \lim_{s \rightarrow -0.2} (s+0.2) \cdot V_{out} ; k_1 = \lim_{s \rightarrow -0.2} \frac{-0.2}{s \cdot (s+0.5)}$$

$$k_1 = \frac{-0.2}{(-0.2)(-0.2+0.5)}$$

$$k_1 = 10/3$$

$$k_2 = \lim_{s \rightarrow -0.5} (s+0.5) \cdot V_{out} ; k_2 = \lim_{s \rightarrow -0.5} \frac{-0.2}{s(s+0.2)}$$

$$k_2 = \frac{-0.2}{-0.5 \cdot (-0.5+0.2)}$$

$$k_2 = -4/3$$


$$\text{Hence, } V_{out} = \frac{-2}{s} + \frac{10/3}{s+0.2} - \frac{4/3}{s+0.5}$$

$$V_{out}(t) = -2 \cdot u(t) + \frac{10}{3} e^{-0.2t} u(t) - \frac{4}{3} e^{-0.5t} u(t)$$

Zero-state:
response

$$V_{out}(t) = - \left(2 - 3.33 e^{-0.2t} + 1.33 e^{-0.5t} \right) u(t)$$

• Zero-input response

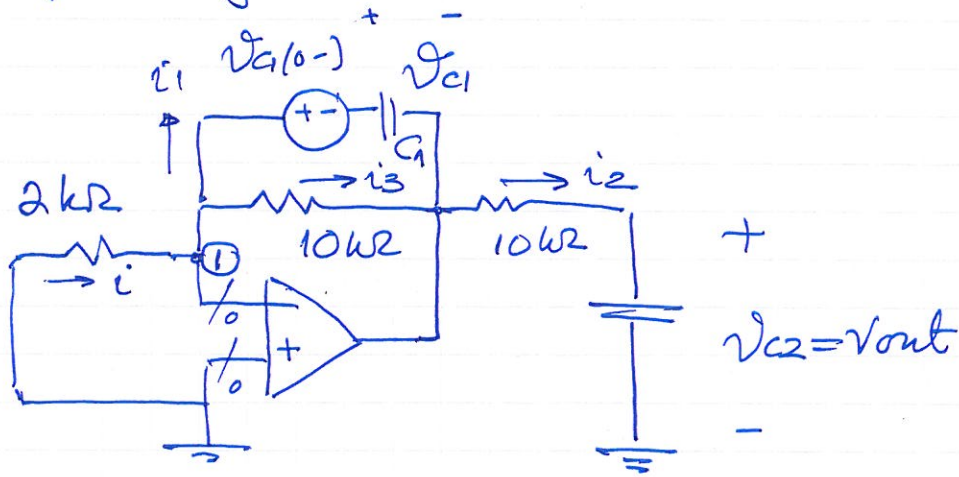

After applying Laplace transform:

$$(6) \quad I \times 2 \times 10^3 = 0 \Rightarrow I = 0$$

$$(7) \quad \frac{v_{C1}(0^-)}{s} + \frac{1}{C_1 s} \times I_1 - 10 \times 10^3 \cdot I_3 = 0$$

$$\frac{80 \times 10^{-3}}{s} + \frac{1}{0.2 \times 10^{-3} s} \cdot I_1 = 10^4 \cdot I_3$$

$$(8) \quad I_1 + I_3 = 0$$

$$\frac{80 \times 10^{-3}}{s} = \left(\frac{10^3}{0.2 s} + 10^4 \right) \cdot I_3$$

$$I_3 = \frac{80 \times 10^{-3}}{s} \cdot \frac{0.2 s}{10^3 + 2 \cdot 10^3 s}$$

$$I_3 = \frac{16 \times 10^{-6}}{1 + 2s}; \quad I_3 = \frac{8 \times 10^{-6}}{s + 0.5}$$

$$I_1 = - \frac{8 \times 10^{-6}}{s + 0.5}$$

KVL around the outer loop gives:

$$(9) \quad 10 \times 10^3 \cdot I_3 + 10 \times 10^3 \cdot I_2 + V_{C2} = 0$$

$$(10) \quad V_{C2} = \frac{1}{C_2 S} \cdot I_2$$

$$10^4 \cdot \frac{8 \times 10^{-6}}{S+0.5} + 10^4 \times C_2 S \cdot V_{C2} + V_{C2} = 0$$

$$V_{C2} = - \frac{8 \times 10^{-2}}{S+0.5} \cdot \frac{1}{10^4 \times 0.5 \times 10^{-3} S + 1}$$

$$V_{C2} = - \frac{8 \times 10^{-2}}{S+0.5} \times \frac{1}{5S+1}$$

$$V_{C2} = - \frac{1.6 \times 10^{-2}}{(S+0.2)(S+0.5)}$$

Inverse Laplace Transform:

$$V_{C2} = \frac{K_1}{S+0.2} + \frac{K_2}{S+0.5} \quad ; \quad V_{out} = \frac{K_1}{S+0.2} + \frac{K_2}{S+0.5}$$

$$K_1 = \lim_{S \rightarrow -0.2} (S+0.2) \cdot \frac{-1.6 \times 10^{-2}}{(S+0.2)(S+0.5)} \quad ; \quad K_1 = \frac{-1.6 \times 10^{-2}}{-0.2+0.5}$$

$$K_1 = - \frac{16}{3} \times 10^{-2}$$

$$K_1 = -0.0533$$

$$K_2 = \lim_{S \rightarrow -0.5} (S+0.5) \cdot \frac{-1.6 \times 10^{-2}}{(S+0.2)(S+0.5)} \quad ; \quad K_2 = \frac{-1.6 \times 10^{-2}}{-0.5+0.2} \quad ; \quad K_2 = \frac{16}{3} \times 10^{-2}$$

$$K_2 = 0.0533$$

Zero-input response.

(6)

$$v_{out}(t) = \left(-0.0133 e^{-0.2t} + 0.0133 e^{-0.1t} \right) u(t)$$

• Complete Response

$$v_{out}(t) = - \left(2 - 0.33 e^{-0.2t} + 1.33 e^{-0.1t} \right) u(t) \\ + \left(-0.0133 e^{-0.2t} + 0.0133 e^{-0.1t} \right) u(t)$$

$$v_{out}(t) = - \left(2 - 3.28 e^{-0.2t} + 1.28 e^{-0.1t} \right) u(t)$$

• General form of the natural response:

$$v_{nat}(t) = \left(K_1 e^{-0.2t} + K_2 e^{-0.1t} \right) u(t)$$


due to natural frequencies only.

• Transient response:

$$v_{out, \text{tran}}(t) = \left(3.28 e^{-0.2t} - 1.28 e^{-0.1t} \right) u(t)$$

• Steady state response:

$$v_{out, \text{ss}}(t) = -2u(t)$$

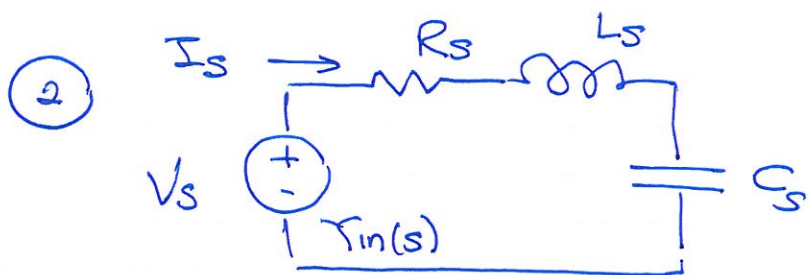

$$H(s) = \frac{I_s}{V_s}$$

$$V_s = \left(R_s + s \cdot L_s + \frac{1}{s C_s} \right) \cdot I_s$$

$$H(s) = \Upsilon_{in}(s)$$

$$\Upsilon_{in}(s) = \frac{1}{R_s + s L_s + \frac{1}{s C_s}}$$

$$\Upsilon_{in}(s) = \frac{s C_s}{1 + s R_s C_s + s^2 L_s C_s} \quad ; \quad \Upsilon_{in}(s) = \frac{\frac{1}{L_s} \cdot s}{s^2 + \frac{R_s}{L_s} s + \frac{1}{L_s C_s}}$$

• peak frequ.

$$\Upsilon_{in}(j\omega) = \frac{1}{L_s} \cdot \frac{j\omega}{\left(\frac{1}{L_s C_s} - \omega^2 \right) + j \cdot \frac{R_s}{L_s} \omega}$$

$$|\Upsilon_{in}(j\omega)| = \frac{\omega}{L_s} \cdot \frac{1}{\sqrt{\left(\frac{R_s}{L_s} \omega \right)^2 + \left(\frac{1}{L_s C_s} - \omega^2 \right)^2}}$$

Peak frequency: $\omega_m = \frac{1}{\sqrt{L_s C_s}}$

• Half-power frequencies ω_1 and ω_2 :

$$\left(\frac{R_s}{L_s} \omega\right)^2 = \left(\frac{1}{L_s C_s} - \omega^2\right)^2$$

$$\pm \frac{R_s}{L_s} \omega = \frac{1}{L_s C_s} - \omega^2$$

$$\omega^2 \pm \frac{R_s}{L_s} \omega - \frac{1}{L_s C_s} = 0$$

$$\omega_{1/2} = -\frac{R_s}{2L_s} \pm \sqrt{\left(\frac{R_s}{2L_s}\right)^2 + \frac{1}{L_s C_s}}$$

$$\omega_{3/4} = \frac{R_s}{2L_s} \pm \sqrt{\left(\frac{R_s}{2L_s}\right)^2 + \frac{1}{L_s C_s}}$$

Positive ω only: $\omega_1 = -\frac{R}{2L_s} + \sqrt{\left(\frac{R_s}{2L_s}\right)^2 + \frac{1}{L_s C_s}}$

$$\omega_3 = \frac{R}{2L_s} + \sqrt{\left(\frac{R_s}{2L_s}\right)^2 + \frac{1}{L_s C_s}}$$

• Bandwidth $B_w = \omega_3 - \omega_1$

$$B_w = \frac{R_s}{L_s}$$

• $Q_{circ} = \frac{\omega_m}{B_w}$; $Q_{circ} = \frac{1}{L_s C_s} \cdot \frac{L_s}{R_s}$

$$Q_{circ} = \frac{1}{R_s} \sqrt{\frac{L_s}{C_s}}$$

• Frequen: $\Im H(j\omega) = 0$


i.e., $H(j\omega) = \text{Real}$

$$\frac{1}{LsC} - \omega^2 = 0 ; \omega = \frac{1}{\sqrt{LC}}$$

$$\Im H(j\omega) = \frac{1}{Ls} \cdot \frac{j\omega}{j \cdot \frac{Rs}{Ls} \cdot \omega}$$

$$\Im H(j\omega) = \frac{1}{Rs} \quad (\text{resonant frequency})$$

3

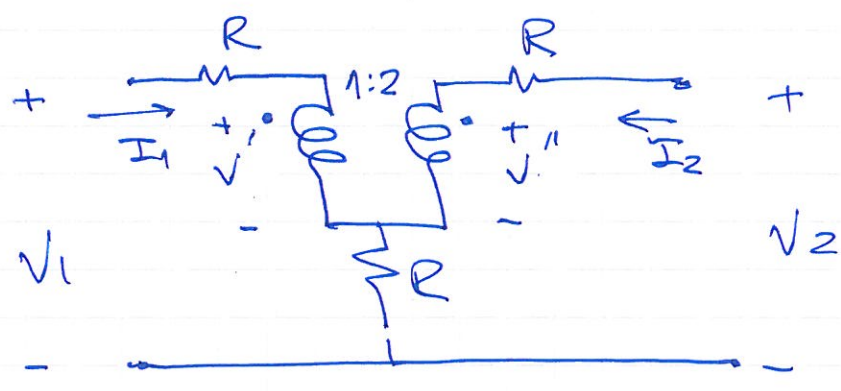

parameters

$$\frac{V'}{V''} = 1/2$$

ideal transformer

$$\frac{I_1}{I_2} = -2$$

$$\begin{cases} V_1 - R \cdot I_1 - V' - R \cdot (I_1 + I_2) = 0 \\ V_2 - R \cdot I_2 - V'' - R \cdot (I_1 + I_2) = 0 \end{cases}$$

$$V_1 - 2R \cdot I_1 - R \cdot I_2 - V' = 0$$

$$V_2 - R \cdot I_1 - 2R \cdot I_2 - V'' = 0$$

$$V'' = 2 \cdot V'$$

$$I_1 = -2I_2$$

$$V_1 - 2R \cdot I_1 - R \cdot I_2 - V' = 0 \quad (/(-2) \text{ multiply with } (-2))$$

$$V_2 - R \cdot I_1 - 2R \cdot I_2 - 2V' = 0$$

Add:

$$-2V_1 + 4R \cdot I_1 + 2R \cdot I_2 + V_2 - R \cdot I_1 - 2R \cdot I_2 = 0$$

$$-2V_1 + V_2 + 3R \cdot I_1 = 0 ; I_1 = \frac{2V_1 - V_2}{3R}$$

$$I_2 = -\frac{1}{2} \cdot I_1$$

$$I_2 = \frac{V_2 - 2V_1}{6R}$$

Hence: $2V_1 - V_2 = 3R \cdot I_1$

$$-2V_1 + V_2 = 6R \cdot I_2$$

$$\begin{pmatrix} 2 & -1 \\ -2 & 1 \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} 3R & 0 \\ 0 & 6R \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

det = 2 - 2 = 0

• Z-parameters do not exist

• $I_1 = \frac{2}{3R} \cdot V_1 - \frac{1}{3R} \cdot V_2$

$$I_2 = -\frac{1}{3R} \cdot V_1 + \frac{1}{6R} \cdot V_2$$

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 2/3R & -1/3R \\ -1/3R & 1/6R \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

Y-parameters: $\frac{1}{R} \cdot \begin{pmatrix} 2/3 & -1/3 \\ -1/3 & 1/6 \end{pmatrix}$

or $\frac{1}{6R} \cdot \begin{pmatrix} 4 & -2 \\ -2 & 1 \end{pmatrix}$

t-parameters:

$$2V_1 - V_2 = 3R \cdot I_1$$

$$-2V_1 + V_2 = 6R \cdot I_2 \quad (\text{or: } I_1 = -2I_2)$$

Hence: $2V_1 = V_2 + 3R \cdot (-2I_2)$

$$I_1 = -2I_2$$

$$V_1 = \frac{1}{2}V_2 - 3R \cdot I_2$$


$$I_1 = -2I_2$$

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} 1/2 & -3R \\ 0 & -2 \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ I_2 \end{pmatrix}$$

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} 1/2 & 3R \\ 0 & 2 \end{pmatrix} \cdot \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

t-parameters: $\begin{pmatrix} 1/2 & 3R \\ 0 & 2 \end{pmatrix}$

(4)

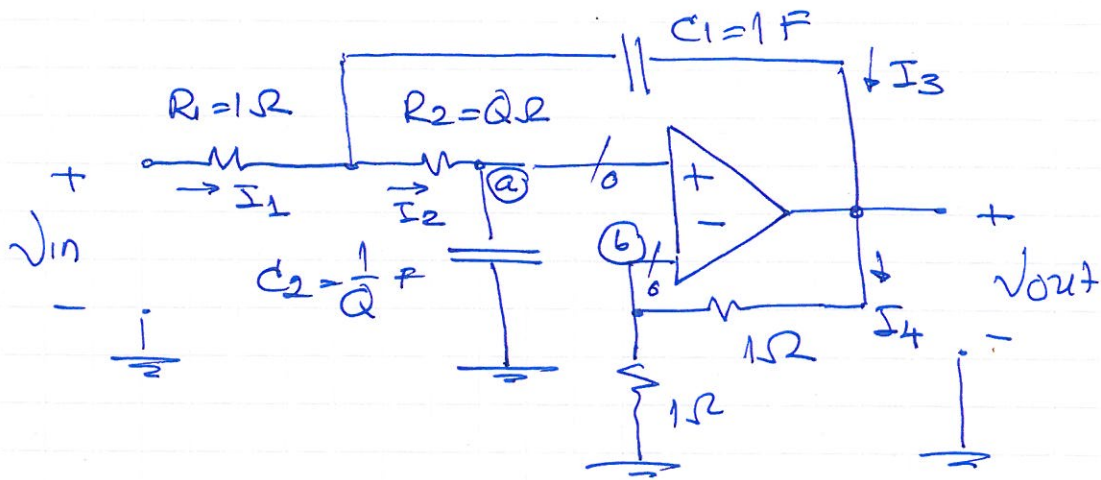

$$\begin{aligned} R_1 &= 1\Omega \\ R_2 &= Q\Omega \\ C_1 &= 1F \\ C_2 &= 1/Q F \end{aligned}$$

KVL:

$$V_{in} = R_1 \cdot I_1 + \left(R_2 + \frac{1}{C_2 s} \right) \cdot I_2 \quad (1)$$

$$V_a = \frac{1}{C_2 s} \cdot I_2 \quad (2)$$

$$V_b = V_a$$

$$V_{out} = 1 \times I_4 + 1 \times I_4 ; V_{out} = 2 \times I_4$$

$$V_b = 1 \times I_4$$

Hence:

$$V_{out} = 2 \times V_b ; V_b = \frac{V_{out}}{2}$$

Since $V_a = V_b \Rightarrow V_a = \frac{V_{out}}{2}$

From (2): $I_2 = C_2 s \cdot V_a ; I_2 = \frac{C_2 s}{2} \times V_{out}$

KVL:

$$V_{in} - R_1 \cdot I_1 - \frac{1}{C_1 s} \cdot I_3 - V_{out} = 0 \quad (3)$$

KCL:

$$I_3 - I_4 + I_2 = 0 \quad (4)$$

From (3):

$$V_{in} = R_1 \cdot I_1 + \frac{1}{C_1 S} \cdot I_3 + V_{out}$$

Substituting (4) into (3) gives:

$$(3): I_3 = I_1 - I_2$$

$$V_{in} = R_1 \cdot I_1 + (I_1 - I_2) \cdot \frac{1}{C_1 S} + V_{out}$$

Since: $I_2 = \frac{C_2 S}{2} V_{out}$

We have:

$$V_{in} = R_1 \cdot I_1 + \frac{1}{C_1 S} \cdot (I_1 - \frac{C_2 S}{2} \cdot V_{out}) + V_{out}$$

$$V_{in} = (R_1 + \frac{1}{C_1 S}) I_1 + (1 - \frac{C_2}{2C_1}) \cdot V_{out} \quad (4')$$

Hence:

$$(1) \quad V_{in} = R_1 \cdot I_1 + (R_2 + \frac{1}{C_2 S}) I_2$$

$$(4') \quad V_{in} = (R_1 + \frac{1}{C_1 S}) I_1 + (1 - \frac{C_2}{2C_1}) V_{out}$$

Since: $I_2 = \frac{C_2 S}{2} V_{out}$, (1) becomes

$$(1) \quad V_{in} = R_1 \cdot I_1 + (R_2 + \frac{1}{C_2 S}) \cdot \frac{C_2 S}{2} \cdot V_{out}$$

$$(4') \quad V_{in} = (R_1 + \frac{1}{C_1 S}) I_1 + (1 - \frac{C_2}{2C_1}) V_{out}$$

Eliminate I_1 by substituting (1) into (4')

$$(4') \quad V_{in} = (R_1 + \frac{1}{C_1 S}) \cdot \frac{V_{in} - (R_2 + \frac{1}{C_2 S}) \cdot \frac{C_2 S}{2} \cdot V_{out}}{R_1} + (1 - \frac{C_2}{2C_1}) V_{out}$$

Hence,

$$V_{in} \left(1 - \frac{R_1 + \frac{1}{C_1 s}}{R_4} \right) = - \left(R_1 + \frac{1}{C_1 s} \right) \cdot \frac{(R_2 + \frac{1}{C_2 s}) \cdot \frac{C_2 s}{2}}{R_4} V_{out} + \left(1 - \frac{C_2}{2C_1} \right) \cdot V_{out}$$

$$H(s) = \frac{V_{out}}{V_{in}}$$

$$H(s) = \frac{1 - \frac{R_1 + \frac{1}{C_1 s}}{R_4}}{- \left(R_1 + \frac{1}{C_1 s} \right) \left(R_2 + \frac{1}{C_2 s} \right) \cdot \frac{C_2 s}{2R_4} + \left(1 - \frac{C_2}{2C_1} \right)}$$

$$H(s) = \frac{- \frac{1}{C_1 s}}{- \left(R_1 + \frac{1}{C_1 s} \right) \cdot \left(R_2 + \frac{1}{C_2 s} \right) \cdot \frac{C_2 s}{2} + \left(1 - \frac{C_2}{2C_1} \right) R_4}$$

$$H(s) = \frac{1}{(1 + R_1 C_1 s) \cdot (1 + R_2 C_2 s) \cdot \frac{1}{2} - \left(1 - \frac{C_2}{2C_1} \right) \cdot R_1 \cdot C_1 s}$$

$$H(s) = \frac{1 \times 2}{(1 + R_1 C_1 s)(1 + R_2 C_2 s) - (2C_1 - C_2) \cdot R_1 s}$$

Let $R_1 = 1$
 $R_2 = 2$
 $C_1 = 1$
 $C_2 = 1/2$

Then $H(s) = \frac{2}{(1+s)(1+s) - \left(2 - \frac{1}{2}\right) \cdot s}$

$$H(s) = \frac{2}{s^2 + 2s + 1 - 2s + \frac{s}{2}}$$

$$H(s) = \frac{2}{s^2 + \frac{1}{Q}s + 1}$$

• Zeros: Two zeros at infinity

Poles: $s^2 + \frac{1}{Q}s + 1 = 0$

$$s_{1/2} = -\frac{1}{2Q} \pm \sqrt{\left(\frac{1}{2Q}\right)^2 - 1}$$

$$s_{1/2} = -\frac{1}{2Q} \pm j \sqrt{1 - \left(\frac{1}{2Q}\right)^2}$$

• $H(j\omega) = \frac{2}{1 - \omega^2 + \frac{1}{Q}j\omega}$

$$|H(j\omega)| = \frac{2}{\sqrt{(1 - \omega^2)^2 + \left(\frac{\omega}{Q}\right)^2}}$$

$$\angle H(j\omega) = -\arctan \frac{\omega/Q}{1 - \omega^2}$$

• Type of the circuit: $\omega = 0 : H(0) = 2$
 $\omega \rightarrow \infty : H(\infty) = 0$

1/2 power: $(1 - \omega^2)^2 = \left(\frac{\omega}{Q}\right)^2 ; 1 - \omega^2 = \pm \omega/Q$

$$\omega^2 \pm \frac{\omega}{Q} - 1 = 0$$

$$\omega_{1/2} = -\frac{\omega}{2Q} \pm \sqrt{\left(\frac{\omega}{2Q}\right)^2 + 1} ; \omega_{3/4} = \frac{\omega}{2Q} \pm \sqrt{\left(\frac{\omega}{2Q}\right)^2 + 1}$$

Bandwidth: $\omega_3 - \omega_1 = \frac{\omega}{Q}$

(17)

Peak: $y = (1 - \omega^2)^2 + \left(\frac{\omega}{Q}\right)^2$

Minimum of y occurs at:

$$\frac{dy}{d\omega} = 0; \quad \frac{dy}{d\omega} = 2(1 - \omega^2) \times 2\omega + 2 \frac{\omega}{Q} \cdot \frac{1}{Q}$$

$$\frac{dy}{d\omega} = 0 \text{ for } \omega = 0$$
$$4(1 - \omega^2) + 2 \cdot \frac{1}{Q^2} = 0$$

$$4\omega^2 = 4 + \frac{2}{Q^2}$$

$$\omega^2 = 1 + \frac{1}{2Q^2}$$

in general, this is a low pass filter since $H(0) = 2$

Butterworth design

this could be a bandpass filter if Q is chosen properly.