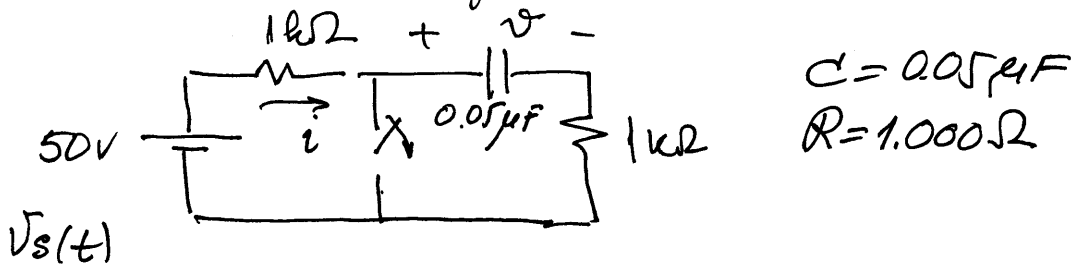


$t < 0$ : switch is closed

$$v(0^-) = 0 \quad 1^{st} \text{ initial condition}$$

$t = 0$ : switch opens



$$v_s(t) - 2 \cdot R \cdot i - v = 0$$

$$i = C \cdot \frac{dv}{dt}$$

$$2RC \cdot \frac{dv}{dt} + v = v_s(t)$$

$$2 \times 1 \times 10^3 \times 0.05 \times 10^{-6} \cdot \frac{dv}{dt} + v = 50$$

$$0.1 \times 10^{-3} \cdot \frac{dv}{dt} + v = 50$$

(Differential equation)

Characteristic equation:

$$0.1 \times 10^{-3} \cdot s + 1 = 0 \quad ; \quad s = -10^4$$

Time constant:

$$\tau = 10^{-4} \text{ s}$$

$$\tau_1 = 100 \mu\text{s}$$

Solution to the differential equation:

$$v = k e^{-\frac{t}{10^{-4}}} + A$$

$v_p(t)$  : particular solution

$$v(0+) = 0$$

$$0 = k + A \quad ; \quad k = -A$$

$$v_p(t) = A : \text{constant}$$

It should satisfy the differential equation:

$$0.1 \times 10^{-3} \frac{dv}{dt} + v = 50$$

$$0 + A = 50 \quad ; \quad A = 50$$

Hence,  $k = -50$

Solution:


$$v = 50 \left( 1 - e^{-\frac{t}{10^{-4}}} \right) \quad t: \text{in microseconds}$$

$v$  in Volts

\* If  $t$  in microseconds

$$v = 50 \left( 1 - e^{-\frac{t}{100}} \right)$$

At  $t = 100 \mu s$ , the switch closes

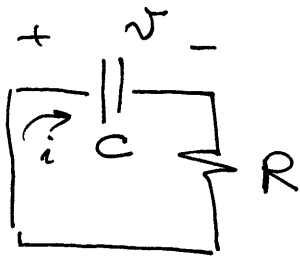

$$v = 50 (1 - e^{-t/100})$$

At  $t = 100 \mu s$  seconds

$$\begin{aligned} v(100-) &= 50 \cdot (1 - e^{-\frac{100}{100}}) \\ &= 50 (1 - e^{-1}) \\ &= 50 \cdot \frac{e-1}{e} \end{aligned}$$

$$v(100+) = v(100-)$$

Hence:  $v(100+) = 50 \frac{e-1}{e}$

KVL:  $v + Ri = 0$

$$i = C \frac{dv}{dt}$$

$$RC \cdot \frac{dv}{dt} + v = 0$$

$$1000 \times 0.05 \times 10^{-6} \cdot \frac{dv}{dt} + v = 0$$

$$50 \times 10^{-6} \cdot \frac{dv}{dt} + v = 0$$

Character equation:  $50 \times 10^{-6} \cdot s + 1 = 0$       $s = - \frac{10^6}{50}$

$$s = -20 \times 10^4$$

(4)

Time constant  $\tau_2 = 50 \times 10^{-6}$  in seconds

$$\tau_2 = 50 \mu\text{sec.}$$

Solution:

$$V = K \cdot e^{-\frac{t}{50 \times 10^{-6}}}$$

$$V(100\mu) = 50 \cdot \frac{e-1}{e}$$

$$50 \cdot \frac{e-1}{e} = K \cdot e^{-\frac{100 \times 10^{-6}}{50 \times 10^{-6}}}$$


$$K = 50 \cdot \frac{e-1}{e} \cdot e^2$$

$$K = 50e(e-1)$$


$$V = 50e(e-1) \times e^{-\frac{t}{50 \times 10^{-6}}} \quad t \text{ in seconds}$$

\* If  $t$  in  $\mu\text{seconds}$ .

$$V = 50e(e-1) \cdot e^{-\frac{t}{50}}$$

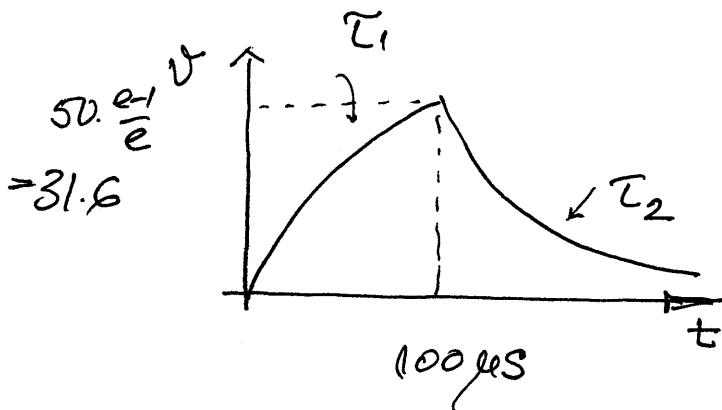

$$e = 2.718281828$$

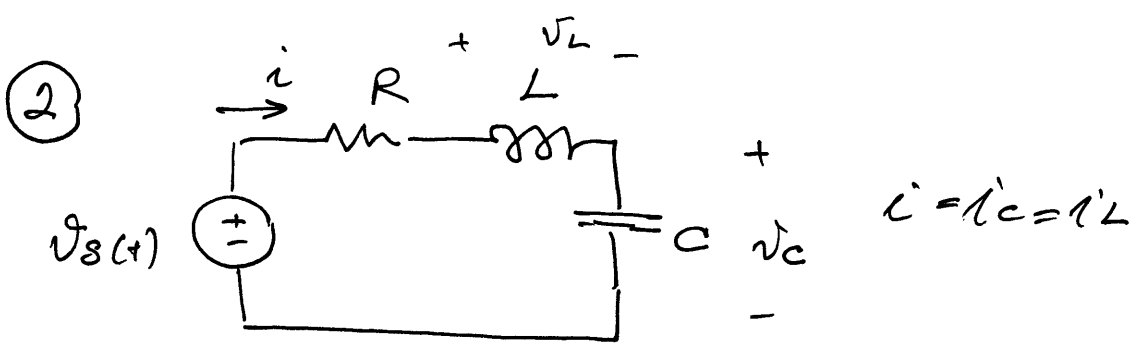

KVL:  $V - Ri - v_L - v_C = 0$

↑ Ohm's Law

$$i = C \cdot \frac{dv_C}{dt}$$

$$v_L = L \cdot \frac{di}{dt}$$

$$R \cdot i + L \cdot \frac{di}{dt} + v_C = v_S$$

$$i_L = C \cdot \frac{dv_C}{dt}$$

$$\left. \begin{aligned} \frac{di_L}{dt} &= -\frac{R}{L} \cdot i_L - \frac{1}{L} \cdot v_C + \frac{1}{L} \cdot v_S(t) \\ \frac{dv_C}{dt} &= \frac{1}{C} \cdot i_L \end{aligned} \right\}$$

$$\frac{d}{dt} \begin{pmatrix} i_L \\ v_C \end{pmatrix} = \begin{pmatrix} -R/L & -1/L \\ 1/C & 0 \end{pmatrix} \cdot \begin{pmatrix} i_L \\ v_C \end{pmatrix} + \begin{pmatrix} 1/L \\ 0 \end{pmatrix} \cdot v_S(t)$$

$$\det(sI - A) = 0$$

$$\det \left( s \cdot \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} - \begin{pmatrix} -R/L & -1/L \\ 1/C & 0 \end{pmatrix} \right) = 0$$

(6)

$$\det \begin{pmatrix} s + R/L & 1/L \\ -1/C & s \end{pmatrix} = 0$$

$$s(s + R/L) + \frac{1}{LC} = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Case:

#1:  $s_1 \neq s_2$ ; both natural frequencies are real

#2:  $s_1 = s_2$  :  $\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} = 0$

$$\frac{R}{2L} = \frac{1}{\sqrt{LC}}$$

$$R = 2 \cdot \sqrt{\frac{L}{C}}$$

Natural frequencies are real and identical

#3  $s_1 \neq s_2$  : both natural frequencies are complex (conjugate)

$$s_{1/2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

Classification:

#1: Overdamped


#2: Critically damped

#3: Underdamped

Special case:  $R=0$ :  $s_{1/2} = \pm j \cdot \frac{1}{\sqrt{LC}}$  : underdamped case

(3)

a)

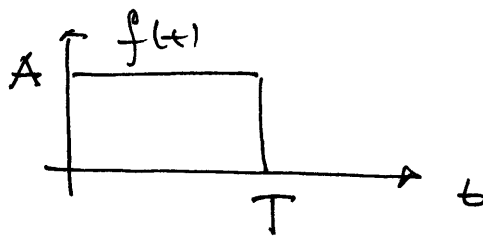


$$f(t) = A \cdot (u(t) - u(t-T))$$

$$F(s) = A \cdot \left( \frac{1}{s} - \frac{1}{s} \cdot e^{-Ts} \right)$$

$$F(s) = A \cdot \frac{1 - e^{-Ts}}{s}$$

b)

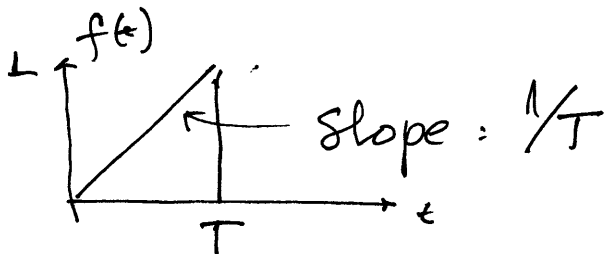

$$f(t) = \frac{1}{T} t \cdot [u(t) - u(t-T)]$$

$$f(t) = \frac{1}{T} \cdot t \cdot u(t) - \frac{1}{T} \cdot t \cdot u(t-T)$$

$\uparrow$   
 $t-T+T$


$$f(t) = \frac{1}{T} t \cdot u(t) - \frac{1}{T} \cdot (t-T+T) \cdot u(t-T)$$

$$f(t) = \frac{1}{T} \cdot t \cdot u(t) - \frac{1}{T} \cdot (t-T) \cdot u(t-T) - u(t-T)$$

$$F(s) = \frac{1}{T} \cdot \frac{1}{s^2} - \frac{1}{T} \cdot \frac{1}{s^2} \cdot e^{-Ts} - \frac{1}{s} \cdot e^{-Ts}$$

$$F(s) = \frac{1 - e^{-Ts}}{Ts^2} - \frac{e^{-Ts}}{s}$$

(f)

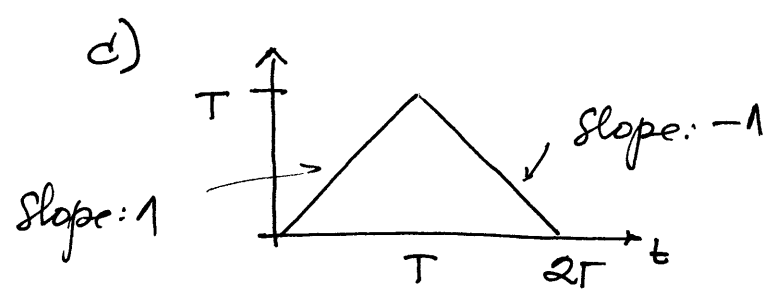


$$f(t) = t \cdot [u(t) - u(t-T)] - (t-2T) \cdot [u(t-T) - u(t-2T)]$$

$$f(t) = t \cdot u(t) - t \cdot u(t-T) - (t-2T)u(t-T) + (t-2T) \cdot u(t-2T)$$

$$f(t) = t \cdot u(t) - 2(t-T) \cdot u(t-T) + (t-2T) \cdot u(t-2T)$$
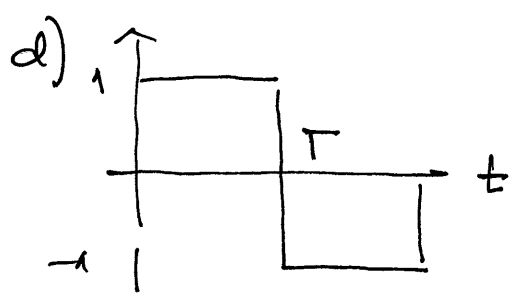
$$F(s) = \frac{1}{s^2} - \frac{2}{s^2} e^{-Ts} + \frac{1}{s^2} e^{-2Ts}$$



$$f(t) = u(t) - u(t-T) - (u(t-T) - u(t-2T))$$

$$f(t) = u(t) - 2u(t-T) + u(t-2T)$$

$$F(s) = \frac{1}{s} - \frac{2}{s} e^{-Ts} + \frac{1}{s} e^{-2Ts}$$



(4)

$$F(s) = \frac{s^2 + 2s + 2}{s(s+2)^2}$$

(9)

$$F(s) = \frac{A}{s} + \frac{B}{s+2} + \frac{C}{(s+2)^2}$$

partial fraction  
expansion

$$A = \lim_{s \rightarrow 0} s \cdot F(s) ; A = 1/2$$

$$B = \lim_{s \rightarrow -2} \frac{d}{ds} (s+2)^2 \cdot F(s)$$

$$= \lim_{s \rightarrow -2} \frac{d}{ds} \cdot \frac{s^2 + 2s + 2}{s}$$

$$= \lim_{s \rightarrow -2} \frac{d}{ds} \left( s + 2 + \frac{2}{s} \right)$$

$$= \lim_{s \rightarrow -2} \left( 1 - \frac{2}{s^2} \right)$$

$$= 1 - \frac{2}{4}$$

$$= 1/2$$

$$C = \lim_{s \rightarrow -2} (s+2)^2 \cdot F(s)$$

$$= \lim_{s \rightarrow -2} \frac{s^2 + 2s + 2}{s}$$

$$= \frac{4 - 4 + 2}{-2} ; C = -1$$

Hence,

10

$$F(s) = \frac{1}{2s} + \frac{1}{2(s+2)} - \frac{1}{(s+2)^2}$$

$$f(t) = \frac{1}{2} \cdot u(t) + \frac{1}{2} e^{-2t} u(t) - t \cdot e^{-2t} u(t)$$

$$f(t) = \left( \frac{1}{2} + \frac{1}{2} e^{-2t} - t e^{-2t} \right) u(t)$$

$$* F(s) = \frac{2s e^{-2s}}{(s+1)(s+3)}$$

$$\hat{F}(s) = \frac{2s}{(s+1)(s+3)}$$

Partial fraction expansion.

$$\hat{F}(s) = \frac{A}{s+1} + \frac{B}{s+3}$$

$$A = \lim_{s \rightarrow -1} (s+1) \cdot \hat{F}(s)$$

$$= \lim_{s \rightarrow -1} \frac{2s}{s+3} ; A = -1$$

$$B = \lim_{s \rightarrow -3} (s+3) \cdot \hat{F}(s)$$

$$= \lim_{s \rightarrow -3} \frac{2s}{s+1} ; B = 3$$

$$\hat{F}(s) = \left( -\frac{1}{s+1} + \frac{3}{s+3} \right) ; F(s) = \left( -\frac{1}{s+1} + \frac{3}{s+3} \right) e^{-2s}$$

$$\hat{f}(t) = \left( -e^{-t} + 3e^{-3t} \right) u(t)$$

$$f(t) = \left( -e^{-(t-2)} + 3e^{-3(t-2)} \right) u(t-2)$$