

SIMON FRASER UNIVERSITY  
SCHOOL OF ENGINEERING SCIENCE

Spring 2008  
ENSC 320: ELECTRIC CIRCUITS II

Midterm Examination No. 2

March 19, 2008

*Duration: 50 minutes. Attempt all four problems. Questions are **not** equally weighted. Closed book and closed notes. Calculators, PDAs, laptops, and wireless phones are not permitted.*

1. **(25 points)** Consider the circuits shown in Fig. 1, where  $R_1 = 50 \Omega$ ,  $R_2 = 200 \Omega$ , and  $C = 2.5 \text{ mF}$ .

- Find its transfer function.
- Let  $v_{in}(t) = 10e^{-2t}u(t) \text{ V}$  and  $v_c(0_-) = 4 \text{ V}$ .
  - Use Laplace transform to find the complete response of the circuit by first finding the zero-state response and the zero-input response.
  - Identify the circuit's forced response and natural response.
  - Identify the circuit's steady-state response and transient response.

2. **(40 points)**

Consider the circuit shown in Figure 2. Assume that the op-amp is ideal.

- Find transfer function  $H(s) = V_{out}/V_{in}$ .
- Find zeros and poles of  $H(s)$ .
- Find the magnitude and the phase of the frequency response.
- Plot the magnitude as functions of  $\omega$  and identify the type of the circuit.

3. **(20 points)** Consider the circuits shown in Fig. 3, where  $R = 0.25 \Omega$  and  $C = 1 \text{ F}$ .

- Find the transfer function  $H(s)$  and the impulse response  $h(t)$ .
- If  $i_{in}(t) = 3e^{-t}u(t) \text{ A}$ , find  $v_c(t)$  using the convolution integral.

4. **(15 points)**

Consider the circuit shown in Figure 4. Find:

- input impedance  $Z(s)$
- the circuit's resonant frequency  $\omega_r$ .
- input impedance at  $\omega_r$ .

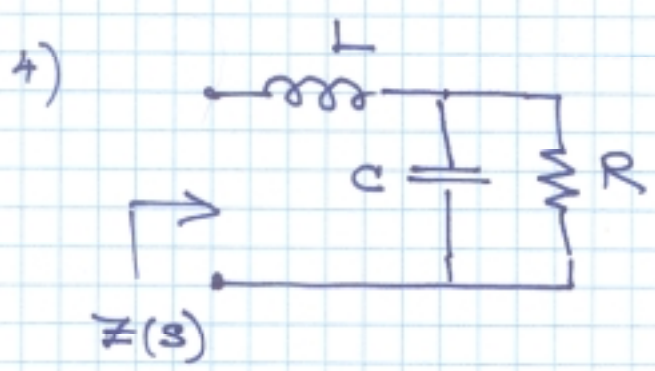
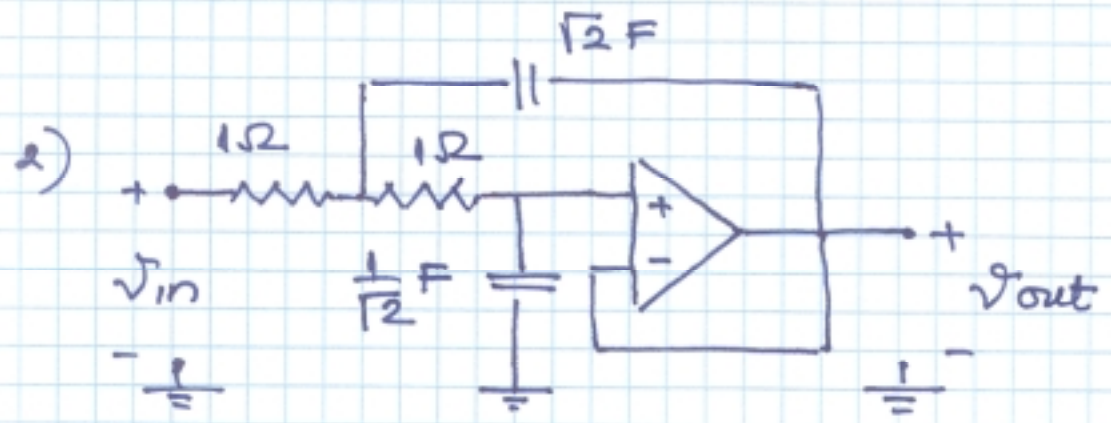
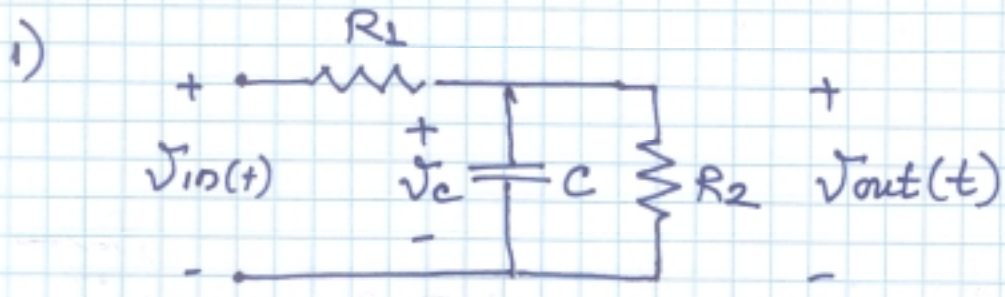


TABLE 13.1 Laplace Transform Pairs

Item number	$f(t)$	$\mathcal{L}[f(t)] = F(s)$
1	$K\delta(t)$	$K$
2	$Ku(t)$ or $K$	$\frac{K}{s}$
3	$t$	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at} u(t)$	$\frac{1}{s+a}$
6	$te^{-at} u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at} u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t) u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t) u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t) u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t) u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t) u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t) u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \phi) u(t)$	$\frac{s \sin(\phi) + \omega \cos(\phi)}{s^2 + \omega^2}$
15	$\cos(\omega t + \phi) u(t)$	$\frac{s \cos(\phi) - \omega \sin(\phi)}{s^2 + \omega^2}$
16	$e^{-at} [\sin(\omega t) - \omega t \cos(\omega t)] u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t) u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[ C_1 \cos(\omega t) + \left( \frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[ \omega t - \tan^{-1} \left( \frac{B}{A} \right) \right]$	$\frac{A + jB}{s+a+j\omega} + \frac{A - jB}{s+a-j\omega}$
20	$2\sqrt{A^2 + B^2} te^{-at} \cos \left[ \omega t - \tan^{-1} \left( \frac{B}{A} \right) \right]$	$\frac{A + jB}{(s+a+j\omega)^2} + \frac{A - jB}{(s+a-j\omega)^2}$