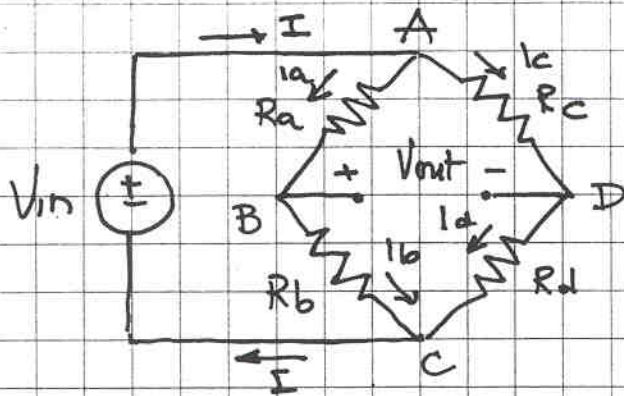


①



$$\text{KCL: } I = I_a + I_c \quad ; \quad I_a = I_b \quad ; \quad I_c = I_d$$

$$\text{KVL: } V_{out} + R_a I_a - R_c I_c = 0 \Rightarrow V_{out} = R_c I_c - R_a I_a$$

$$V_{out} - R_b I_b + R_d I_d = 0 \Rightarrow V_{out} = R_b I_b - R_d I_d$$

$$V_{out} = 0,$$

$$\text{Hence: } R_c I_c = R_a I_a$$

$$R_b I_b = R_d I_d$$

$$\text{Since } I_c = I_d$$

$$I_a = I_b$$

$$\text{We have: } R_c \cdot I_d = R_a \cdot I_b \Rightarrow \frac{R_c}{R_a} = \frac{I_b}{I_d}$$



$$R_b \cdot I_b = R_d \cdot I_d \Rightarrow \frac{R_d}{R_b} = \frac{I_b}{I_d}$$

$$\text{and } \frac{R_c}{R_a} = \frac{R_d}{R_b} \quad \text{or} \quad R_b R_c = R_a R_d$$

if the bridge is balanced.

$$\text{Grewbettes: } \frac{R_a}{R_b} = \frac{R_c}{R_d}$$

2

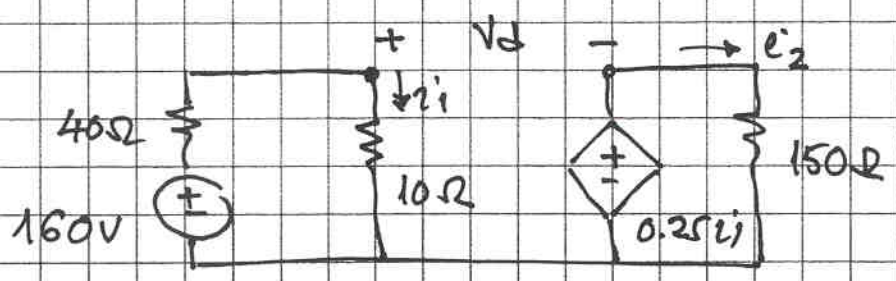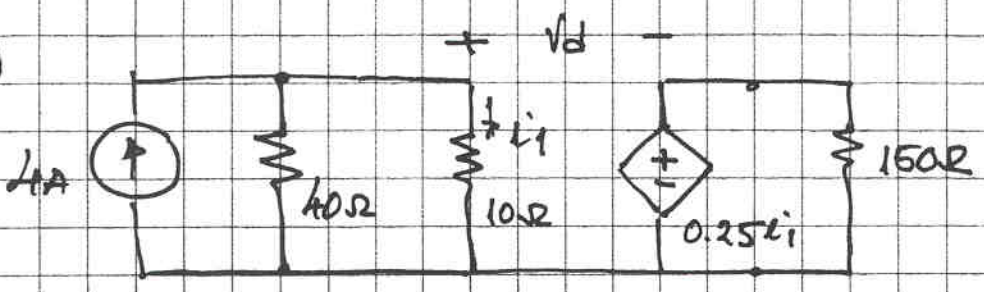

$$i_1 = \frac{160}{40+10} \text{ A}$$

$$i_1 = \frac{16}{5} \text{ A}; \quad i_1 = 3.2 \text{ A}$$

$$i_2 = \frac{0.25i_1}{150}; \quad i_2 = \frac{0.25 \times 3.2}{150} \text{ A}; \quad i_2 = \frac{16}{3} \text{ mA}$$



KVL:  $V_d - 10i_1 + 0.25i_2 = 0$

$$V_d = 9.75i_1$$

$$V_d = 9.75 \times 3.2 \text{ V}$$

$$V_d = 31.2 \text{ V}$$

3

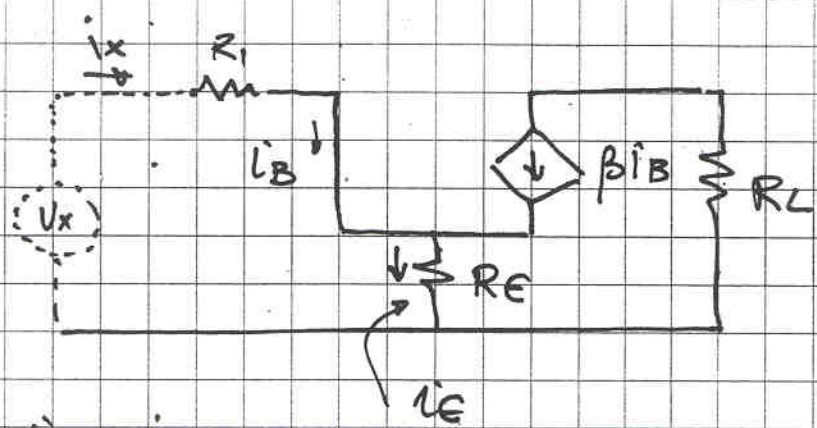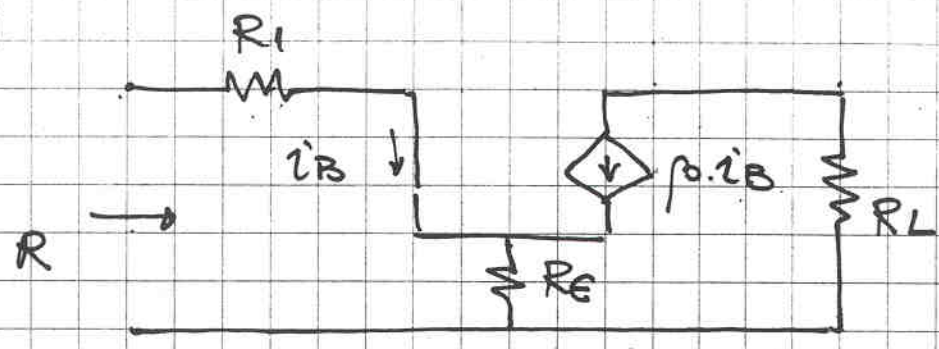

$$i_x = i_B$$


$$i_E = i_B + \beta \cdot i_B \quad ; \quad i_E = (1 + \beta) i_B$$

$$V_x = R_1 \cdot i_B + R_E \cdot (1 + \beta) \cdot i_B$$

$$V_x = (R_1 + R_E(1 + \beta)) i_B$$

$$\frac{V_x}{i_x} = R_1 + (1 + \beta) R_E$$

(4)

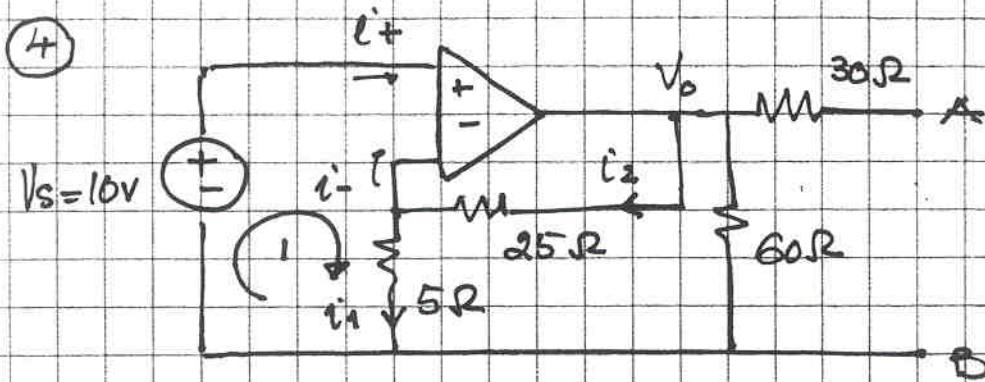

Ideal op amp

$$i_+ = 0$$

$$i_- = 0$$

$$V_d := V_+ - V_- = 0 ; r_d = 0$$

4 (a) Thevenin voltage:

RVL: Loop #1

$$V_s - V_d - 5 \cdot i_1 = 0 ; i_1 = 2A$$

RCL:  $i_1 = i_2$

$$i_2 = 2A$$

RVL:  $V_o = 25 \cdot i_2 + 5 \cdot i_1$


$$V_o = 60V$$

$$V_{AB} \text{ (when AB open circuited)} = V_{th}$$

$$V_{th} = 30 \times 0 + V_o ; V_{th} = 60V$$

4 (b) Thevenin resistance:

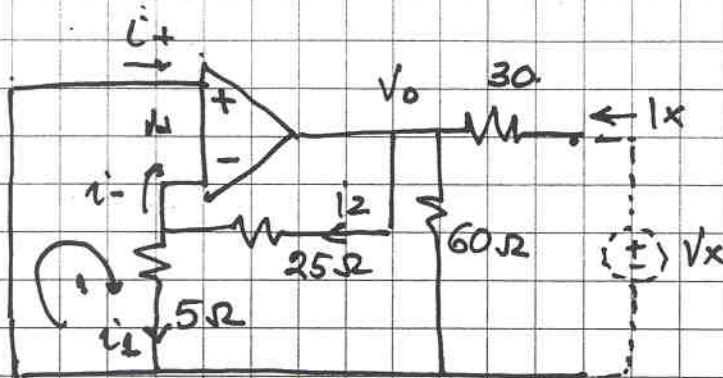Independent voltage source short-circuited:



$$R_{th} = \frac{V_x}{i_x}$$

$$KVL: 0 + V_d + 5 \cdot i_1 = 0 \Rightarrow i_1 = 0$$

$$KCL: i_- = 0 \Rightarrow i_2 = 0$$

$$i_1 = 0 \Rightarrow i_2 = 0$$

$$KVL \text{ (or Ohm's Law)} \quad V_0 = 25 \cdot i_2 + 5 \cdot i_1$$

$$V_0 = 0$$

$$KVL: V_x - 30 \cdot i_x - V_0 = 0$$

$$V_x = 30 i_x$$

$$\frac{V_x}{i_x} = 30$$

$$R_{th} = 30 \Omega$$