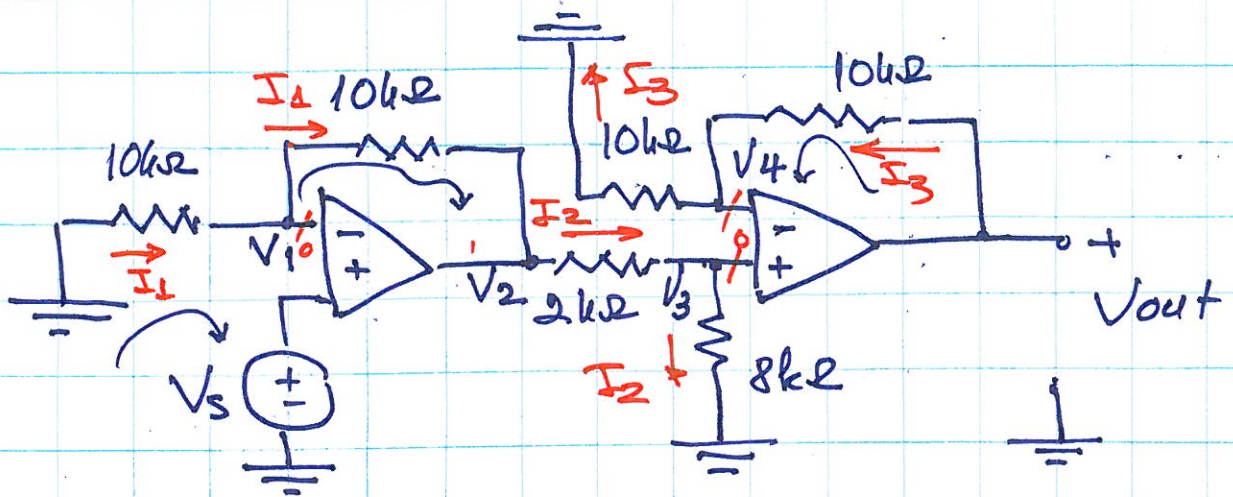


(1)



$$V_1 = V_s$$

$$I_1 \times 10 \times 10^3 + V_s = 0 \Rightarrow I_1 = -\frac{V_s}{10^4}$$

$$V_2 + 10 \times 10^3 \cdot I_1 - V_s = 0$$

$$V_2 = V_s - 10^4 \times I_1$$

$$V_2 = V_s - 10^4 \cdot \left(-\frac{V_s}{10^4}\right)$$

$$V_2 = 2V_s$$

$$-V_2 - 2 \times 10^3 \cdot I_2 - 8 \times 10^3 \cdot I_2 = 0$$

$$V_2 - 10 \times 10^3 \cdot I_2 = 0$$

$$I_2 = \frac{V_2}{10^4} ; I_2 = \frac{2 \cdot V_s}{10^4}$$

$$V_3 = 8 \times 10^3 \cdot I_2$$

$$V_3 = 8 \times 10^3 \cdot \frac{2V_s}{10^4} ; V_3 = 1.6 \cdot V_s$$

$$V_{out} - 10 \times 10^3 \cdot I_3 - V_4 = 0$$

$$V_4 = V_3 ; V_4 = 1.6 V_s$$

$$V_4 = 10 \times 10^3 \cdot I_3$$

$$I_3 = 10^{-4} \cdot V_4 ; I_3 = 10^{-4} \cdot 1.6 \cdot V_s$$

$$I_3 = + 1.6 \times 10^{-4} \cdot V_s$$

$$V_4 = 1.6 \cdot V_s$$

Hence;


$$V_{out} = 10^4 \cdot I_3 + V_4$$

$$V_{out} = 10^4 \times 1.6 \times 10^{-4} \cdot V_s + 1.6 \cdot V_s$$

$$V_{out} = 3.2 V_s$$

$$\frac{V_{out}}{V_s} = 3.2$$


2

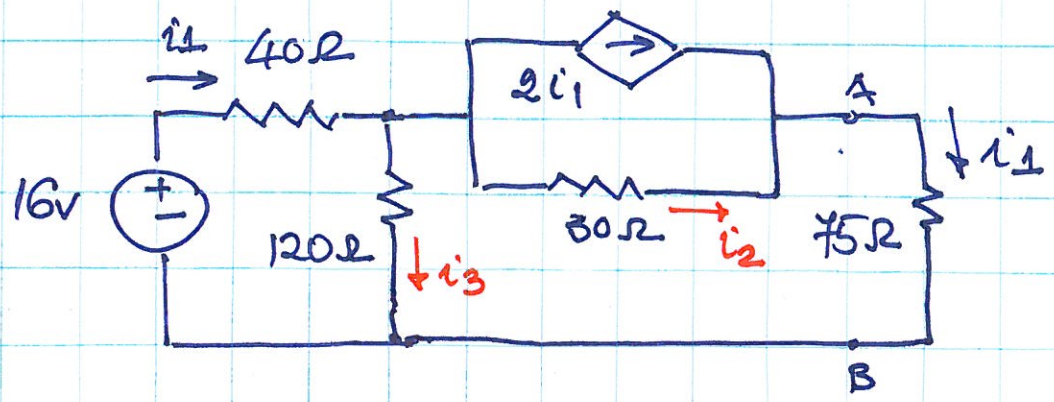

Thévenin equivalent:

R_{th} :

Disconnect the independent sources:

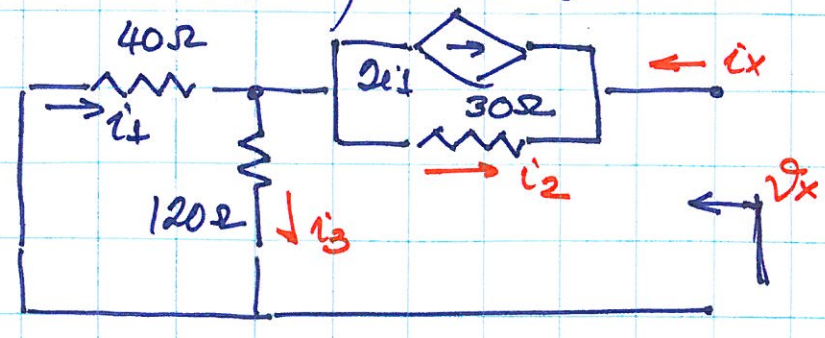

$$40 \cdot i_1 + 120 i_3 = 0 \Rightarrow i_1 + 3 i_3 = 0 \quad (1)$$

$$i_1 - i_3 - 2i_1 - i_2 = 0 \Rightarrow i_2 + i_3 = 0 \quad (2)$$

$$i_x = -i_2 - 2i_1 \quad (3)$$

From (1): $i_3 = -\frac{1}{3} i_1$

→ (2): $i_2 = -i_3 = \frac{1}{3} i_1$

(3) $i_x = -i_2 - 2i_1 = -\frac{1}{3} i_1 - 2i_1 = -\frac{7}{3} i_1$

$$i_x = -\left(-\frac{2}{3} i_1\right) - 2i_1$$

$$i_x = -\frac{4}{3} i_1$$

Then: $i_x + 30 \cdot i_2 - 120 \cdot i_3 = 0$

$$V_x = -30 \cdot \left(-\frac{2}{3} \cdot i_x\right) + 120 \cdot \left(-\frac{1}{3} \cdot i_x\right)$$

$$V_x = 20 i_x - 40 i_x$$

$$V_x = -20 \cdot i_x$$

Since $i_x = -\frac{4}{3} i_x$


$$\Rightarrow i_x = -\frac{3}{4} i_x$$

$$V_x = -20 \cdot \left(-\frac{3}{4} \cdot i_x\right)$$

$$\frac{V_x}{i_x} = 15; \quad R_{Th} = 15 \Omega$$

$$V_{Th} = ?$$

Consider terminals A and B open:

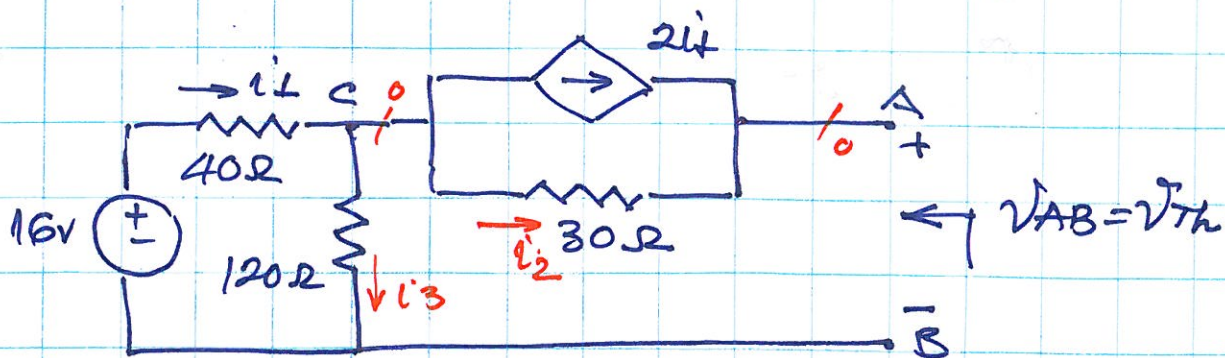

KCL for node A: $2i_x + i_2 = 0$
 $i_2 = -2i_x$

KCL for node C: $i_1 - i_3 = 0$; $i_3 = i_1$

Hence:

$$V_{AB} + 30 \cdot i_2 - 120 \cdot i_3 = 0$$

$$V_{AB} = -30 \cdot (-2i_x) + 120 \cdot (i_x)$$

$$V_{AB} = 180 i_x$$

KVL: $16 - 40i_x - 120 \cdot i_3 = 0$; $16 - 40i_x - 120i_x = 0$

$$i_x = \frac{16}{160}; \quad i_x = 0.1 \text{ A}$$


hence:

$$V_{AB} = 180 \times 0.1$$

$$= 18V$$

Thevenin equivalent: $V_{Th} = 18V$
 $R_{Th} = 15\Omega$

Equivalent circuit:

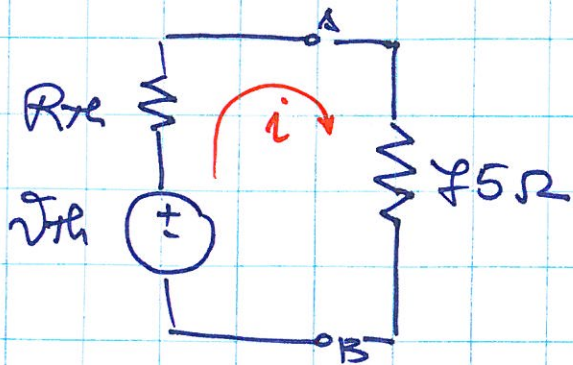

$$V_{Th} - R_{Th} \cdot i - 75 \times i = 0$$

$$i = \frac{V_{Th}}{R_{Th} + 75} ; i = \frac{18}{15 + 75} \quad i = 0.2A$$


$$P = 75 \times i^2$$

$$P = 75 \times (0.2)^2$$


$$P = 3W$$

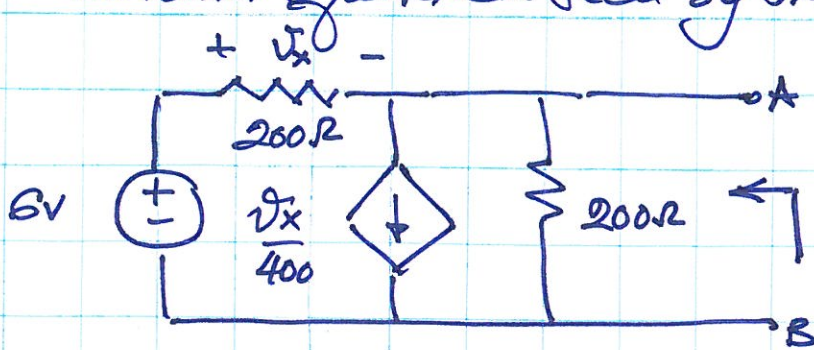(6)

③ Thevenin equivalent seen by the capacitor:



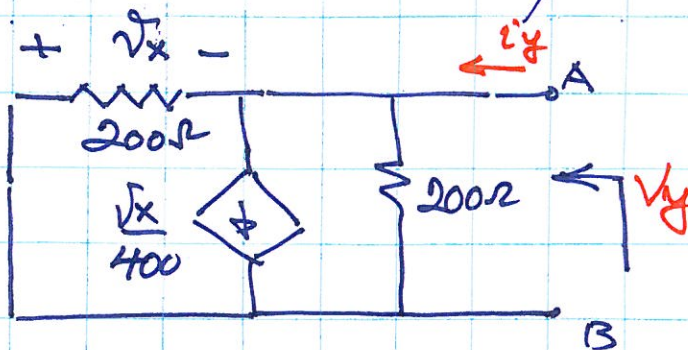$R_{th} = ?$ Disconnect the independent sources:



$$R_{th} = v_y / i_y$$

Nodal equation for node A:

$$\frac{v_A}{200} + \frac{v_x}{400} + \frac{v_A}{200} = i_y$$


Since $v_x = -v_A$

$$v_A \left(\frac{1}{200} + \frac{1}{200} \right) - \frac{v_A}{400} = i_y$$

$$-v_A \cdot \frac{3}{400} = i_y; \quad v_A = -\frac{400}{3} i_y$$

Note that $v_A = -v_y$

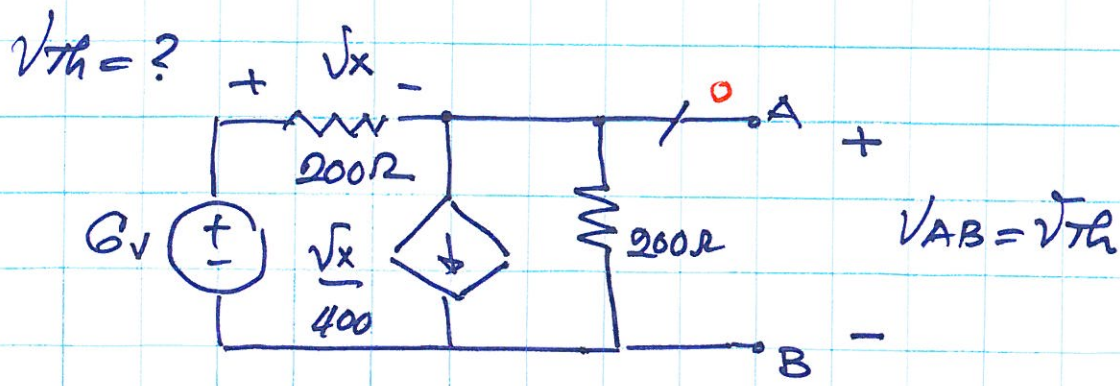Hence: $v_y = \frac{400}{3} i_y$ $R_{th} = \frac{v_y}{i_y}; R_{th} = \frac{400}{3} \Omega$



Node equation

$$\frac{V_A - 6}{200} + \frac{V_x}{400} + \frac{V_A}{200} = 0$$

$$2(V_A - 6) + V_x + 2V_A = 0$$

$$4V_A + V_x = 12 \quad (1)$$

KVL around the outer loop:

$$V_A + V_x - 6 = 0$$

$$V_A + V_x = 6 \quad (2)$$

From (1) : $V_x = 12 - 4V_A$


Then:

$$V_A + (12 - 4V_A) = 6$$

$$-3V_A = -6 \quad ; \quad V_A = 2$$

$$V_{th} = 2V$$

Equivalent circuit:

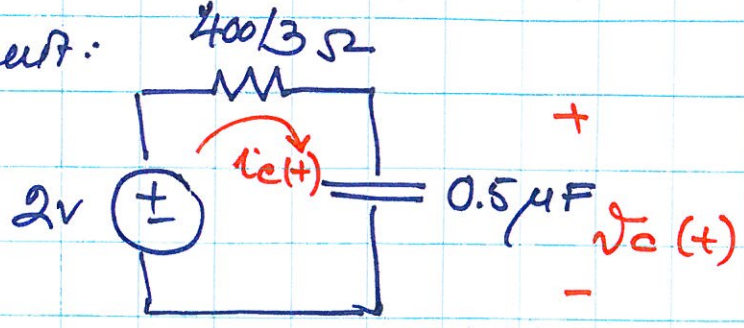

$$2 - \frac{400}{3} \cdot i_c - V_c = 0 \quad ; \quad i_c = C \frac{dV_c}{dt}$$

Hence:

$$\frac{400}{3} \cdot 0.5 \times 10^{-6} \frac{dv_c}{dt} + v_c = 2$$

$$\frac{200}{3} \times 10^{-6} \frac{dv_c}{dt} + v_c = 2$$

$$\frac{dv_c}{dt} + \frac{3}{200} \times 10^6 v_c = 2 \times \frac{3}{200} \times 10^6$$

Solution:

$$v_c(t) = v_p(t) + v_h(t)$$

↑ particular soln. ↑ homogeneous soln.

$$v_p(t) = A ; \frac{dv_p(t)}{dt} = 0$$

Hence,

$$\frac{3}{200} \times 10^6 \cdot A = 2 \times \frac{3}{200} \times 10^6$$

$$A = 2$$

$$v_p(t) = 2V$$

$$v_h(t) = k e^{st} ; \text{Then } \frac{dv_h}{dt} = k s e^{st}$$

From the differential equation:

$$k \cdot s e^{st} + \frac{3}{200} \times 10^6 \cdot k e^{st} = 0 \quad \leftarrow \text{homogeneous part}$$

$$s = -\frac{3}{200} \times 10^6 \quad ; \quad s = -1.5 \times 10^4$$

$$v_c(t) = k e^{-15000t} + 2$$


Assumption: $v_c(0^-) = -6V ; v_c(0^+) = 6V$

Hence:


$$-6 = k + 2 ; k = -8$$

$$v_c(t) = (2 - 8 e^{-15000t}) u(t)$$

(4) The circuit with switch closed:

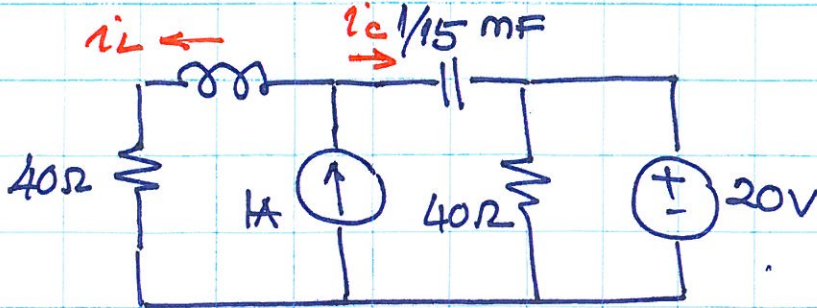

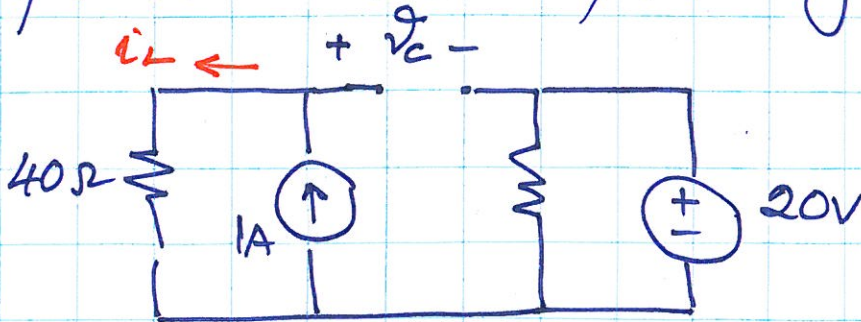If the switch was closed for a long time:



$$i_L(0^-) = 1A$$

$$20 + v_C(0^-) - 40 \times i_L(0^-) = 0 \text{ Hence: } v_C(0^-) = 20V$$

$$i_L(0^+) = i_L(0^-) \Rightarrow i_L(0^+) = 1A$$

$$v_C(0^+) = v_C(0^-) \Rightarrow v_C(0^+) = 20V$$

$$i_C(0^+) = ? \text{ In general, } i_C(0^+) \neq i_C(0^-)$$

$$\text{KCL: } i_C + i_L = 1$$


$$i_C = 1 - i_L \text{ (for any } t)$$

$$i_C(0^+) = 1 - i_L(0^+)$$


$$i_C(0^+) = 1 - 1 \text{ ; } i_C(0^+) = 0A$$

At $t \rightarrow \infty$, the switch has been open for a long time.

The circuit with the switch open:

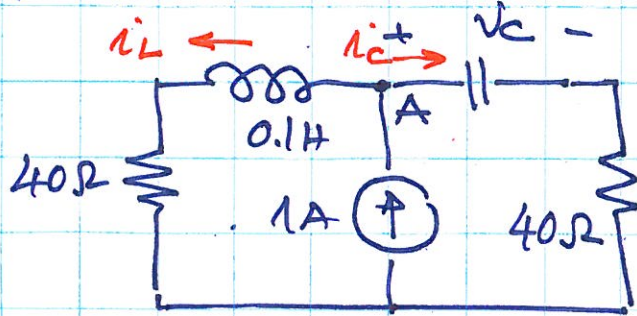

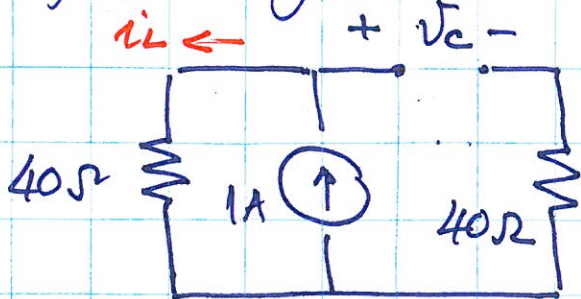After a long time ($t \rightarrow \infty$), the circuit looks as:



$$i_L(\infty) = 1A$$

$$v_C(\infty) - 40 \times i_L(\infty) = 0 ; \text{ Hence: } v_C(\infty) = 40V$$

Differential equations for the circuit with the switch open are:


$$(1) \quad i_L + i_C = 1 \quad (\text{KCL})$$

for node A

$$(2) \quad v_C - v_L - R_1 \cdot i_L + R_2 \cdot i_C = 0$$

$$i_C = C \frac{dv_C}{dt}$$

$$v_L = L \frac{di_L}{dt}$$

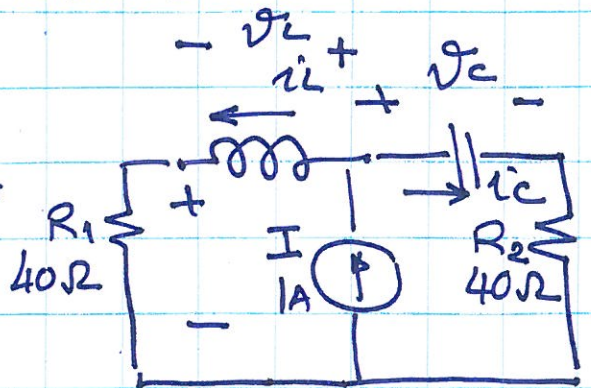

$$R_1 = 40\Omega$$
$$R_2 = 40\Omega$$

Hence:

$$V_c - L \frac{di_L}{dt} - R_1 \cdot i_L + R_2 C \frac{dv_c}{dt} = 0$$

or $R_2 C \frac{dv_c}{dt} - L \frac{di_L}{dt} + V_c - R_1 \cdot i_L = 0$

Since

$$i_c = I - i_L$$

$$C \frac{dv_c}{dt} = I - i_L$$

Two state equations:

$$C \frac{dv_c}{dt} + i_L = I$$

$$R_2 C \frac{dv_c}{dt} - L \frac{di_L}{dt} + V_c - R_1 \cdot i_L = 0$$

} *

From the first equation: $i_L = I - C \frac{dv_c}{dt}$

Hence: $\frac{di_L}{dt} = -C \frac{d^2v_c}{dt^2}$

Substituting into the second equation gives:

$$R_2 C \cdot \frac{dv_c}{dt} - L \cdot (-C \frac{d^2v_c}{dt^2}) + V_c - R_1 \cdot (I - C \frac{dv_c}{dt}) = 0$$

$$LC \cdot \frac{d^2v_c}{dt^2} + C \cdot (R_1 + R_2) \cdot \frac{dv_c}{dt} + V_c = R_1 \cdot I$$

$$\frac{d^2v_c}{dt^2} + \frac{R_1 + R_2}{L} \cdot \frac{dv_c}{dt} + \frac{1}{LC} \cdot v_c = \frac{R_1}{LC} \cdot I$$

Characteristic equation:

$$s^2 + \frac{R_1 + R_2}{L} \cdot s + \frac{1}{LC} = 0$$

$$s^2 + (40 + 40) \cdot \frac{1}{0.1} \times s + \frac{1}{0.1 \cdot \frac{1}{15} \times 10^{-3}} = 0$$

$$s^2 + 800s + 15 \times 10^4 = 0$$

$$s_{1/2} = -400 \pm \sqrt{(400)^2 - 15 \times 10^4}$$

$$s_{1/2} = -400 \pm \sqrt{160000 - 150000}$$

$$= -400 \pm 100 \quad ; \quad \begin{matrix} s_1 = -300 & \text{Natural} \\ s_2 = -500 & \text{frequency.} \end{matrix}$$

General form of the complete solution:

$$v_C(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} + v_{cp}(t)$$

$$i_L(t) = k_3 e^{s_1 t} + k_4 e^{s_2 t} + i_{lp}(t)$$

Particular solution.

$$v_{cp}(t) = A \quad ; \quad \frac{dv_{cp}(t)}{dt} = 0 \quad ; \quad \frac{d^2 v_{cp}(t)}{dt^2} = 0$$

From the state equation:

$$\frac{d^2 v_C}{dt^2} + 800 \cdot \frac{dv_C}{dt} + 15 \times 10^4 v_C = \frac{40}{0.1 \cdot \frac{1}{15} \times 10^{-3}} \cdot 1$$

$$15 \times 10^4 \cdot v_{cp}(t) = 40 \times 15 \times 10^4$$

$$v_{cp}(t) = 40 \text{ V} \quad (\text{as expected.})$$

Recall: $v_C(\infty) = 40 \text{ V}$

$$i_{lp}(t) = B$$

From the state equation:

$$C \frac{di_L}{dt} + i_L = I$$

$$C \frac{di_{lp}(t)}{dt} + i_{lp}(t) = I \quad ; \quad C \cdot 0 + B = I \quad ; \quad B = I$$

Hence, $i_C(t) = 1 \text{ A}$ (as expected)
 Recall: $i_L(\infty) = 1 \text{ A}$

(13)

$$v_C(t) = k_1 e^{s_1 t} + k_2 e^{s_2 t} + 40$$

$$i_L(t) = k_3 e^{s_1 t} + k_4 e^{s_2 t} + 1$$

$$s_1 = -300$$

$$s_2 = -500$$

$$v_C(0^+) = 20 ; i_L(0^+) = 1$$

Hence:

$$k_1 + k_2 + 40 = 20$$

$$k_3 + k_4 + 1 = 1$$

$$k_1 + k_2 = -20$$

$$k_3 + k_4 = 0$$

We need two additional equations in order to find all unknown constants

Note that: $\frac{dv_C(t)}{dt} = k_1 s_1 + k_2 s_2$

$$\frac{di_L(t)}{dt} = k_3 s_1 + k_4 s_2$$

From the differential equations: (*)

$$C \frac{dv_C}{dt} + i_L = 1 ; \frac{1}{15} \times 10^{-3} \frac{dv_C}{dt} + i_L = 1$$

$$40 \times \frac{1}{15} \times 10^{-3} \frac{dv_C}{dt} - 0.1 \frac{di_L}{dt} + v_C - 40 \cdot i_L = 0$$

at $t = 0^+$:

$$\frac{1}{15} \times 10^{-3} \cdot \frac{dv_C}{dt} \Big|_{0^+} + i_L(0^+) = 1$$

$$\text{Note that } i_L(0^+) = 1$$

$$\text{Hence } \frac{dv_C}{dt} \Big|_{0^+} = 0$$

$$\text{Then: } 40 \cdot \frac{1}{15} \times 10^{-3} \cdot 0 - 0.1 \cdot \frac{di_L}{dt} \Big|_{0^+} + v_C(0^+) - 40 \cdot i_L(0^+) = 0$$

$$-0.1 \frac{di_L}{dt} |_{0^+} + 20 - 40 \cdot 1 = 0$$

$$-0.1 \frac{di_L}{dt} |_{0^+} = 20 \quad ; \quad \frac{di_L}{dt} |_{0^+} = -200$$

Hence:

$$k_1 \cdot (-300) + k_2 \cdot (-500) = 0$$
$$k_3 \cdot (-300) + k_4 \cdot (-500) = -200$$

Again:

$$k_1 + k_2 = -20 \quad k_1 + k_2 = -20 \quad / \times 5$$
$$-300k_1 - 500k_2 = 0 \Rightarrow -3k_1 - 5k_2 = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{add}$$
$$(5-3)k_1 = -100$$
$$k_1 = -50$$
$$k_2 = 30$$

And:

$$k_3 + k_4 = 0$$
$$-300k_3 - 500k_4 = -200$$

OR:

$$k_3 + k_4 = 0 \quad ; \quad k_4 = -k_3$$
$$-3k_3 - 5k_4 = -2 \quad ; \quad 3k_3 + 5k_4 = 2$$
$$3k_3 - 5k_3 = 2 \quad ; \quad k_3 = -1$$
$$k_4 = 1$$

Finally:

$$v_c(t) = \left(-50e^{-300t} + 30e^{-500t} + 40 \right) u(t)$$
$$i_L(t) = \left(-e^{-300t} + e^{-500t} + 1 \right) u(t)$$

Check:

$$v_c(0^+) = 20 \quad ; \quad v_c(\infty) = 40$$
$$i_L(0^+) = 4 \quad ; \quad i_L(\infty) = 1$$