

SIMON FRASER UNIVERSITY  
SCHOOL OF ENGINEERING SCIENCE

Fall 2016  
ENSC 220: ELECTRIC CIRCUITS I

Midterm Examination No. 2  
Monday, November 14, 2016

*Duration: 110 minutes. Attempt all problems. Questions are not equally weighted. Closed book and closed notes. Simple calculators (with no graphing/programming functions) are permitted. PDAs, laptops, and wireless phones are not permitted. Please write legibly. Illegible text will not be graded.*

1. (15 points) For the circuit shown in Figure 1, find the voltage ratio  $V_{out}/V_s$ .
2. (20 points) For the circuit shown in Figure 2, find:
  - (a) Thévenin equivalent circuit.
  - (b) Norton equivalent circuit.
  - (c) If a load resistor  $R_L$  is attached across the output terminals, find the value of  $R_L$  for which the load absorbs maximum power.
  - (d) Calculate the maximum power transferred to the load.
3. (25 points) In the circuit shown in Figure 3, suppose  $i_s(t) = 4\sin(4t)$  A.
  - (a) Find and sketch  $v_L(t)$ .
  - (b) Find and sketch  $i_C(t)$ .
  - (c) For  $t \geq 0$ , compute the energy stored in:
    - the inductor.
    - the capacitor.
4. (40 points) The circuit shown in Figure 4 has an ideal op-amp.
  - (a) Write nodal analysis equations.
  - (b) Obtain the differential equations for  $v_o(t)$ .
  - (c) Let  $R_1 = 4\Omega$ ,  $R_2 = 10\Omega$ ,  $C = 0.5$  F. If  $v_i(t) = 6u(t)$  and  $v_C(0_-) = 4$  V, find and sketch  $v_o(t)$  for  $t > 0$ .
  - (d) Find and sketch  $i_C(t)$ .

Figure 1:

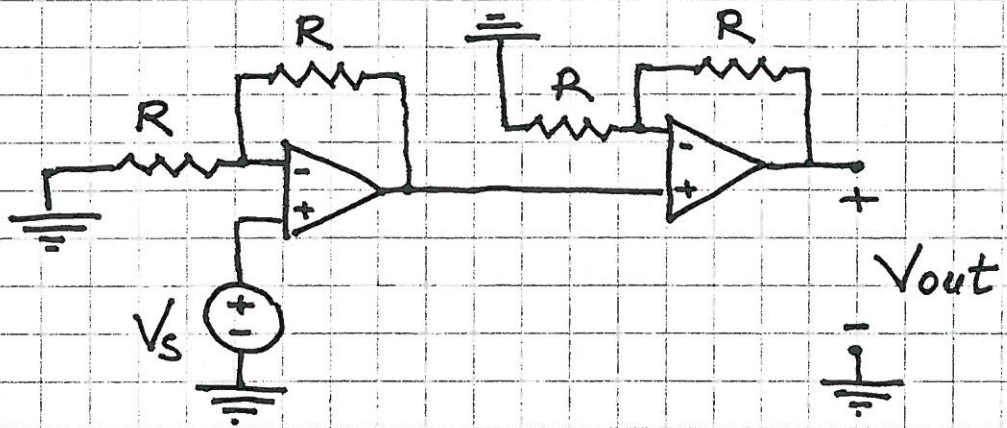


Figure 2:

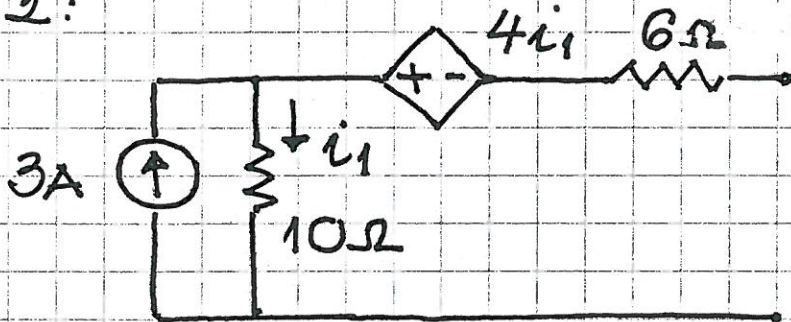


Figure 3:

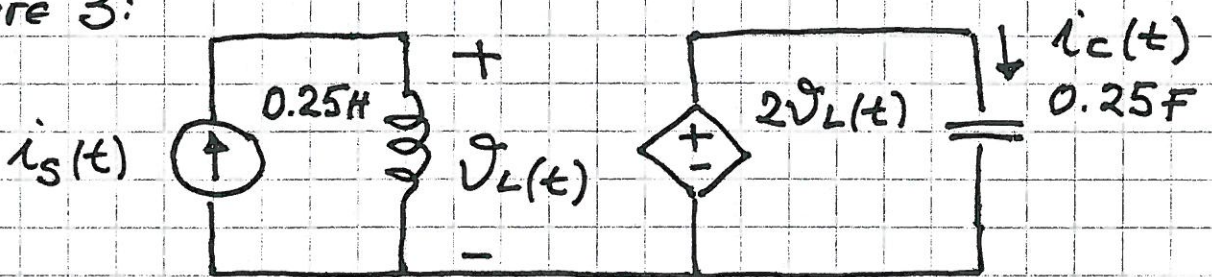


Figure 4:

