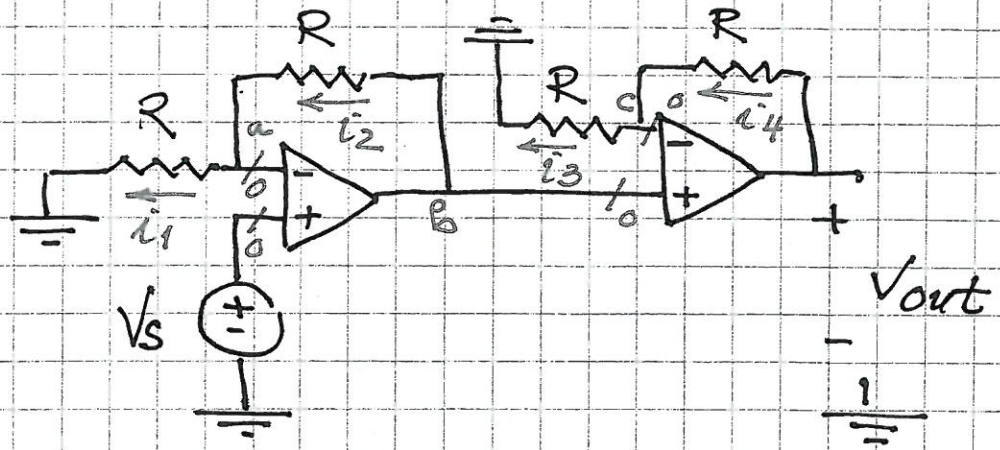


①

①



Ideal op-amp:  $i_- \equiv 0; i_+ \equiv 0$   
 $v_- - v_+ \equiv 0$

$$v_a = v_s$$

$$v_a - R \cdot i_1 = 0; i_1 = \frac{v_a}{R}$$

$$i_2 = i_1 \text{ Hence, } i_2 = \frac{v_a}{R}$$

$$v_b - v_a = R \cdot i_2$$

$$\text{Hence, } v_b = v_a + R \cdot i_2$$

$$v_b = v_s + R \cdot \frac{v_a}{R}$$

$$v_b = v_a + v_a$$

$$v_b = 2v_a; v_b = 2 \cdot v_s$$

$$v_c = v_b; v_c = 2 \cdot v_s$$

$$v_c - R \cdot i_3 = 0; i_3 = \frac{v_c}{R}; i_3 = \frac{2v_s}{R}$$


$$i_4 = i_3 \text{ Hence, } i_4 = \frac{2v_s}{R}$$

$$v_c = R \cdot i_3 \text{ Hence, } v_c = R \cdot \frac{2v_s}{R}; v_c = 2v_s$$

$$v_{out} - v_c = R \cdot i_4; v_{out} = v_c + R \cdot i_4 = 2v_s + R \cdot \frac{2v_s}{R}; \frac{v_{out}}{v_s} = 4$$

2

2

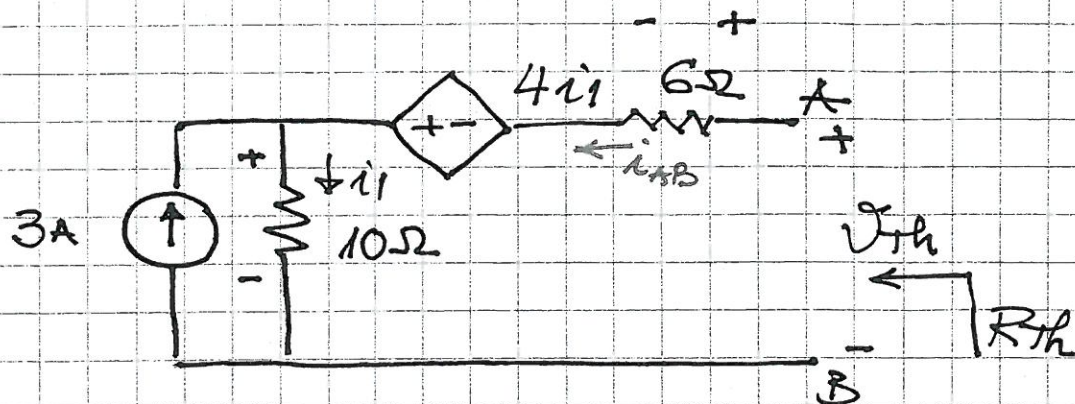

(a)

Thevenin equivalent:

$V_{th}$  with terminals open-circuited:  $i = 0$

$$\text{KCL: } 3 + i_{AB} = i_1 \quad ; \quad i_1 = 3A$$

$$\text{KVL: } V_{th} - 6 \cdot i_{AB} + 4 \cdot i_1 - 10 \cdot i_1 = 0$$

$$V_{th} = 6 \cdot 0 - 4 \cdot i_1 + 10 \cdot i_1$$

$$V_{th} = 6 \cdot i_1 \quad ; \quad V_{th} = 6 \cdot 3 \quad ; \quad V_{th} = 18V$$

$R_{th} = \frac{V_x}{i_x}$  with all independent sources disconnected.

$$\text{KCL: } i_x = i_1$$

KVL:


$$V_x - 6 \cdot i_x + 4 \cdot i_1 - 10 \cdot i_1 = 0$$

$$V_x = 6 \cdot i_x + 6 \cdot i_1$$


$$V_x = 6 \cdot i_x + 6 \cdot i_x \quad ; \quad V_x = 12 i_x$$

$$\frac{V_x}{i_x} = 12$$


$$R_{th} = 12\Omega$$

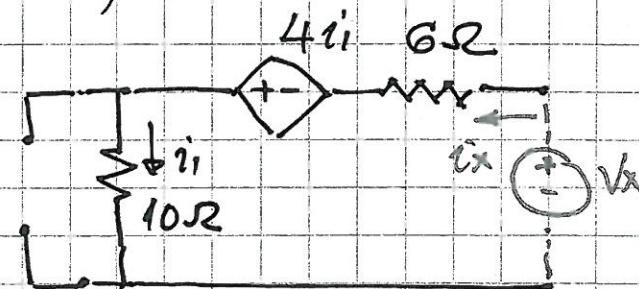

(b) Norton equivalent:

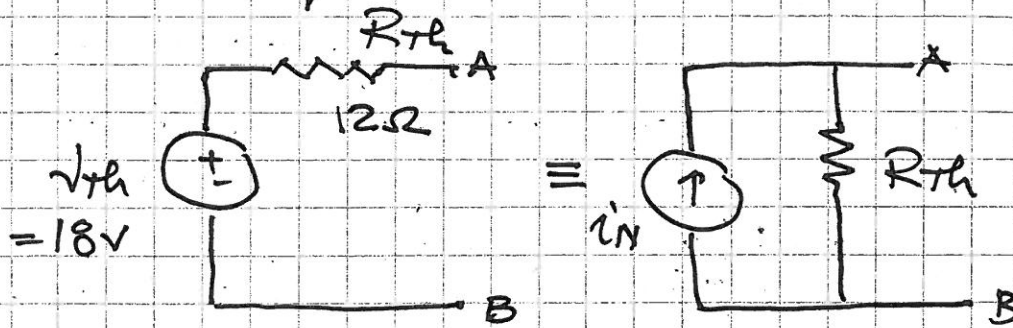
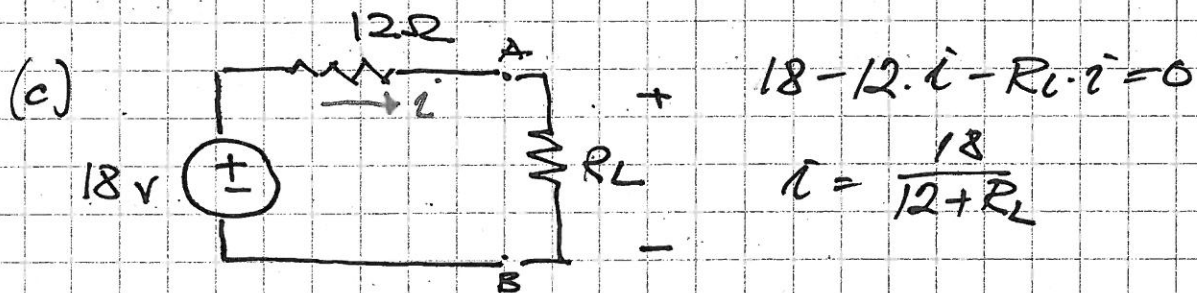
$$i_N = \frac{V_{th}}{R_{th}} ; i_N = \frac{18}{12} ; i_N = 1.5A$$



Power dissipated in  $R_L$ :  $P_L = i \cdot V$

$$P_L = \frac{18}{12+R_L} \cdot R_L \cdot \frac{18}{12+R_L}$$

$$P_L = R_L \cdot \left( \frac{18}{12+R_L} \right)^2 ; \frac{\partial P_L}{\partial R_L} = 18^2 \cdot \frac{\partial}{\partial R_L} \left\{ \frac{R_L}{(12+R_L)^2} \right\}$$

$$\frac{\partial P_L}{\partial R_L} = 324 \cdot \frac{(12+R_L)^2 - R_L \cdot 2 \cdot (12+R_L)}{(12+R_L)^{2 \cdot 2}}$$

$$\frac{\partial P_L}{\partial R_L} = 0 \text{ if: } 12+R_L - 2R_L = 0 ; R_L = 12\Omega$$

4

Maximum power transfer:

$$P_{\max} = R_L \cdot \left( \frac{18}{12 + R_L} \right)^2 \quad \text{for } R_L = 12 \Omega$$

$$P_{\max} = 12 \times \frac{18^2}{(2 \times 12)^2}$$

$$= \frac{324}{4 \times 12}$$


$$= \frac{81}{12}$$

$$= \frac{27}{4}$$

$$= 6.75 \text{ Watts}$$

3

5

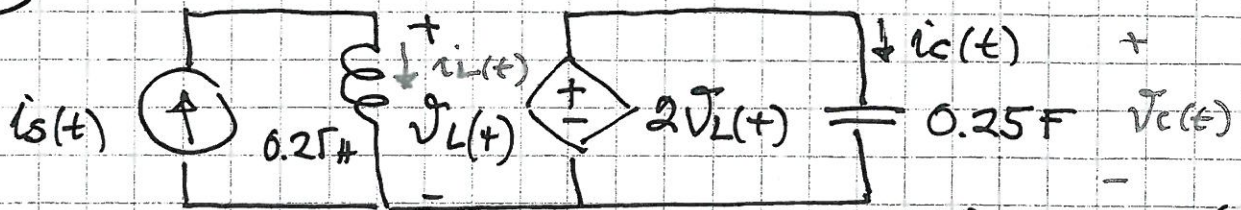

$$i_s(t) = 4 \sin(4t) \text{ A}$$


(a)  $v_C(t) = ?$

$$i_L = i_s$$

$$v_L = L \frac{di_L}{dt} ; v_L = 0.25 \times \frac{d}{dt} (4 \sin(4t))$$

$$v_L = 0.25 \times 4 \times 4 \times \cos(4t)$$

$$v_L = 4 \cos(4t) \text{ V}$$

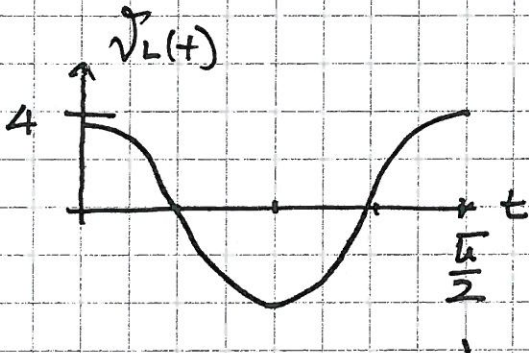

$$\omega = 4 \text{ rad/sec}$$

$$\omega = 2\pi \frac{1}{T} ; T = \frac{2\pi}{\omega}$$

$$T = \frac{2\pi}{4}$$

$$T = \pi/2$$

(b)  $i_C(t) = ?$

$$\text{KVL: } 2v_L(t) - v_C(t) = 0$$


$$v_C = 2 \cdot v_L ; v_C = 8 \cos(4t)$$

$$i_C = C \frac{dv_C}{dt} ; i_C = 0.25 \times \frac{d}{dt} (8 \cos(4t))$$

$$i_C = 0.25 \times 8 \cdot 4 \cdot (-\sin(4t))$$

$$i_C = -8 \sin(4t) \text{ A}$$

6

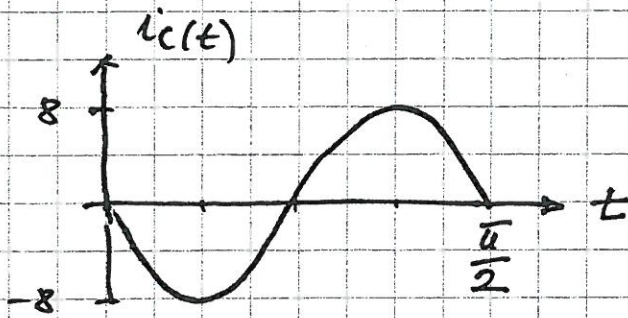

(c) Energy stored:

- inductor:  $P_L = i_L \cdot v_L$

$$P_L = i_L(t) \cdot v_L(t)$$

$$P_L = 4 \sin 4t \cdot 4 \cos 4t$$

$$P_L = 16 \sin 4t \cdot \cos 4t$$

$$\text{Note: } 2 \sin \alpha \cos \alpha \\ = \sin 2\alpha$$

$$P_L = 8 \sin 8t$$

$$W_L = \int_0^t 8 \sin 8x \cdot dx ; W_L = 8 \cdot \left(-\frac{1}{8}\right) \cdot \cos 8x \Big|_0^t$$

$$W_L = -(\cos 8t - 1)$$

$$W_L = (1 - \cos 8t) \text{ Watts}$$

- capacitor:

$$P_C = i_C \cdot v_C$$

$$P_C = (-8 \sin(4t)) \cdot 8 \cos(4t)$$

$$P_C = -64 \sin(4t) \cdot \cos(4t)$$

$$P_C = -32 \sin(8t)$$


$$W_c = \int_0^t (-32 \times \sin(8x)) dx$$

$$W_c = -32 \times \frac{1}{8} \cdot (-\cos 8x) \Big|_0^t$$

$$W_c = 4 (\cos 8t - 1) \text{ Watts}$$

7

4

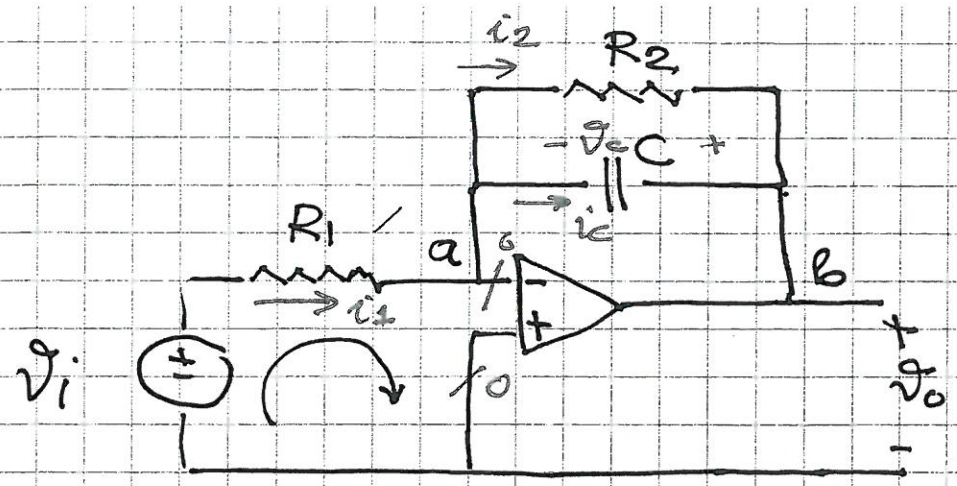


Ideal op amp:  $V_- - V_+ \equiv 0$ ;  $V_- = 0$

KCL:  $i_1 - i_2 - i_c = 0$

KVL:

4

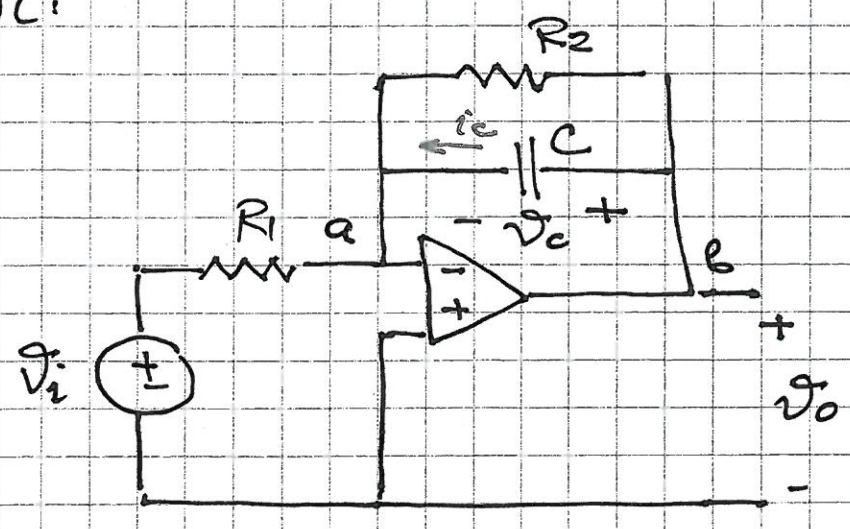

(a)

Nodal equations:  $\frac{V_a - V_i}{R_1} + \frac{V_a - V_b}{R_2} - i_c = 0$

$V_a \equiv 0$

Ideal op amp:  $V_- - V_+ = 0$

$V_- \equiv 0$

$V_a \equiv 0$

$-\frac{V_i}{R_1} - \frac{V_b}{R_2} - i_c = 0$

Note that  $V_b = V_c$

Hence,  $-\frac{V_i}{R_1} - \frac{V_c}{R_2} - i_c = 0$



$$i_c = C \frac{dv_c}{dt}$$

$$C \frac{dv_c}{dt} + v_c \cdot \frac{1}{R_2} = -v_i \cdot \frac{1}{R_1}$$

or:

$$\frac{dv_c}{dt} + \frac{1}{CR_2} \cdot v_c = -\frac{1}{R_1} \cdot v_i$$

Since  $v_o \equiv v_b$

(b)  $v_o = v_c$

Differential equation:

$$\frac{dv_o}{dt} + \frac{1}{CR_2} \cdot v_o = -\frac{1}{CR_1} \cdot v_i$$

(c)  $R_1 = 4\Omega$ ;  $R_2 = 10\Omega$ ,  $C = 0.5F$

$$v_i(t) = 6u(t)$$

$$v_c(0^-) = 4V$$

$$\frac{dv_o}{dt} + \frac{1}{0.5 \times 10} \cdot v_o = -\frac{1}{0.5 \times 4} \cdot v_i$$

$$\frac{dv_o}{dt} + \frac{1}{5} \cdot v_o = -\frac{1}{2} \times 6u(t)$$

$$\frac{dv_o}{dt} + \frac{1}{5} \cdot v_o = -3u(t) \quad \text{for } t \geq 0$$

$$\frac{dv_o}{dt} + \frac{1}{5} v_o = -3$$

Homogeneous equation:  $\frac{dv_o}{dt} + \frac{1}{5} v_o = 0$

$$v_{oh} = k e^{st}$$

$$\frac{dv_{oh}}{dt} = k s e^{st}$$

Hence:  $k \cdot s e^{st} + \frac{1}{5} \cdot k e^{st} = 0$  ;  $s = -\frac{1}{5}$   
 natural frequency

$$v_{oh} = k e^{-t/5}$$

Particular solution:

$$v_{op}(t) = A \quad (\text{constant})$$

$$\frac{dv_{op}(t)}{dt} = 0$$

Hence, differential equation becomes:

$$0 + \frac{1}{5}A = -3 \quad A = -15$$

$$v_{op}(t) = -15$$


Complete solution:

$$v_o(t) = k e^{-t/5} - 15$$

Initial conditions:  $v_c(0^-) = 4V$ ;  $v_c(0^+) = 4V$   
 or  $v_o(0^+) = 4V$

Hence:  $4 = k \cdot e^{-0/5} - 15$  ;  $k = 19$

$$v_o(t) = 19 e^{-t/5} - 15$$

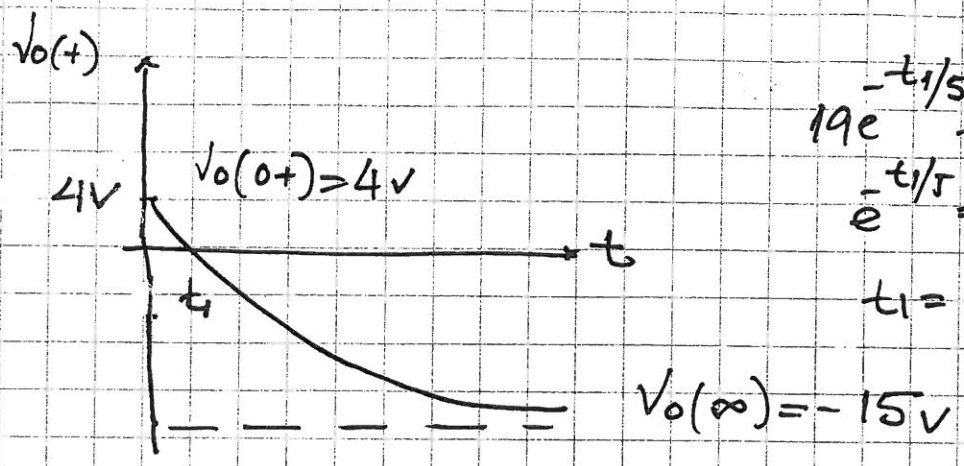

$$19e^{-t/5} - 15 = 0$$

$$e^{-t/5} = \frac{15}{19}$$

$$t_1 = 5 \ln \frac{19}{15}$$

(d)  $i_c(t) = C \cdot \frac{dv_c}{dt}$

$$i_c(t) = C \cdot \frac{dv_o}{dt}$$

$$i_c = 0.5 \times \frac{d}{dt} (19e^{-t/5} - 15)$$

$$i_c = 0.5 \times 19 \cdot \left(-\frac{1}{5}\right) e^{-t/5}$$

$$i_c = -1.9 e^{-t/5}$$

