
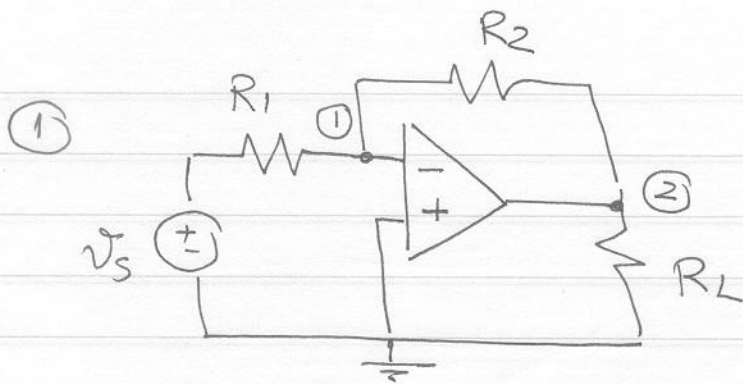


(1)

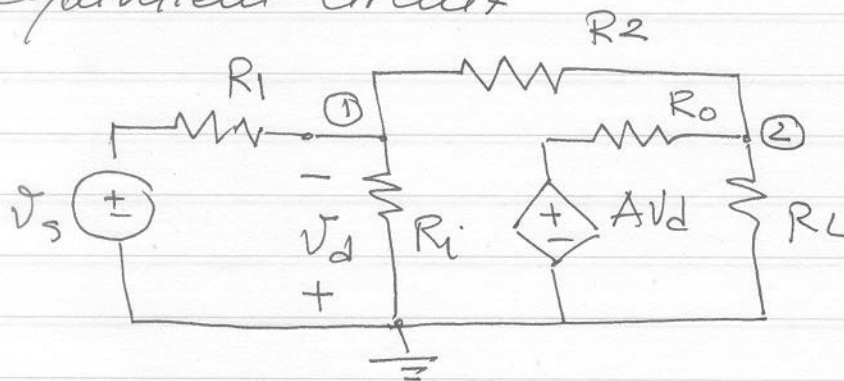

Op-amp is not ideal.
Equivalent circuit



Nodal equations:

$$\textcircled{1} \quad \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_i} + \frac{V_1 - V_2}{R_2} = 0$$

$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - A V_d}{R_o} + \frac{V_2}{R_L} = 0$$

Note: $V_d = -V_1$

$$\text{Hence: } V_1 \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_o} \right) - \frac{1}{R_2} \cdot V_2 = \frac{1}{R_1} \cdot V_s$$

$$\left(\frac{A}{R_o} - \frac{1}{R_2} \right) V_1 + \left(\frac{1}{R_2} + \frac{1}{R_L} + \frac{1}{R_o} \right) V_2 = 0$$


In matrix form:

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_0} & -\frac{1}{R_2} \\ \frac{A}{R_0} - \frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_L} + \frac{1}{R_0} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} \\ 0 \end{bmatrix}$$


① Note: if $A = 0$ (no dependent source)
 the nodal-admittance matrix is symmetric
 because it represents a circuit consisting of
 resistors only.

- ② All diagonal elements positive
- ③ Off diagonal elements negative, except
 for $\frac{A}{R_0}$ that comes from the dependent source.
 If $A = 0$, all off-diagonal elements are
 negative.

Output voltage: $V_0 = V_2$.

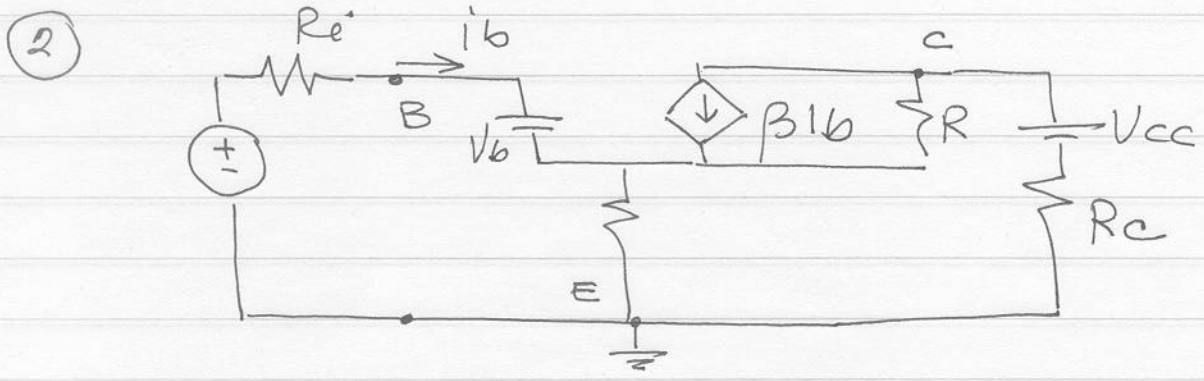

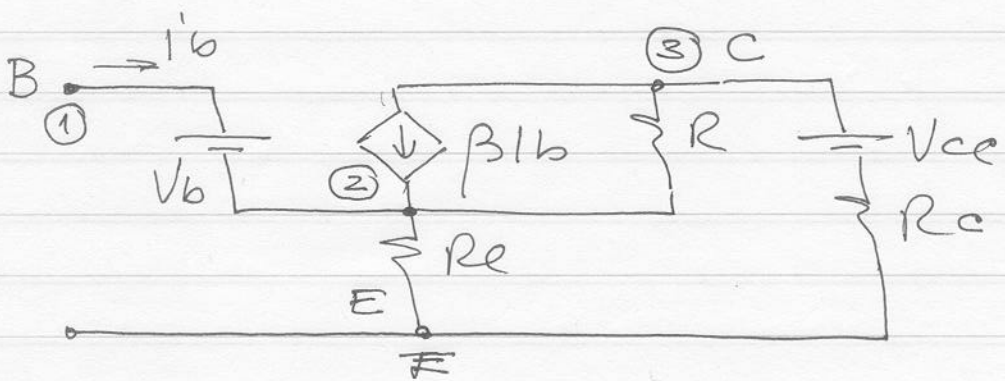The circuit used to find Thévenin's equivalent between B and E is:



To find V_{th} , nodes B and E should be kept open-circuited. Hence

$$I_b = 0$$

Nodal equations are:

$$V_1 - V_2 = V_b$$

$$\frac{V_2}{R_e} - \beta \cdot I_b + \frac{V_2 - V_3}{R} = 0$$

$$\beta I_b + \frac{V_3 - V_2}{R} + \frac{V_3 - V_{cc}}{R_c} = 0$$

Since $I_b = 0$, the equations become:

$$V_1 - V_2 = V_b$$

$$V_2 \cdot \left(\frac{1}{R_e} + \frac{1}{R} \right) - \frac{V_3}{R} = 0$$

$$-\frac{1}{R} \cdot V_2 + V_3 \cdot \left(\frac{1}{R_c} + \frac{1}{R} \right) = \frac{V_{cc}}{R_c}$$

Note that $V_{th} = V_d$

Since $V_1 = V_2 + V_b$, it is sufficient to find V_2 from the nodal equations

$$\text{Since } V_3 = R \cdot \left\{ \frac{1}{R_e} + \frac{1}{R} \right\} \cdot V_2$$

$$\text{Then } -\frac{1}{R} \cdot V_2 + R \cdot \left(\frac{1}{R_e} + \frac{1}{R} \right) \cdot \left(\frac{1}{R_c} + \frac{1}{R} \right) V_2 = \frac{V_{cc}}{R_c}$$

And

$$V_2 = \frac{V_{cc}}{R_c} \cdot \frac{1}{-\frac{1}{R} + \frac{R}{R_e} \left(\frac{1}{R_c} + \frac{1}{R} \right) + \frac{1}{R_c} + \frac{1}{R}}$$


$$V_2 = \frac{V_{cc}}{R_c} \cdot \frac{1}{\frac{R}{R_e \cdot R_c} + \frac{1}{R_e} + \frac{1}{R_c}}$$

$$\text{Or: } V_2 = V_{cc} \cdot \frac{R_e}{R + R_e + R_c}$$


Finally, $V_{th} = V_2 + V_b$

$$V_{th} = V_b + \frac{R_e}{R + R_e + R_c} V_{cc}$$

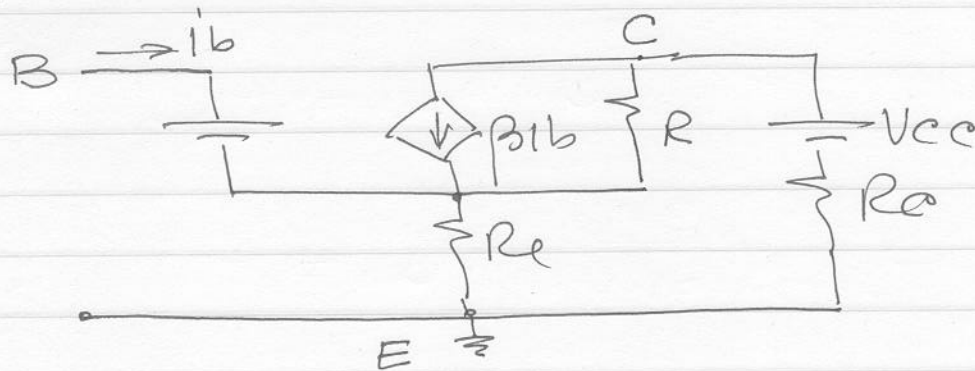③ The same circuit, but with all independent sources properly disconnected, is used to find Thevenin's resistance between B-E:




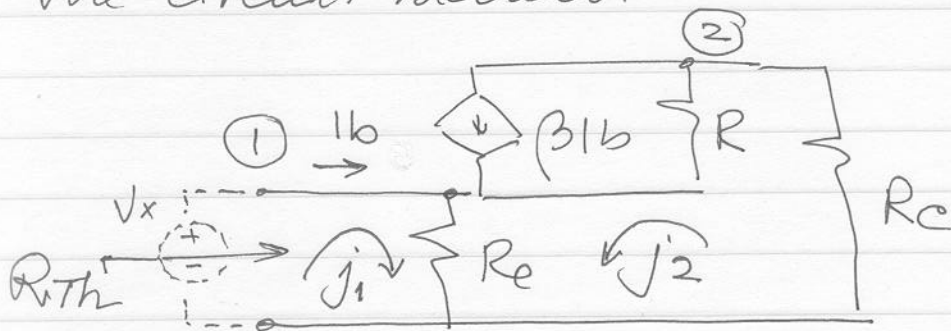When independent sources are disconnected, the circuit becomes:



To find R_{Th} , assume a voltage source V_s is connected between

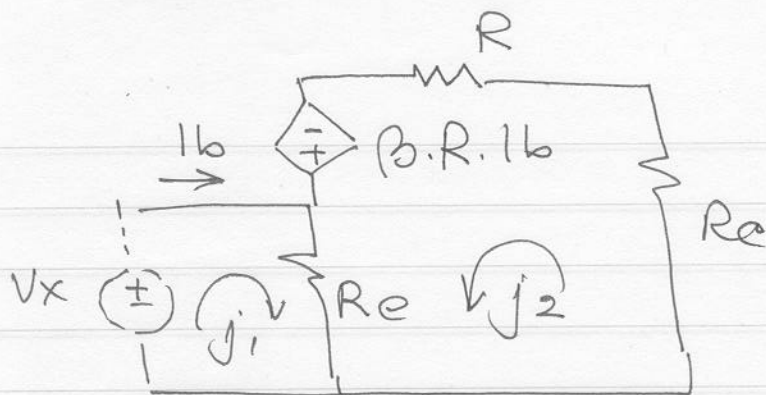Note that the parallel connection of the dependent current source and resistor can be transformed into a series connection of a dependent voltage source and the same resistor. (This will reduce the number of meshes.)



Mesh equation:

$$V_x - R_e \cdot (j_1 + j_2) = 0$$

$$\beta R \cdot i_b - R_e (j_1 + j_2) - (R + R_c) j_2 = 0$$

Note that: $i_b = j_1$

$$\text{Hence: } R_e \cdot j_1 + R_e \cdot j_2 = V_x$$

$$-(R_e - \beta R) j_1 - (R_e + R + R_c) j_2 = 0$$

$$\text{Note that } R_{Th} = \frac{V_x}{j_1}$$

$$\text{From above equation: } j_2 = -j_1 + \frac{V_x}{R_e}$$

$$\text{and } -(R_e - \beta R) j_1 - (R_e + R + R_c) \left(-j_1 + \frac{V_x}{R_e}\right) = 0$$

$$j_1 \cdot (\beta R + R + R_c) = \frac{R_e + R + R_c}{R_e} \cdot V_x$$

Hence,

$$j_1 = \frac{R_e + R + R_c}{R_e(\beta R + R + R_c)} V_x$$

Ans

$$R_{th} = \frac{V_x}{j_1}$$

$$R_{th} = \frac{R_e(\beta R + R + R_c)}{R_e + R + R_c}$$

or:


$$R_{th} = R_e \cdot \frac{(1 + \beta)R + R_c}{R_e + R + R_c}$$

$$\beta \rightarrow 0: R_{th} = R_e \cdot \frac{R + R_c}{R_e + R + R_c}$$

From the circuit: R and R_c in series, and connected in parallel to R_e .

$$\beta \rightarrow 0, R \rightarrow \infty: R_{th} = R_e \quad (\text{the rest of the circuit is open!})$$

4

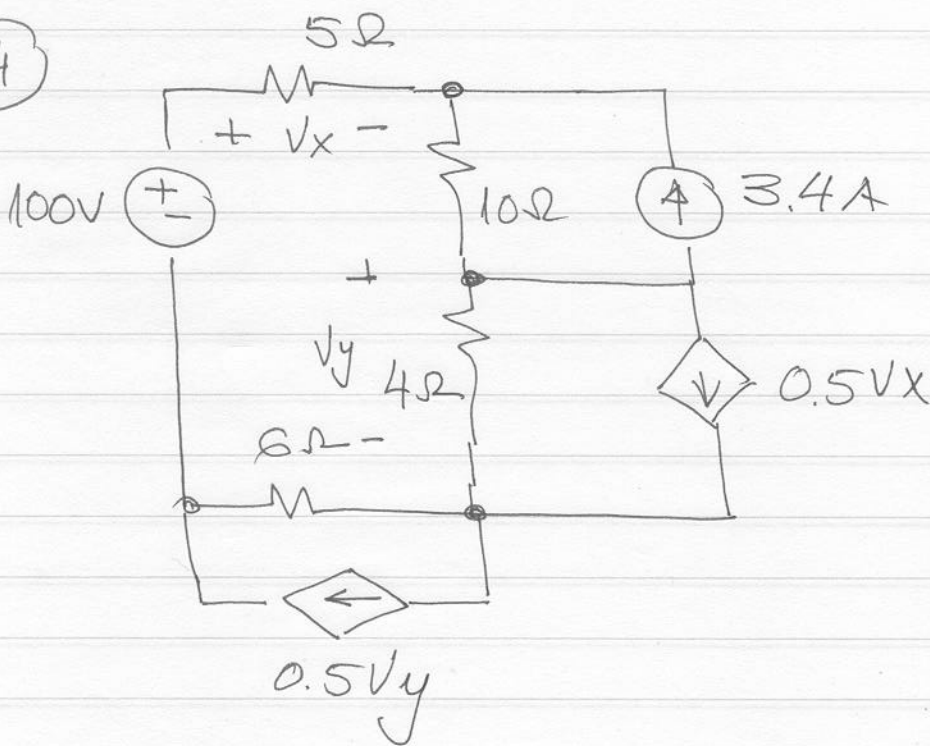

$n = 4$ nodes


$b = 4$ (generalized) branches

No. of independent node equations: $n - 1 = 3$

No. of mesh equations: $b - (n - 1) = \underline{1}$

Hence, mesh equations produce a smaller set of equations. (one equation):

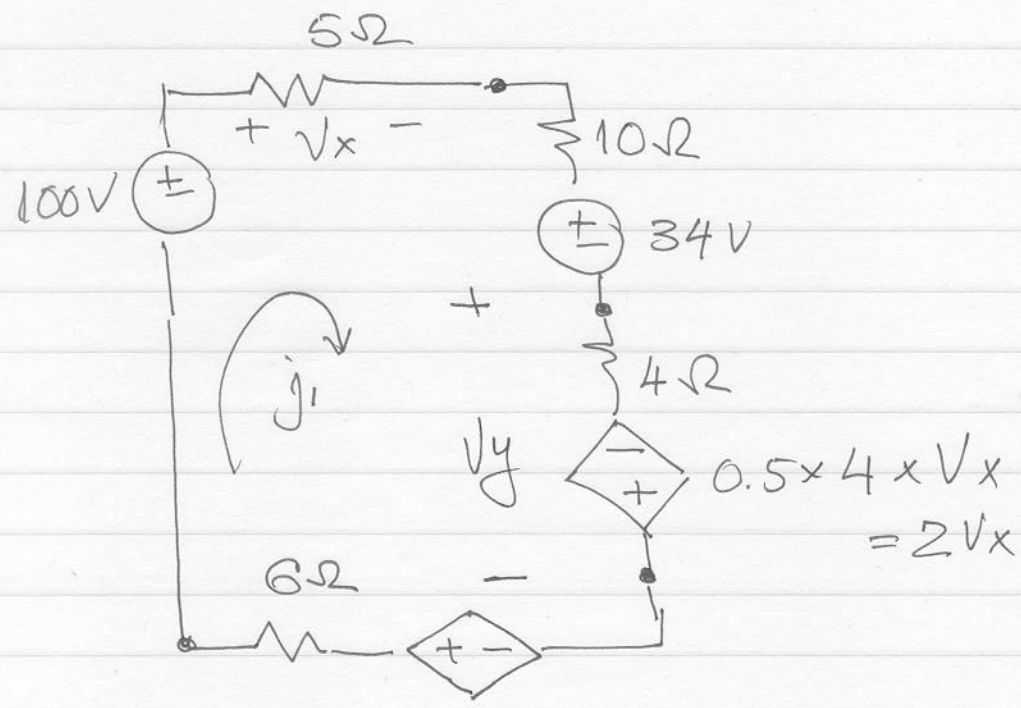Transform all current sources into voltage sources:



$$0.5 \cdot 6 \times V_y = 3V_y$$

$$100 - 5 \cdot j_1 - 10 \cdot j_1 - 34 - 4 \cdot j_1 + 2V_x + 3V_y - 6j = 0$$

Since $V_x = 5j_1$

$$\begin{aligned} V_y &= 4j_1 - 2V_x \\ &= 4j_1 - 2 \cdot (5j_1) \\ &= -6j_1 \end{aligned}$$

Hence: $66 - 25j_1 + 2 \cdot 5j_1 + 3 \cdot (-6j_1) = 0$

$j_1 = 2A$