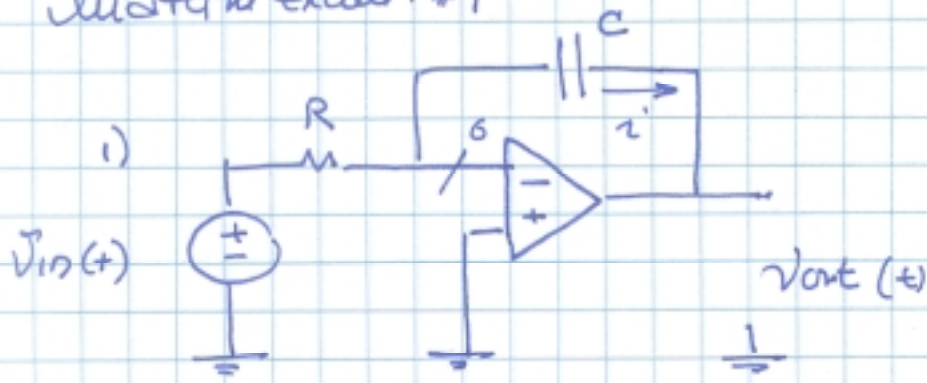


Matern exam: #1

1



$$v_{in} = R \cdot i$$

$$i = -C \cdot \frac{dv_{out}}{dt}$$

$$v_{in} = -RC \cdot \frac{dv_{out}}{dt}$$

$$v_{out} = -\frac{1}{RC} \int_0^t v_{in} dt$$

This is an integrator circuit

If $v_{in}(t) = \cos(250t)$

$$R = 4 \text{ k}\Omega$$


$$C = 1 \mu\text{F}$$

$$RC = 4 \times 10^{-3} \text{ s}$$

$$v_{out} = -\frac{1}{4 \times 10^{-3}} \int_0^t (\cos(250t)) dt$$

$$v_{out} = -\frac{1}{4 \times 10^{-3}} \cdot \frac{1}{250} \cdot \sin(250t)$$

$$v_{out} = -\sin(250t)$$

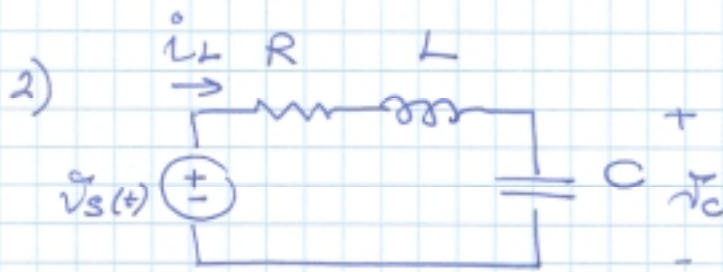

$$v_s = R i_L + L \frac{di_L}{dt} + v_C \quad \text{Notation: } v_s = v_s(t)$$

$$i_L = C \frac{dv_C}{dt} \quad (\text{Note: } i_C = i_L)$$

$$v_L = L \frac{di_L}{dt}$$

Hence:

$$R \cdot i_L + L \frac{di_L}{dt} + v_C = v_s$$

$$i_L = C \frac{dv_C}{dt}$$

And:

$$\frac{di_L}{dt} = -\frac{R}{L} \cdot i_L - \frac{1}{L} v_C + \frac{1}{L} v_s$$

$$\frac{dv_C}{dt} = \frac{1}{C} \cdot i_L$$

Matrix form:

$$\frac{d}{dt} \begin{pmatrix} i_L \\ v_C \end{pmatrix} = \begin{pmatrix} -R/L & -1/L \\ 1/C & 0 \end{pmatrix} \begin{pmatrix} i_L \\ v_C \end{pmatrix} + \begin{pmatrix} 1/L \\ 0 \end{pmatrix} v_s$$

Natural frequency:

$$\det(sI - A) = 0$$

$$\det \left[s \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} - \begin{pmatrix} -R/L & -1/L \\ 1/C & 0 \end{pmatrix} \right] = 0$$

$$\det \begin{pmatrix} s + R/L & 1/L \\ -1/C & s \end{pmatrix} = 0$$

$$s(s + R/L) + \frac{1}{LC} = 0$$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

$$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

Cases:

- 1. $s_1 \neq s_2$ and both real

$$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

- 2. $s_1 = s_2$, real and identical

$$\left(\frac{R}{2L}\right)^2 - \frac{1}{LC} = 0$$

i.e., $R = 2L/\sqrt{LC}$

$$R = 2\sqrt{\frac{L}{C}}$$

- 3. $s_1 \neq s_2$ and complex (conjugate)

$$s_{1/2} = -\frac{R}{2L} \pm j \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

Waveforms:


1. overdamped : $s_1 \neq s_2$ and real
2. critically damped : $s_1 = s_2$
3. underdamped : $s_1 \neq s_2$ and complex.
4. undamped

Special case: $R=0$

Ideal LC circuit with no resistance.

$$s_{1/2} = \pm j \frac{1}{\sqrt{LC}}$$

undamped sustained oscillations

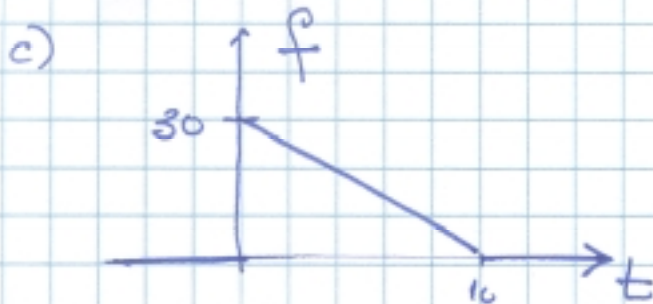


$$f(t) = -\frac{30}{10} \cdot t \cdot (u(t) - u(t-10))$$

$$f(t) = -3t u(t) + 3t u(t-10)$$

$$f(t) = -3t u(t) + 3(t-10) \cdot u(t-10) + 30 u(t-10)$$
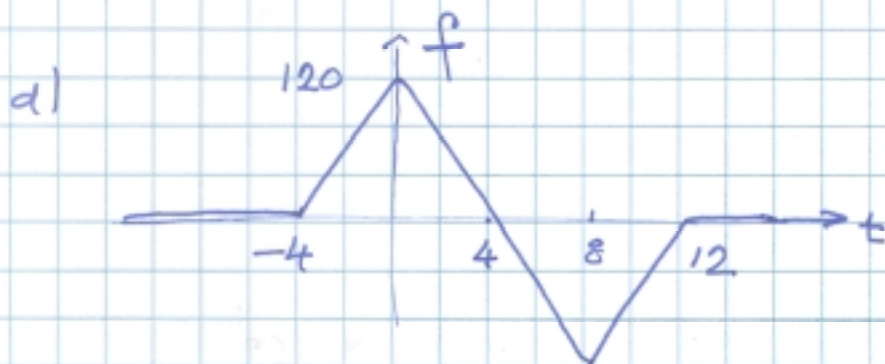
$$F(s) = -\frac{3}{s^2} + \frac{3}{s^2} e^{-10s} + \frac{30}{s} e^{-10s}$$



$$f(t) = 30(t+4) \cdot [u(t+4) - u(t)]$$

$$-30(t-4) [u(t) - u(t-8)]$$

$$+30(t-12) [u(t-8) - u(t-12)]$$

$$f(t) = 30(t+4)u(t+4) - 30(t+4)u(t)$$

$$-30(t-4)u(t) + 30(t-4)u(t-8)$$

$$+30(t-12)u(t-8) - 30(t-12)u(t-12)$$

6

$$f(t) = 30(t+4)u(t+4) - 30t u(t) - 120u(t) \\ - 30t u(t) + 120u(t) + 30(t-8)u(t-8) + 120u(t-8) \\ + 30(t-8)u(t-8) - 120u(t-8) - 30(t-12)u(t-12)$$

$$f(t) = 30(t+4)u(t+4) - 60t u(t) + \\ + 60(t-8)u(t-8) - 30(t-12)u(t-12)$$

$$F(s) = \frac{30}{s^2} e^{4s} - \frac{60}{s^2} + \frac{60}{s^2} e^{-8s} - \frac{30}{s^2} e^{-12s}$$

$$4. \quad a. \quad F(s) = \frac{3s+1}{(s+2)(s^2+4s+8)}$$

$$b. \quad F(s) = \frac{s(s+2)e^{-3s}}{(s+1)^2 \cdot (s+4)}$$

$$a) \quad F(s) = \frac{3s+1}{(s+2)(s^2+4s+8)}$$

$$= \frac{A}{s+2} + \frac{Bs+C}{s^2+4s+8}$$

$$A = \lim_{s \rightarrow -2} (s+2) \cdot F(s)$$

$$A = \lim_{s \rightarrow -2} \frac{3s+1}{s^2+4s+8}$$

$$A = \frac{-6+1}{4-8+8}$$

$$A = -\frac{5}{4}$$

Hence: $F(s) = -\frac{5}{4} \cdot \frac{1}{s+2} + \frac{Bs+C}{s^2+4s+8}$

Hence: $\frac{Bs+C}{s^2+4s+8} = \frac{3s+1}{(s+2)(s^2+4s+8)} + \frac{5}{4} \cdot \frac{1}{s+2}$

Note that

$$\begin{aligned} & \frac{3s+1}{(s+2)(s^2+4s+8)} + \frac{5}{4(s+2)} \\ &= \frac{4(3s+1) + 5 \cdot (s^2+4s+8)}{4(s+2)(s^2+4s+8)} \\ &= \frac{5s^2+32s+44}{4(s+2)(s^2+4s+8)} \\ &= \frac{5s(s+2) + 22(s+2)}{4(s+2)(s^2+4s+8)} \\ &= \frac{5s+22}{4(s^2+4s+8)} \\ &= \frac{5s+22}{4[(s+2)^2+4]} \\ &= \frac{5(s+2)}{4[(s+2)^2+4]} + \frac{12}{4[(s+2)^2+4]} \end{aligned}$$

$$F(s) = -\frac{5}{4(s+2)} + \frac{5(s+2)}{4[(s+2)^2+4]} + \frac{3}{(s+2)^2+4}$$

$$f(t) = \left\{ -\frac{5}{4} e^{-2t} + \frac{5}{4} \cos 2t e^{-2t} + \frac{3 \sin 2t}{2} e^{-2t} \right\} u(t)$$

$$f(t) = \frac{1}{4} \left\{ -5 + 5 \cos 2t + 6 \sin 2t \right\} e^{-2t} u(t)$$