

SIMON FRASER UNIVERSITY
SCHOOL OF ENGINEERING SCIENCE

Summer 2007
ENSC 320: ELECTRIC CIRCUITS II

Midterm Examination No. 2

July 11, 2007

*Duration: 50 minutes. Attempt all three problems. Questions are **not** equally weighted.
Closed book and closed notes. Calculators, PDAs, laptops, and wireless phones are not
permitted.*

1. (30 points) For the ideal op amp circuit shown in Fig. 1:

- Find the transfer function in terms of R_1 , R_2 , and C .
- If it is desired to obtain

$$H(s) = \frac{s + 4}{s + 2}$$

with $C = 1 \mu F$, then find R_1 and R_2 .

- Find the circuit's step response.

2. (50 points) Consider the circuits shown in Fig. 2, where $R_1 = 50 \Omega$, $R_2 = 200 \Omega$ and $C = 2.5 mF$.

- Find its transfer function.
- Let $v_{in}(t) = 10e^{-2t}u(t) V$ and $v_c(0_-) = 4 V$.
 - Find the zero-state response, the zero-input response, and the complete response
 - Find the forced response and the natural response.
 - Find the steady-state response and the transient response.
- If $v_{in}(t) = 10e^{-10t}u(t) V$ and $v_c(0) = 0 V$, is the forced response well defined. Justify your answer.

3. (20 points) Consider the circuits shown in Fig. 3, where $R = 0.25 \Omega$ and $C = 1 F$.

- Find the transfer function $H(s)$ and the impulse response $h(t)$.
- If $i_{in}(t) = 3e^{-t}u(t) A$, find $v_c(t)$ using the convolution integral.

Figure 1:

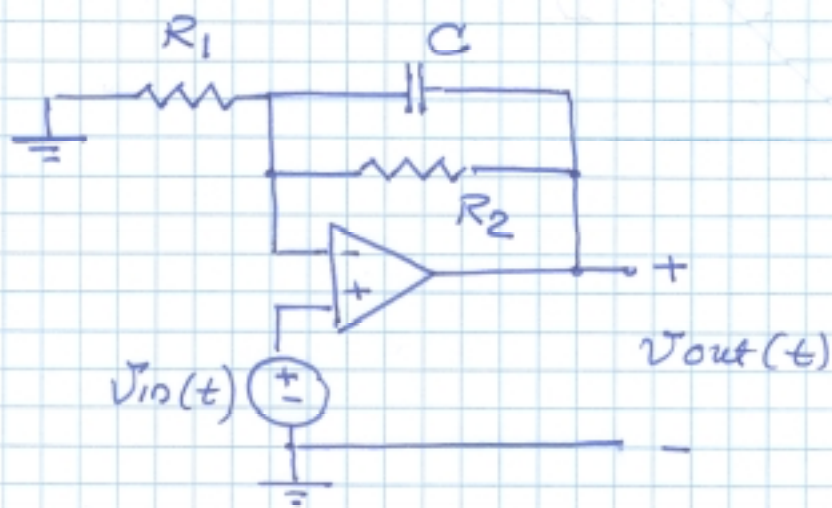


Figure 2:

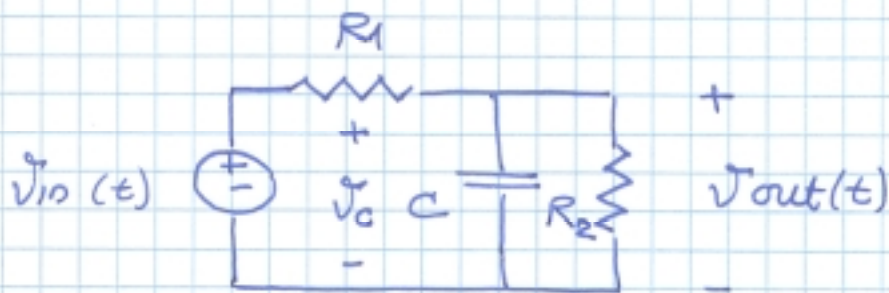


Figure 3:

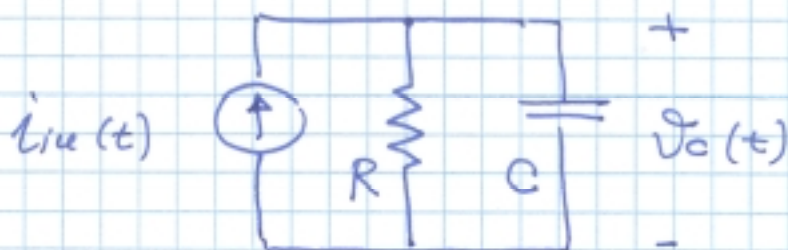


TABLE 13.1 Laplace Transform Pairs

Item number	$f(t)$	$\mathcal{L}[f(t)] = F(s)$
1	$K\delta(t)$	K
2	$Ku(t)$ or K	$\frac{K}{s}$
3	t	$\frac{1}{s^2}$
4	$t^n u(t)$	$\frac{n!}{s^{n+1}}$
5	$e^{-at} u(t)$	$\frac{1}{s+a}$
6	$te^{-at} u(t)$	$\frac{1}{(s+a)^2}$
7	$t^n e^{-at} u(t)$	$\frac{n!}{(s+a)^{n+1}}$
8	$\sin(\omega t) u(t)$	$\frac{\omega}{s^2 + \omega^2}$
9	$\cos(\omega t) u(t)$	$\frac{s}{s^2 + \omega^2}$
10	$e^{-at} \sin(\omega t) u(t)$	$\frac{\omega}{(s+a)^2 + \omega^2}$
11	$e^{-at} \cos(\omega t) u(t)$	$\frac{s+a}{(s+a)^2 + \omega^2}$
12	$t \sin(\omega t) u(t)$	$\frac{2\omega s}{(s^2 + \omega^2)^2}$
13	$t \cos(\omega t) u(t)$	$\frac{s^2 - \omega^2}{(s^2 + \omega^2)^2}$
14	$\sin(\omega t + \phi) u(t)$	$\frac{s \sin(\phi) + \omega \cos(\phi)}{s^2 + \omega^2}$
15	$\cos(\omega t + \phi) u(t)$	$\frac{s \cos(\phi) - \omega \sin(\phi)}{s^2 + \omega^2}$
16	$e^{-at} [\sin(\omega t) - \omega t \cos(\omega t)] u(t)$	$\frac{2\omega^3}{[(s+a)^2 + \omega^2]^2}$
17	$te^{-at} \sin(\omega t) u(t)$	$2\omega \frac{s+a}{[(s+a)^2 + \omega^2]^2}$
18	$e^{-at} \left[C_1 \cos(\omega t) + \left(\frac{C_2 - C_1 a}{\omega} \right) \sin(\omega t) \right] u(t)$	$\frac{C_1 s + C_2}{(s+a)^2 + \omega^2}$
19	$2\sqrt{A^2 + B^2} e^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right]$	$\frac{A + jB}{s+a+j\omega} + \frac{A - jB}{s+a-j\omega}$
20	$2\sqrt{A^2 + B^2} te^{-at} \cos \left[\omega t - \tan^{-1} \left(\frac{B}{A} \right) \right]$	$\frac{A + jB}{(s+a+j\omega)^2} + \frac{A - jB}{(s+a-j\omega)^2}$