

Digital System Design

by

Dr. Lesley Shannon

Email: Ishannon@ensc.sfu.ca

Course Website: <http://www.ensc.sfu.ca/~Ishannon/courses/ensc350>



Simon Fraser University

Slide Set: 11


Date: March 9, 2009

Slide Set Overview

- Datapath Circuits
 - Large digital systems are more than state machines and combinational logic. Generally these systems can be divided into two parts:
 - Control
 - Datapath
 - We'll use examples to understand how to do this:
 - There is no real “recipe” for designing these things, but with experience, you get to be good at it.


Real Systems

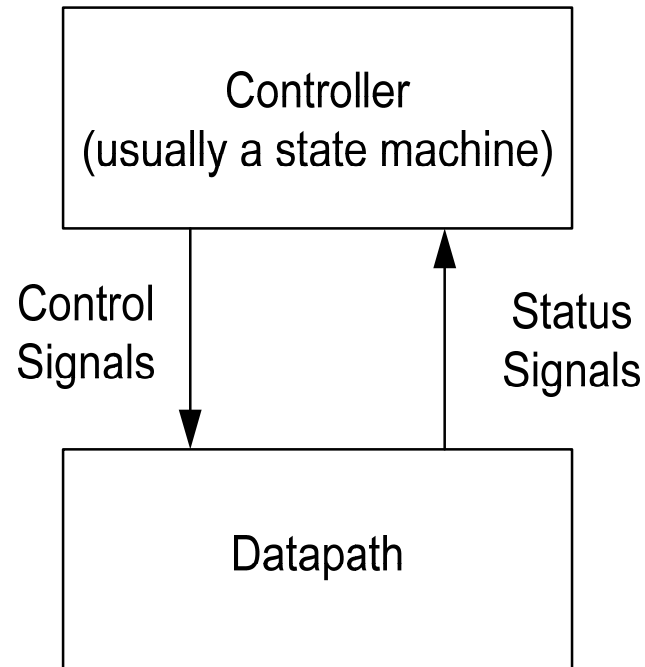- All but the simplest systems have two parts:




Exponent

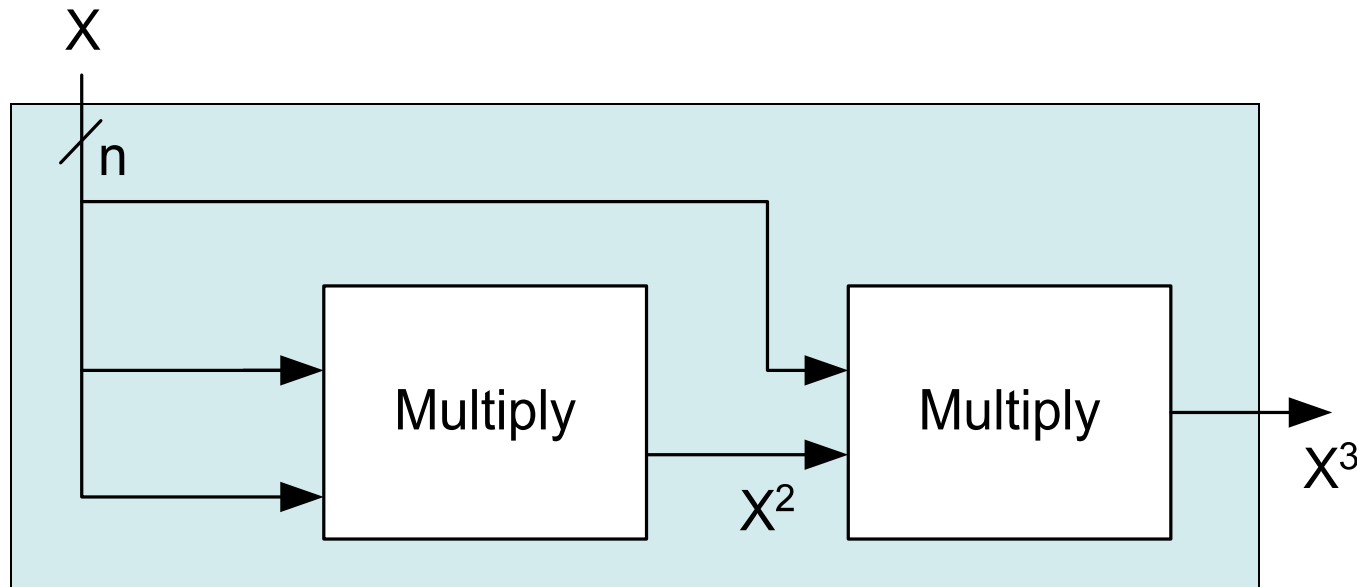- Suppose we want to build a circuit to calculate X^3
 - X is an n -bit input, and assume that the result also fits in n -bits for now
 - This is a relatively simple circuit



Exponent: A bit more complicated

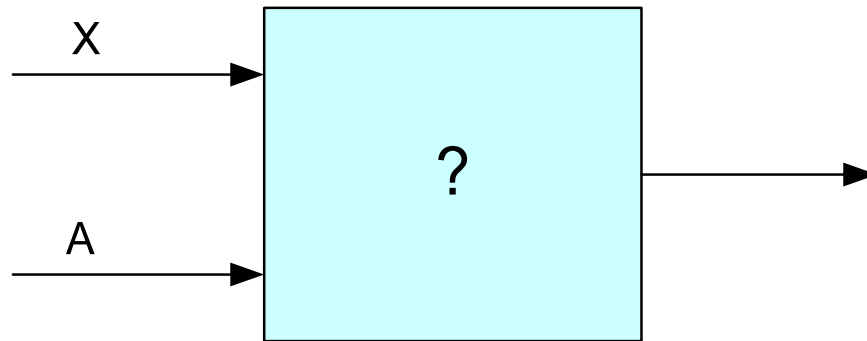- What if we want to compute X^A where X and A are both inputs?



- If A was fixed, we could figure out how many multipliers we need (as in the previous example)
- But, during the operation of this circuit, suppose A can change. How do we know how many hardware units to put down?

Exponent: A bit more complicated

The algorithm to be implemented in this block:

```
P = 1; CNT = A;  
while (CNT > 0) do  
    P = P * X;  
    CNT = CNT - 1;  
end while;
```


Note 1: this isn't VHDL or C, it just is pseudo-code to illustrate the algorithm.

Note 2: We could write this in VHDL, but it would **not** be **synthesizable**. So, we have to design it using smaller processes (each one synthesizable)

Rule that has never mattered before: **A synthesizable process can only describe what happens in one clock cycle.** This would take more than one clock cycle. So, it would not be synthesizable

Exponent: A bit more complicated


Consider this simple datapath

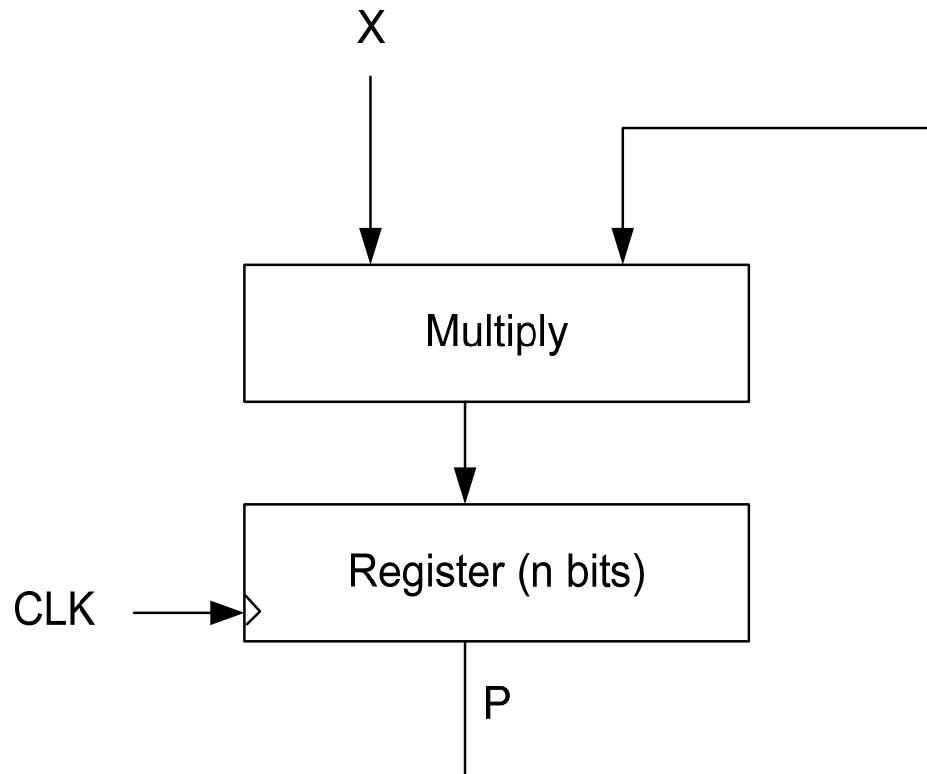

If we let this run for $A+1$ clock cycles, we will produce the desired result.



This will work for any value of A

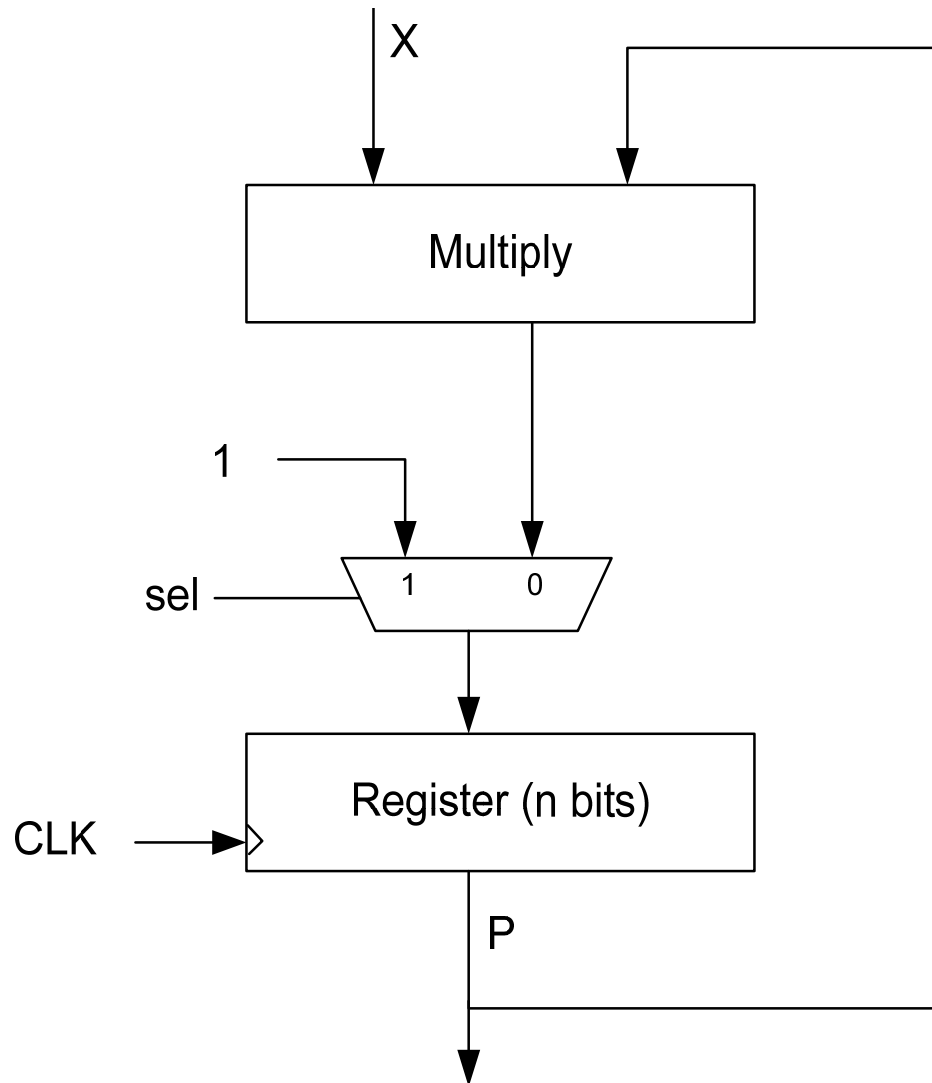Need a way to initialize P to 1 at the start:




First cycle, set sel to 1, and this will initialize P to 1

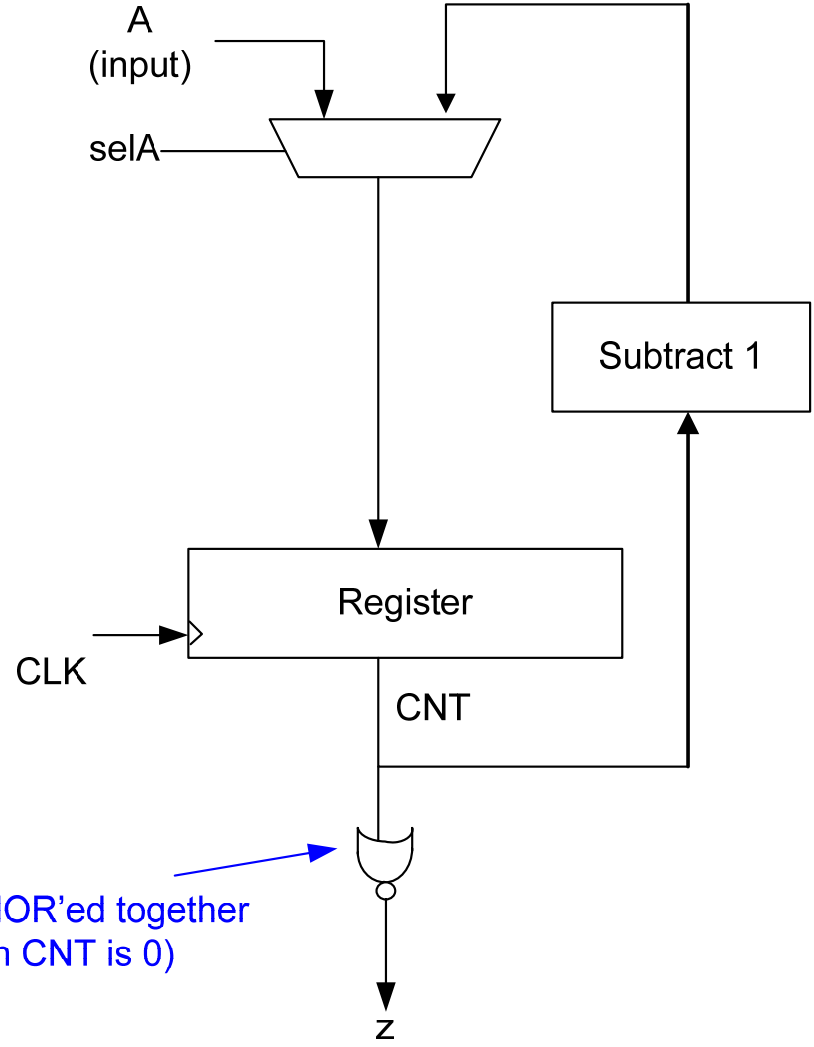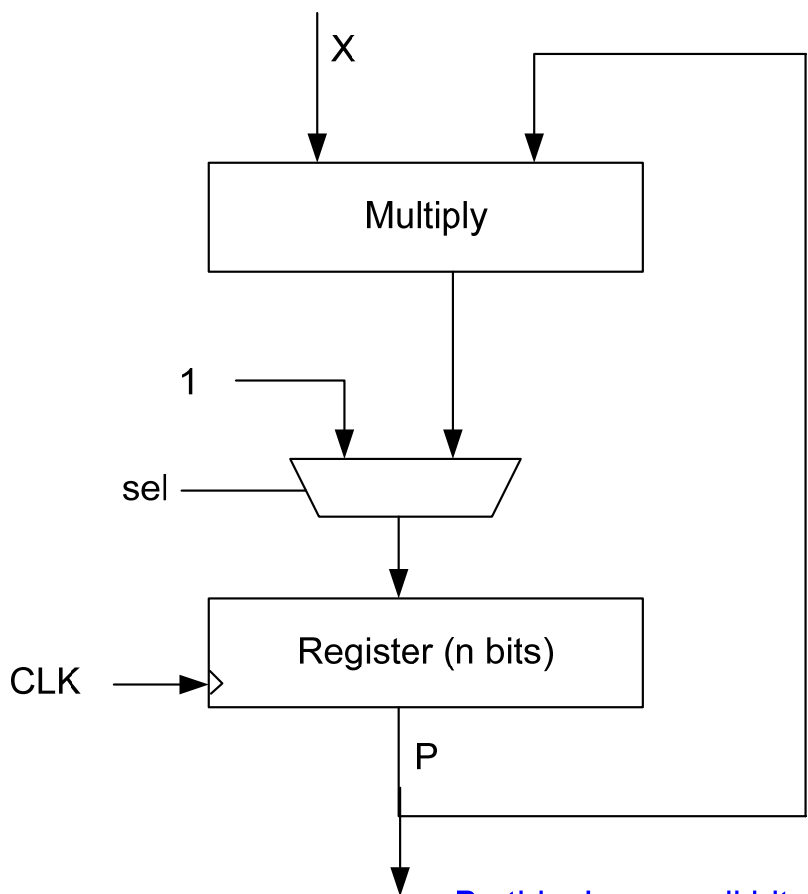We have to let this run for A cycles. We need some sort of counter to keep track of this.



By this, I mean all bits are NOR'ed together
(this produces a 1 when CNT is 0)

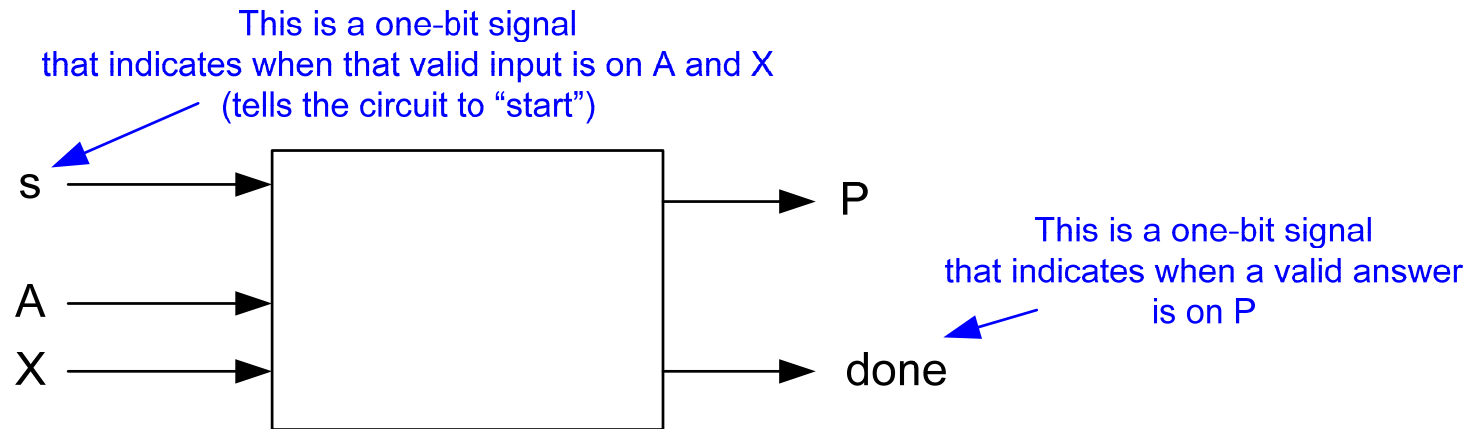But we are not there yet. What we really want is:



So to implement this, we need a controller that:


when **s** goes high:

set **sel** and **selA** to 1 for one cycle


wait until **z** goes high

when it does, assert **done**, and go back to the start

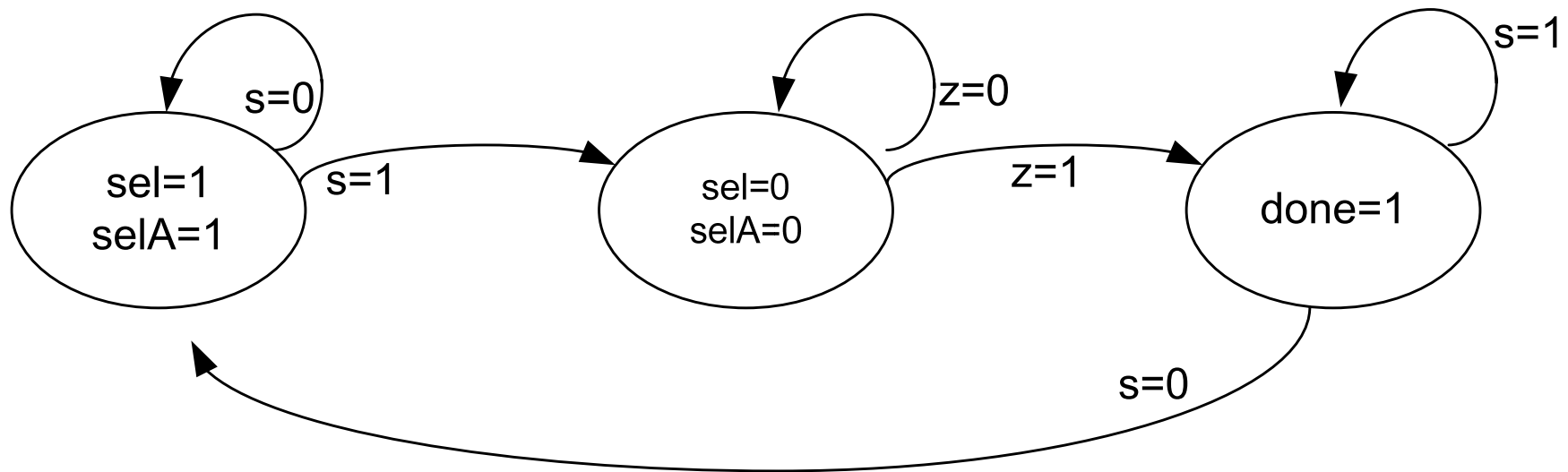- Here is a simple controller that does that:



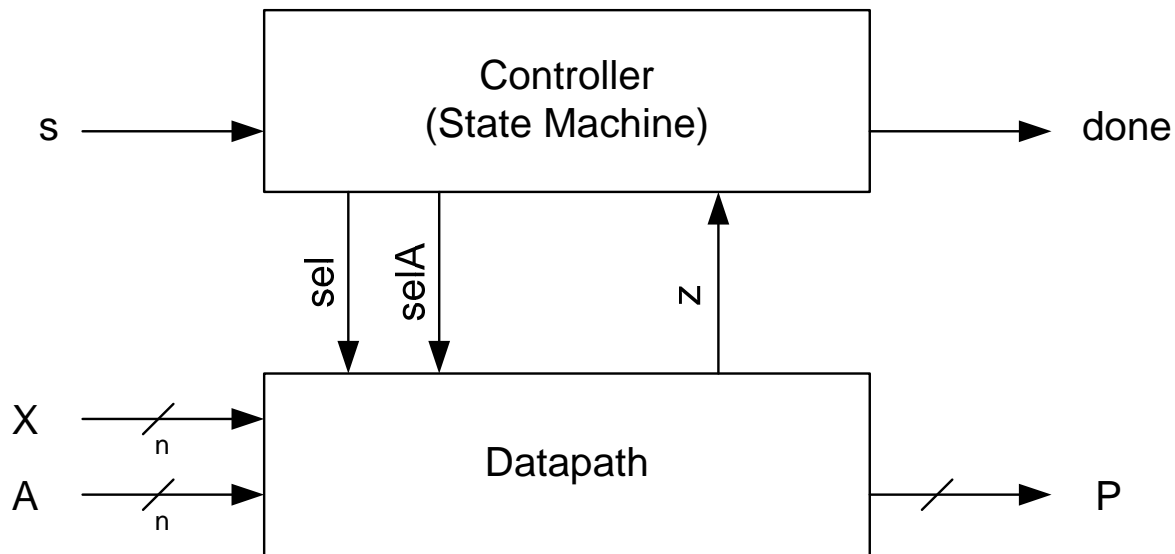- Now combine the state machine and the datapath into one circuit:



```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;
```

entity top is

```
    port(A, X : in std_logic_vector(7 downto 0);  
          s, clk : in std_logic;  
          P : out std_logic_vector(7 downto 0);  
          done : out std_logic);
```

end top ;

architecture behavioural of top is

```
signal curr_state: std_logic_vector(1 downto 0) := "00";  
signal z, sel, selA : std_logic;  
signal P_int: std_logic_vector(7 downto 0);  
signal cnt: std_logic_vector(7 downto 0);
```

....

```

begin
  -- Datapath

  process(clk)
  variable tmp_mul_result : std_logic_vector(15 downto 0);
  begin
    if (clk = '1') then
      if (sel = '1') then
        P_int <= "00000001";
      else
        tmp_mul_result := X * P_int;
        P_int <= tmp_mul_result(7 downto 0);
      end if;
    end if;
  end process;
  P <= P_int;

```

--NOTE THIS STILL ISN'T SYNTHESIZABLE BECAUSE MULTIPLICATION IS NOT SYNTHESIZABLE (BUT YOU CAN SIMULATE IT)

.....

```
process(clk)
begin
  if (clk = '1') then
    if (selA = '1') then
      cnt <= A;
    else
      cnt <= cnt - 1;
    end if;
  end if;
end process;
```

```
process(cnt)
begin
  if (cnt = "00000000") then
    z <= '1';
  else
    z <= '0';
  end if;
end process;
```

-- Controller

```
process(clk)
begin
  if (clk = '1') then
    case curr_state is
      when "00" =>
        if (s = '0') then
          curr_state <= "00";
        else
          curr_state <= "01";
        end if;
      when "01" =>
        if (z = '0') then
          curr_state <= "01";
        else
          curr_state <= "10";
        end if;
      when others =>
        if (s = '0') then
          curr_state <= "00";
        else
          curr_state <= "10";
        end if;
    end case;
  end if;
end process;
```

```
process(curr_state)
begin
  case curr_state is
    when "00" =>
      sel <= '1'; selA <= '1'; done <= '0';
    when "01" =>
      sel <= '0'; selA <= '0'; done <= '0';
    when others =>
      sel <= '0'; selA <= '0'; done <= '1';
  end case;
end process;
end behavioural;
```

Consider simulating this description to see the circuit's behaviour in Altera's waveform viewer.

Serial Multiplier

How do you implement a multiplier (multiply two numbers)

Decimal

$$\begin{array}{r} 13 \\ \times 11 \\ \hline 13 \\ 13 \\ \hline 143 \end{array}$$

Binary

$$\begin{array}{r} 1101 \\ \times 1011 \\ \hline 1101 \\ 1101 \\ 0000 \\ 1101 \\ \hline 10001111 \end{array}$$

Serial Multiplier Algorithm


Inputs A and B, Output P:

```
  1 1 0 1
x 1 0 1 1
-----
  1 1 0 1
 1 1 0 1
 0 0 0 0
 1 1 0 1
-----
1 0 0 0 1 1 1 1
```


```
P=0
for (i=0 to n-1)
  if (B(i) = 1) then
    P = P + A
  end if;
  left shift A
end for;
```

As before, we could implement this psuedo-code using VHDL. But, it would not be synthesizable. So, we have to break it into smaller processes (a.k.a. design the hardware)


Top level diagram of what we will build:

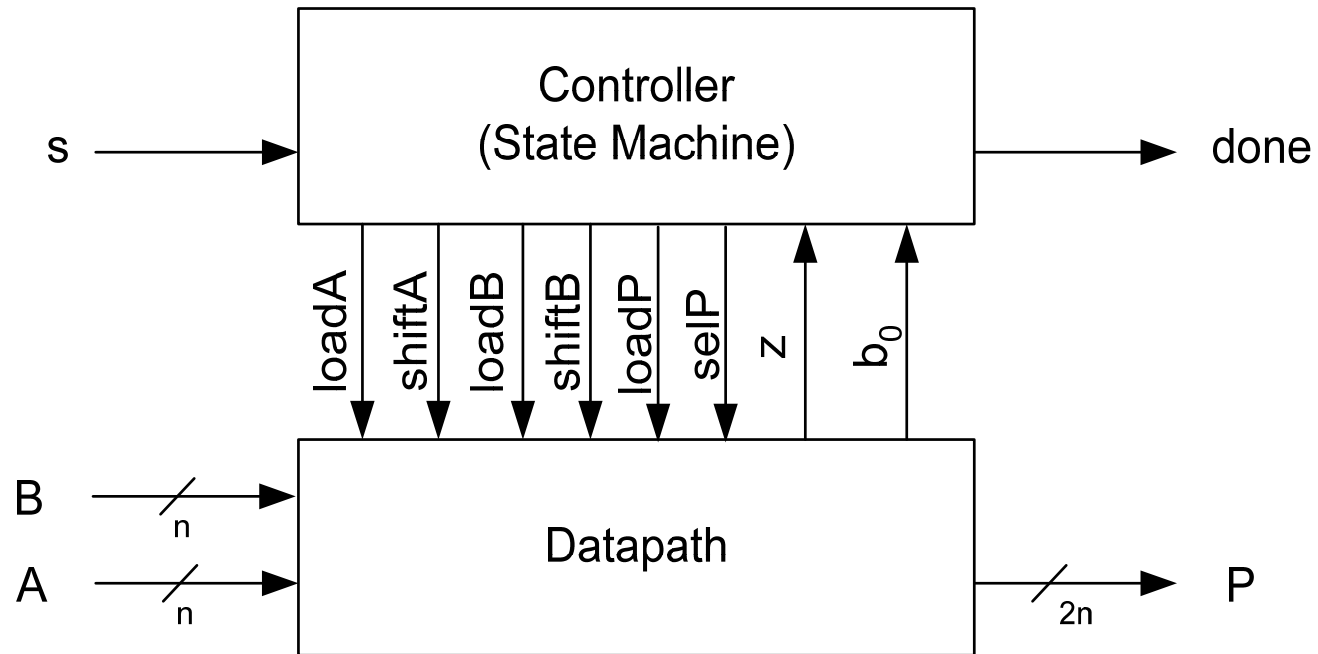

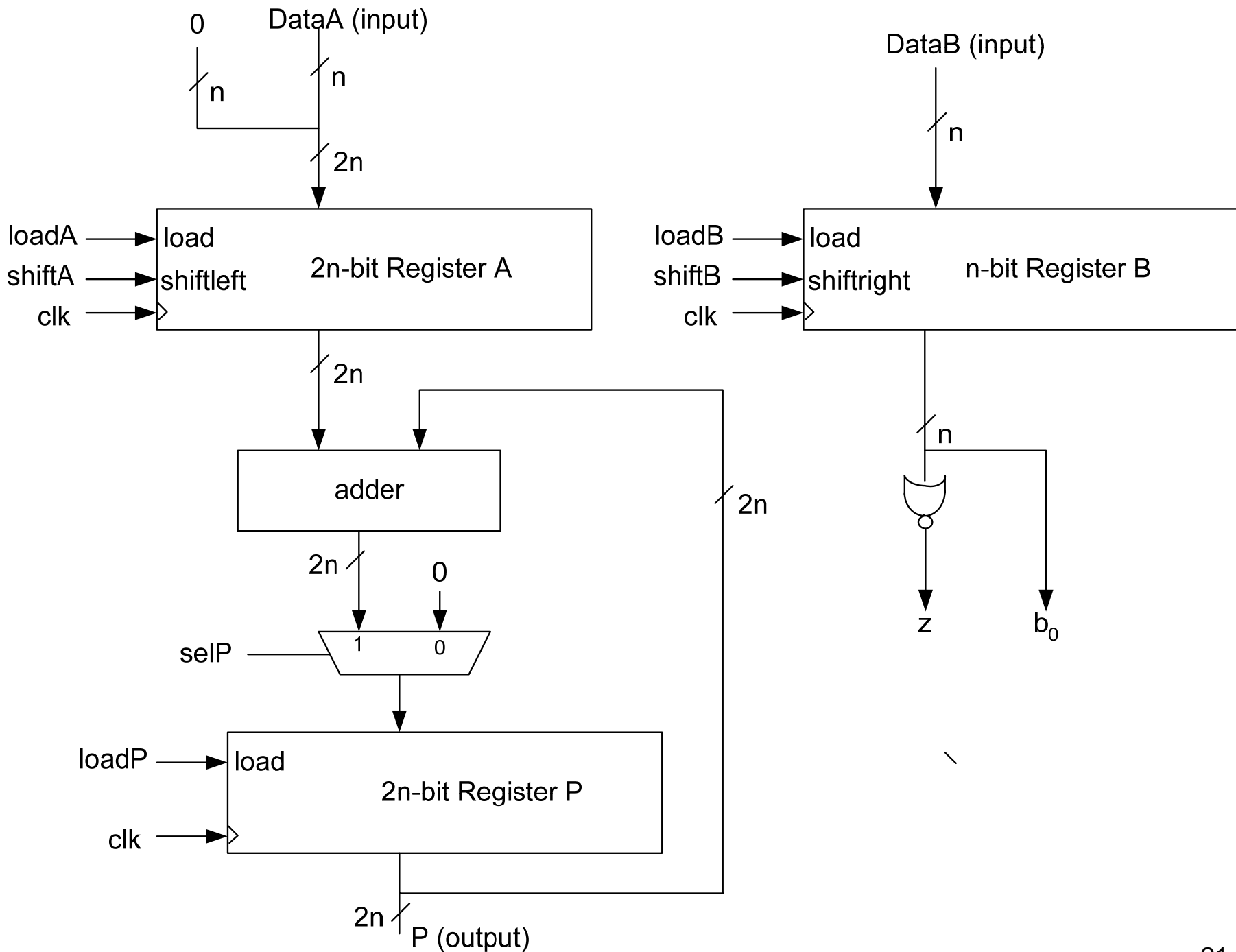When s goes high, a new n -bit values available on A and B . The machine then multiplies, and when it is finished, asserts **done** and puts the result on P .



- State Machine:

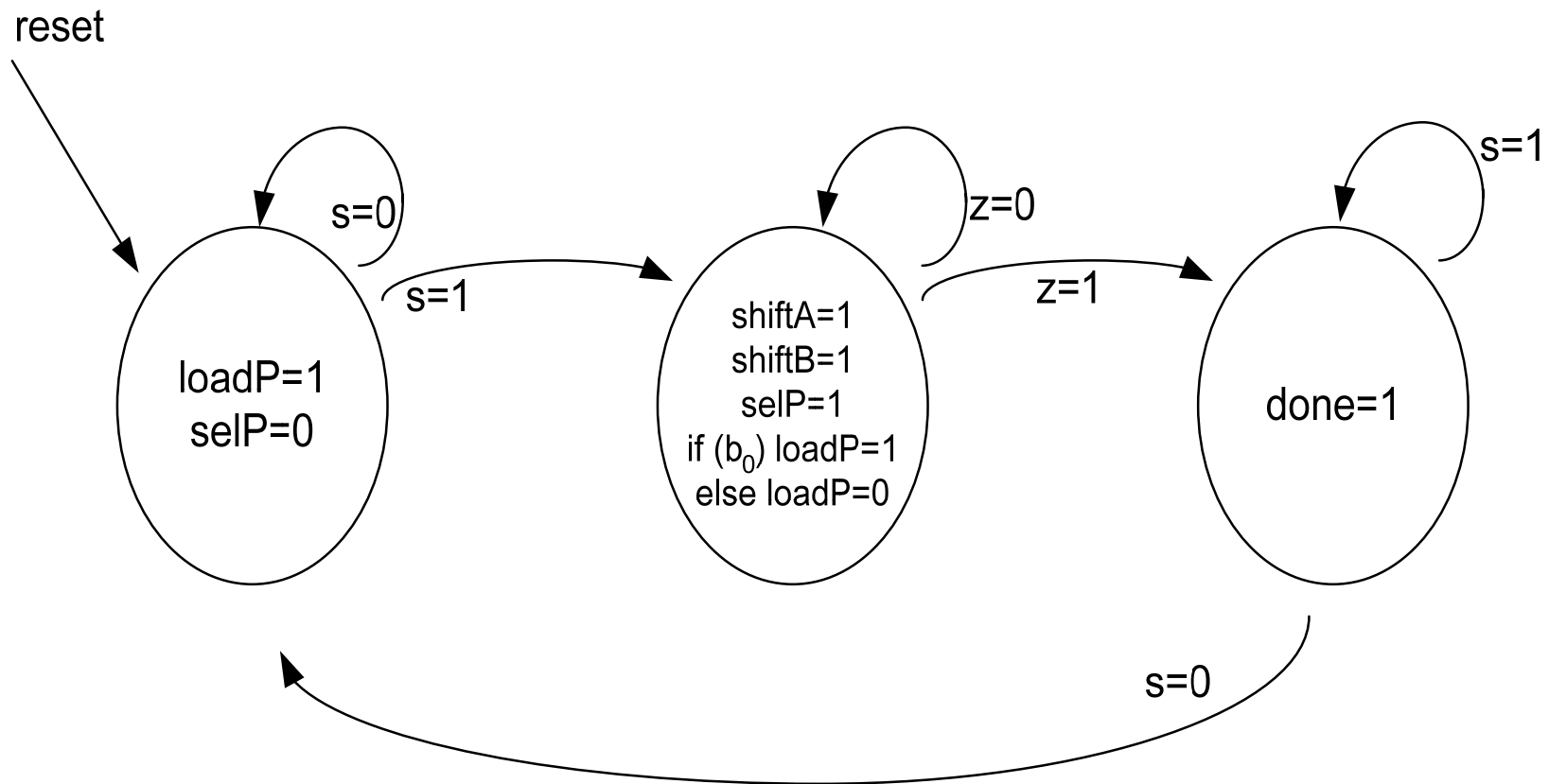

Together, the state machine and datapath implement the serial multiply. The state machine is a Mealy Machine, so you would need two processes to describe it. The datapath can be described using simple components.

Bit Counting Circuit



Suppose we want to count the number of '1's in a word.


Algorithm to do this:

```
B=0  
while (A ≠ 0) do  
  if (a0 = 1) then  
    B = B + 1  
  end if  
  Right shift A  
end while
```

Note 1: this isn't VHDL or C, it just is pseudo-code to illustrate the algorithm.


Note 2: We could write this in VHDL, but it would not be synthesizable. So, we have to design it using smaller processes (each one synthesizable)

Top level diagram of what we will build:

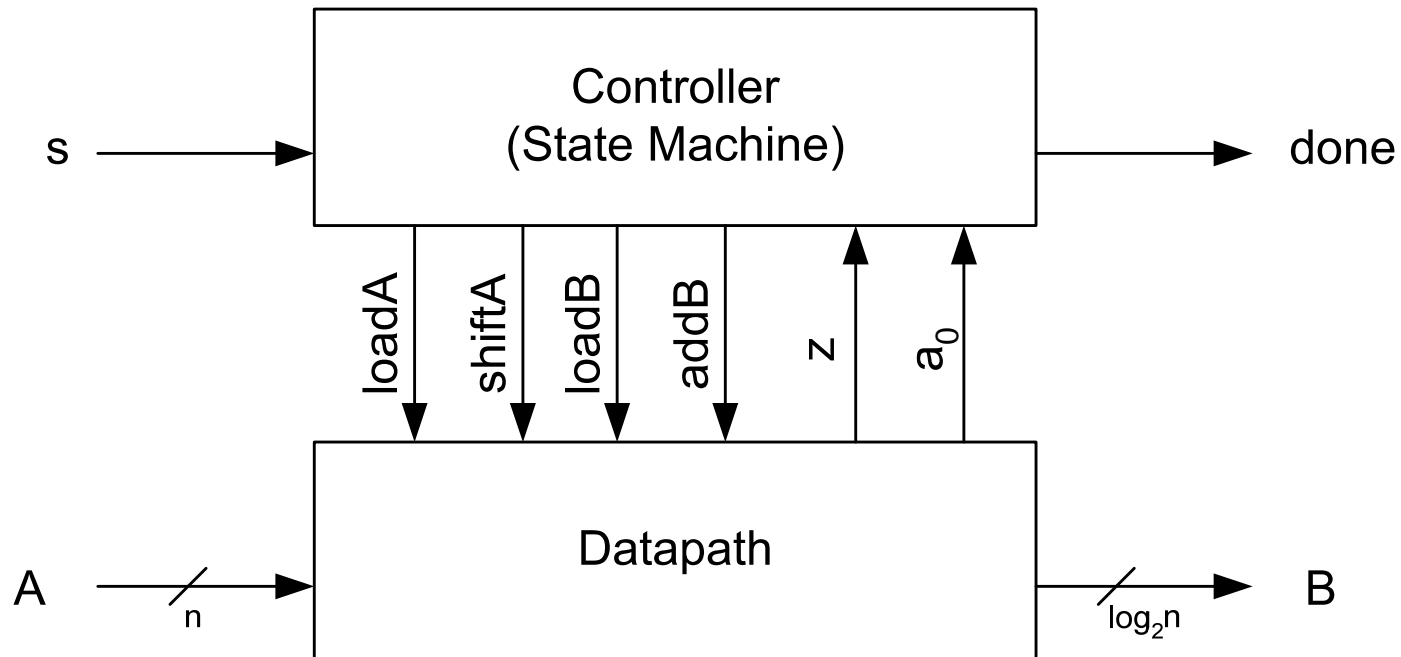


When s goes high, a new n -bit value is available on A . The machine then counts the bits, and when it is finished, asserts **done** and puts the result on B .

Datapath:

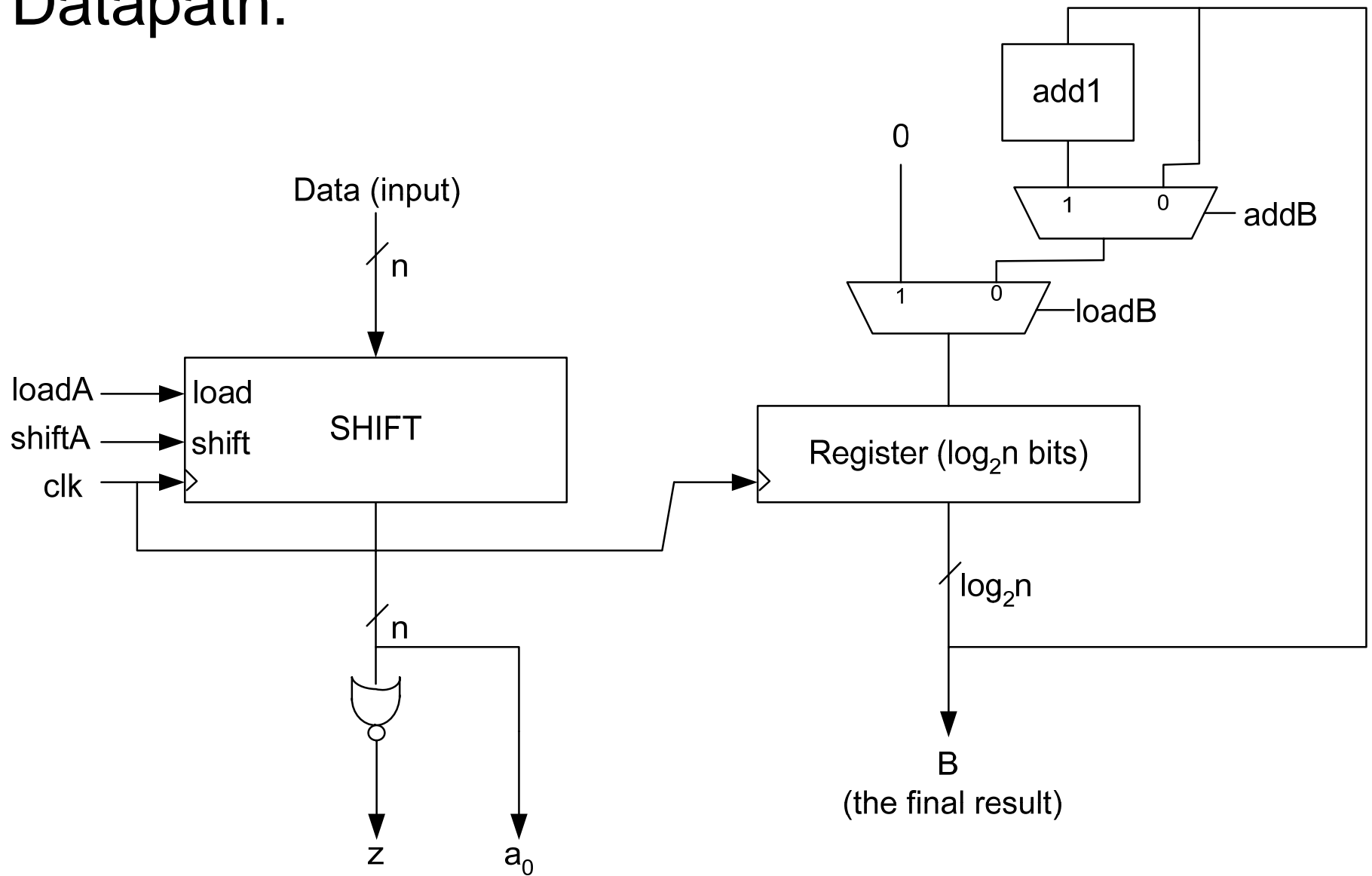

- State Machine:

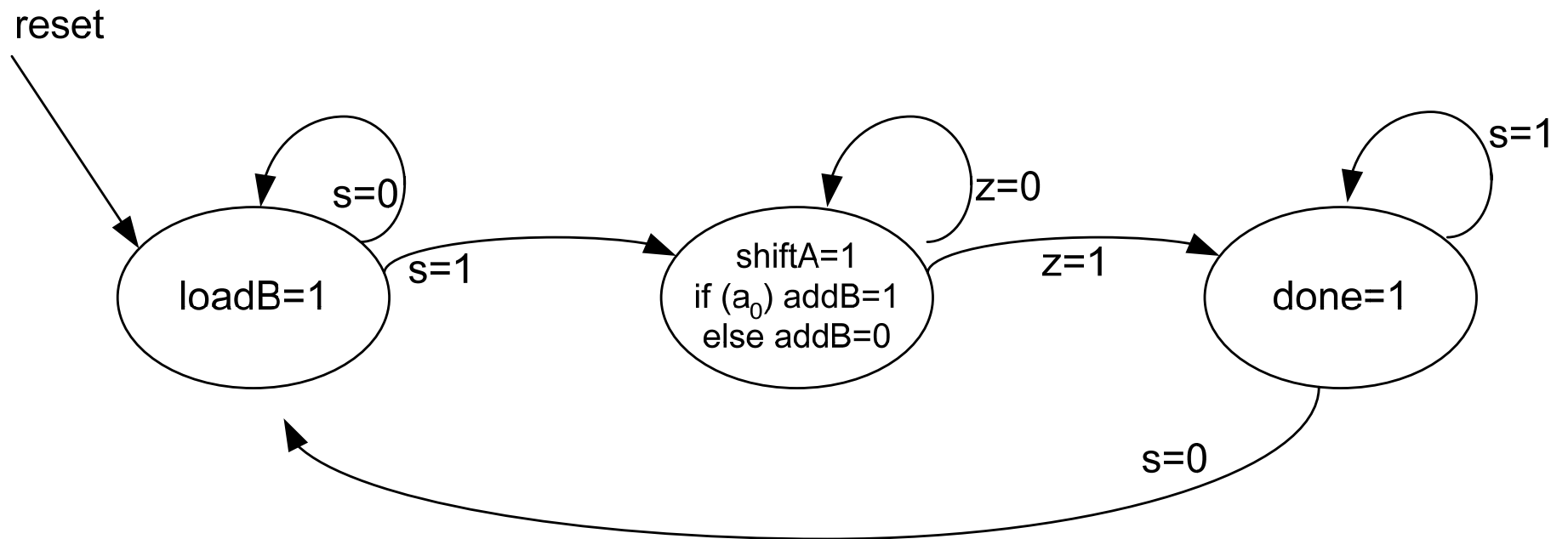

Together, the state machine and datapath implement the bit-counting operation. The state machine is a Mealy Machine, so you would need two processes to describe it. The datapath can be described using simple components.

For practice you can try writing the HDL from this description

How would you design a divider?

Start

1. Load in the divisor into the 8-bit Divisor register and the dividend into the 16-bit Remainder register. Shift the remainder left by 1 bit.


2. Subtract the Divisor register from the left half of the Remainder register, and place the result in the left half of the Remainder register


Remainder ≥ 0

Test Remainder


Remainder < 0


3b. Restore the original value by adding

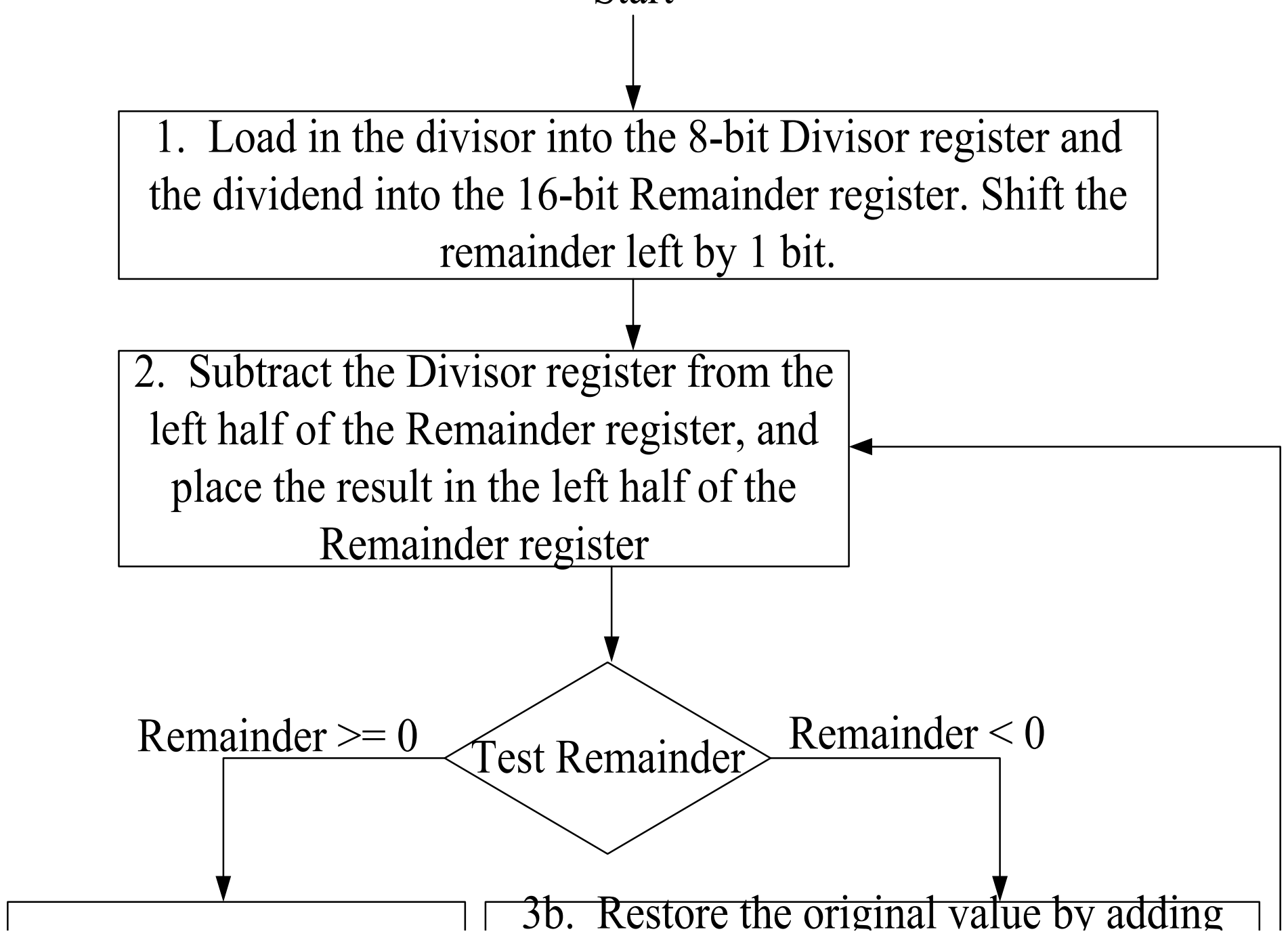


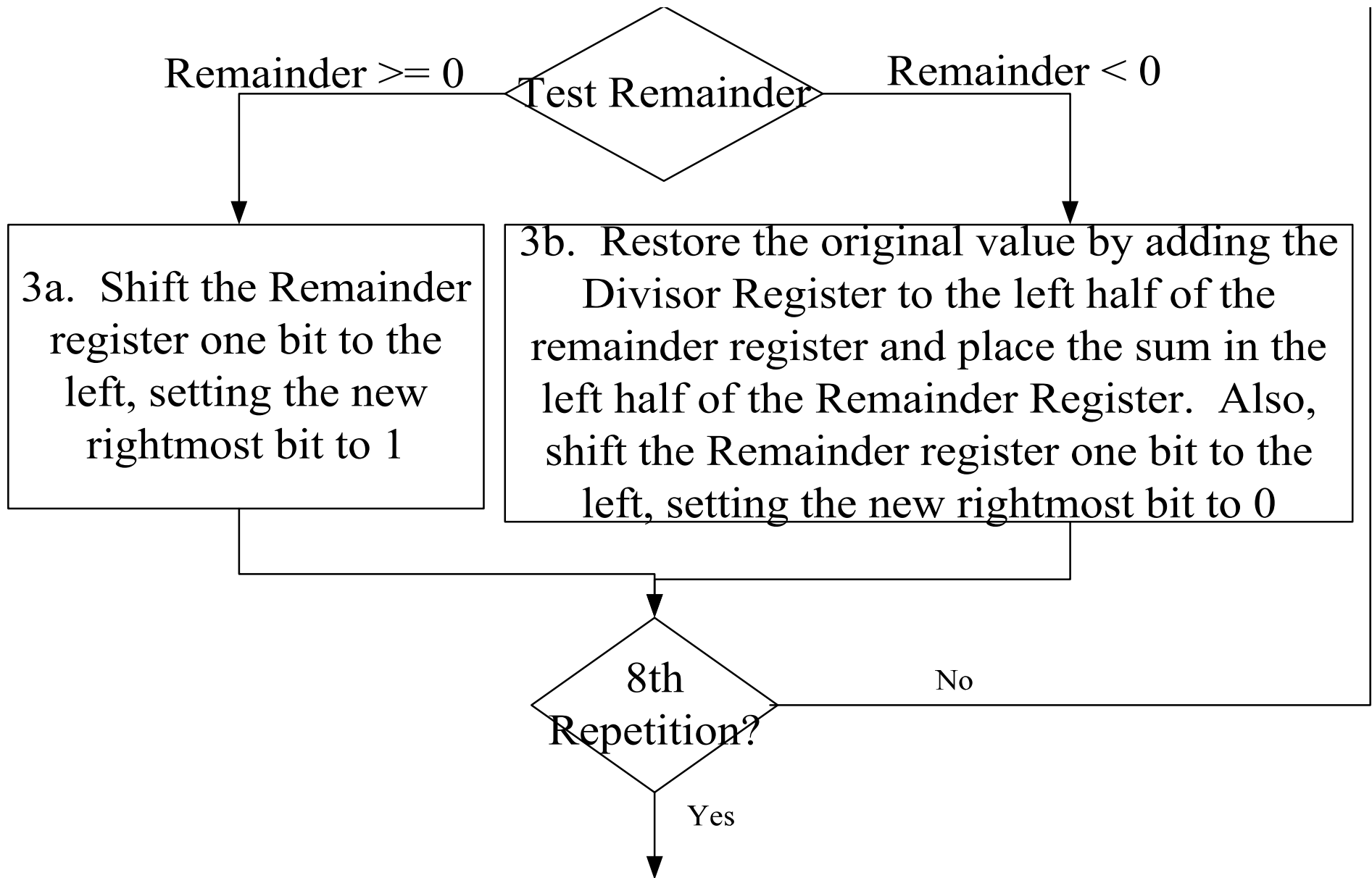

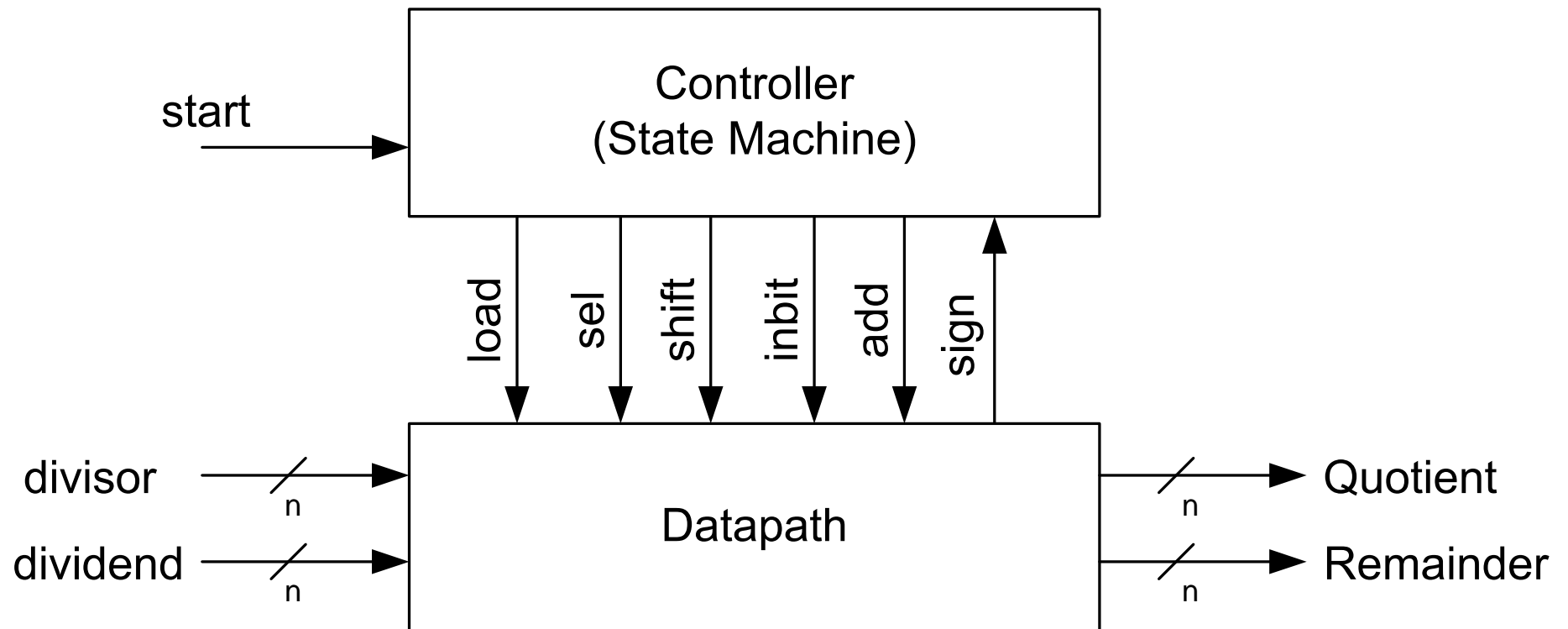Done. Quotient is in bits (7:0) of Remainder Register and
 Remainder is in bits (15:9) of Remainder Register
 (note that bit 8 is ignored)




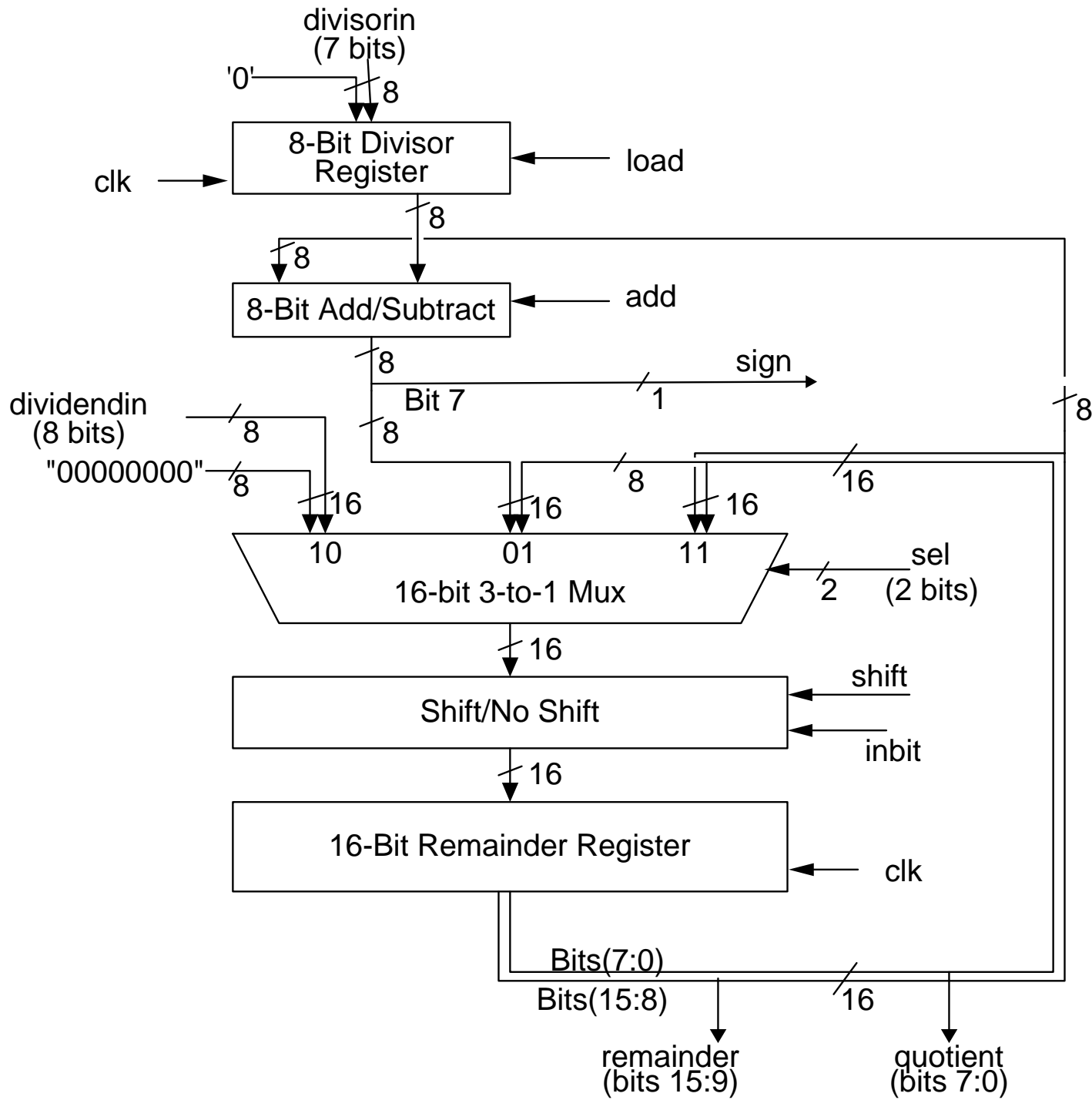


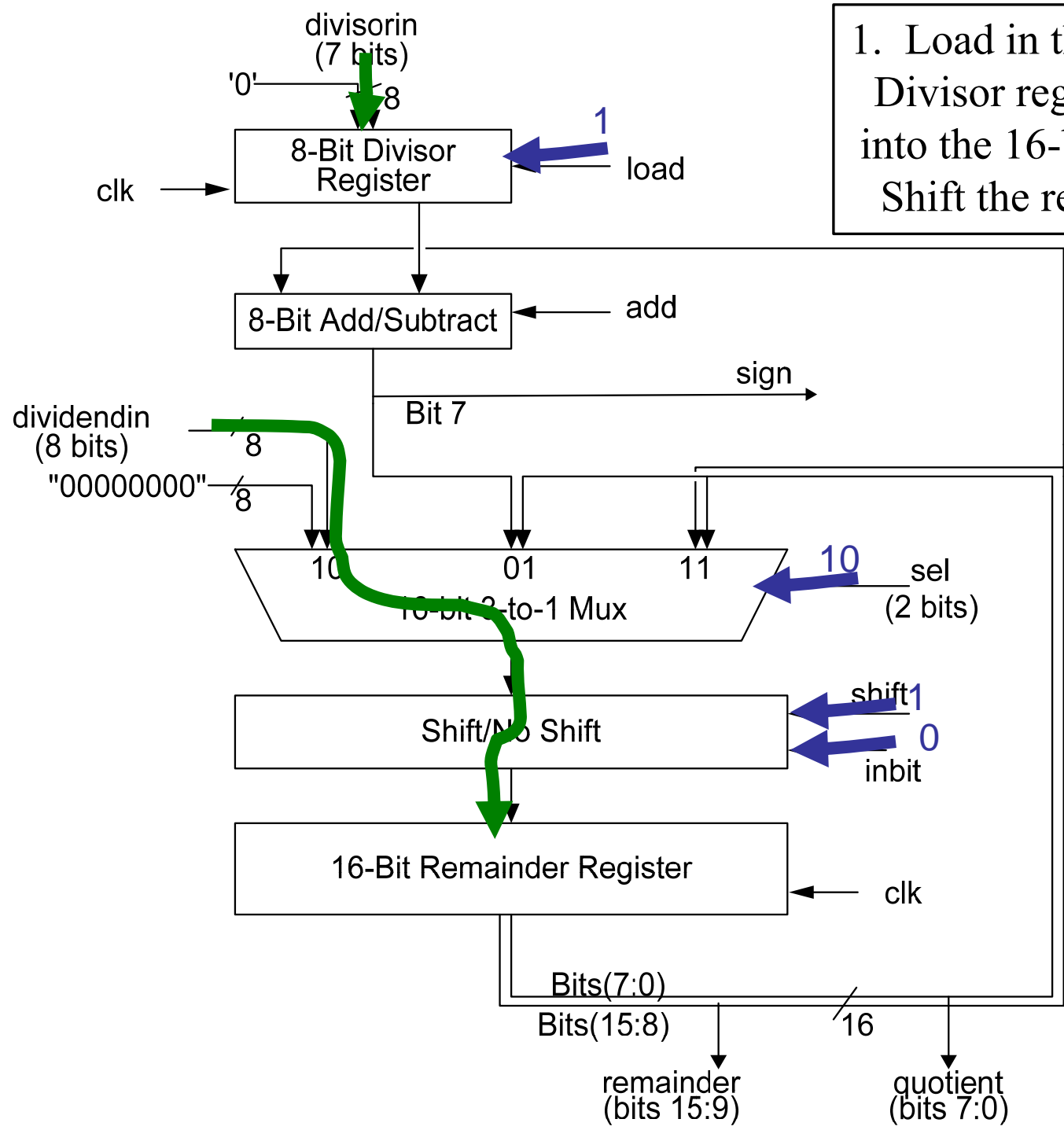



1. Load in the divisor into the 8-bit Divisor register and the dividend into the 16-bit Remainder register. Shift the remainder left by 1 bit.

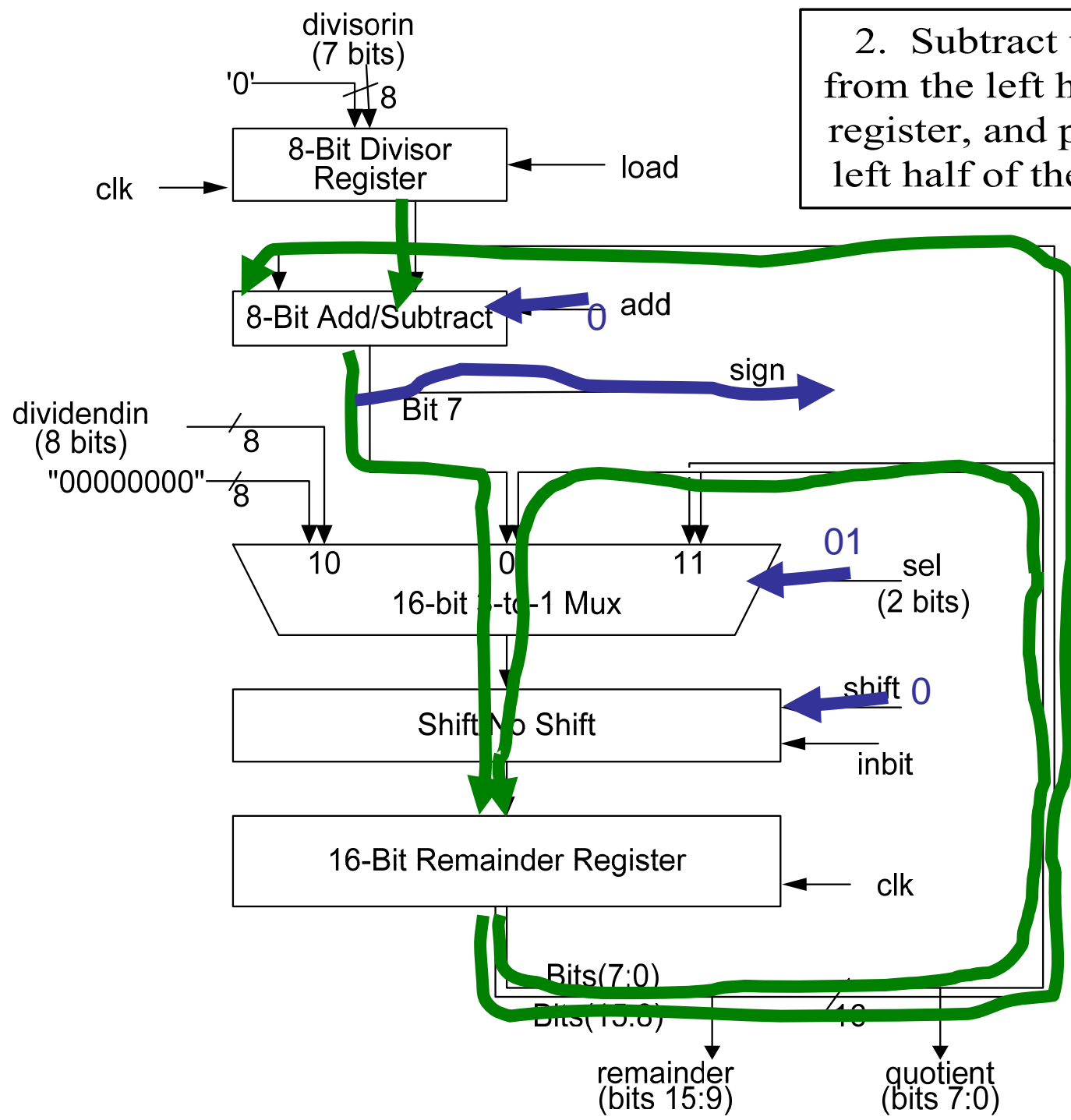2. Subtract the Divisor register from the left half of the Remainder register, and place the result in the left half of the Remainder register



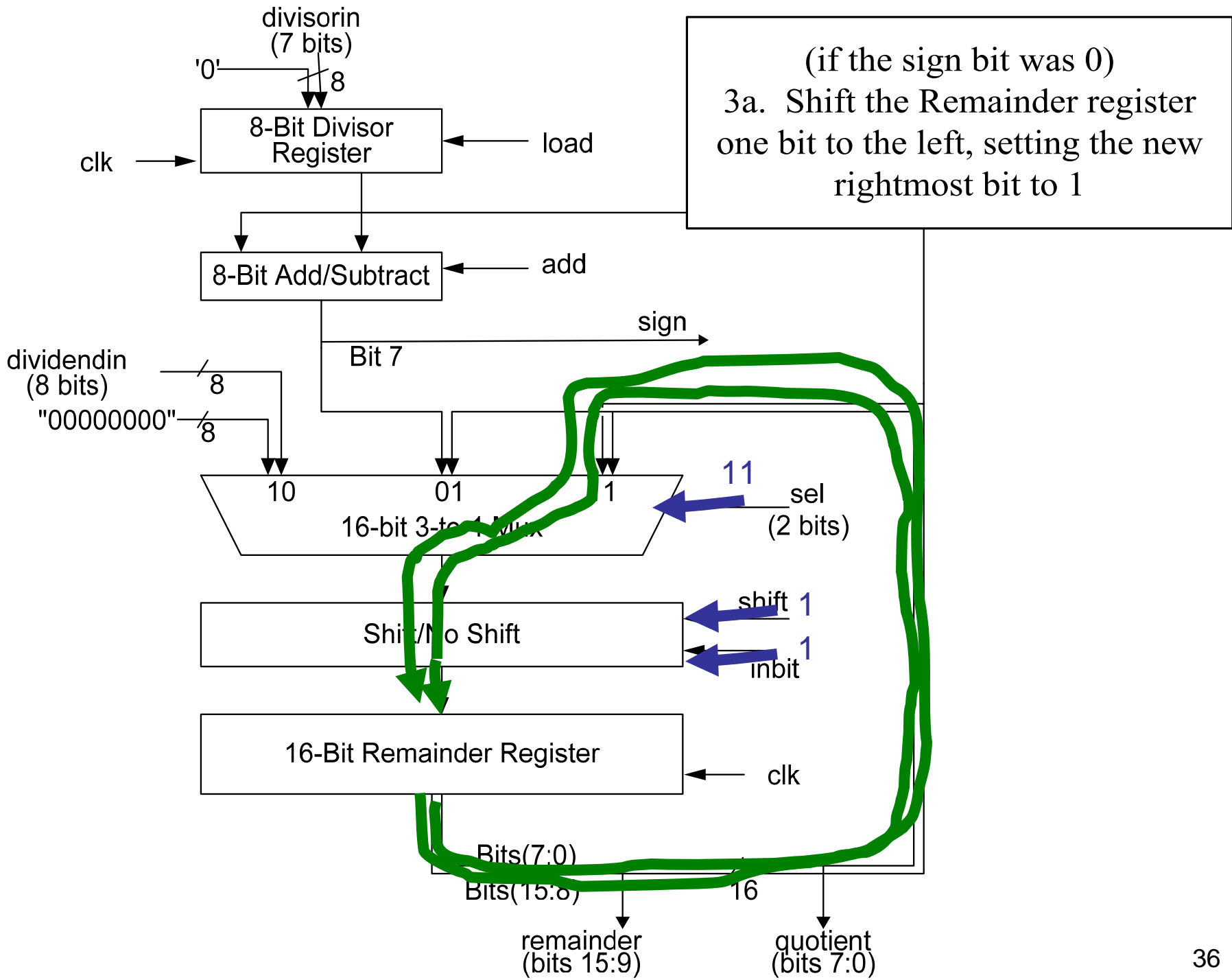

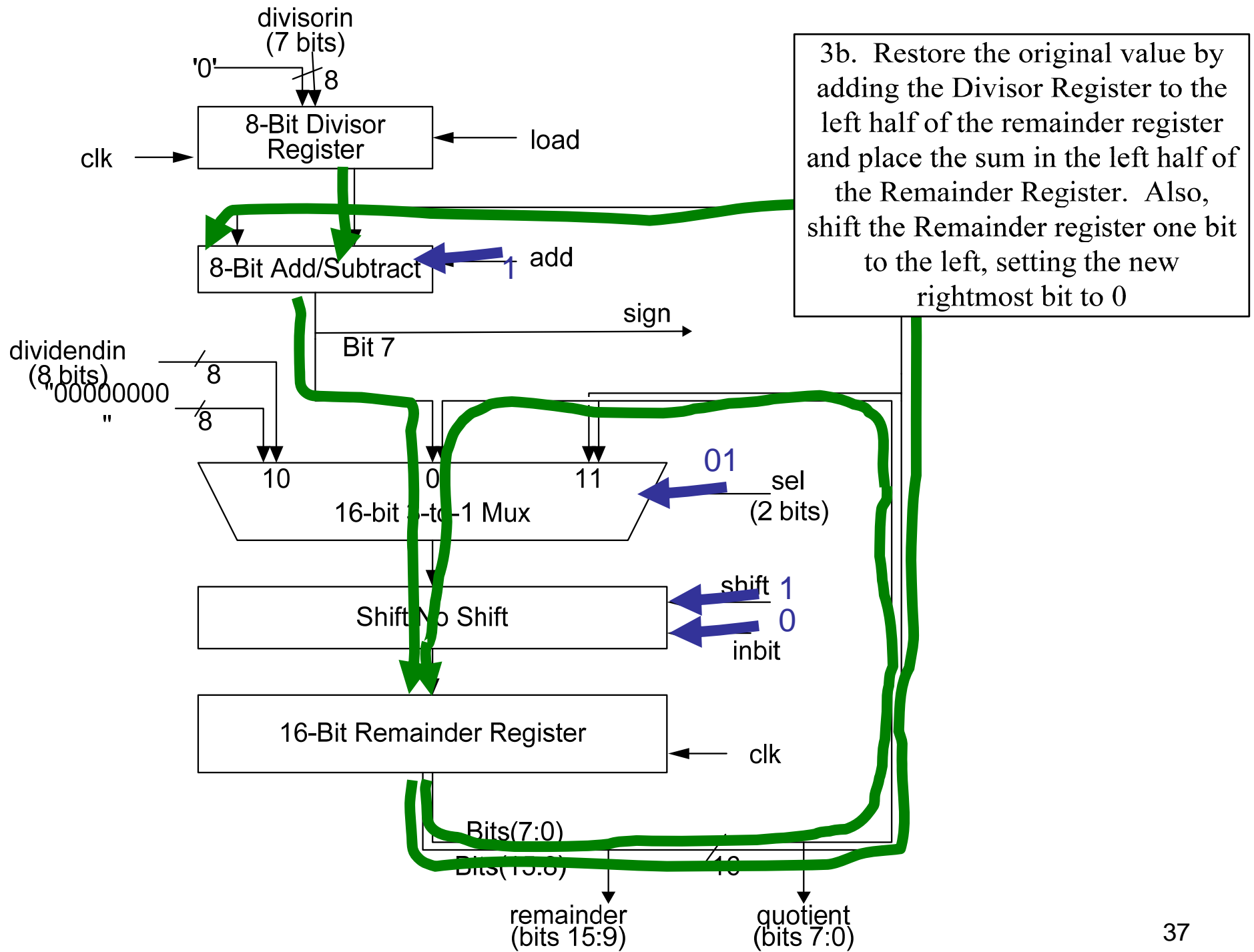

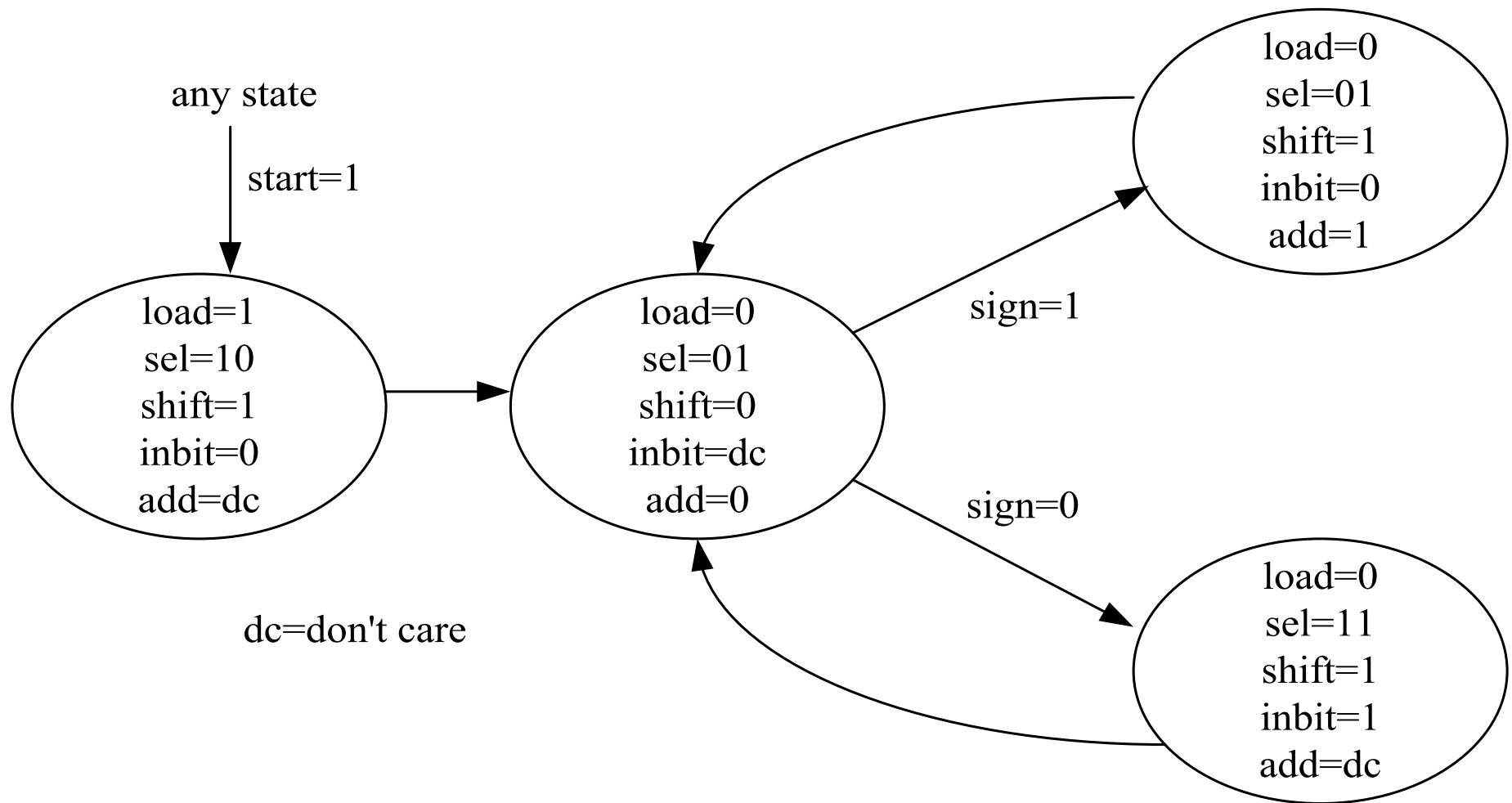

Controller State Machine

So both Lab 2 and Lab 3 have datapaths!

Yes, but Lab 2 was only the DES datapath and Lab 3 allows a Master to configure (provide a different key) and obtain the status of the datapath ...



Sorting

Sorting is the type thing that really makes sense to do in software (since it is so sequential). That being said, there may be times that you want to do it in hardware. Let's look at a fairly complex datapath that will perform sorting.

We will consider two approaches:


- Fully parallel (big)
- Serial (slow, but smaller)



The serial version is described in the textbook in great detail.


Fully-Parallel Sorting

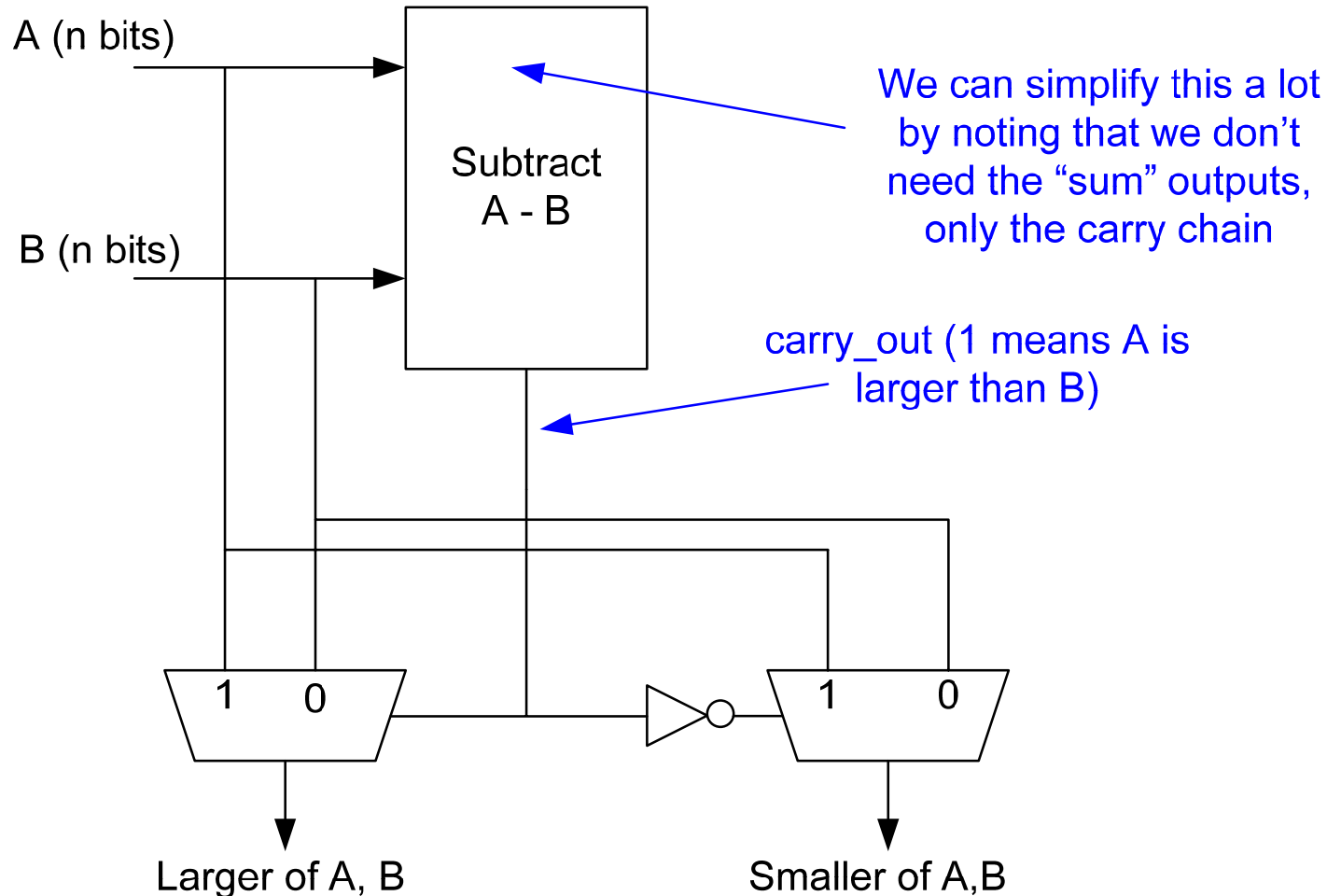- First consider designing a block that sorts two input numbers:



- Note that this is purely combinational (no clock required)

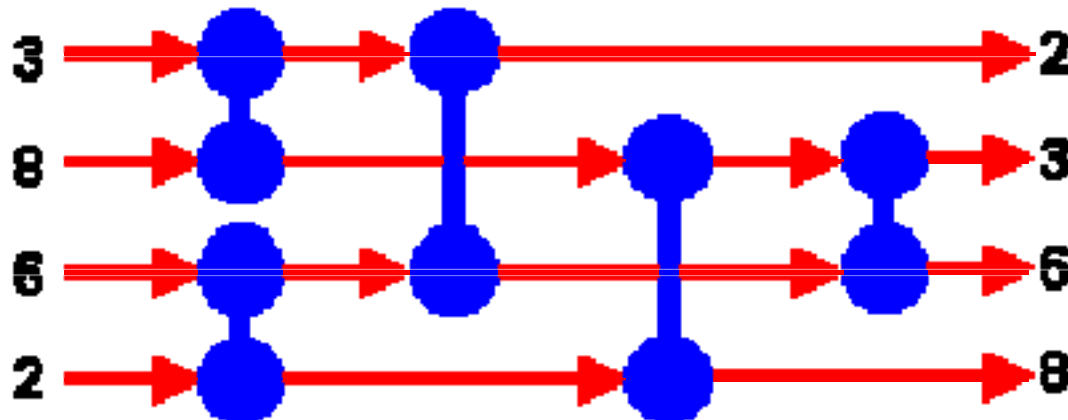Now build a network of these building blocks:



This will sort four numbers of any bit-width in one cycle

Problems:


- Gets big if there are more numbers to sort


Best known: $O(n \log n)$ blocks for n inputs


- Can't use this if n is arbitrary (not known when the chip is designed)

Suppose we want to sort k numbers:
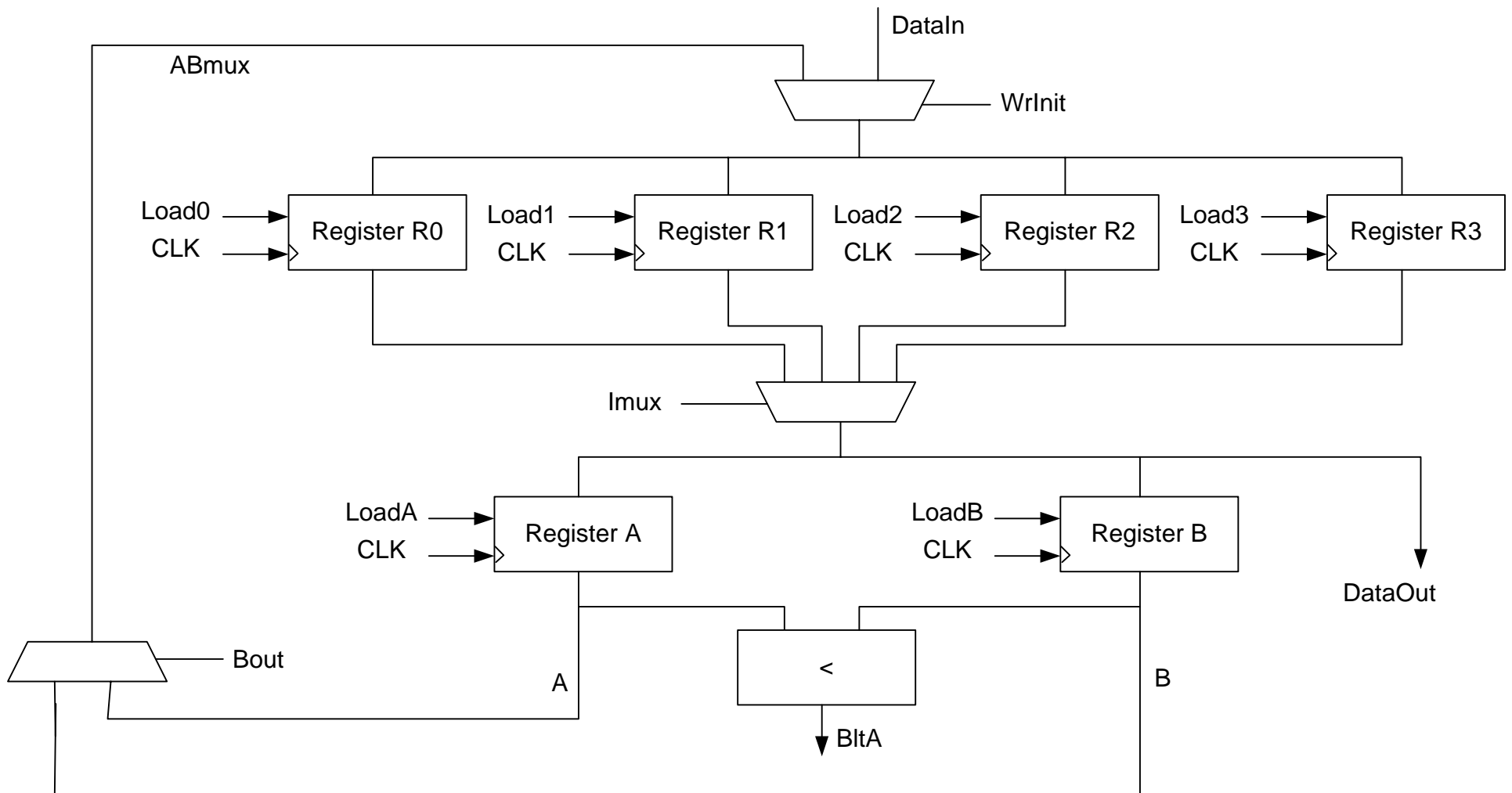
```
for (i=0 to k-2) do
  A = Ri;
  for (j=i+1 to k-1) do
    B = Rj
    if (B < A) then
      Ri = B
      Rj = A
      A = Ri
    end if;
  end for;
end for;
```



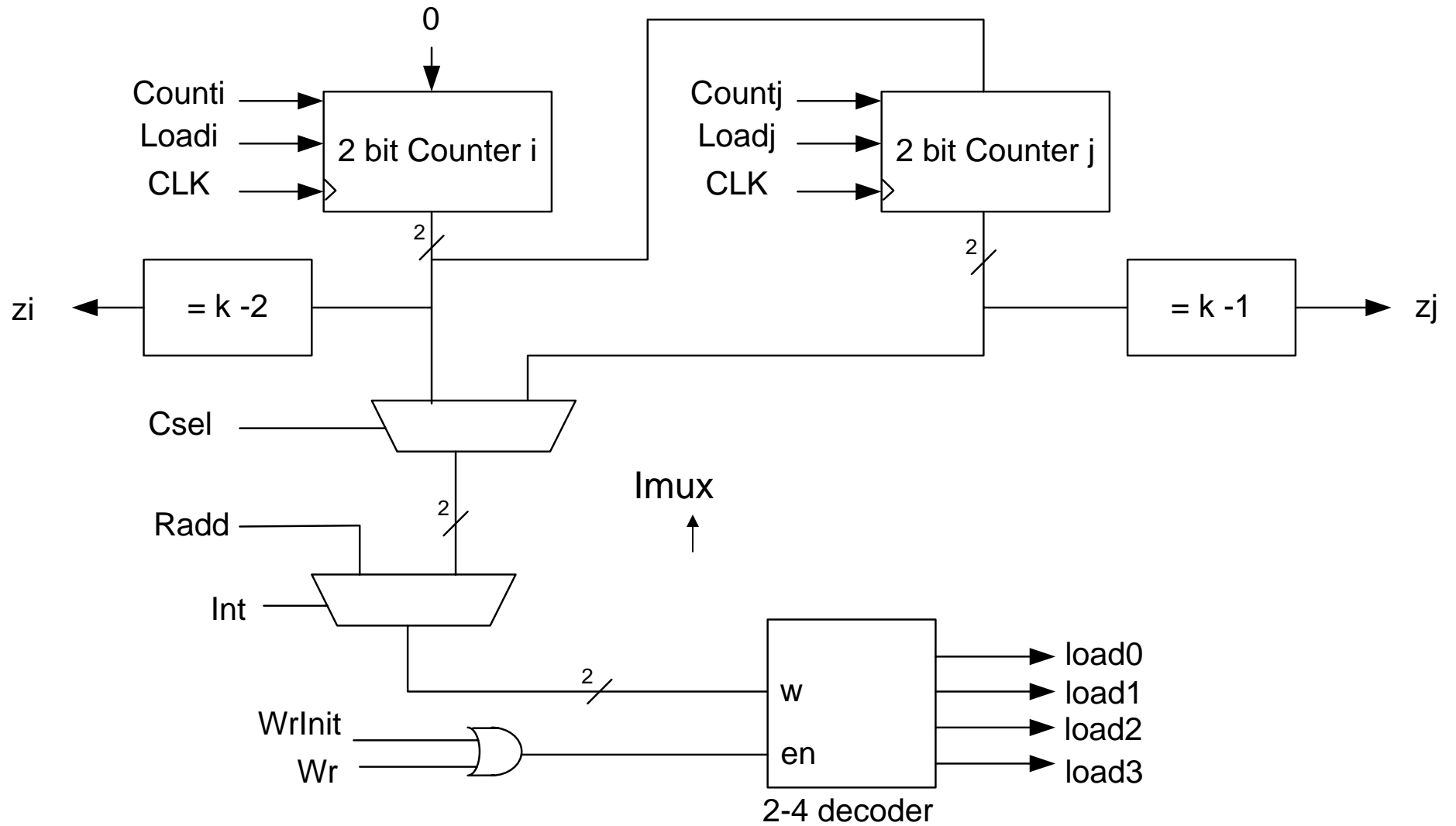


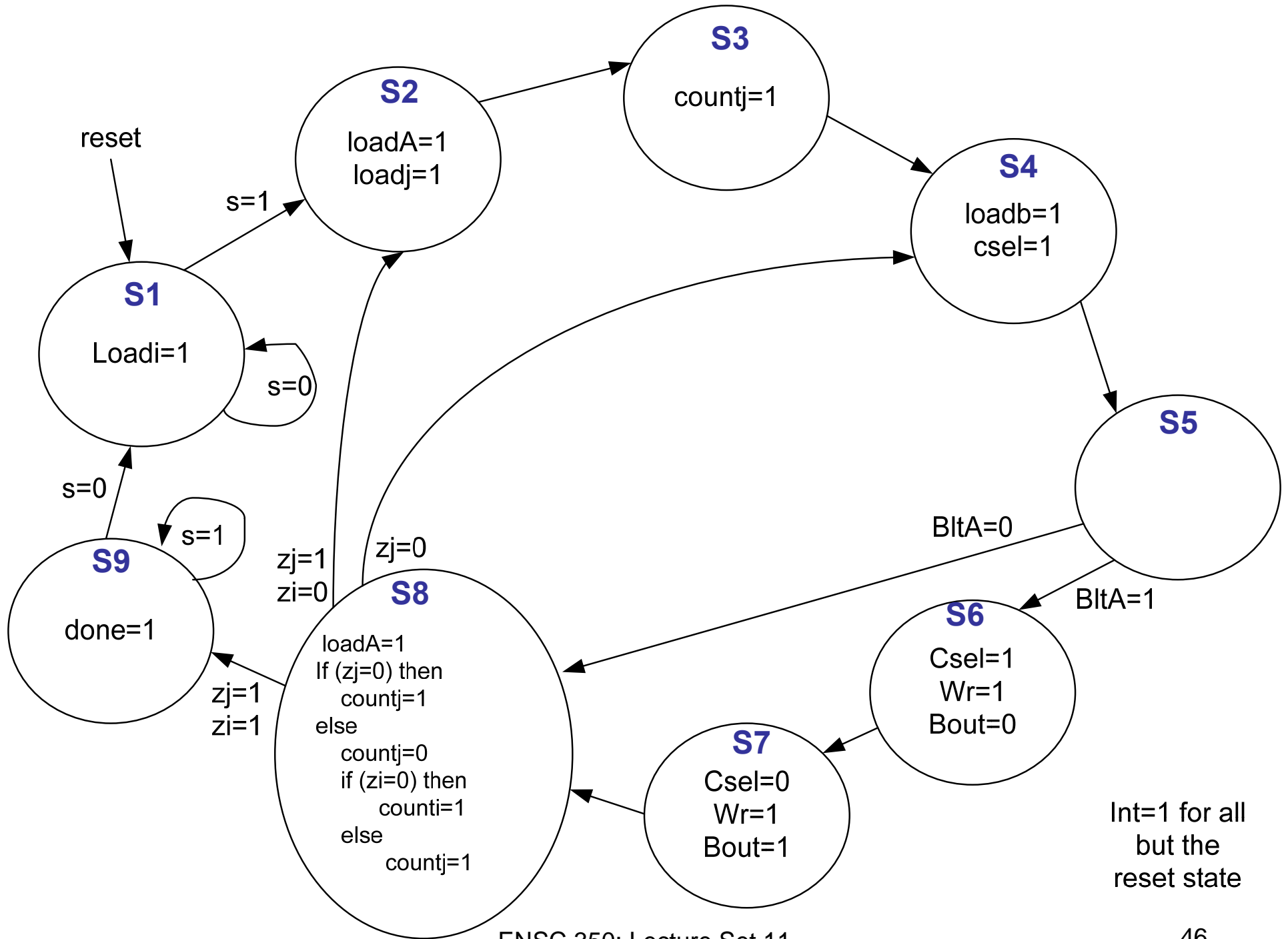


Int=1 for all but the reset state

Assume that the values to be sorted are in Registers R1 to R4 (circuitry is provided to do this, but assume it has already been done)

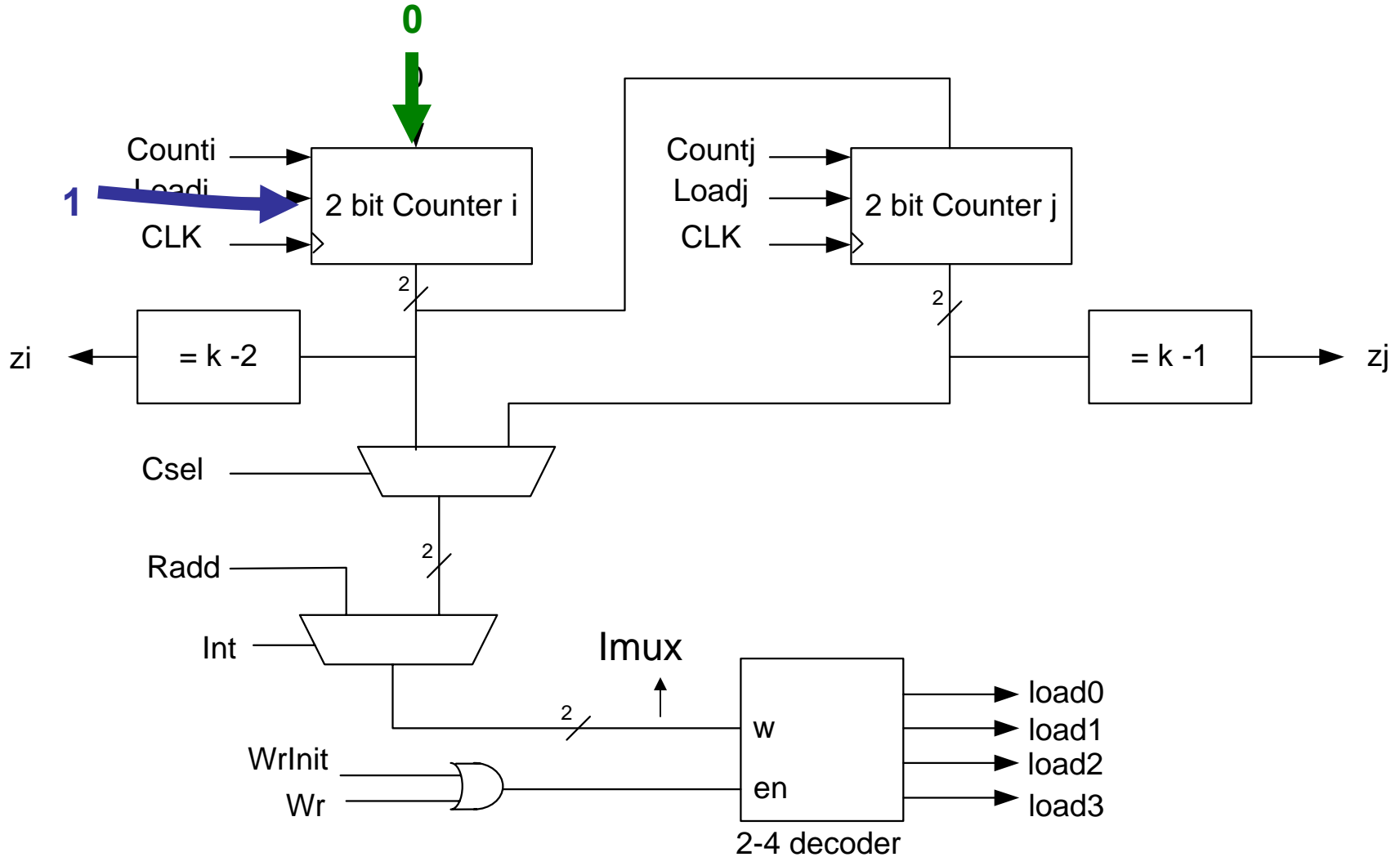
State S1: Initialize i (outer loop) to zero



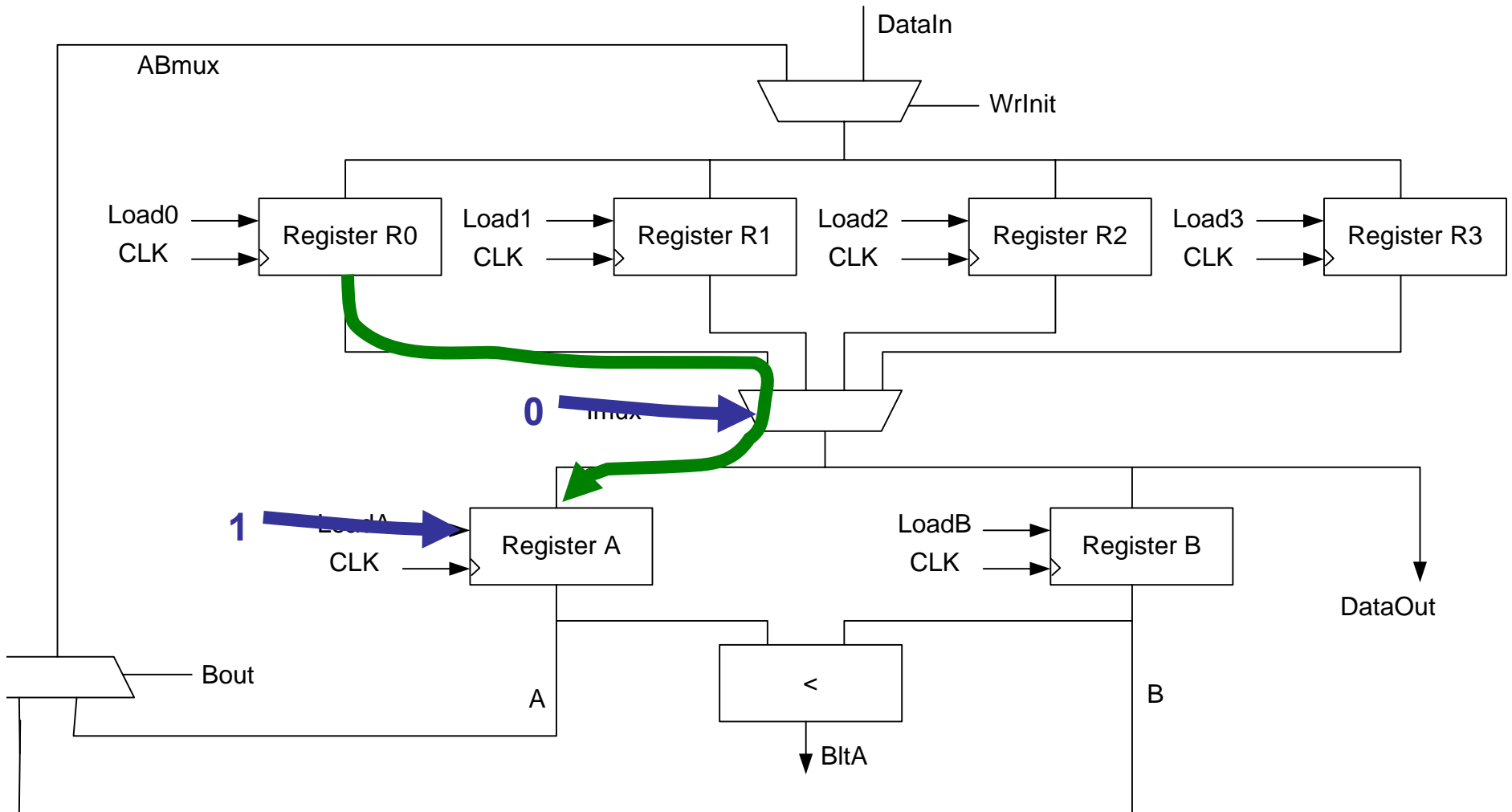
State S2: Load Register A with Ri and initialize j to value of i



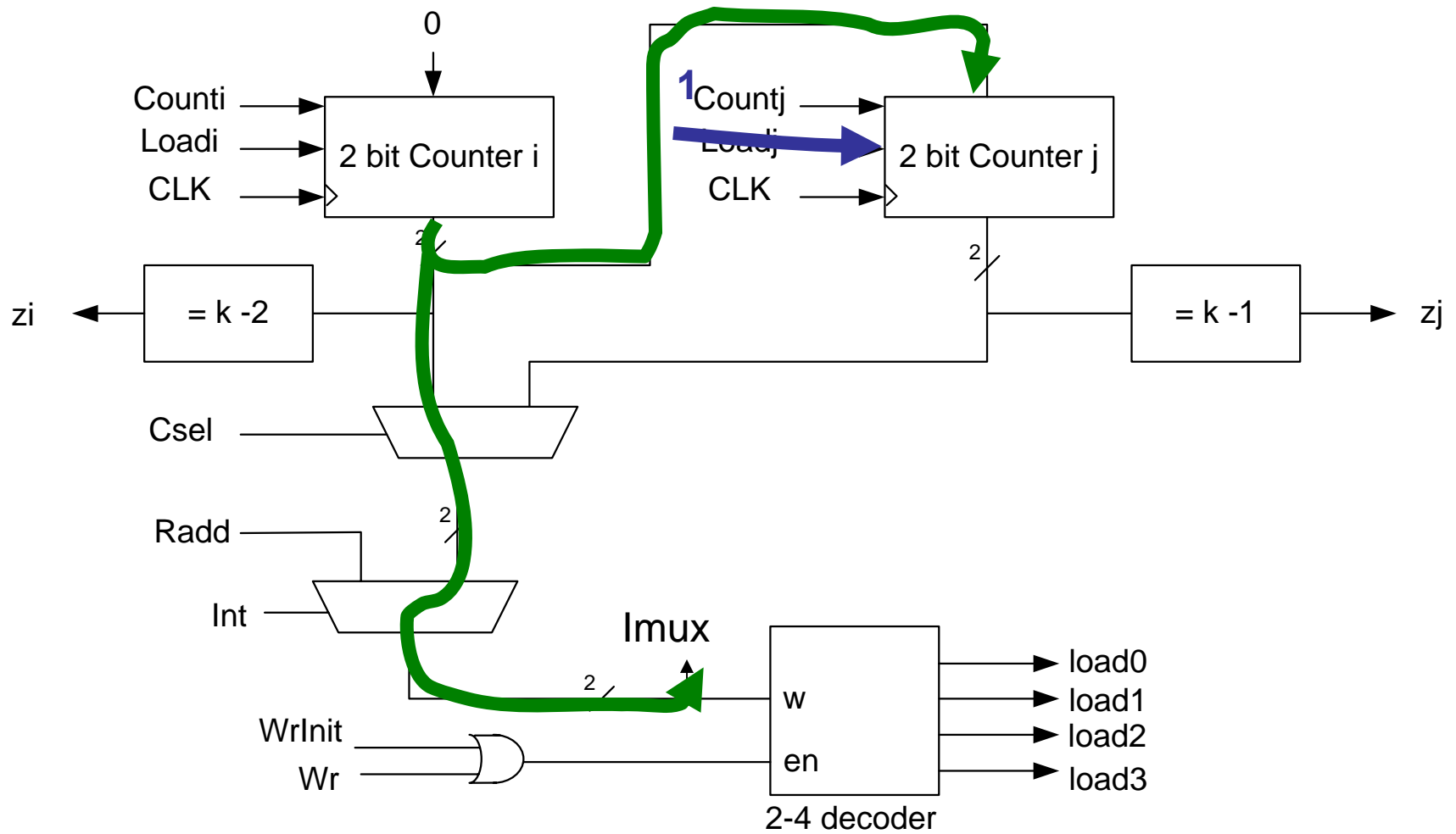
State S2: Load Register A with R_i and initialize j to value of i




State S3: Increment j so it equals i+1

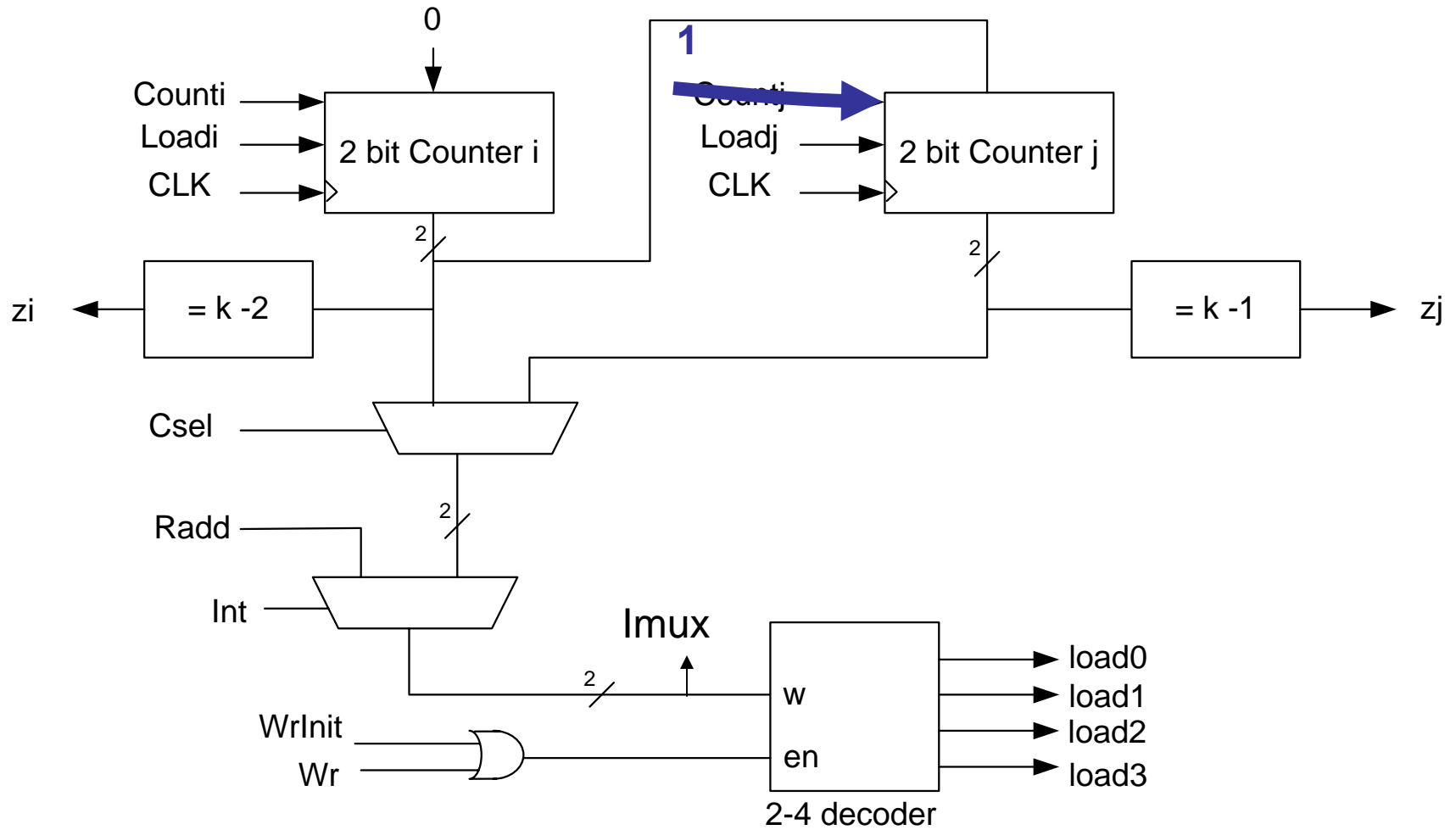


State S4: Load value of Rj into B

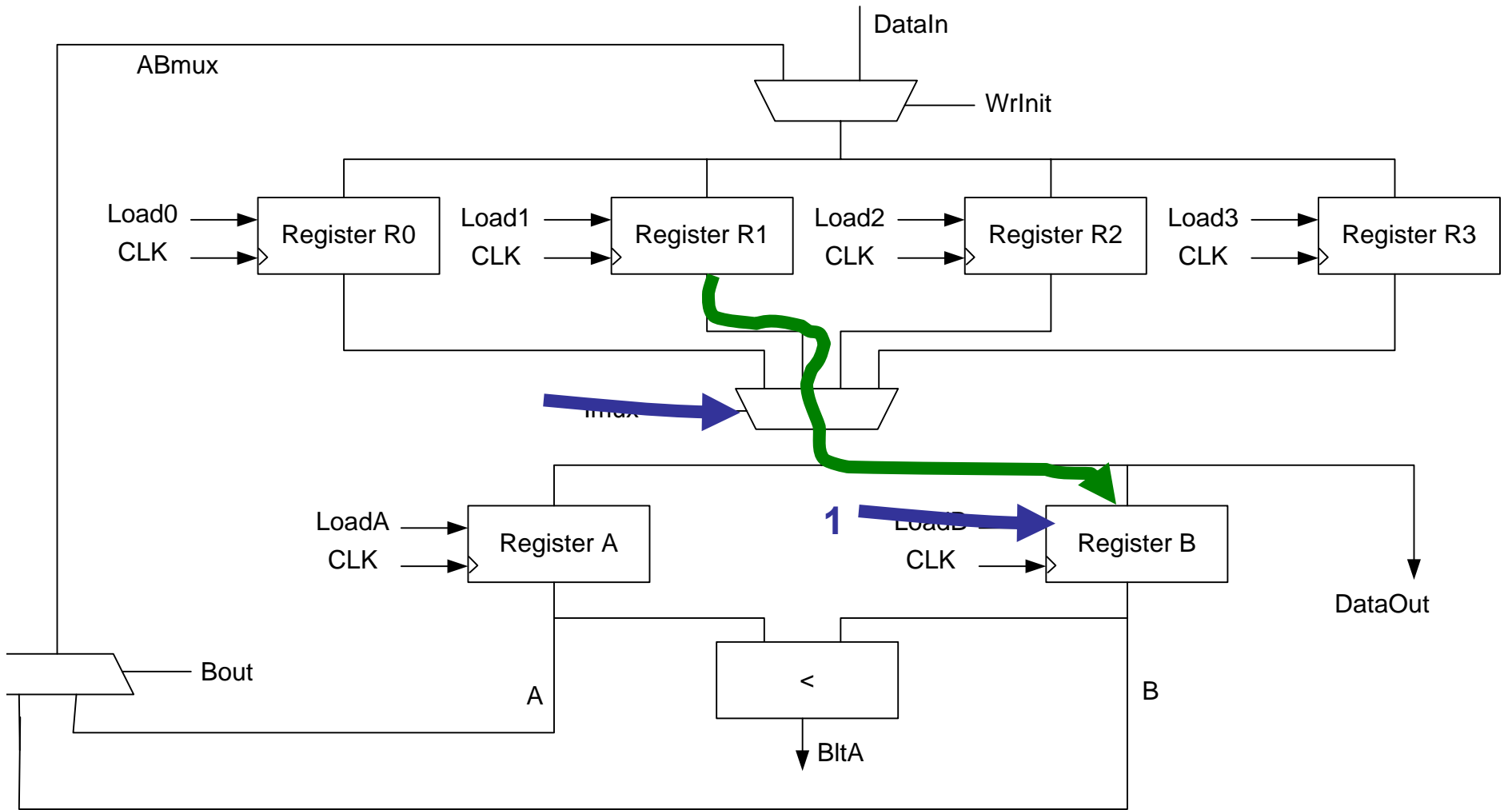


Where does Imux come from in S4?

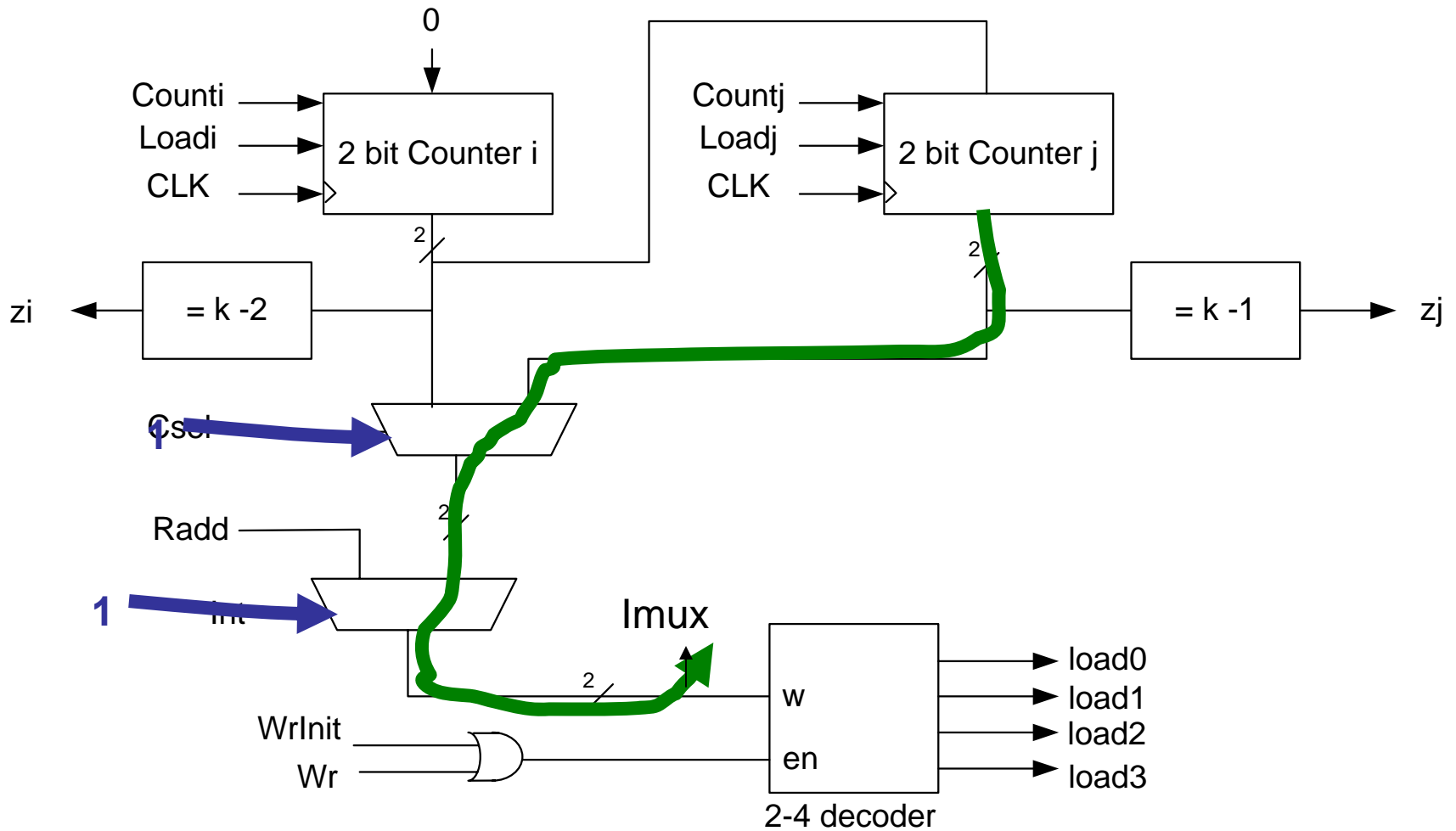

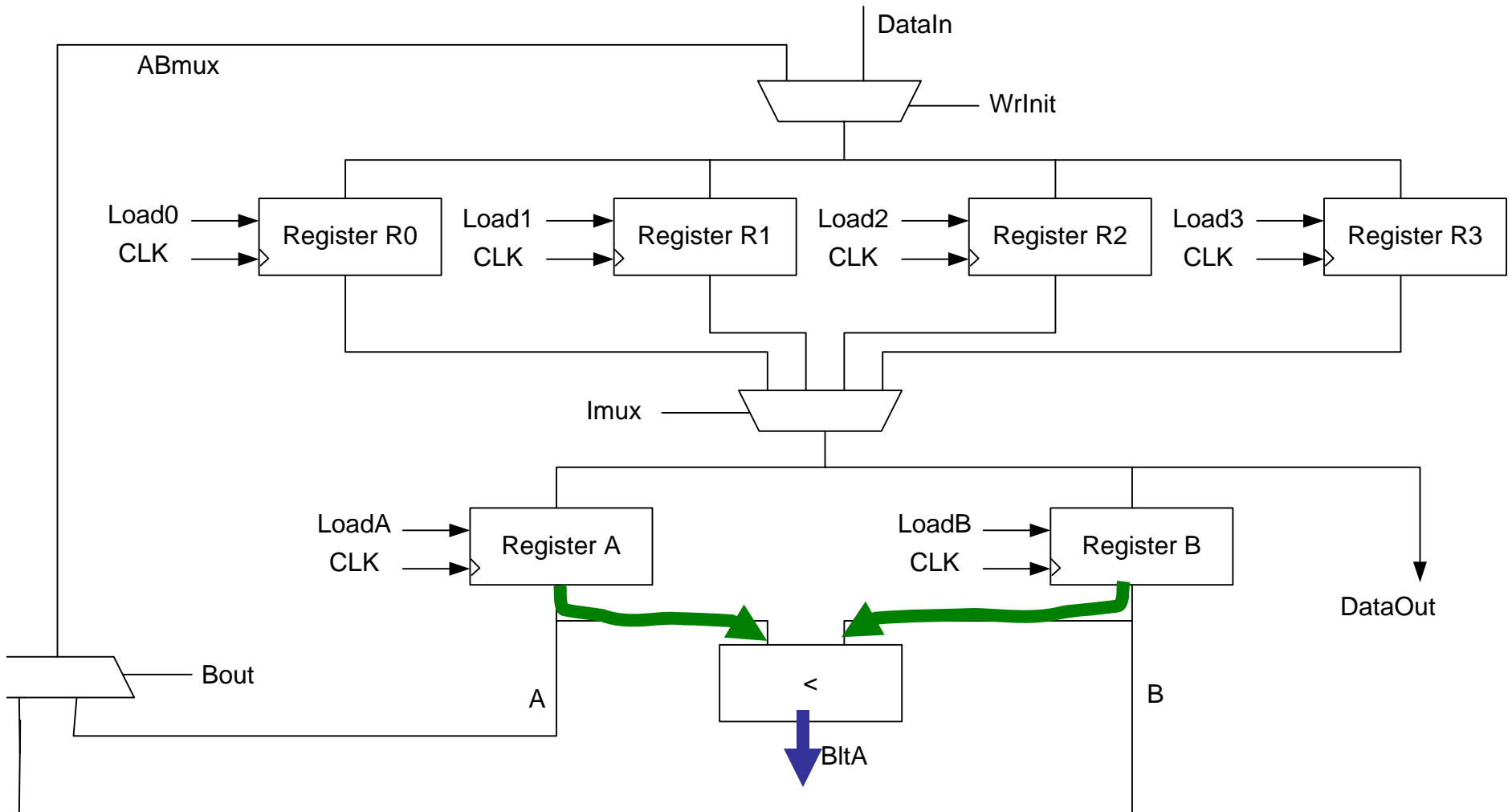State S5: A and B are compared, and if $B < A$, goes into State 6




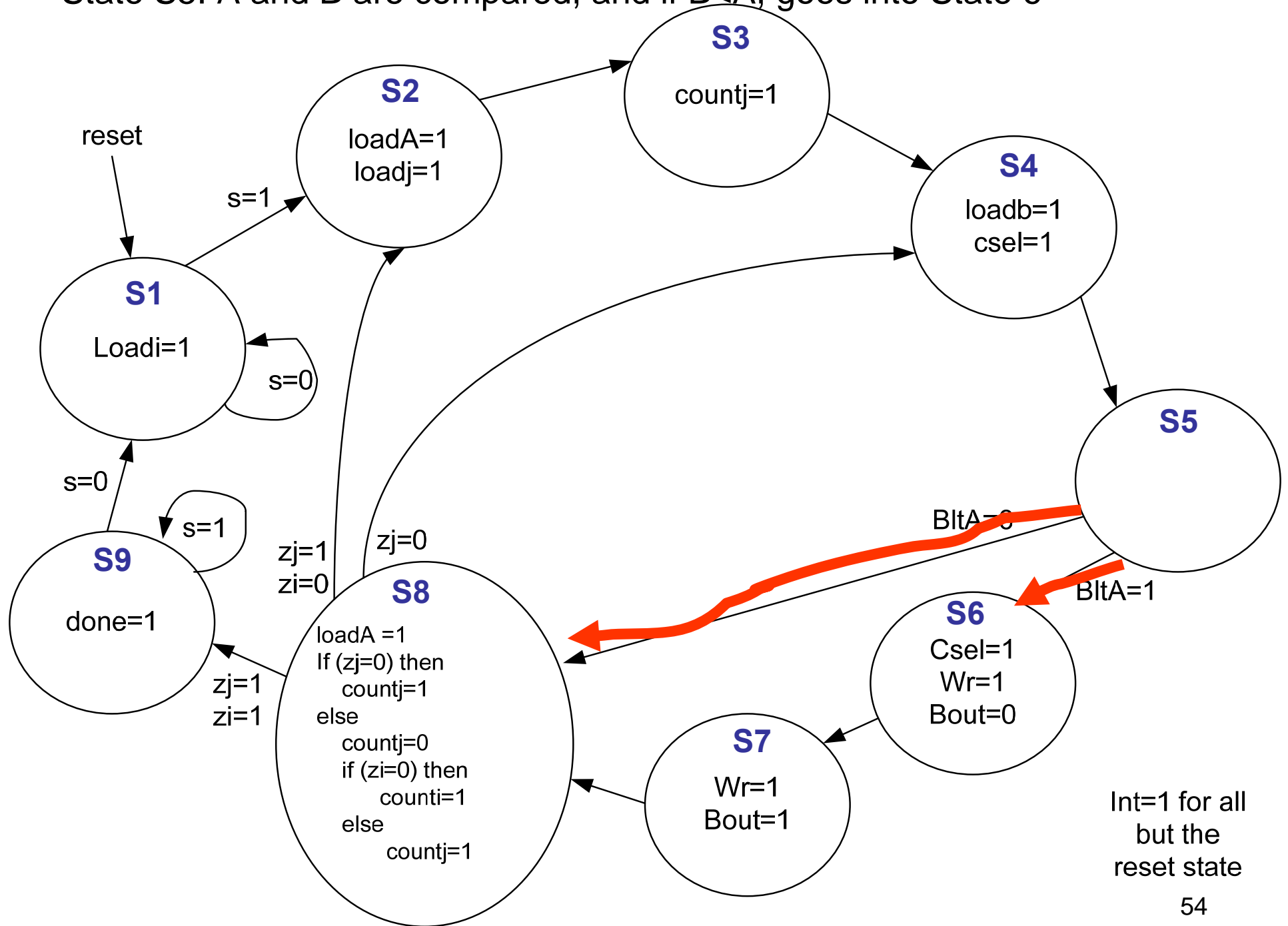State S5: A and B are compared, and if $B < A$, goes into State 6




Int=1 for all
but the
reset state


State 6: Swap Ri and Rj (part 1)

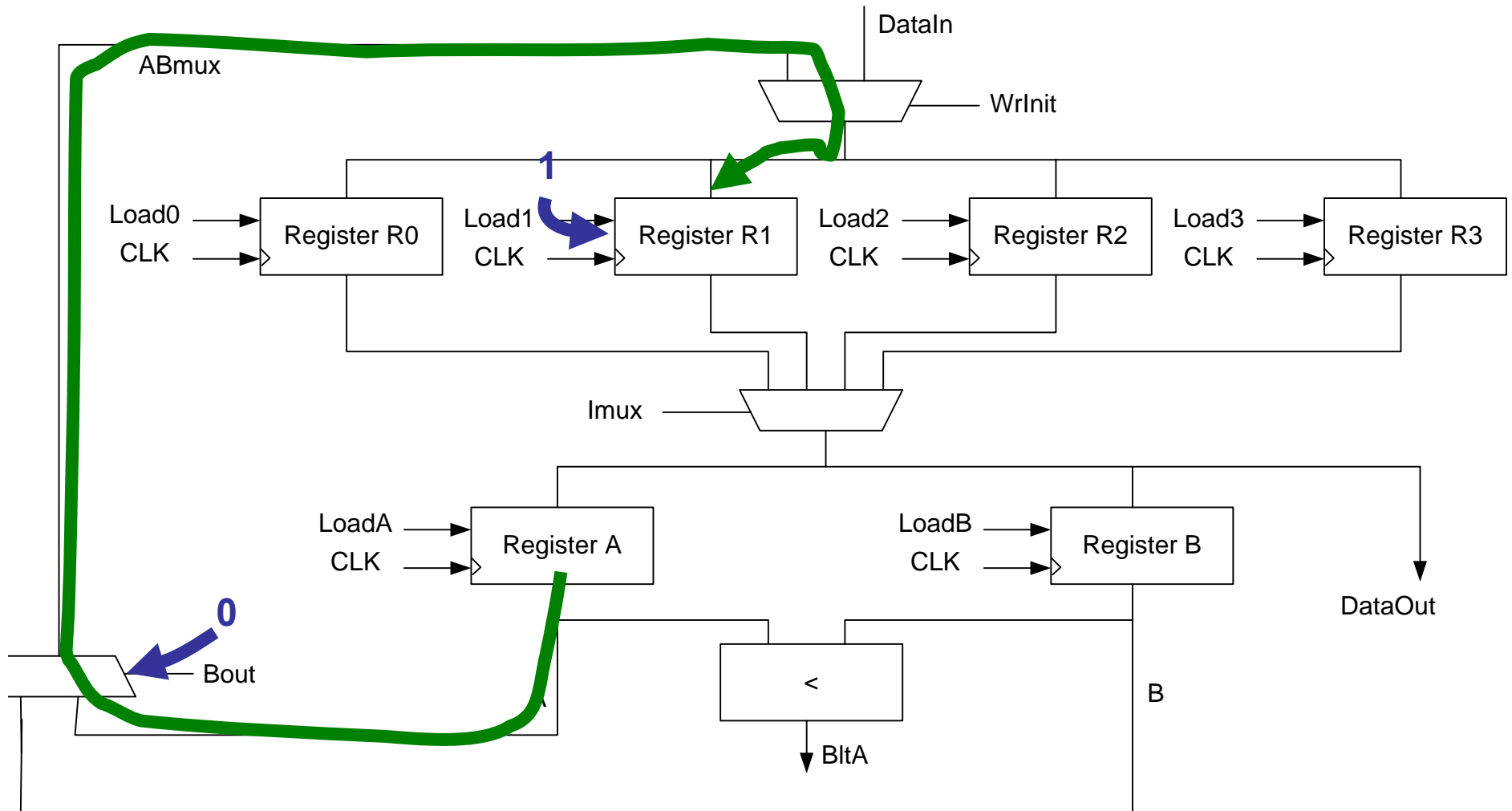


How did it know which loadj to assert?

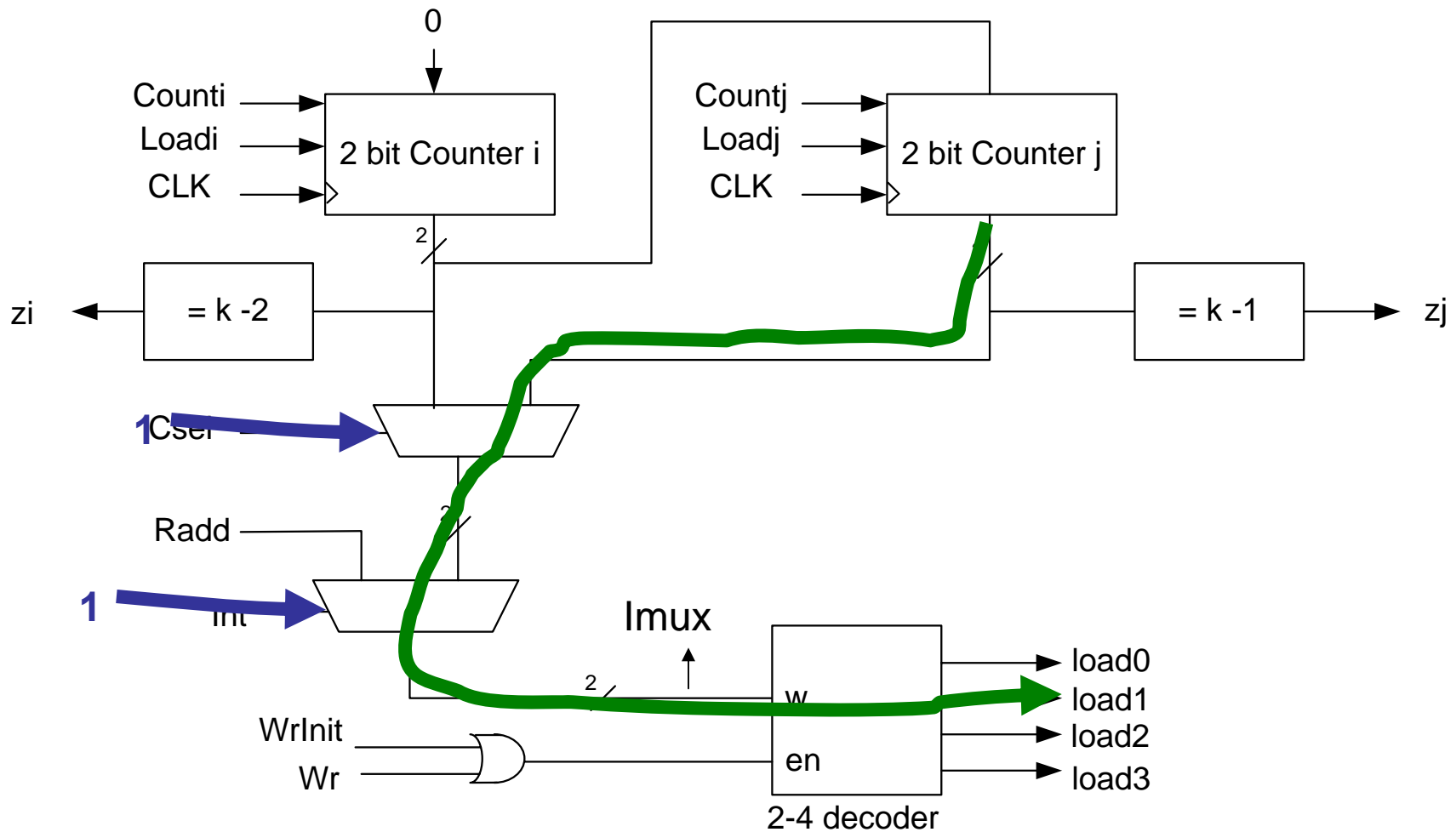


State S7: Swap Ri and Rj (part 2)

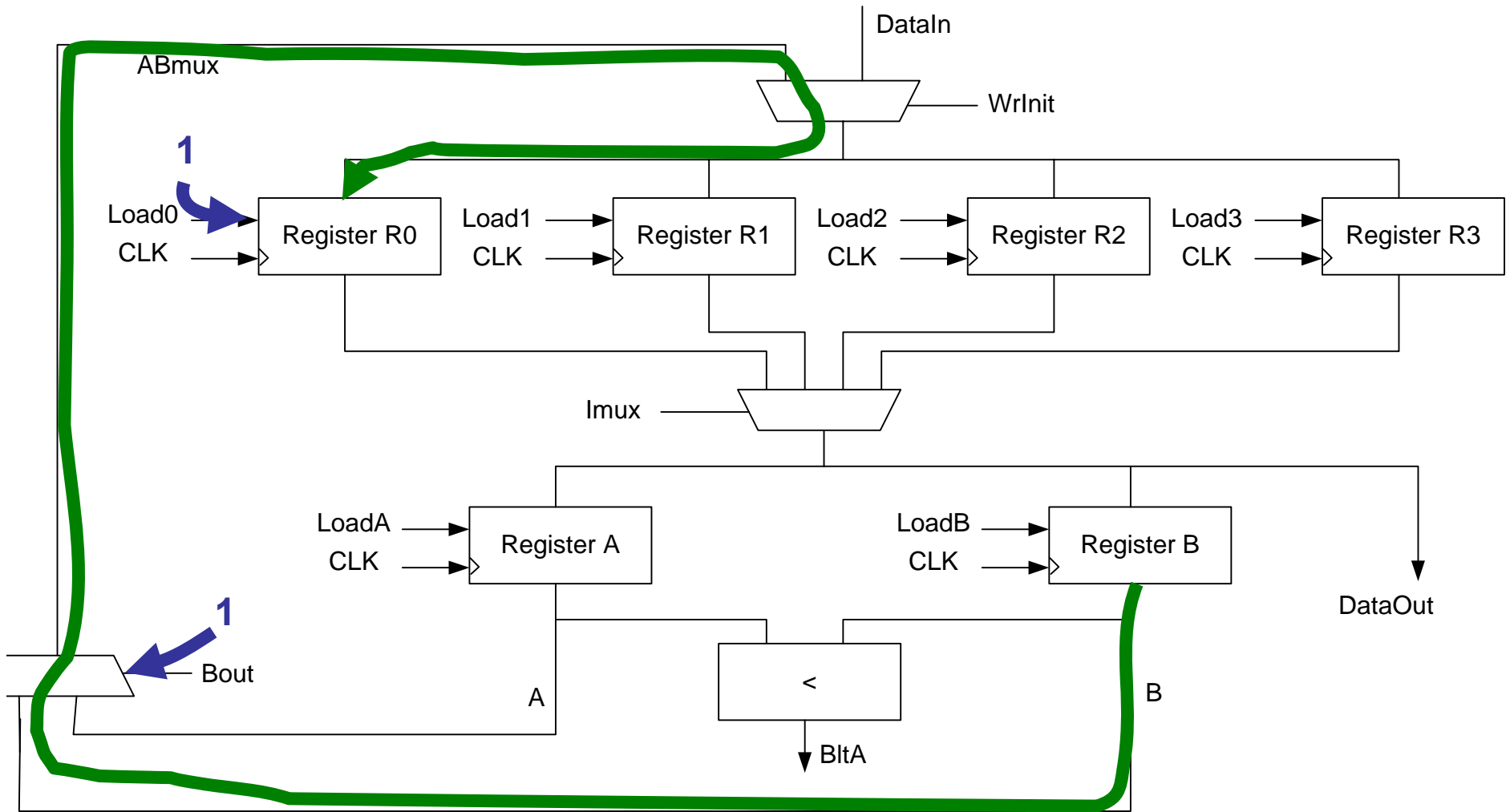


How did it know which loadi to assert?

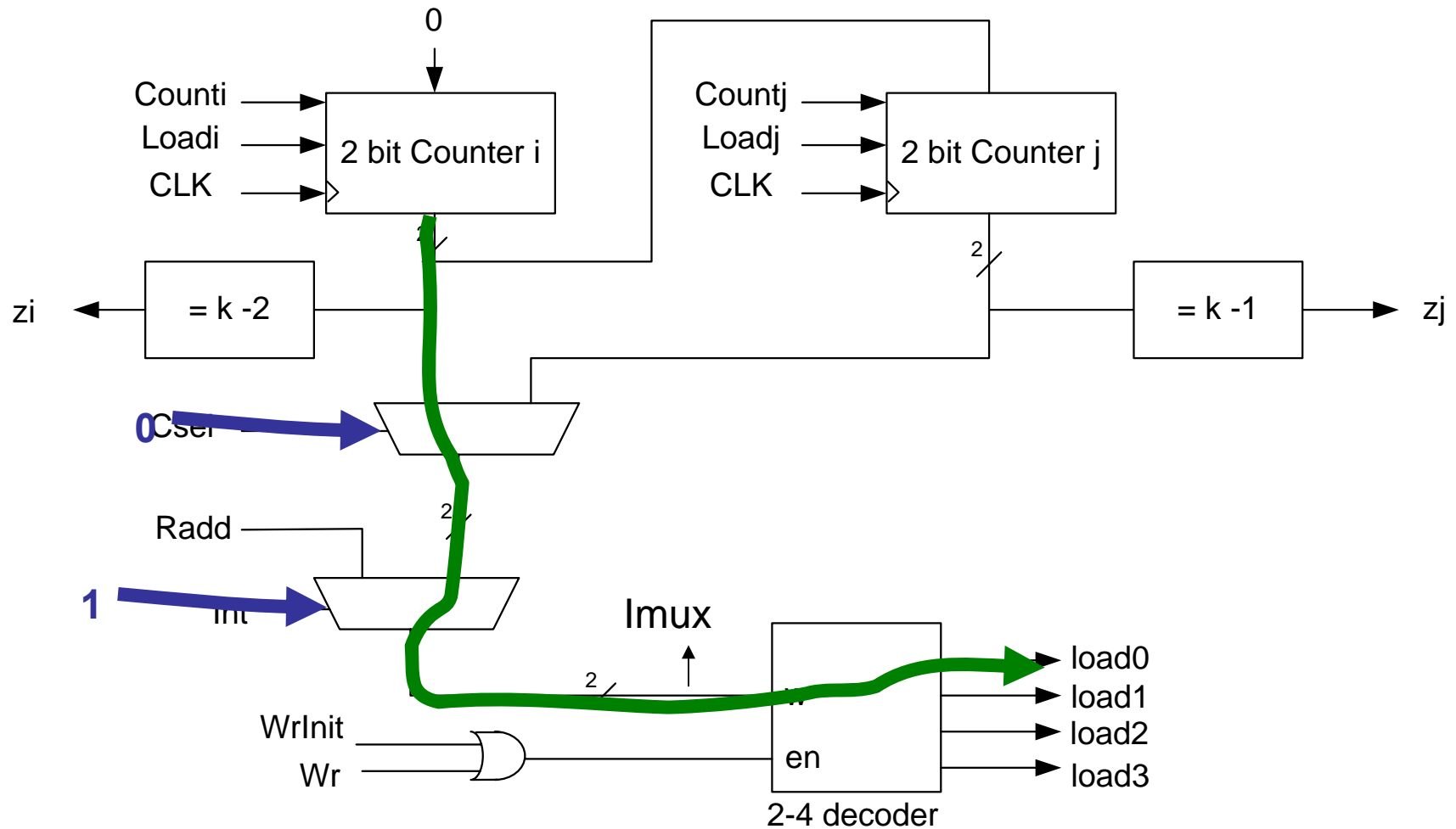


State S8: Load A from Ri

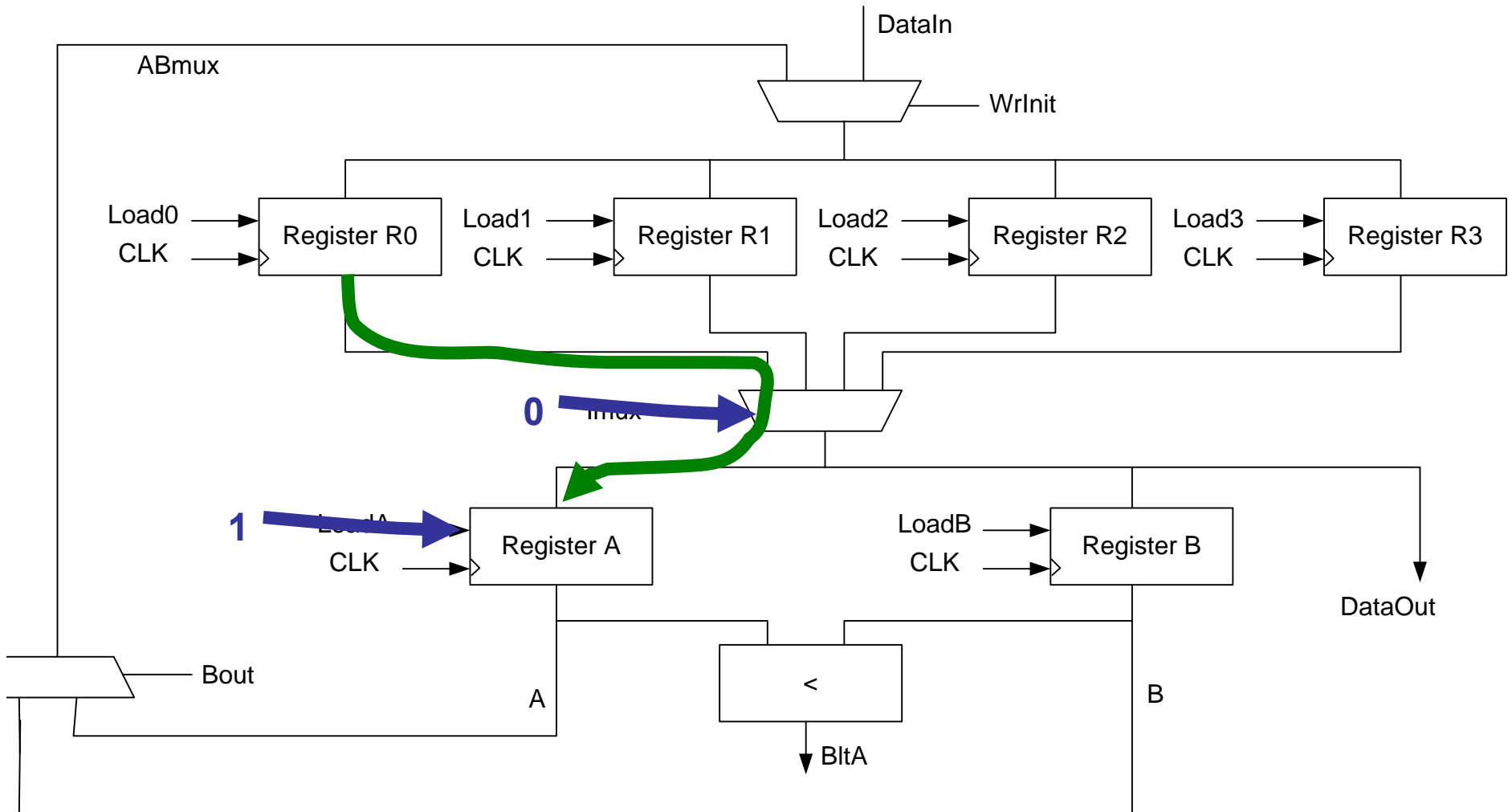

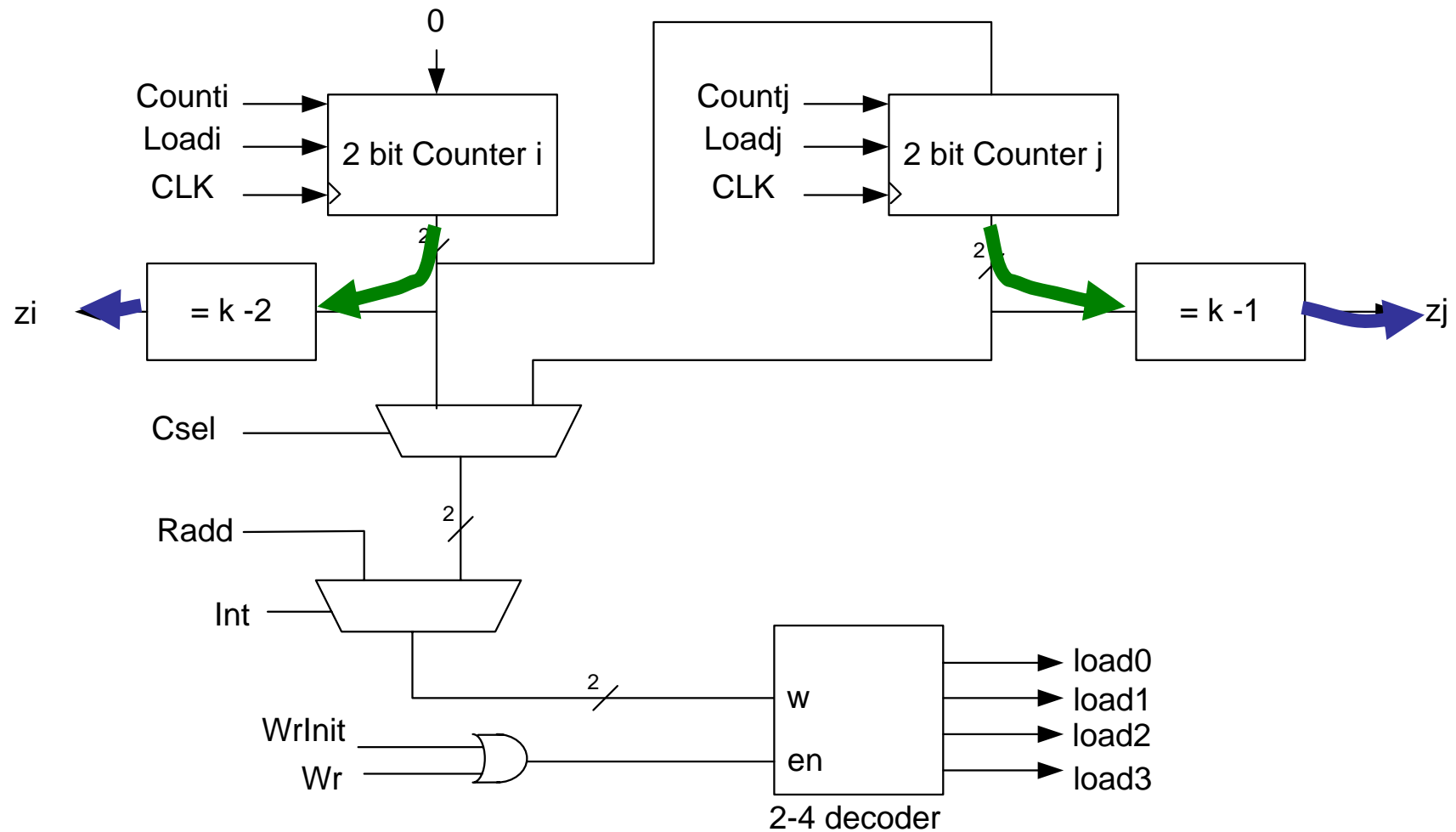State S8: This was being done all the time, but now we will use z_i and z_j




State S8:

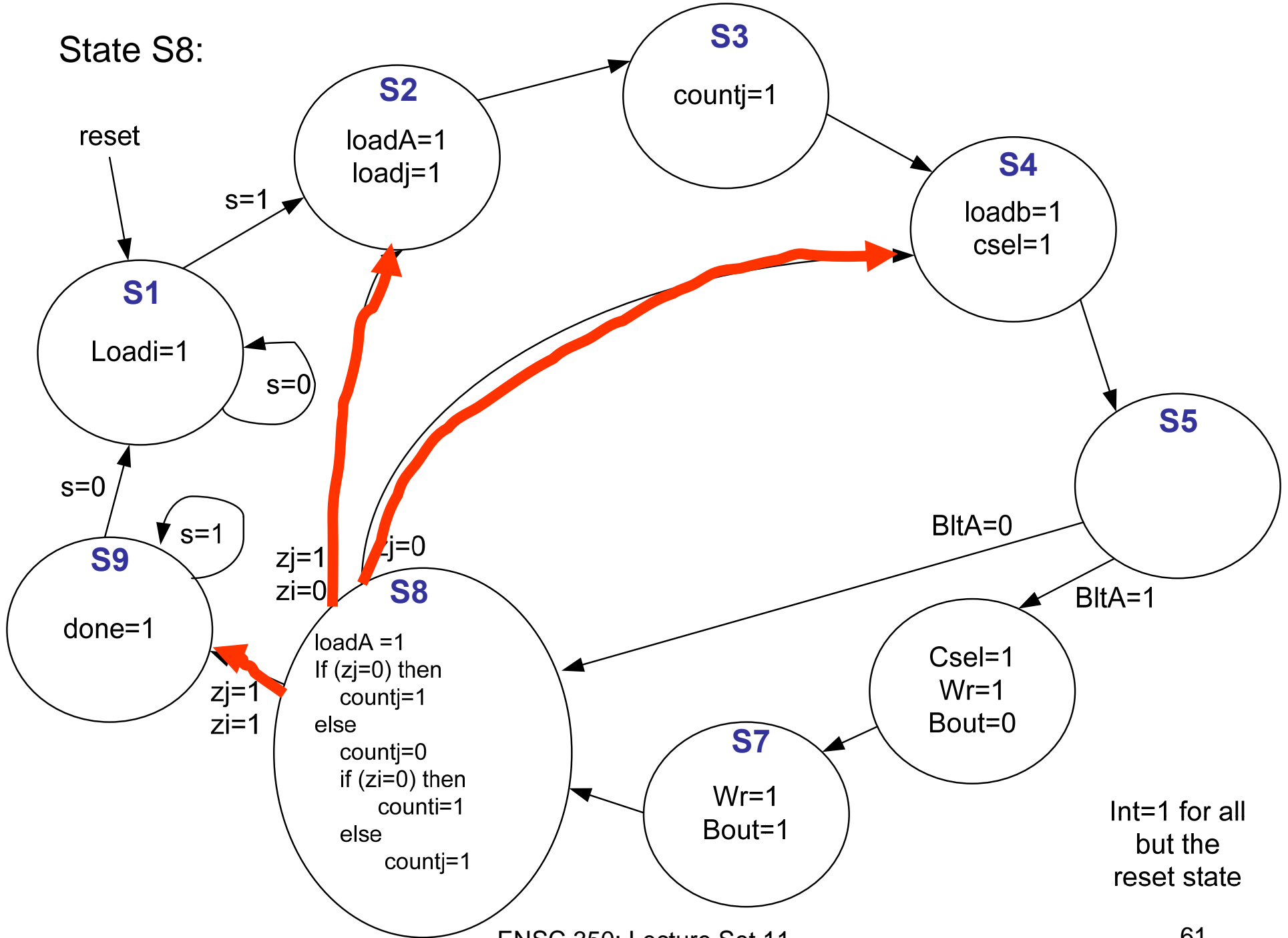

Int=1 for all
but the
reset state

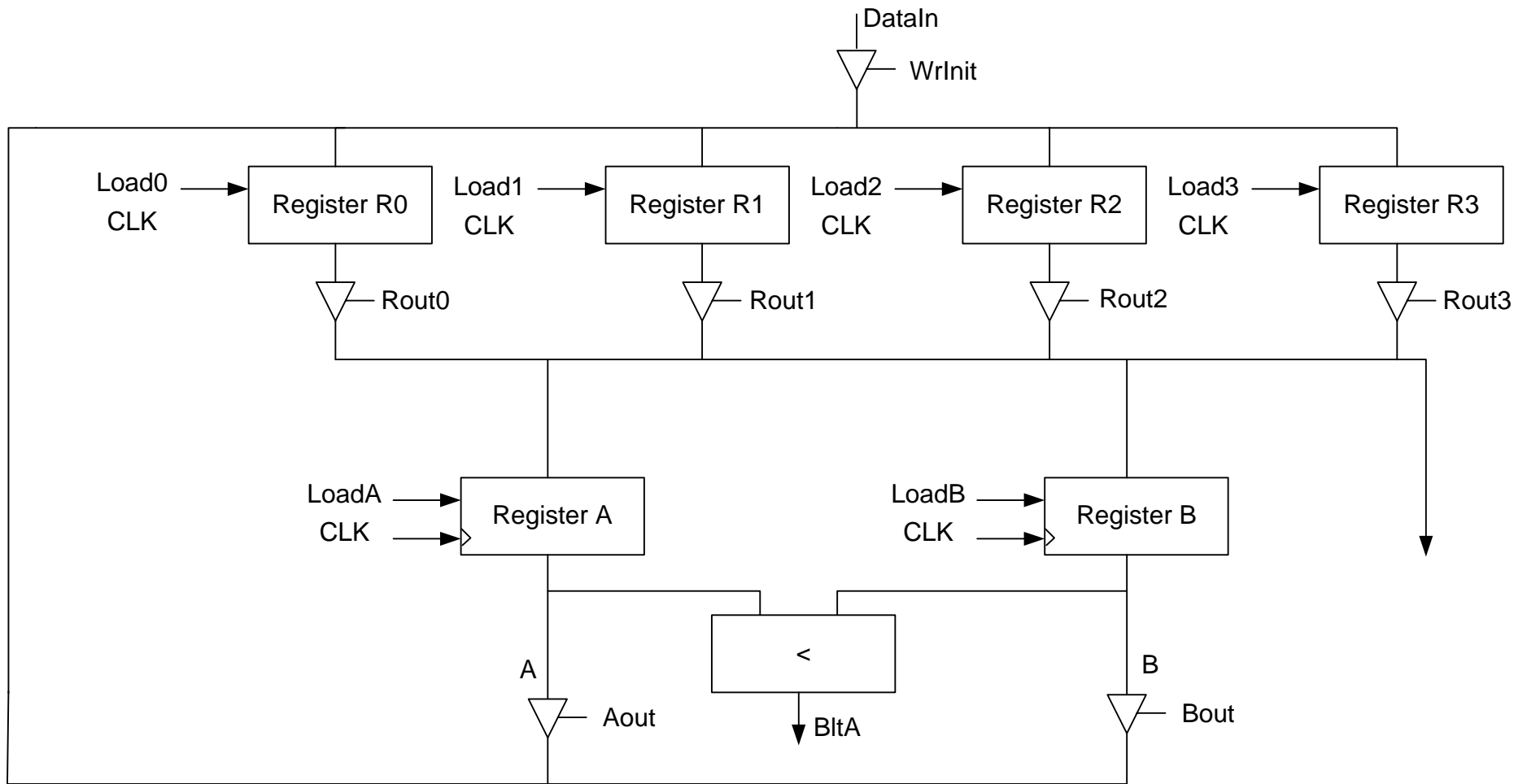An alternative datapath: Tri-state buffer based datapath



Area vs. Speed

In this example, we saw two implementations:

Big and Fast

Small and Slow

In general, you can trade off area for speed. Ideally, if you double the number of functional units, then you can reduce the number of cycles by half. Rarely can you achieve this.

Which is the right implementation? Depends on how fast you need the circuit to produce results. Larger circuits cost more (more chip area, more power, higher prob. of defects), so if you don't need the speed, a small implementation is probably better.


There is no general rule: as an engineer, it is up to you to choose a good implementation based on the specs you are designing to

Summary of this long Slide Set

We saw a lot of examples of datapath and control circuits

Do you need to regurgitate all the details of any of these examples on a test?

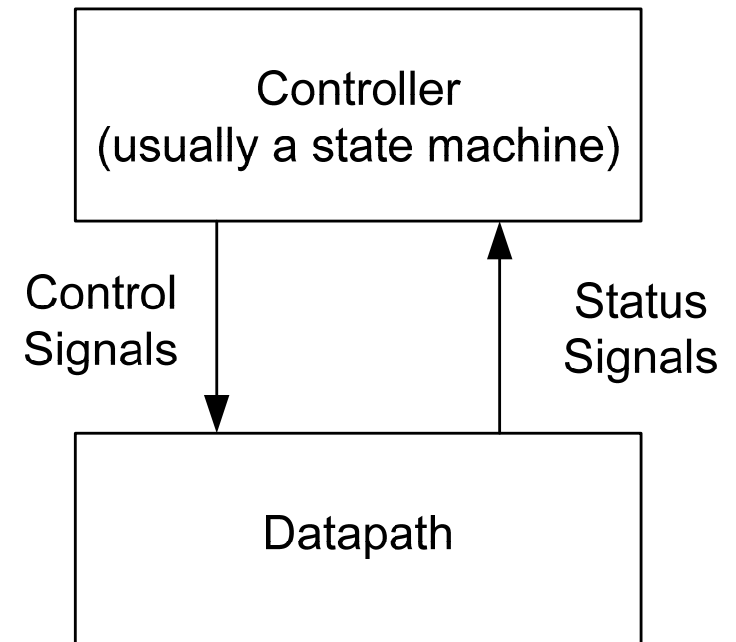No, but you might be asked to design a simple system that contains both a datapath and controller. But, if you understand these examples, you'll be in a good position to do the design on a test, and more importantly, in the real world once you graduate (or go on co-op)



Summary of this slide set

- All of these examples – except the divider - can be found in this textbook (pages 673-712)
- They use ASM charts as opposed to FSMs
- There are no review questions for this slide set, just these examples to guide your thought process

