

Digital System Design

by

Dr. Lesley Shannon

Email: Ishannon@ensc.sfu.ca

Course Website: <http://www.ensc.sfu.ca/~Ishannon/courses/ensc350>



Simon Fraser University


Slide Set: 9

Date: March 2, 2009

Slide Set Overview

- The remainder of this semesters lectures will cover other useful odds and ends and some design examples (as time permits)
 - E.g. buses, floating point calculations, balancing a pipeline, asynchronous circuitry, datapaths, CPU design, and memories
- This lecture will cover
 - Tri-state drivers
 - Generate statements

Tri-State Drivers

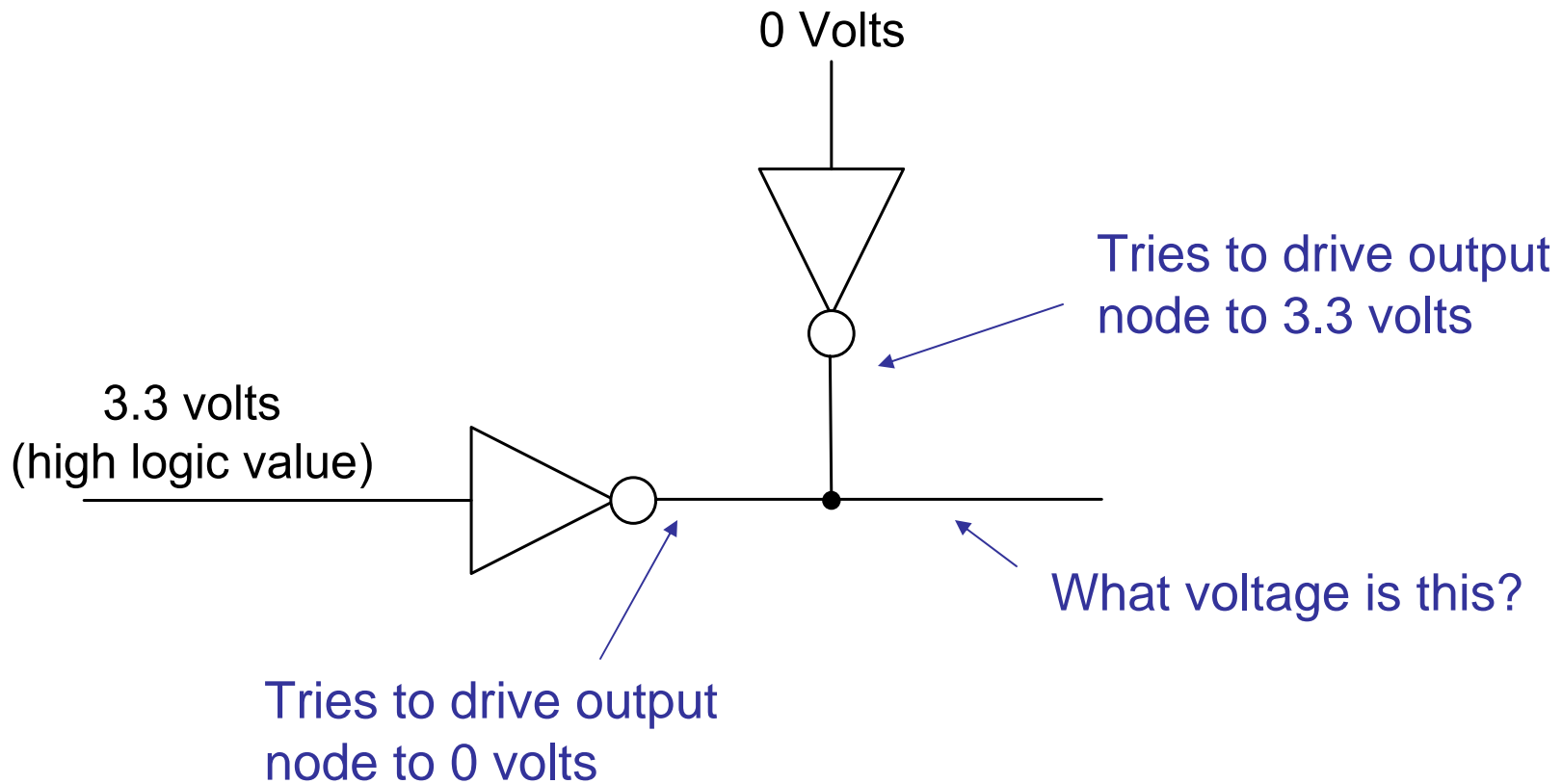

Fighting

- This is an example of “fighting”
 - What happens depends on the the circuits are implemented
 - For CMOS (most chips are designed using CMOS), fighting can cause high currents and even damage the chip!




- Interesting question: what would happen if we measure the voltage of such a wire?

Simulation

- Now think of what happens if we simulate a VHDL specification of this circuit...
- What should the value of this output node be?
 - A signal of type “bit” can be 0 or 1
 - But neither of those is the right answer.
 - One of the possible values of a signal of type ‘std_logic’ is X
 - X stands for unknown
- When the VHDL simulator sees this fighting, it sets the value of the output to X. That tells you something is wrong.
- Remember, in the real circuit, the node will have some value... (can't measure an X in the lab)

Tri-State Drivers

 

If “enable” is 1, then out is driven with the value on in.

If “enable” is 0, then out is *not driven*.

- What does that mean? If no one else is driving this signal, then the signal is “floating”
- What happens if you try to measure the voltage of a floating signal in the lab?

Simulation

- Now think of what happens if we simulate a VHDL specification of this circuit...
- If enable is zero, what should the simulation say the output is?
 - One of the possible values of a signal of type 'std_logic' is Z
 - Z stands for high impedance

in	enable	out
0	0	z
1	0	z
0	1	0
1	1	1

Remember: in the real world, a signal will have a voltage, even if it is not being driven

- Can't measure Z in the lab

```
entity tristatedriver is  
  port( A, enable : in std_logic;  
    Q : out std_logic);  
end tristatedriver;
```

architecture behavioural of tristatedriver is

```
begin  
  process (A, enable)  
  begin  
    if (enable = '1') then  
      Q <= A;  
    end if;  
  end process;  
end behavioural;
```


WRONG!

The problem with the previous specification is that if enable is zero, the output is not driven. VHDL syntax says that in this case, the output maintains its old value.

- Not the behaviour we want to specify

```
entity tristatedriver is  
    port(  A, enable : in std_logic;  
          Q : out std_logic);  
end tristatedriver;  
  
architecture behavioural of tristatedriver is  
begin  
    process (A, enable)  
    begin  
        if (enable = '1') then  
            Q <= A;  
        else  
            Q <= 'Z';  
        end if;  
    end process;  
end behavioural;
```

How a tri-state driver is usually used

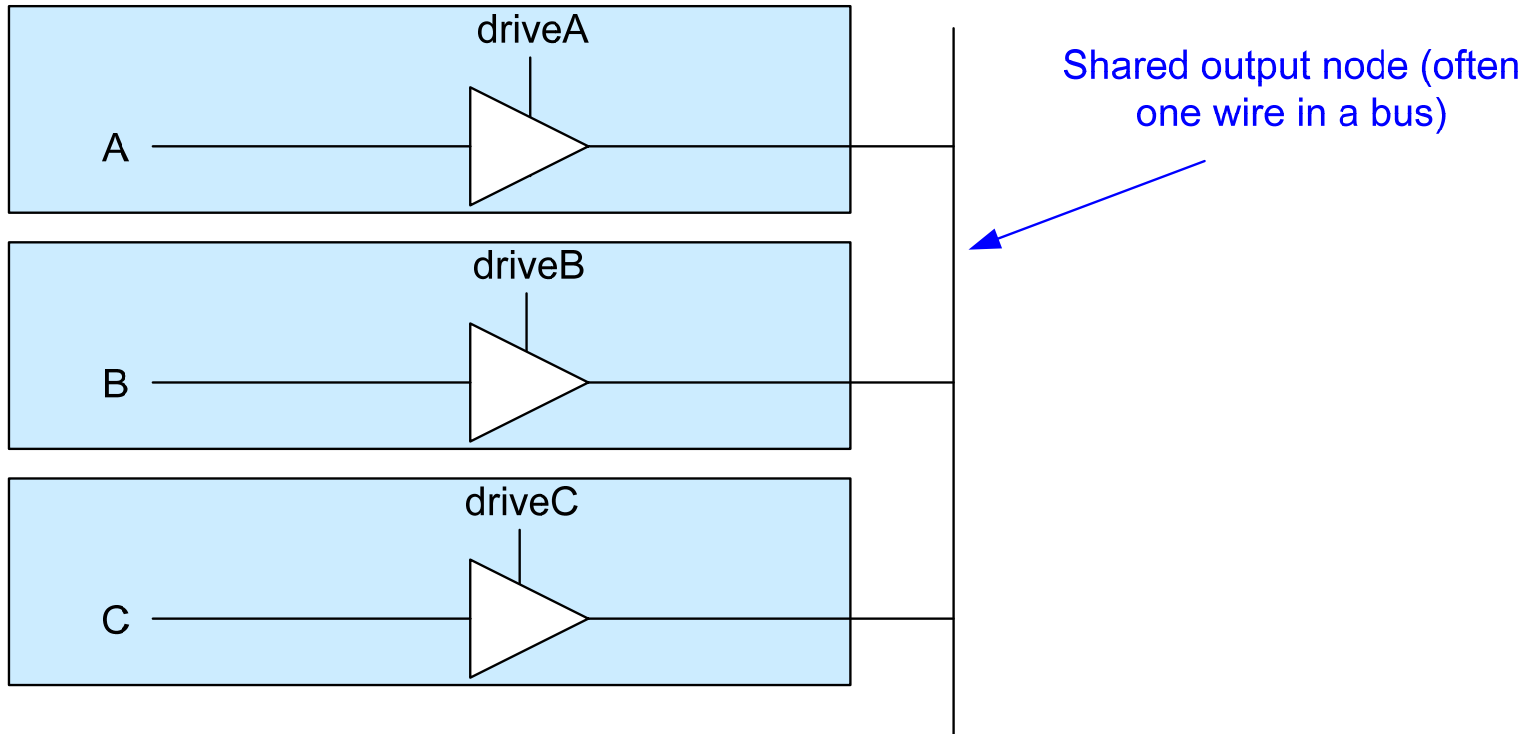

Some Technical Details


Each “type” in VHDL has an associated *resolution function*

A resolution function takes all the values being driven on a certain wire and calculates what the resulting value on that wire should be.

<u>input</u>	<u>output</u>	
1	1	When you use the std_logic_1164 package, the resolution function for std_logic is already defined
0	0	
0, 1	X	
0, 0, 0, 0	0	
0, 0, 0, 1	X	
Z, 0	0	
Z, 1, 1, 1	1	
Z, 0, 1	X	

Structural Descriptions – why generate

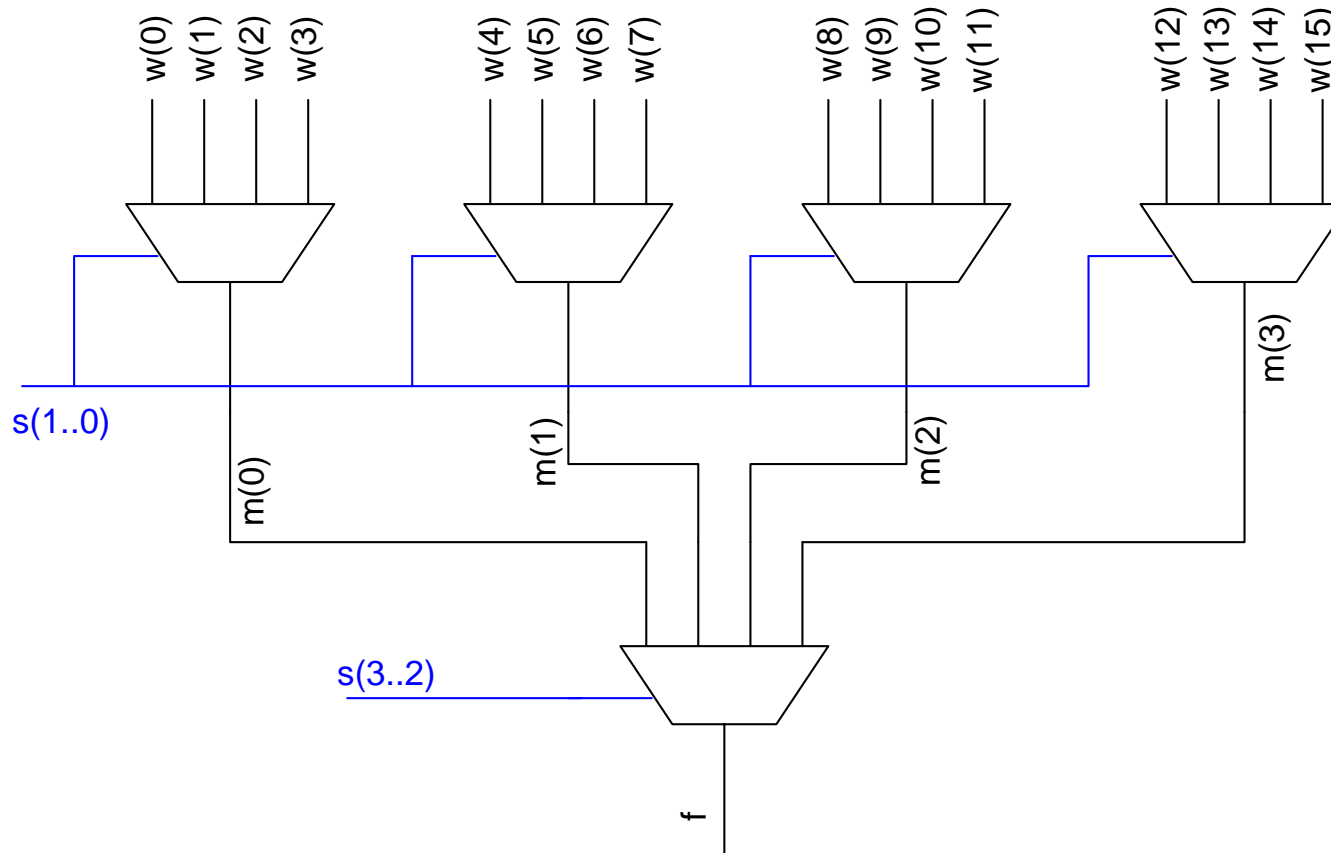- Suppose we want to design this circuit:



- Further, suppose we already have a 4-input 1-bit mux cell and we want to create a structural description

architecture structural of mux16to1 is

Assume we've already
defined this block

```
signal m : std_logic_vector(0 to 3);
```

```
begin
```

```
u1: mux4to1 port map
```

```
( w(0), w(1), w(2), w(3), s(1 downto 0), m(0) );
```

```
u2: mux4to1 port map
```

```
( w(4), w(5), w(6), w(7), s(1 downto 0), m(1) );
```

```
u3: mux4to1 port map
```

```
( w(8), w(9), w(10), w(11), s(1 downto 0), m(2) );
```

```
u4: mux4to1 port map
```

```
( w(12), w(13), w(14), w(15), s(1 downto 0), m(3) );
```

```
u5: mux4to1 port map
```

```
( m(0), m(1), m(2), m(3), s(3 downto 2), f );
```

```
end structural
```

architecture structural of mux16to1 is

```
    signal m : std_logic_vector(0 to 3);
```

```
begin
```

```
    g1: for i in 0 to 3 generate
```

```
        muxes: mux4to1 port map
```

```
            ( w(4*i), w(4*i+1), w(4*i+2), w(4*i+3), s(1 downto 0),  
              m(i) );
```


```
    end generate;
```

```
    u5: mux4to1 port map
```

```
        ( m(0), m(1), m(2), m(3), s(3 downto 2), f );
```

```
end structural
```

 - Another example: 4-bit adder constructed using four full-adders:



architecture structural of add4 is

```
    signal c : std_logic_vector(4 downto 0);
```

```
begin
```

```
    c(0) <= cin;
```

```
    u0: full_adder port map(a(3), b(3), c(3), s(3), c(4));
```

```
    u1: full_adder port map(a(2), b(2), c(2), s(2), c(3));
```

```
    u2: full_adder port map(a(1), b(1), c(1), s(1), c(2));
```

```
    u3: full_adder port map(a(0), b(0), c(0), s(0), c(1));
```

```
    cout <= c(4);
```

```
end structural
```

architecture structural of add4 is

```
    signal c : std_logic_vector(4 downto 0);
```

```
Begin
```

```
    c(0) <= cin;
```

```
    g0: for i in 3 downto 0 generate
```

```
        FA: full_adder port map(a(i), b(i), c(i), s(i), c(i+1));
```

```
    end generate g0;
```

```
    cout <= c(4);
```

```
end structural
```

- Sometimes, individual modules are a little bit different depending on their position in the array
- Example: in our adder, we could argue that:
 - bit 0 is a special case because the carry-in comes from '0'
 - bit 3 is a special case because the carry-out goes to cout signal
- We can write “special cases” using “if... generate”

architecture structural of add4 is

```
    signal c : std_logic_vector(3 downto 1);
```

```
Begin
```

```
    g0: for i in 3 downto 0 generate
```

```
        label0: if i = 0 generate
```

```
            FA: full_adder port map(a(0), b(0), '0' , s(0), c(1));
```

```
        end generate label0;
```

```
        label2: if i >0 and i < 3 generate
```

```
            FA: full_adder port map(a(i), b(i), c(i) , s(i), c(i+1));
```

```
        end generate label2;
```

```
        label3: if i = 3 generate
```

```
            FA: full_adder port map(a(3), b(3), c(3) , s(3), cout);
```

```
        end generate label3;
```


```
    end generate g0;
```

```
end structural
```

- Warning: too many “special cases” make your code ugly. Use this with discretion!



- Another warning: Generate is *only* a tool for helping you describe structural descriptions!
- It doesn't imply any sort of "looping" in the hardware.
- This is different than a "for" statement in a process
 - A process is used to describe the behaviour of a particular module – not to describe structure
 - I'm not going to teach you how to use "for" in a process, because it almost always leads to unsynthesizable code. Once you become good at writing synthesizable code, then you can read about the "for" statement.

 

Summary of this slide set

Part 1:

- Wires of type `std_logic` can have values:
 - X: unknown value (because of fighting usually)
 - Z: high impedance (not driven)
- Really important: These values are not physical voltages
 - You can't measure a Z or X in the lab
- Part 2:
 - Generate statement helps you describe structural descriptions of array-like structures.

Questions

- What is a resolution function?
- Can two outputs drive the same wire?

Questions

- What is a tristate buffer?
- Why do we need/use tristate buffers? Give an example?

Questions

- What is the difference between 'Z' and 'X'?
- What are generate statements? When should they be used?

Questions

- Can you selectively generate circuits?
- Is this like an executable for loop? Why/Why not?